


Modeling, Analysis, and Design of  
Combinational / Sequential Logic

1 Logic Function and Static CMOS Implementation (40 points)

1.1 Truth Table (8 points)

Consider the the circuit using static CMOS. What are the values of A and B (Low or High)?

Low = GND. High = Vdd.

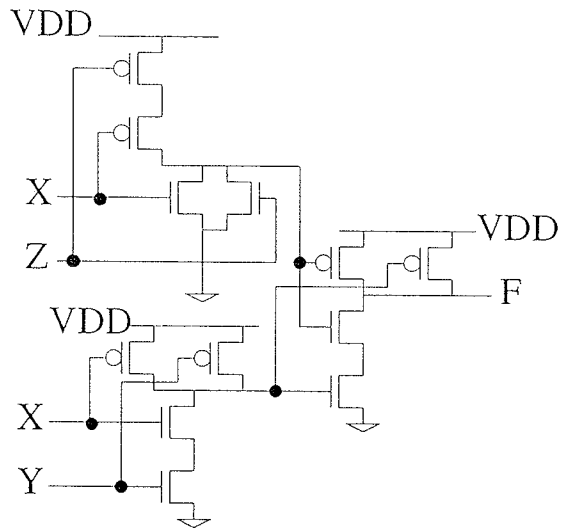

X	Y	Z	F
Low	Low	Low	-
Low	Low	High	-
Low	High	Low	A
Low	High	High	-
High	Low	Low	-
High	Low	High	B
High	High	Low	-
High	High	High	-

**1.2 Logic Function (24 points)**

Write the function  $F(X, Y, Z)$ . The answer should be in the form of canonical sum (of minterms). A minterm is a product that includes all literals:  $X, Y, Z$  or their complements. The product  $X \cdot Y \cdot \bar{Z}$ , for example, is a minterm, but the product  $X \cdot Y$  is not. Use  $\bar{X}$  to express the complement of  $X$ . Notice that  $\overline{XY} = \bar{X} \cdot \bar{Y} = NOT(X \cdot Y)$  is different from  $\bar{X} \cdot \bar{Y} = NOT(X) \cdot NOT(Y)$ .



**1.3 Logic Minimization (8 points)**

Minimize the logic expression. You should use the minimum number of literals.

2 Sequential Circuits (32 points)

Consider the output of the following sequential circuit with positive-edge-triggered D flip flops. Suppose the clock cycle is 10 ns with 50% duty cycle. Ignore the setup time of the flip flops, the delay of the inverter, and the delay of the wires.

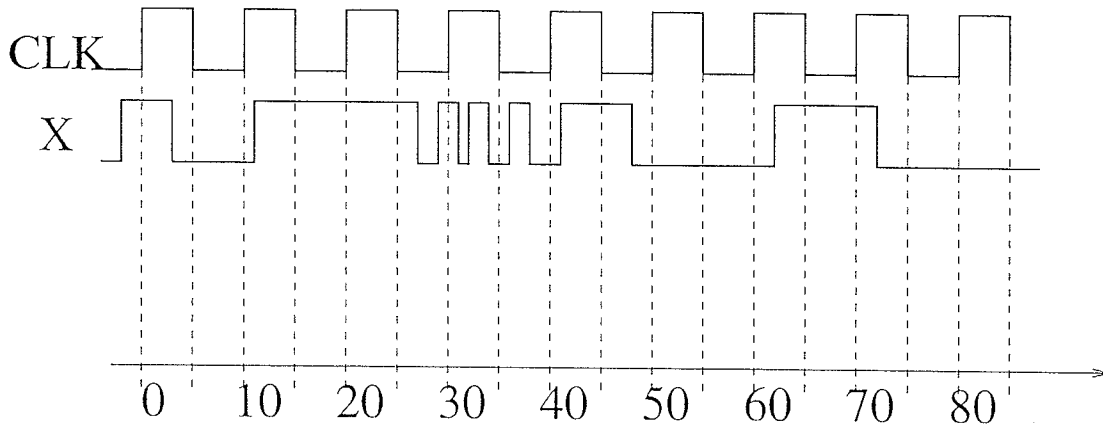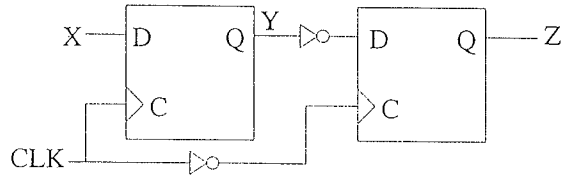Between 11ns and 76ns, how many times does Y change from Low to High? Between 11ns and 76ns, how many times does Z change from Low to High?



3 State Machine (28 points)

In this question, all numbers use decimal representations.

The following is an incomplete Moore state machine that outputs the remainder of 4 from an input stream of decimal numbers. If the present state is  $S_0$  and the input is 1, 5, or 9, the next state is  $S_1$  and the output is 1. If the present state is  $S_1$  and the input is 2 or 6, the next state is  $S_0$  and the output is 0. This can be understood by considering one example: If the input number is 52, the remainder of the first digit 5 is 1 (state  $S_1$ ). When the second digit 2 appears, the number is 52 and it is a multiple of 4. Hence, the output is 0. Assume the machine starts from  $S_0$  and the digits are scanned from MSD (most significant digit) to LSD (least significant digit).

Suppose the machine is now in state  $S_1$  after several input digits. Let  $y$  be a single-digit number that is the next input to the machine. List all possible values of  $y$  that will cause the machine to change to state  $S_3$  from the current state as shown in the thick arrow.

