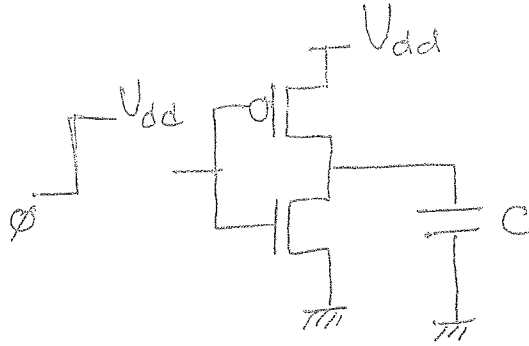
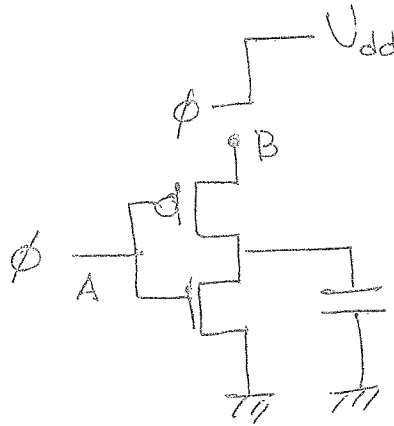


1. Consider the inverter shown in the following figure where a step function is applied to the input of the inverter. Assume that the output fall time,  $t_f$ , is defined to be from  $0.9V_{dd}$  to  $0.01V_{dd}$  of the output. Analytically determine  $t_f$ . Use long channel equations for transistors operating in linear and saturation region. Also assume leakage current to be negligible. State any assumptions that you make. (70)



2. Consider the circuit shown in the following figure. A step function is applied to terminal B. Determine the energy consumption. Show all the steps of your derivation. (30)



*Write in Exam Book Only*