
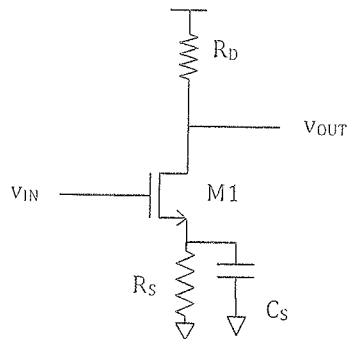


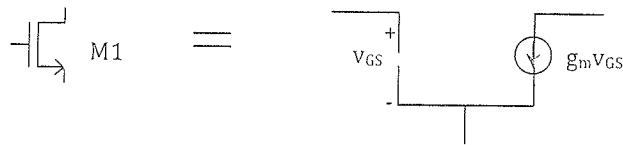1. [25 points] For the circuit shown below, calculate voltage gains ( $v_{out}/v_{in}$ ) at  $f = 0\text{Hz}$  and  $f = \infty\text{ Hz}$ .



Assume M1 can be modeled as an ideal transconductor as shown below.



$$g_m = 20 \text{ mA/V}$$


$$R_D = 1 \text{ k}\Omega$$

$$R_S = 500 \Omega$$

$$C_S = 1 \text{ pF}$$

Write in Exam Book Only

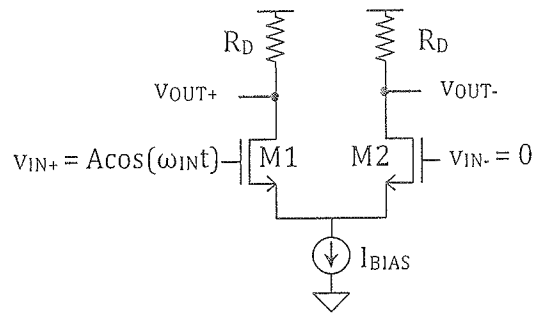2. [25 points] For the circuit shown below, calculate  $v_{OUT+}$  and  $v_{OUT-}$ . Assume M1 and M2 are biased in saturation region. Assume  $I_{BIAS}$  is an ideal current source. Ignore channel length modulation and body effect. Assume  $\omega_{in} \ll \omega_{pole}$ , where  $\omega_{pole}$  is the main pole of the differential amplifier.




$$g_{m1} = g_{m2} = 10 \text{ mA/V}$$

$$R_D = 600 \, \Omega$$

Write in Exam Book Only

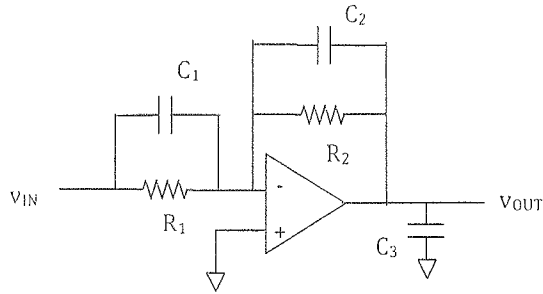3. [25 points] For the circuit shown below, calculate  $H(s) = v_{OUT}/v_{IN}$ . Assume the op-amp is ideal. From the  $H(s)$ , calculate 3-dB bandwidth.



$$C_1 = 0.5C_2$$


$$R_1 = 2R_2$$

Write in Exam Book Only

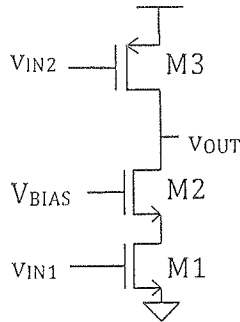4. [25 points] For the circuit shown below, calculate  $v_{OUT}$  as a function of  $v_{IN1}$  and  $v_{IN2}$  at low frequencies (ignore all parasitic capacitances).

Assume:

- M1, M2, and M3 are biased in saturation
- $g_{m1} = g_{m2} = g_{m3} = g_m$
- $r_{o1} = r_{o2} = r_{o3} = r_o$



Write in Exam Book Only