

1. [25 points] In the circuit below, find the transfer function $H(s) = v_{out}/v_{in}$, and plot $|H(s)|$ vs. ω . In the plot, mark the value of $|H(s)|$ when $\omega = 1/(RC)$.

Assume:

- The op-amp is ideal.
- $R1 = R2 = R$
- $C1 = C2 = C$

2. [25 points] In the circuit below, find the small signal output voltage v_{out} .

Assume:

- The op-amp is ideal.
- The DC current source I_{Bias} is ideal.
- The DC voltage sources V_{Bias1} and V_{Bias2} are ideal.
- M1 is biased in saturation region.
- The output resistance of M1, $r_o = 100k\Omega$
- The transconductance of M1, $g_m = 20 \text{ mA/V}$.
- M1 has no parasitic capacitance ($C_{gs} = C_{gd} = C_{sb} = C_{db} = 0$).

3. [25 points] In the circuit below, find the input impedance Z_{in} seen by the voltage signal source v_{in} .

Assume:

- The current source I_{Bias} is ideal.
- M1 is biased in saturation region.
- M1 has no parasitic capacitance ($C_{gs} = C_{gd} = C_{sb} = C_{db} = 0$).
- The output resistance of M1, $r_o = \infty$.

4. [25 points] In the circuit below, find the small signal output voltage v_{out+} .

Assume:

- The circuit is fully symmetric
- M1 and M2 are biased in saturation region.
- The current source is ideal.
- M1 and M2 have no parasitic capacitance ($C_{gs} = C_{gd} = C_{sb} = C_{db} = 0$).
- For both M1 and M2, $r_o = \infty$.
- For both M1 and M2, the transconductance $g_m = 30\text{mA/V}$.
- $R1 = 1 \text{ k}\Omega$
- $R2 = 2 \text{ k}\Omega$
- $C1 = 10 \text{ pF}$