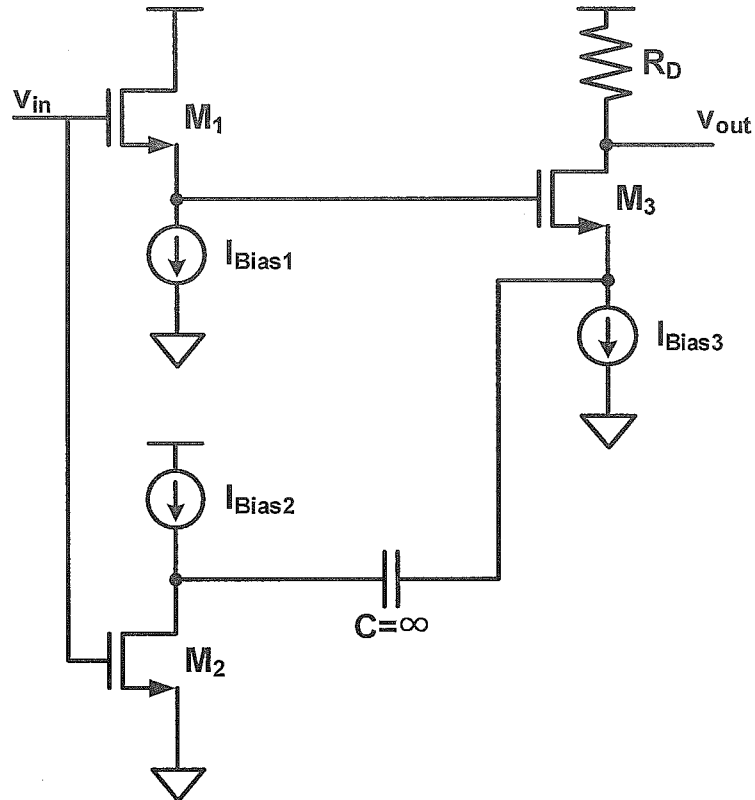


1. [25 points] In the circuit below, find the small signal output voltage  $v_{out}$ .

Assume:

- All transistors are biased in saturation.
- The bias current sources are ideal.
- For all transistors,  $C_{gs} = 0$ ,  $C_{gd} = 0$ ,  $C_{sb} = 0$ ,  $C_{db} = 0$ , and  $r_o = \infty$ .
- $g_{m1} = g_{m2} = g_{m3} = g_m$




Write in Exam Book Only

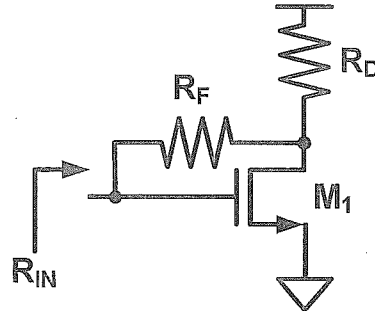2. [25 points] In the circuit below, find the small signal input resistance  $R_{IN}$ .

Assume:

- The transistor is biased in saturation.
- $C_{gs} = 0$ ,  $C_{gd} = 0$ ,  $C_{sb} = 0$ ,  $C_{db} = 0$ , and  $r_o = \infty$ .




Write in Exam Book Only

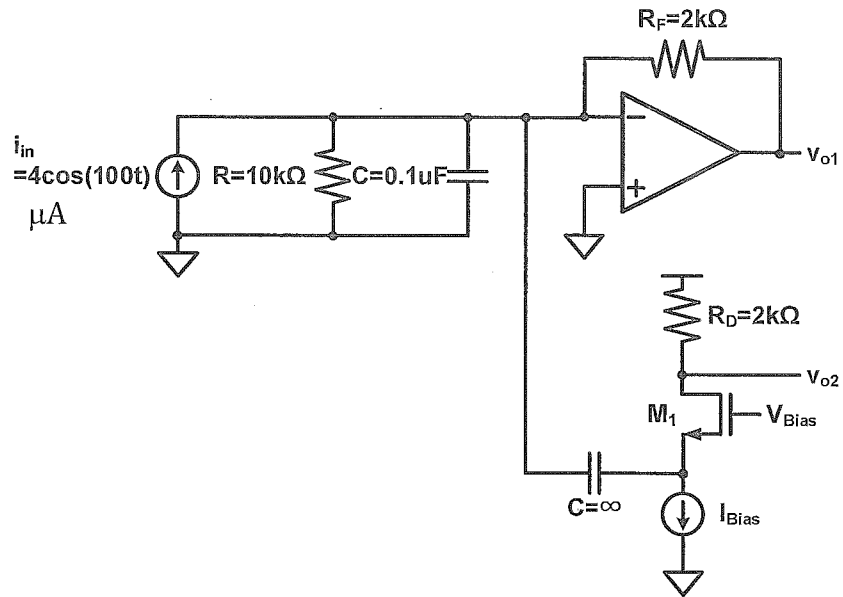3. [25 points] In the circuit below, find the small signal output voltages  $v_{out1}$  and  $v_{out2}$ .

Assume:


- The transistor is biased in saturation.
- The op-amp is ideal.
- The bias current source is ideal.
- $C_{gs} = 0$ ,  $C_{gd} = 0$ ,  $C_{sb} = 0$ ,  $C_{db} = 0$ , and  $r_o = \infty$ .



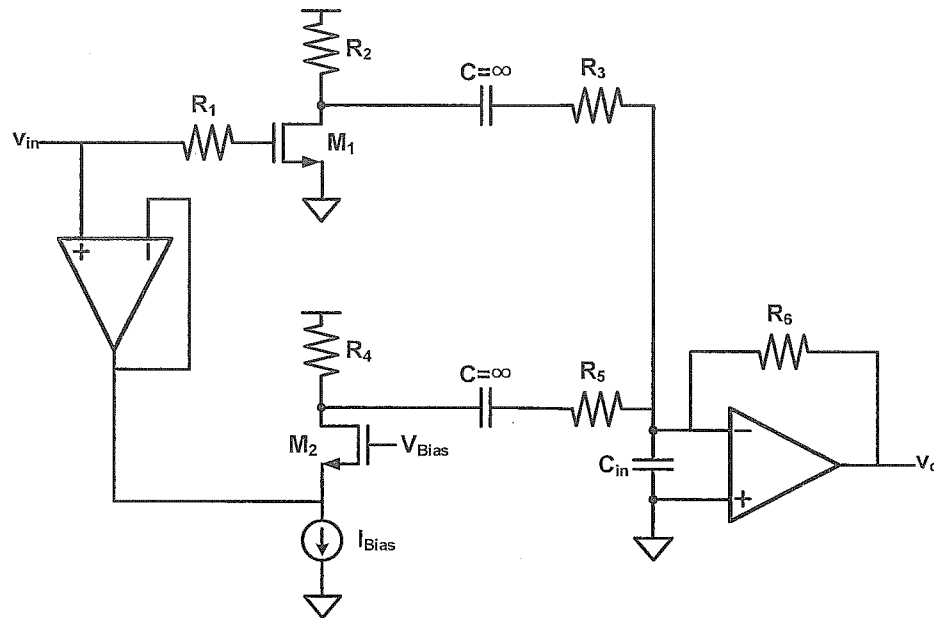4. [25 points] In the circuit below, find the transfer function  $H(s) = V_{out}/V_{in}$ .

Assume:

- The op-amps are ideal.
- All transistors are biased in saturation.
- The bias current source is ideal.
- For all transistors,  $C_{gs} \neq 0$ ,  $C_{gd} = 0$ ,  $C_{sb} = 0$ ,  $C_{db} = 0$ , and  $r_o = \infty$ .
- $g_{m1} = g_{m2} = g_m$
- $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R$



Write in Exam Book Only