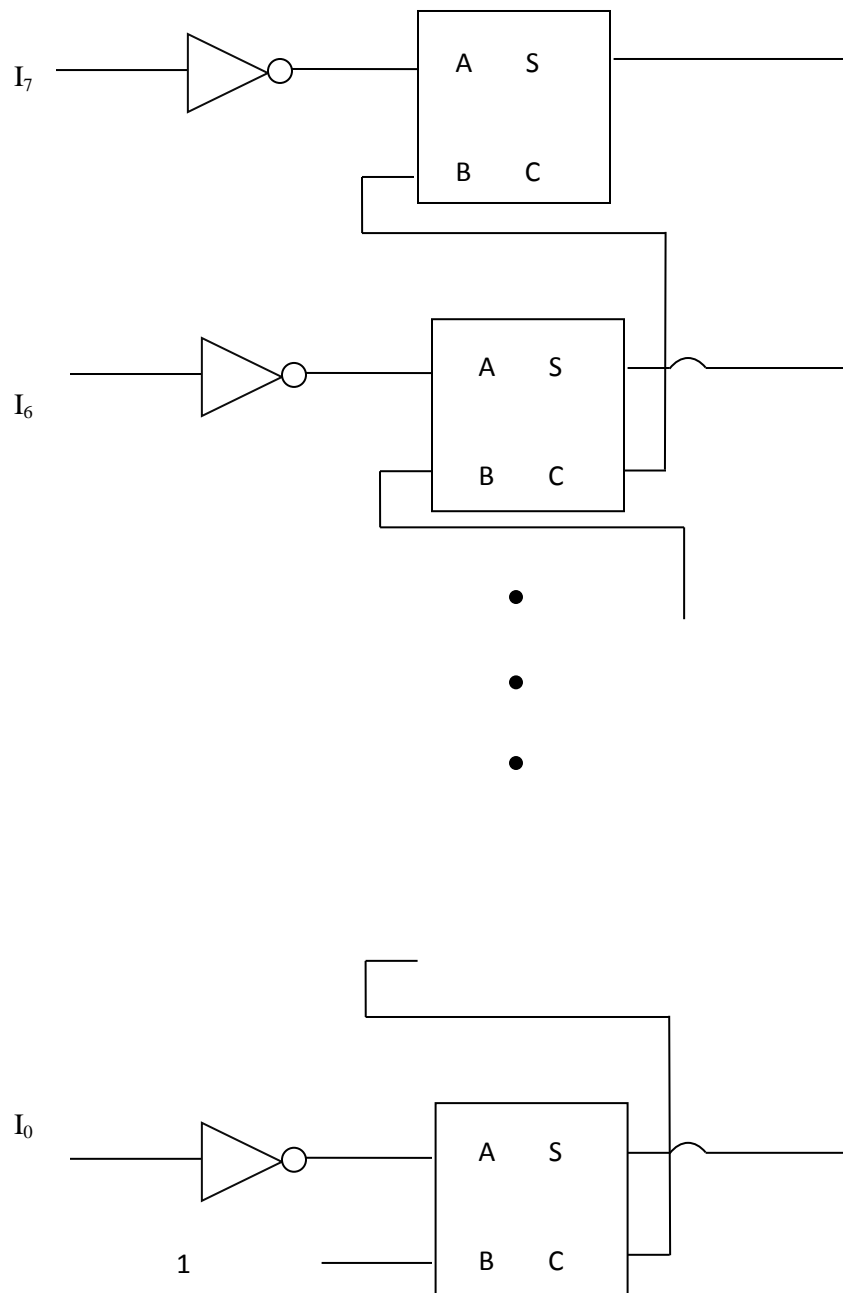


# Homework #2-1



## Homework 2-2

(a). Bollinger B-5

$$\text{a. } \underbrace{11011}_{\text{B}} \underbrace{0111}_7 = 1\text{B}7_{16}$$

$$\text{d. } \underbrace{1011}_{\text{B}} \underbrace{.0111}_7 = \text{B}.7_{16}$$

(b). Bollinger B-7

$$-346_{10} = 1111111010100110_2$$


$$2242_{10} = 0000100011000010_2$$

$$-3465_{10} = 1111001001110111_2$$

3.


a) half subtractor

A	B	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

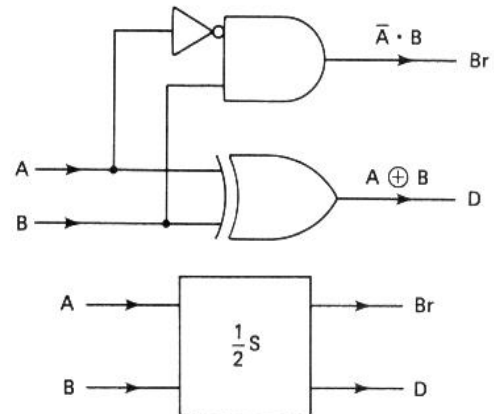



b) Full borrowor

A	B	B <sub>in</sub>	D	B <sub>out</sub>
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

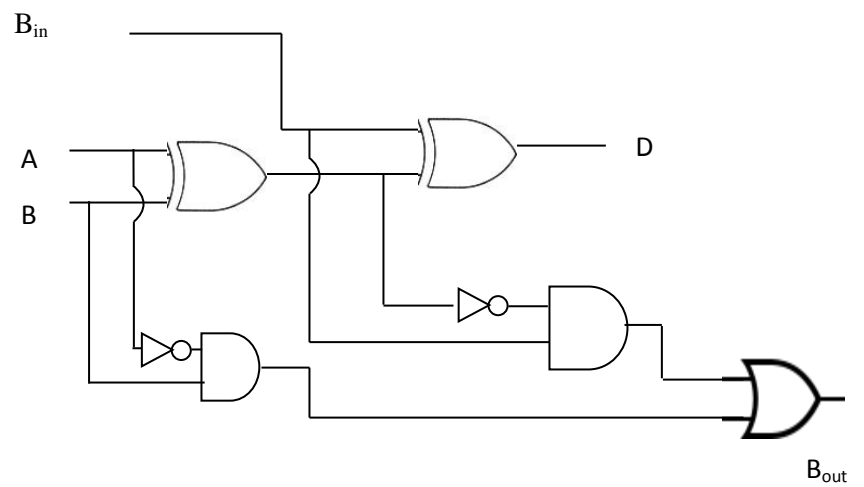


Type equation here.

#2-4

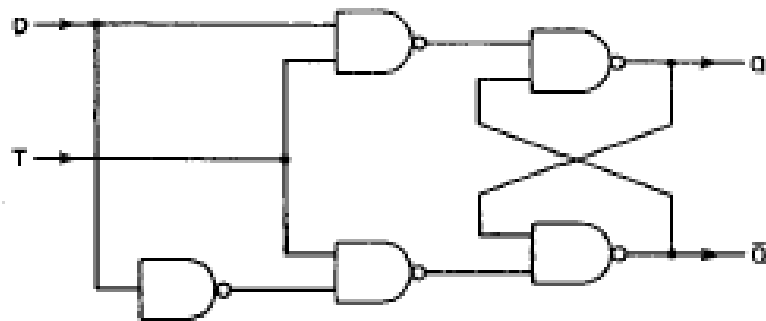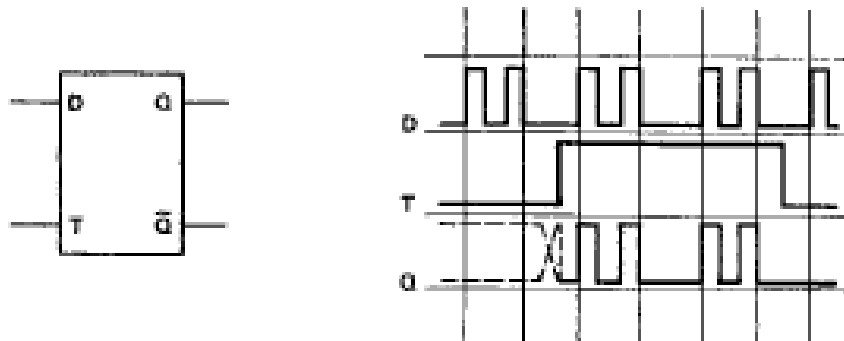


(b)

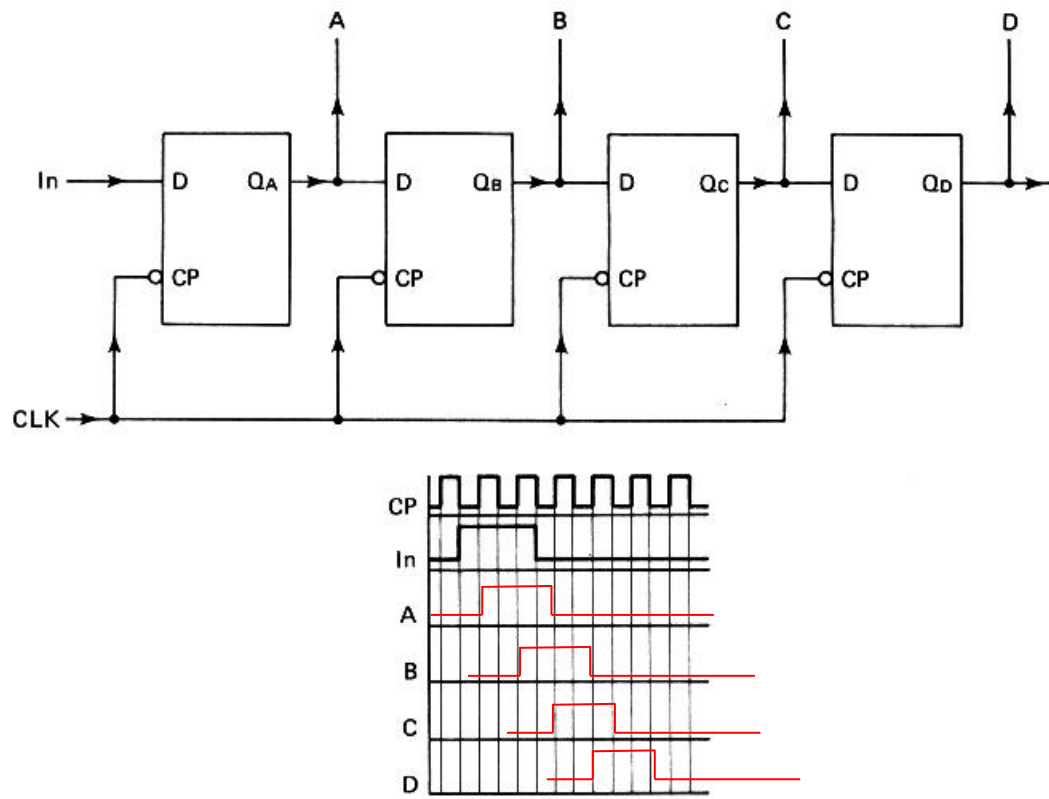

(a) Complete the truth table for the following circuit

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

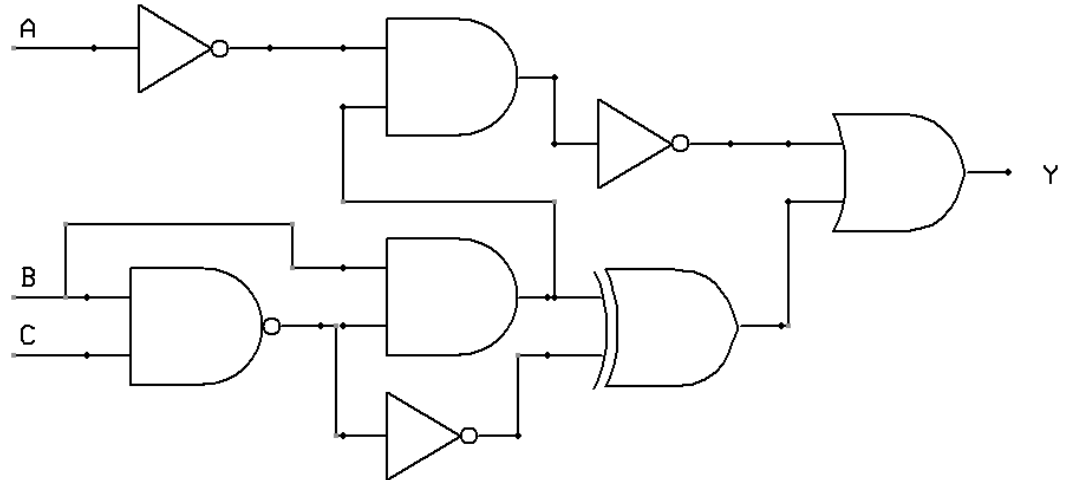

$$\begin{aligned}
 y &= \overline{(\overline{A} \cdot B \cdot \overline{(B \cdot C)})} + B \cdot C \oplus B \cdot \overline{(B \cdot C)} \\
 &= A + \overline{B} + B \cdot C + \overline{(B \cdot C)} \cdot B \cdot \overline{(B \cdot C)} + B \cdot C \cdot \overline{(B \cdot \overline{(B \cdot C)})} \\
 &= A + \overline{B}(1 + C) + B \cdot C + B(\overline{B} + \overline{C}) + B \cdot C \cdot (\overline{B} + B \cdot C) \\
 &= A + \overline{B} + C + B \cdot \overline{C} + B \cdot C \\
 &= A + \overline{B} + C + B \\
 &= A + 1 + C = 1
 \end{aligned}$$