

ECE 477 Digital Systems Senior Design Project

Module 9 Documentation Standards

Reading Assignment: Wakerly *DDPP* –
3rd Ed., pp. 311-337; 4th Ed., pp. 342-370

Instructional Objectives:

- **To review the foundations of structured digital system design**
- **To review combinational logic design documentation standards**
- **To review how to draw timing diagrams and use timing specifications**


Outline

- Documentation standards
- Active levels for pins
- Drawing layout
- Timing diagrams and specifications


Documentation Standards

- Good documentation is essential for correct design and efficient maintenance
- A documentation package should contain:
 - abstract
 - specification
 - block diagram
 - schematic diagram
 - PCB layout diagram
 - timing diagram
 - structured logic device description
 - circuit description (narrative text)
 - software description (narrative text)

SHIFT-AND-ADD MULTIPLIER

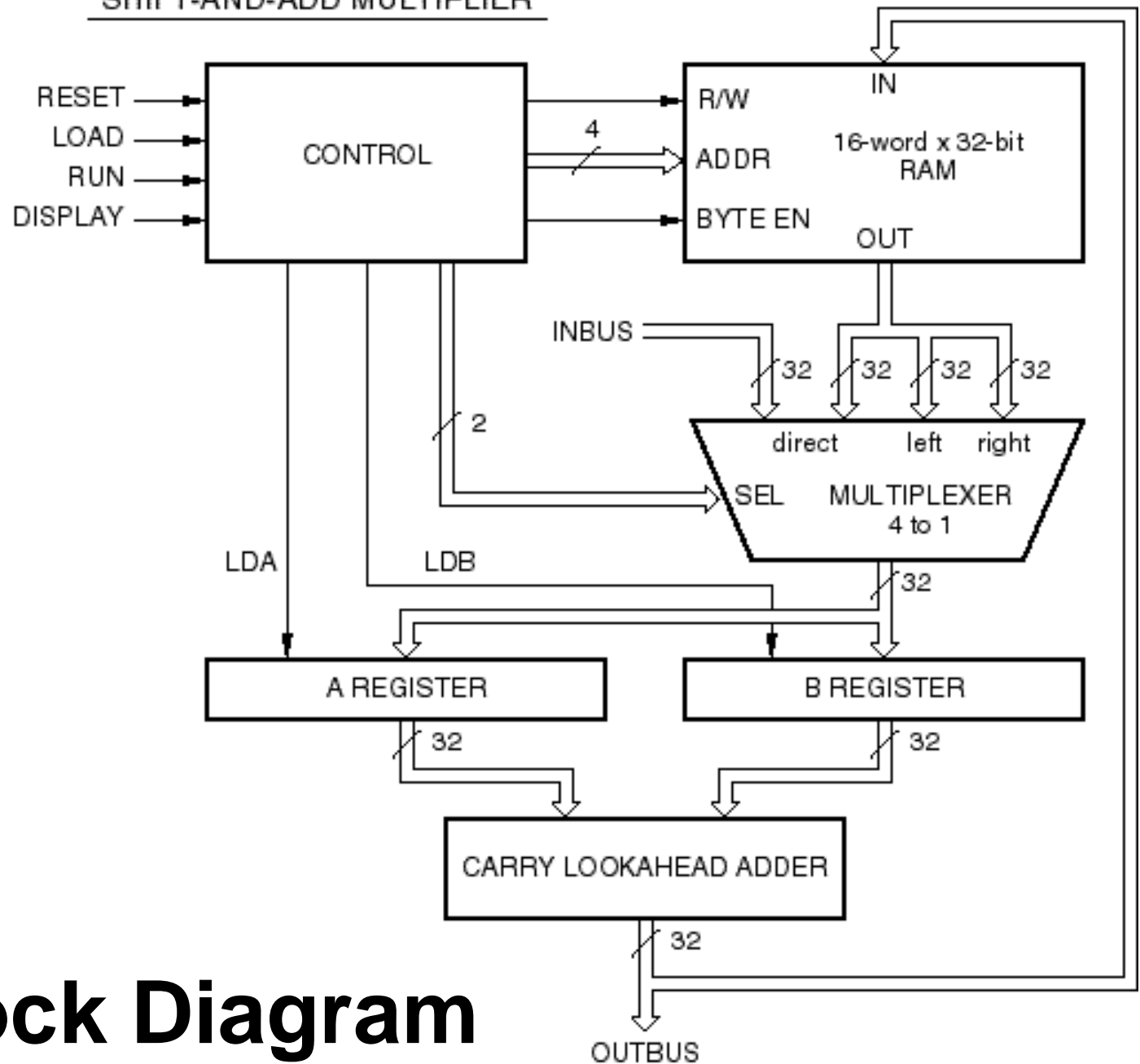


Equivalent Gate Symbols

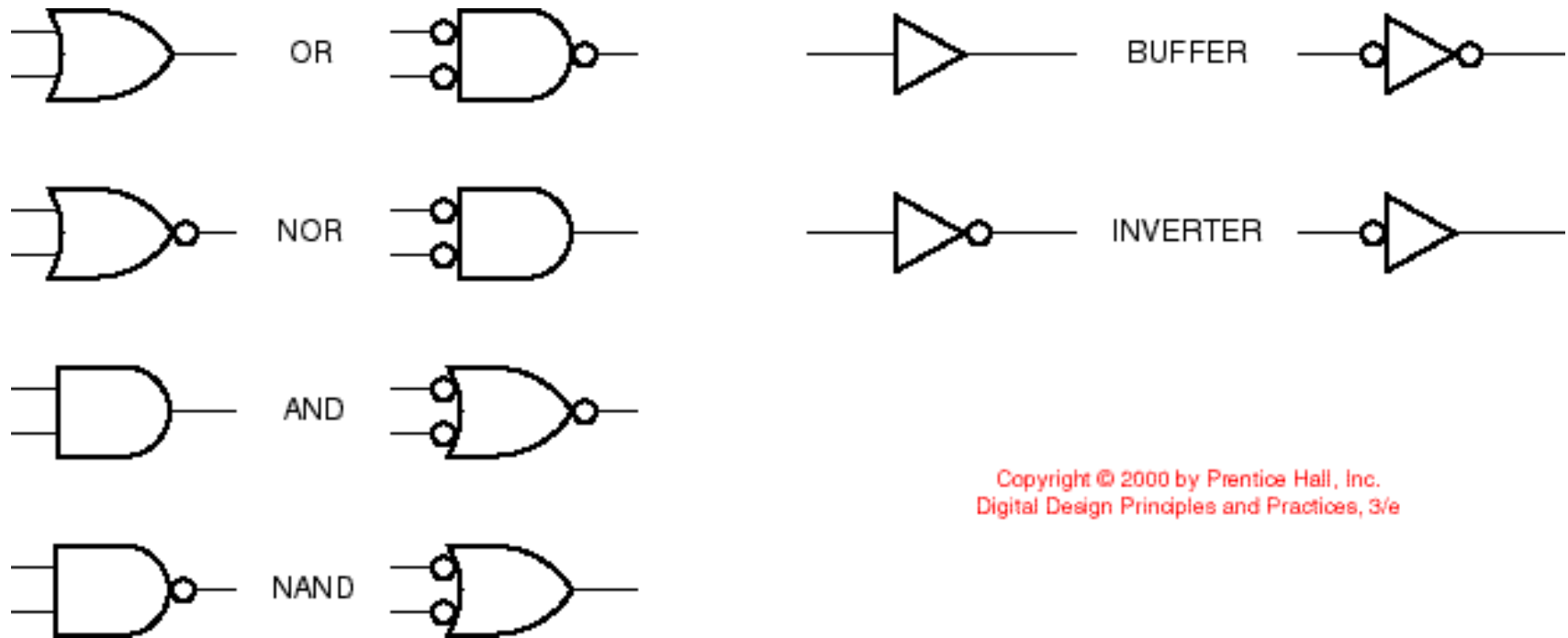


Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Active Levels for Pins

 - When we draw a logic symbol, we think of a function being performed “inside” that symbolic outline
- Use *inversion bubbles* to indicate pins that are *active low*




(a)

 


(b)

Active Levels for Pins

 - It is very helpful to use net aliases with “_L” suffix to indicate active low for those signals that are active low




(a)

 


(b)

 
Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e



(c)

 

(d)

 

(a)






(b)

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e



Schematic Guidelines

- Logic diagrams and schematics should be drawn with gates in their “normal” orientation (inputs on left, outputs on right)
- A complete schematic page should be drawn with system inputs on the left and outputs on the right
- Line crossings and connections

Hand drawn

   

Machine drawn

  

not allowed

crossing

connection

connection

Schematic Guidelines (2)

- Pin names on custom footprints should be descriptive, but not so long that they overlap other pin names (quad packs...)
- Either **physical** or **logical** arrangement is okay, but try to be consistent throughout document.
- Use power / ground symbols
- For power, show net alias on schematic


Schematic Guidelines (3)

44	RB4	RD2	54	PSPd2
45	RB3	RD3	53	PSPd3
46	RB2	RD4	52	PSPd4
47	RB1	RD5/SDA2	51	PSPd5
48	RB0	RD6/SCL2	50	PSPd6
		RD7/nSS2	49	PSPd7

Schematic Guidelines (3)


- Polarized / non-polarized capacitors

 - Value
- Tolerance
- Voltage
- Footprint




- Diode types

 
- PN / Ge, etc.
- Schottky
- Zener
- **designate by part #**



Pin Diagram and Schematic

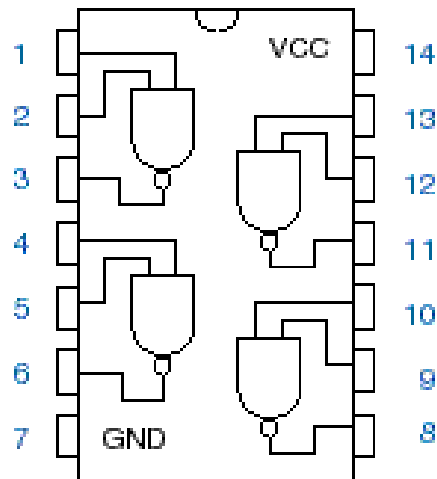

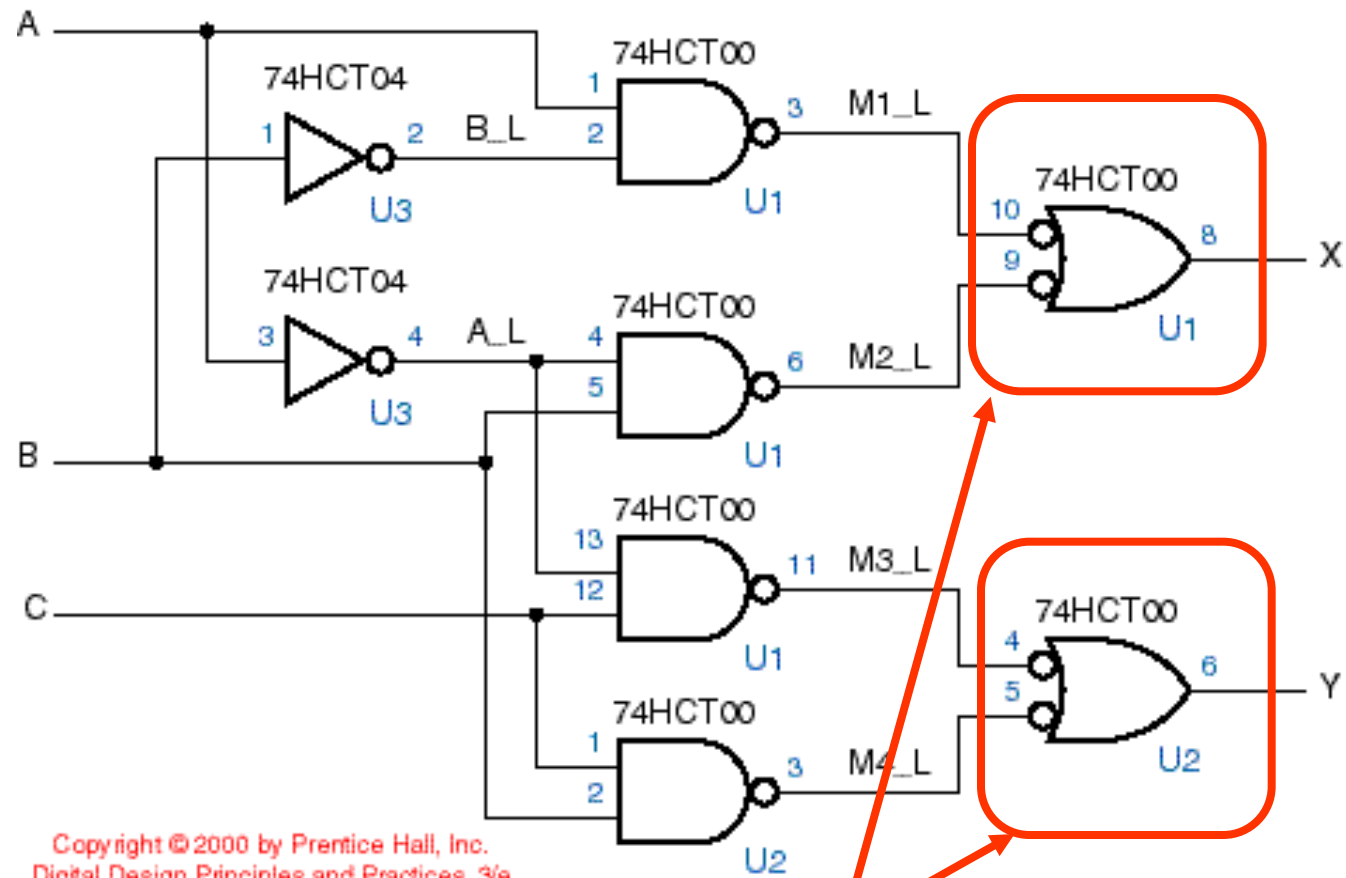Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e



Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e



In ORCAD, these are called the “ALT” symbols

Timing Diagrams

- A **timing diagram** illustrates the logical behavior of signals in a digital circuit as a function of time
- They are used to explain the timing relationship among signals within a system and to define the timing requirements of external signals applied to the system
- Arrows are sometimes drawn to show **causality** (which input transitions cause which output transitions)


Timing Diagrams

  - **Combinational circuit timing diagram**



Timing Diagrams



- Timing diagrams for “data” signals

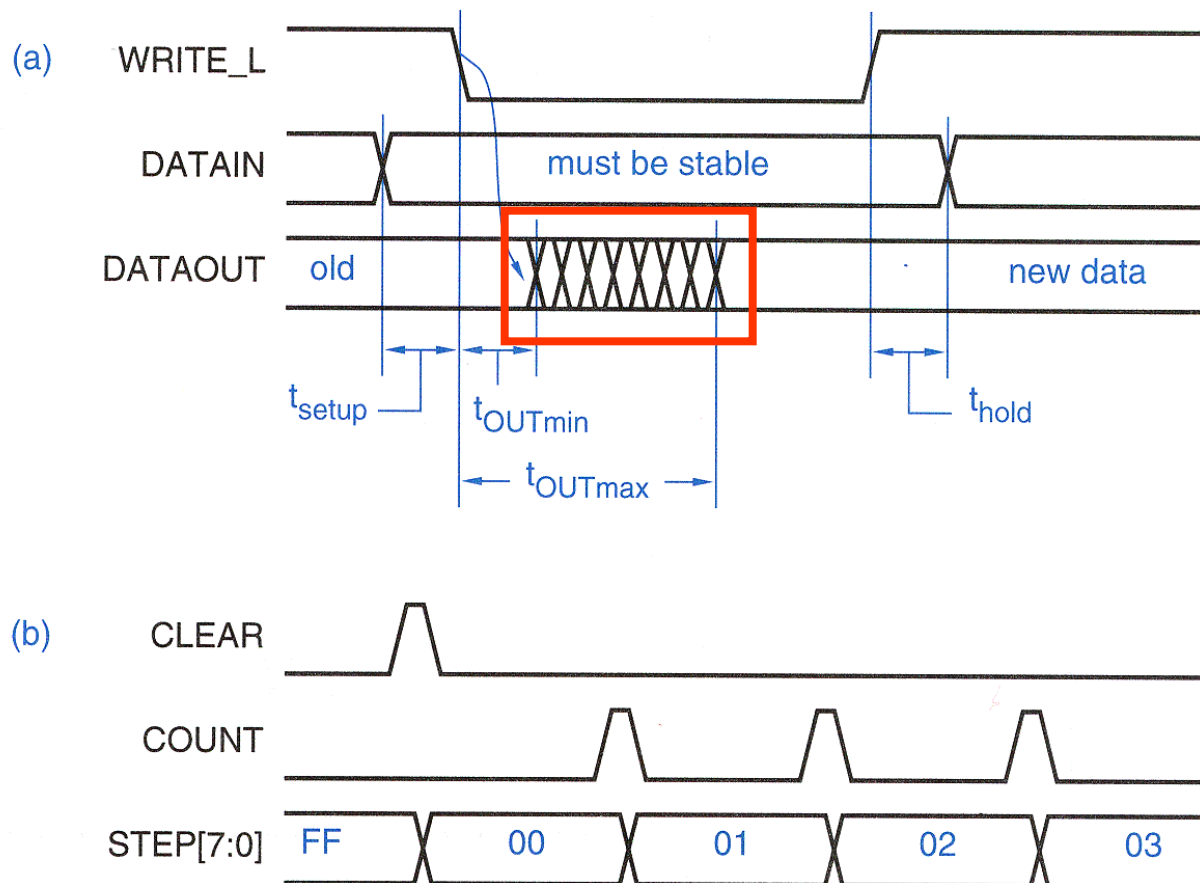

Timing Specifications

- A combinational circuit with many inputs and outputs has many different paths
- Each path in a combinational circuit may have a different propagation delay
- The propagation delay when an output changes from **LOW** to **HIGH** (t_{pLH}) *may be different* than the delay when it changes from **HIGH** to **LOW** (t_{pHL})
- Timing specifications in data sheets usually provide minimum, typical, and maximum values for each propagation delay path


Clock Signals (active high/low)

  

Timing Diagrams and Specifications

- For synchronous systems, timing diagrams can be used to show the relationship between the clock and various input, output, and internal signals

 clock frequency (f) = $1/t_{\text{clk}}$ duty cycle = $t_H/(t_H+t_L)$



External Memory Timing (NE64)


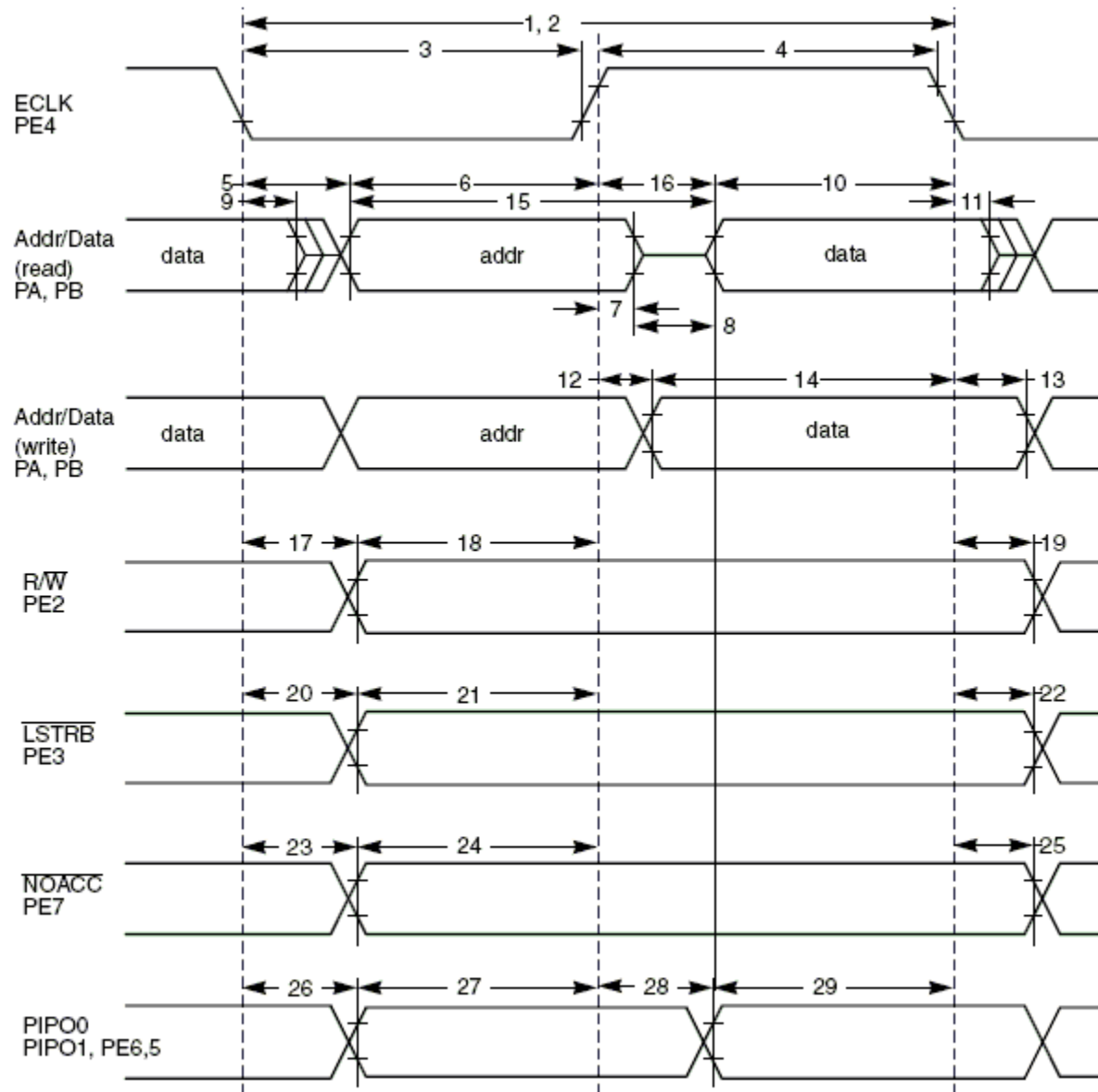


Figure 18-25. General External Bus Timing

Tri-State Buffers

 - Three-state (“tri-state”) devices allow multiple sources to share a single “party line” (provided only one device “talks” on the line at a time)




Basic variations: The buffer may be inverting or non-inverting, and the tri-state enable can either be active low or active high

Tri-State Buffers

- Three-state devices are typically designed so that they **go into** the Hi-Z (high impedance) state faster than they **come out of** the Hi-Z state (i.e., t_{pLZ} and t_{pHZ} are both less than t_{pZL} and t_{pZH})
- Given this “rule”, if one tri-state device is disabled and another tri-state device is enabled simultaneously, then the first device will get **off** the bus before the second one gets **on** – this prevents **fighting** (a.k.a. **bus contention**)

Why we need tri-state buffers:

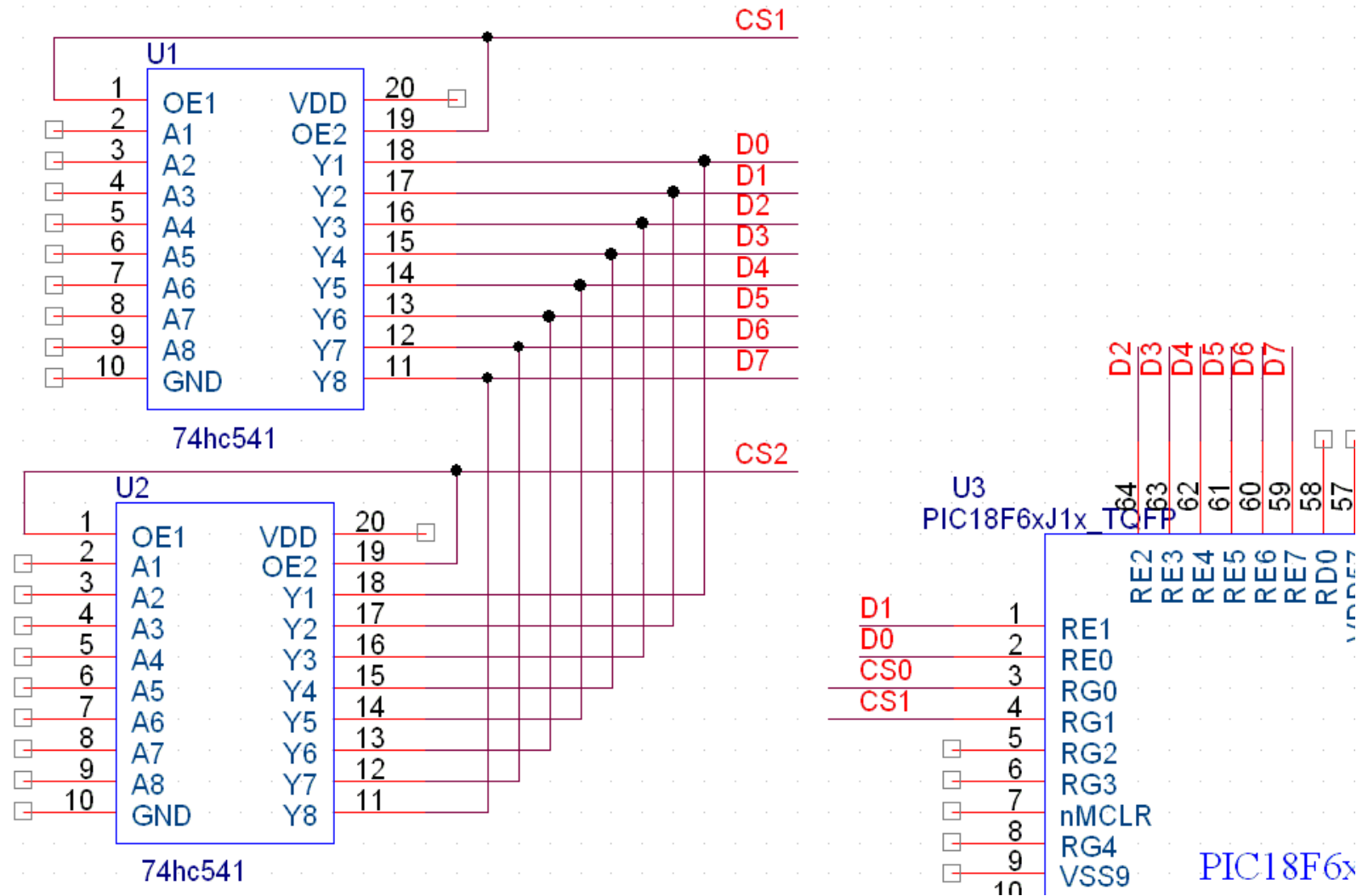

Tri-State Buffers

- In practice it is difficult to ensure that the enable inputs of different tri-state devices change “simultaneously”
- The only **safe** way to use tri-state devices is to design control logic that **guarantees** a **dead time** on the bus line during which none of the buffers is driving it

