

# Major Electrical Interfaces


- Core Power Delivery
  - Physical and electrical view
  - Parasitic inductance estimation
  - Distribution issues, guidelines
- I/O Power Delivery and Signaling
  - Signal return current
- Summary

# Microprocessor Design Constraints

## ■ Power supply impedance

- $Z = (\Delta V_{\text{SPEC}}) / (\Delta I_{\text{ESTIMATE}})$ : Ex.  $1.8\text{-V} \times 5\% / 10\text{-A} = 9\text{-m}\Omega$
- Must deliver power over a broad frequency spectrum

 
## Architectural Power Model To Estimate $\Delta I$



# Microprocessor System

 
## ■ Power perspective

- Package types, attach strategy, board or MCM type, package/board layer assignments, decoupling capacitor requirements.



 
# Decoupling Capacitor Modeling

- Wide range in performance and cost
  - Example: 3 different capacitors




- Parasitics between banks must be included

# Low Frequency Electrical View

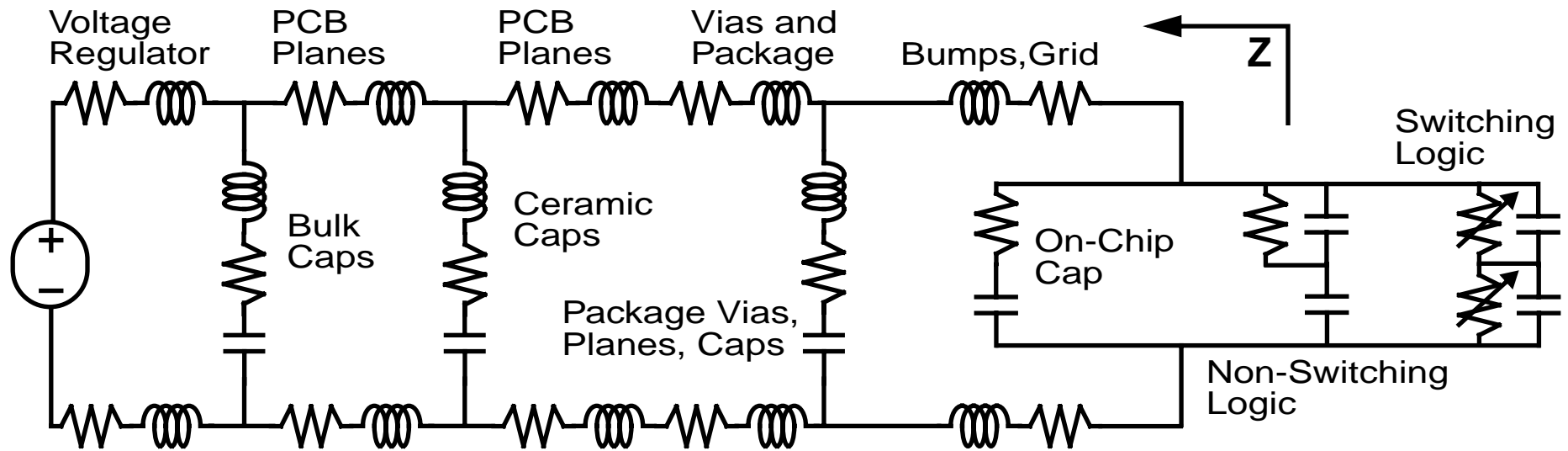

## Qualitative Look At Frequency Domain

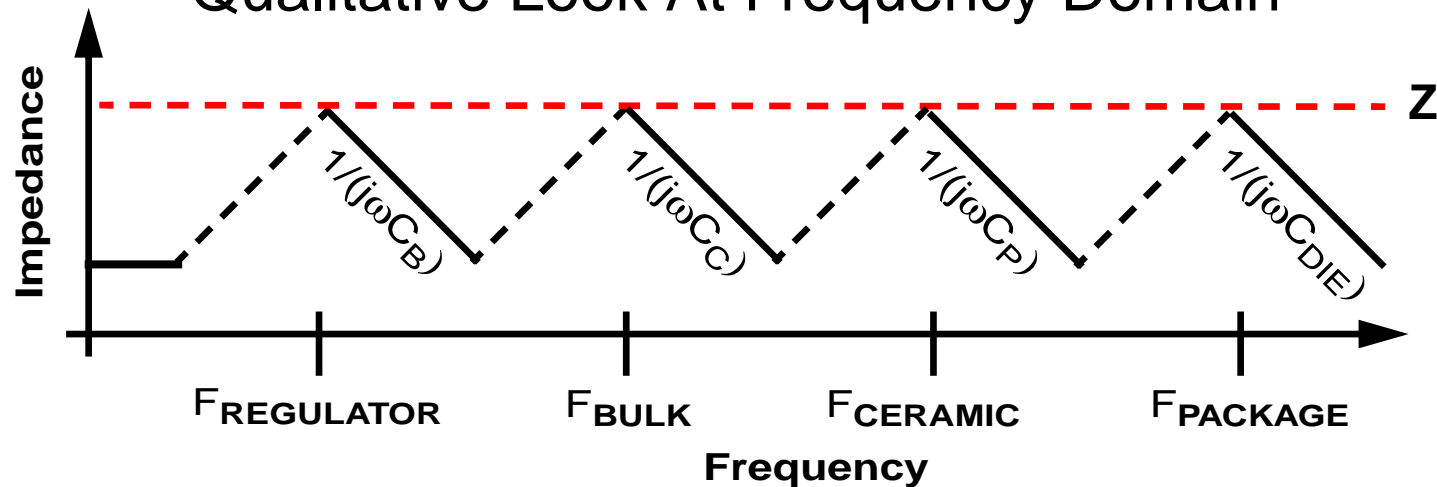


# Inductance of Vias, Pins, Bumps

## ■ Mutual inductance [1],[2]


$$M = \frac{\mu_0}{2\pi} I \left( \ln \left( \frac{l}{s} + \sqrt{1 + \frac{l^2}{s^2}} \right) - \sqrt{1 + \frac{s^2}{l^2}} + \frac{s}{l} \right)$$
 
## ■ Self inductance [1],[2]


$$L = \frac{\mu_0}{2\pi} I \left( \ln \left( 2 \frac{l}{d} + \sqrt{1 + \frac{4l^2}{d^2}} \right) - \sqrt{1 + \frac{0.25d^2}{l^2}} + 0.5 \frac{d}{l} + \frac{\mu_r}{4} \right)$$


 
## ■ Loop inductance of arrays is pattern dependent [3]



POOR

 


BETTER
 
# Power Plane Inductance

- Planes are present in the package and on the board
- Loop inductance [2]:


$$L = \frac{\mu_o}{\pi} l \left( \ln \left( \frac{d}{B + C} \right) + 1.5 \right)$$



- Most planes are actually perforated
- Decrease inductance for multiple pairs by  $2n-1$  dielectrics, where  $n$  is the number of power plane pairs, assuming  $V_{DD}-G_{ND}-V_{DD}-G_{ND}$  stack-up
- Thin spacing decreases inductance
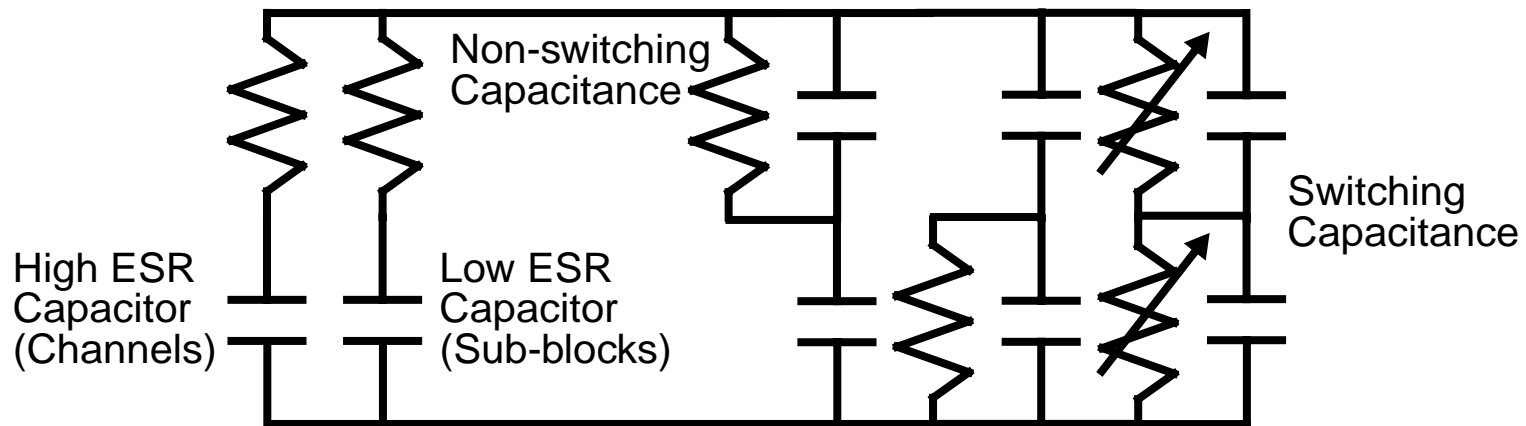
# Low/Mid-Frequency Chip Model


- Estimate switching capacitance from thermal power
  - $C_{\text{SWITCH}} = P / (V^2 f)$
- On-die decoupling capacitance is typically about 10x the switching capacitance (rule of thumb)
  - Yield issue (decoupling is ~15-20% of die area)
  - Scaling issue for process shrinks - leakage
- Equivalent series resistance (ESR)
  - Ratio of one type to the other is design-specific






# Decoupling Capacitor Design

Frequency  
Response

 


Step  
Response


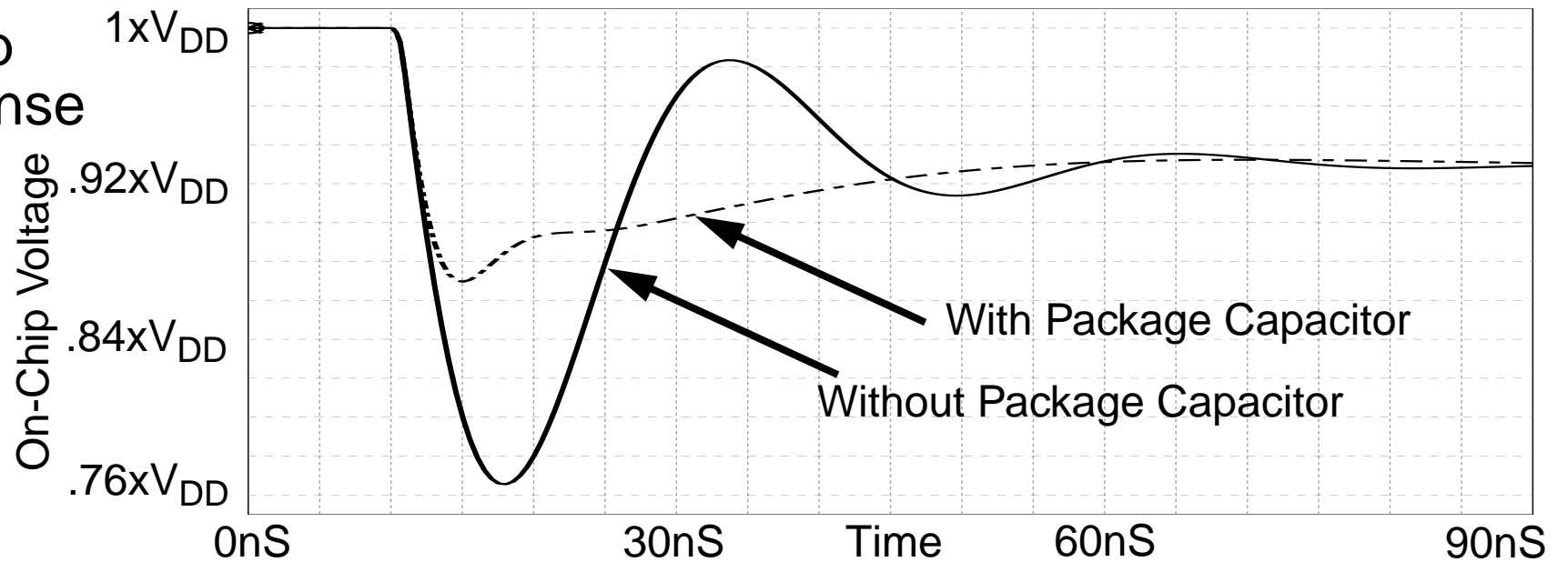

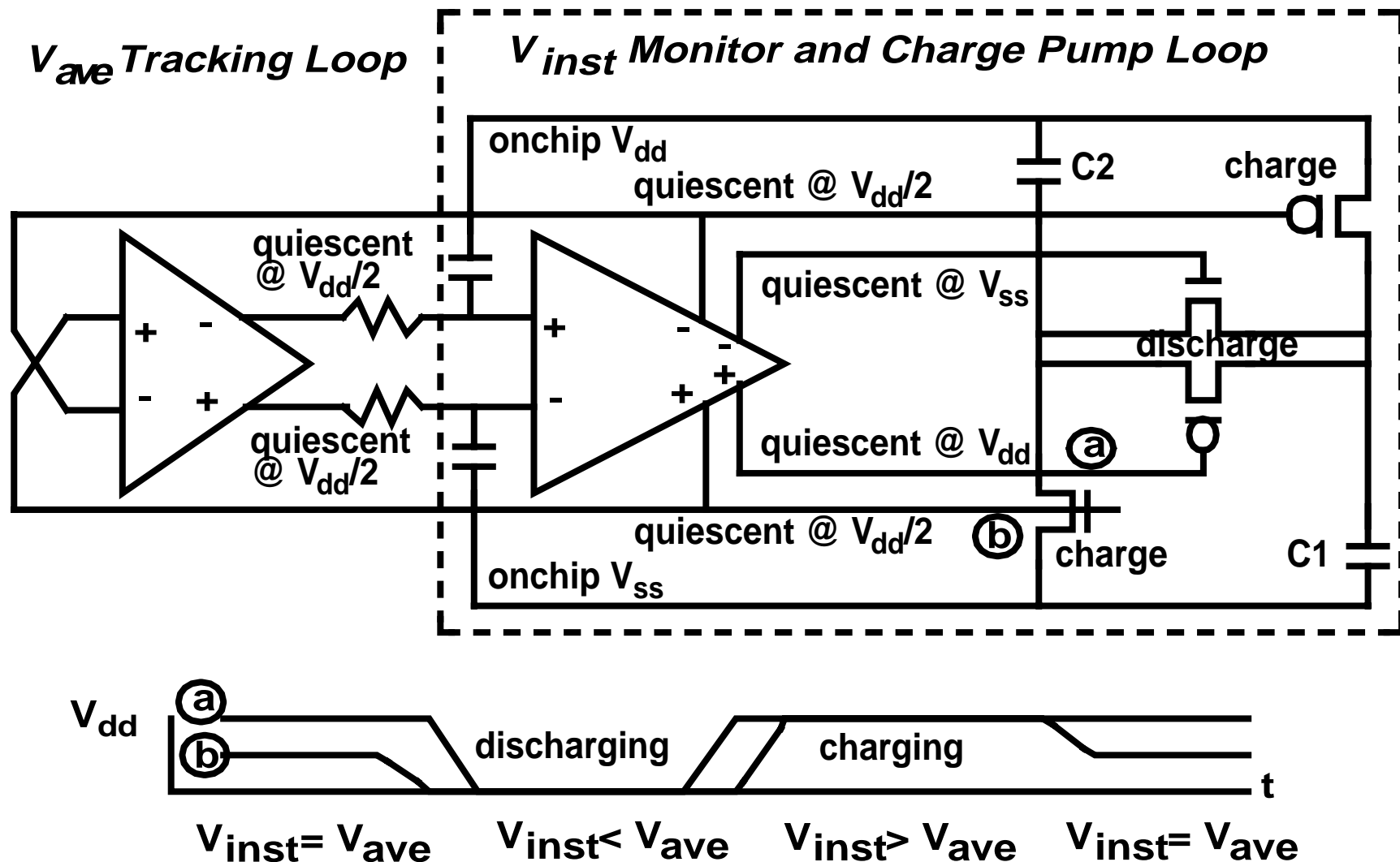
# On-Die Voltage Regulator

- Detect, and actively compensate for voltage swings in the target frequency range [4]:




## Results [4]

  

■ See paper for more details

 
# Higher Frequency Models

- Expand plane / via examples to derive a new model, with smaller 'lumps'
- Mid/high frequency
  - 3-D package/chip models
- Very high frequency
  - Small localized regions
  - 3-D chip model
  - Field solvers


 
# On-Chip Decoupling

- MOS capacitors provide on-die decoupling
  - Effectiveness is proportional to capacitor time constant - a long channel length will not decouple a signal rise time - a small channel length reduces area efficiency
- Distance to capacitor series parasitics
  - Set a guideline based on simulations
  - Scaling issue for process shrinks as rise times and parasitics scale



- Maximize on-die decoupling capacitance subject to yield/area constraints

# On-Chip Power Distribution Guidelines


- Checkerboard bump pattern
  - Close to switching circuits
  - Watch for electromigration
- Dense power-grid
  - Alternate  $V_{DD}/V_{SS}$
- Explore  $\mu$ architectural fix for clock-gating
  - Control ramp-rates of clock gating
- Circuit techniques are also effective
  - Lower the Q of the power supply network or reduce  $\Delta I$

# Off-Chip Power Delivery Guidelines


- Pay attention to the capacitor mounting and shorten the leads
- Place capacitors close to the chip
- Reduce spacing between planes
- Add more  $V_{DD}$ ,  $V_{SS}$  planes in an alternating pattern
- Sockets, vias, bump arrays
  - Use checkerboard patterns where possible
  - Use as many parallel paths as possible, without eating up the entire plane with anti-pads
 
# I/O Signaling


- Two separate paths to consider: power, signal return



**Package Cross-Section**

 



**Package Model**

 




  
# I/O Example

- How does signal return current get from board ( $V_{SS}$  only) to package ( $V_{DD}/V_{SS}$ )?



  - Package capacitors to reduce signal return impedance?



# High-Speed I/O Guidelines

## ■ Power Distribution Impedance

- Same guidelines as core power

## ■ Signal Return Impedance

- Maximize the power/ground pins in the chip, package, and connector pin-out (under cost constraint)
- Careful routing to avoid discontinuities
- Minimize the effects of discontinuities by providing an alternate return path (i.e. through a decoupling capacitor)

# Summary

- Several important aspects of delivering clean power
  - Supplying power across a broad frequency spectrum
  - Decoupling capacitor sizing and placement
  - I/O return current discontinuities and supply impedance
  - Solutions encompass board, package, chip
- Modeling concepts
  - Vias, bumps, pins, power planes, capacitors, and processor
- General guidelines for power distribution