

# ECE 255, Differential Amplifiers

2 November 2017

In this lecture, we study differential amplifiers. Because of the cancellation nature of the amplifier, it rejects unwanted noise, called common-mode noise, from the amplifier circuit.

For instance, in the previous lecture, we have studied discrete amplifiers where the input has only one terminal. As long as an input voltage is induced at the input terminal, there will be an output voltage at the amplifier output. But there are many remnant electric fields in our environment. These remnant electric fields are generated by other electronic/electrical devices not grounded or shielded properly. These undesirable electric fields appear as noise in the amplifier circuits.

One way to overcome this kind of environmental noise (also called electromagnetic interference (EMI) noise) is to operate amplifiers in pair. One amplifier is to receive only a positive signal, while the other amplifier is to receive only a negative signal. If these two amplifiers are balanced, then the environment noise can be canceled. These are called differential amplifiers as shall be studied.

## 1 The MOS Differential Pair

Figure 1 shows a basic MOS differential amplifier. The two transistor  $Q_1$  and  $Q_2$  are made to be as similar to each other as possible. The current source is assumed ideal with an infinite internal impedance. Two identical resistors  $R_D$  are connected to the drain terminals of the MOSFETs, and they are in the saturation regime of operation.

### 1.1 Common-Mode Input Voltage

In this mode, it is assumed that the input voltages to the MOSFETs are equal, namely, that the two gate voltages,  $v_{G1} = v_{G2} = V_{CM}$  where  $V_{CM}$  is the **common-mode voltage**, as shown in Figure 2. Since this circuit is completely symmetrical (an assumption), then  $i_{D1} = i_{D2} = I/2$ . Then the voltage at the source terminal, which is assumed to be identical for both transistors, is

$$V_S = V_{CM} - V_{GS} \quad (1.1)$$

---

*Printed on November 2, 2017 at 16:16: W.C. Chew and Z.H. Chen.*

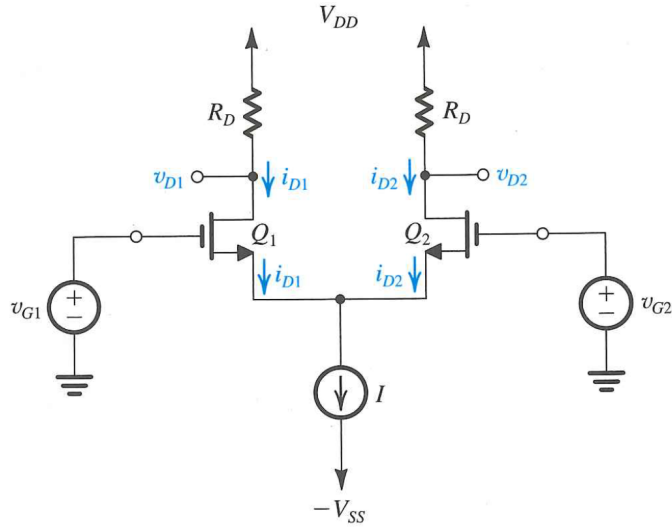


Figure 1: The basic MOSFET differential-pair amplifier configuration (Courtesy of Sedra and Smith).

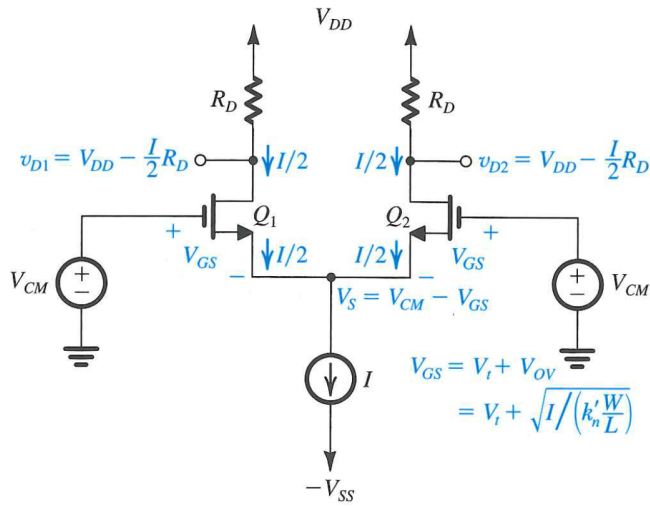


Figure 2: The common-mode operation of the MOSFET differential-pair amplifier configuration (Courtesy of Sedra and Smith).

Neglecting the channel-length modulation effect (Early effect), and that the transistors are in the saturation region, then

$$\frac{I}{2} = \frac{1}{2}k'_n \frac{W}{L}(V_{GS} - V_t)^2 = \frac{1}{2}k'_n \frac{W}{L}V_{OV}^2 \quad (1.2)$$

where the overdrive voltage is  $V_{OV}$  is also given by

$$V_{OV} = \sqrt{I/k'_n(W/L)} \quad (1.3)$$

The voltages at the drain terminals will be identical, namely,

$$v_{D1} = v_{D2} = V_{DD} - \frac{I}{2}R_D \quad (1.4)$$

Hence, there is no difference in the two voltages, and **the differential voltage** is zero. If the common-mode voltage  $V_{CM}$  is changed, by symmetry, the differential voltage output is always zero. Therefore, the differential amplifier rejects common-mode voltages.

To keep the transistors in saturation mode, we want  $V_{DS} > V_{OV}$ . But

$$V_{DS} = V_D - V_S = V_D - (V_{CM} - V_{GS}) = V_{DD} - \frac{I}{2}R_D - (V_{CM} - V_{GS}) > V_{OV} \quad (1.5)$$

Substituting that  $V_{OV} = V_{GS} - V_t$ , and moving  $V_{CM}$  to the right-hand side of the inequality, and  $V_t$  to the left-hand side, one gets

$$V_t + V_{DD} - \frac{I}{2}R_D > V_{CM} \quad (1.6)$$

Consequently,

$$V_{CM\max} = V_t + V_{DD} - \frac{I}{2}R_D \quad (1.7)$$

Next, if one assumes that a minimum voltage of  $V_{CS}$  is needed across the current source for its proper function, then the voltage across the current source, which is  $V_S + V_{SS}$  is such that

$$V_S + V_{SS} > V_{CS}, \text{ or } V_S > -V_{SS} + V_{CS} \quad (1.8)$$

From the above, one gets the inequality that

$$V_{CM} = V_G = V_S + V_{GS} = V_G = V_{CM} > -V_{SS} + V_{CS} + V_{GS} \quad (1.9)$$

Then one gets the bound that

$$V_{CM} \geq V_{CM\min} = -V_{SS} + V_{CS} + V_t + V_{OV} \quad (1.10)$$

where one has used  $V_{GS} = V_t + V_{OV}$ . Note that the value of  $V_{CM\min}$  can be a negative number because  $-V_{SS}$  can be a large negative number. Therefore, the common-mode range of operation is given by

$$V_{CM\min} \leq V_{CM} \leq V_{CM\max} \quad (1.11)$$

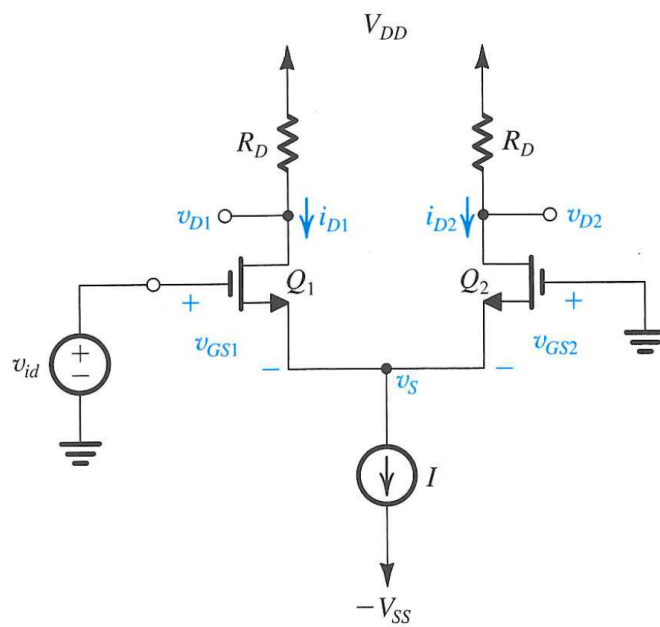


Figure 3: The MOSFET differential-pair amplifier with a differential input signal  $v_{id}$ . Without loss of generality, one can assume that  $V_{CM} = 0$  and hence, the gate of  $Q_2$  is grounded (Courtesy of Sedra and Smith).

 


Figure 4: A simplified picture of MOSFET differential-pair amplifier for deriving transfer characteristics (Courtesy of Sedra and Smith).

## 1.2 Differential Input Voltage

The differential voltage input can be set up by assuming that one of the gate voltages is zero without loss of generality. For instance, one sets  $v_{G2} = 0$ , and apply a small voltage  $v_{id}$  to the gate of  $Q_1$ , as shown in Figure 3. This is because the dynamic range of  $V_{CM}$  ranges from a negative value to a positive value. Within this dynamic range, the transistors are in saturation mode, and hence, their  $i$ - $v$  characteristics remain the same, by ignoring the Early effect. This is the same as setting  $V_{CM}$  to zero, where the common-mode output will still be zero.

Hence, any voltage output at this point is due to the imbalance of the amplifier, or the non-zero value of  $v_{id}$ . Here,  $v_{id}$  is the **differential input signal**, and it invokes the **differential mode** of the differential amplifier.

A simplified picture of the differential pair amplifier is shown in Figure 4. As  $v_{id}$  is increased, one see that the imbalance will increase reaching a point where all the drain current will flow through  $Q_1$ . At this juncture, then

$$I = \frac{1}{2} k'_n \frac{W}{L} (v_{GS1} - V_t)^2 \quad (1.12)$$

Thus

$$v_{GS1} = V_t + \sqrt{2I/k'_n(W/L)} = V_t + \sqrt{2}V_{OV} \quad (1.13)$$

The above  $V_{OV}$  is a special overdrive voltage corresponding to when the transistor has a drain current of  $I/2$  as shown in (1.2). The entire current will be steered into  $Q_1$  is when

$$v_{id\max} = v_{GS1} + v_S = V_t + \sqrt{2}V_{OV} - V_t = \sqrt{2}V_{OV} \quad (1.14)$$

In the above, we assume that the transistor  $Q_2$  is completely turned off so that  $v_S = -V_t$ , with  $v_{G2} = 0$ . If  $v_{id}$  is further increase, then transistor  $Q_2$  is turned off even more, and  $v_{GS1}$  remains to be  $V_t + \sqrt{2}V_{OV}$  in order to produce the necessary drain current  $I$ , but with the additional voltage absorbed by  $Q_2$ .

The same thing happens when one sets  $v_{id}$  to be negative turning off  $Q_1$  and turning on  $Q_2$ . Alternatively, we can shift the common-mode voltage  $V_{CM}$  such that gate of  $Q_1$  is grounded and a small signal  $|v_{id}|$  is sent to the gate of  $Q_2$ . Therefore,

$$-\sqrt{2}V_{OV} \leq v_{id} \leq \sqrt{2}V_{OV} \quad (1.15)$$

where at the extreme ends, the drain current is flowing entirely in one transistor or the other one. The above defines the range for the differential mode operation of the differential amplifier. The transistors are assume to be in saturation mode.

### 1.3 Large Signal Operation

Next, one derives the large signal operation of the differential amplifier for two different drain current  $i_{D1}$  and  $i_{D2}$  when a differential voltage is applied at the gates, namely  $v_{id} = v_{G1} - v_{G2}$ .

To begin, assuming saturation-region operation, the drain currents for  $Q_1$  and  $Q_2$  are

$$i_{D1} = \frac{1}{2}k'_n \frac{W}{L}(v_{GS1} - V_t)^2, \quad i_{D2} = \frac{1}{2}k'_n \frac{W}{L}(v_{GS2} - V_t)^2 \quad (1.16)$$

Taking the square roots of these equations, one obtains

$$\sqrt{i_{D1}} = \sqrt{\frac{1}{2}k'_n \frac{W}{L}}(v_{GS1} - V_t), \quad \sqrt{i_{D2}} = \sqrt{\frac{1}{2}k'_n \frac{W}{L}}(v_{GS2} - V_t) \quad (1.17)$$

Taking the difference of these equations, and letting  $v_{GS1} - v_{GS2} = v_{G1} - v_{G2} = v_{id}$ , squaring the sum of the above equations, and assuming that  $i_{D1} + i_{D2} = I$ , one arrives at the following equation that

$$2\sqrt{i_{D1}i_{D2}} = I - \frac{1}{2}k'_n \frac{W}{L}v_{id}^2 \quad (1.18)$$

One can let  $i_{D2} = I - i_{D1}$  in the above, square the above equation, solve the ensuing quadratic equation to get

$$i_{D1} = \frac{I}{2} \pm \sqrt{k'_n \frac{W}{L}} I \left( \frac{v_{id}}{2} \right) \sqrt{1 - \frac{(v_{id}/2)^2}{I/k'_n \frac{W}{L}}} \quad (1.19)$$

One can have a sanity check to decide on which of the  $\pm$  should be taken in the above equation. For small-signal analysis, incrementing  $v_{id}$  will only increase  $i_{D1}$ ; hence, only the  $+$  sign is acceptable above. The physical answer is

$$i_{D1} = \frac{I}{2} + \sqrt{k'_n \frac{W}{L}} I \left( \frac{v_{id}}{2} \right) \sqrt{1 - \frac{(v_{id}/2)^2}{I/k'_n \frac{W}{L}}} \quad (1.20)$$

The corresponding value of  $i_{D2} = I - i_{D1}$  yielding

$$i_{D2} = \frac{I}{2} - \sqrt{k'_n \frac{W}{L}} I \left( \frac{v_{id}}{2} \right) \sqrt{1 - \frac{(v_{id}/2)^2}{I/k'_n \frac{W}{L}}} \quad (1.21)$$

Again, as a check, the common-mode result should be obtained when  $v_{id} = 0$ , leading to

$$i_{D1} = i_{D2} = \frac{I}{2}, \quad v_{GS1} = v_{GS2} = V_{GS} \quad (1.22)$$

where this particular  $I/2$  is the common-mode  $I/2$  given by

$$\frac{I}{2} = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2 = \frac{1}{2} k'_n \frac{W}{L} V_{OV}^2 \quad (1.23)$$

From the above, one notes that  $I/V_{OV}^2$  can be used to eliminate  $k'_n(W/L)$ , and the above equations in (1.20) and (1.21) can be rewritten as

$$i_{D1} = \frac{I}{2} + \left( \frac{I}{V_{OV}} \right) \left( \frac{v_{id}}{2} \right) \sqrt{1 - \left( \frac{v_{id}/2}{V_{OV}} \right)^2} \quad (1.24)$$

$$i_{D2} = \frac{I}{2} - \left( \frac{I}{V_{OV}} \right) \left( \frac{v_{id}}{2} \right) \sqrt{1 - \left( \frac{v_{id}/2}{V_{OV}} \right)^2} \quad (1.25)$$

Notice that in the above, the relationship between the drain current and the differential voltage input is nonlinear. The normalized plots of  $i_{Di}/I$ ,  $i = 1, 2$ , versus  $v_{id}/V_{OV}$  are shown in Figure 5. These plots express the salient feature of a differential pair MOS amplifiers. When the differential input signal is small, the differential amplifier displays linear behavior but not when the input signal is large.

Assuming small signals, one can arrive at the following linearization approximations, namely,

$$i_{D1} \approx \frac{I}{2} + \frac{I}{V_{OV}} \frac{v_{id}}{2}, \quad i_{D2} \approx \frac{I}{2} - \frac{I}{V_{OV}} \frac{v_{id}}{2} \quad (1.26)$$

In other words, there is a small differential current that is proportional to the differential voltage input  $v_{id}$ , i.e.,

$$i_d = \frac{I}{V_{OV}} \frac{v_{id}}{2} \quad (1.27)$$

Figure 6 shows the dependence of the  $i$ - $v$  plots of the differential amplifier for different  $V_{OV}$ . A larger  $V_{OV}$  is seen to improve the linearity of the amplifier at the expense of reducing the gain. When the transistor is in saturation mode, the drain current is related to the overdrive voltage by

$$I_D = \frac{1}{2} k'_n \frac{W}{L} V_{OV}^2 \quad (1.28)$$

 


Figure 5: Normalized plots of the currents in a MOSFET differential-pair amplifier. The  $V_{OV}$  here is the overdrive voltage when the drain current is  $I/2$  (Courtesy of Sedra and Smith).

 


Figure 6: Similar plots to Figure 5 showing their dependence on  $V_{OV}$ . Enlarging  $V_{OV}$  makes the problem more linear (Courtesy of Sedra and Smith).



To maintain the same drain current, the overdrive voltage  $V_{OV}$  can be increased by decreasing  $W/L$ . Since the transconductance is given by

$$g_m = \sqrt{2k'_n(W/L)I_D} \quad (1.29)$$

decreasing  $W/L$  will decrease the transconductance lowering the gain of the amplifier.