

# ECE 255, Differential Amplifiers, Cont.

9 November 2017

In this lecture, we will focus on the common-mode rejection of differential amplifiers.

## 1 Common-Mode Rejection

For a perfectly matched differential amplifier, the common-mode signals are exactly canceled out. We will study the case when the design of the amplifier is not completely symmetrical or matched, and how the imperfections will influence the common-mode rejection.

### 1.1 The MOS Case

As shown in Figure 1, for small signal analysis, we can replace the voltage source with short circuits in the analysis, and assume a small  $v_{icm}$  on top the the background common-mode voltage  $V_{CM}$ . Using the equivalent circuit model, it is seen that

$$v_{icm} = \frac{i}{g_m} + 2iR_{SS}, \text{ or } i = \frac{v_{icm}}{1/g_m + 2R_{SS}} \quad (1.1)$$

We can next find that

$$v_{o1} = v_{o2} = -R_D i = -\frac{R_D}{1/g_m + 2R_{SS}} v_{icm} \approx -\frac{R_D}{2R_{SS}} v_{icm} \quad (1.2)$$

where  $2R_{SS} \gg 1/g_m$  has been assumed.

#### 1.1.1 Effect of Mismatch

The critical thing to study here is that if the two  $R_D$ 's are mismatched, namely, the load of  $Q_1$  is  $R_D$  while that of  $Q_2$  is  $R_D + \Delta R_D$ . Then following the above analysis,

$$v_{o1} \approx -\frac{R_D}{2R_{SS}} v_{icm}, \text{ and } v_{o2} \approx -\frac{R_D + \Delta R_D}{2R_{SS}} v_{icm} \quad (1.3)$$

---

*Printed on November 28, 2017 at 15:34: W.C. Chew and Z.H. Chen.*

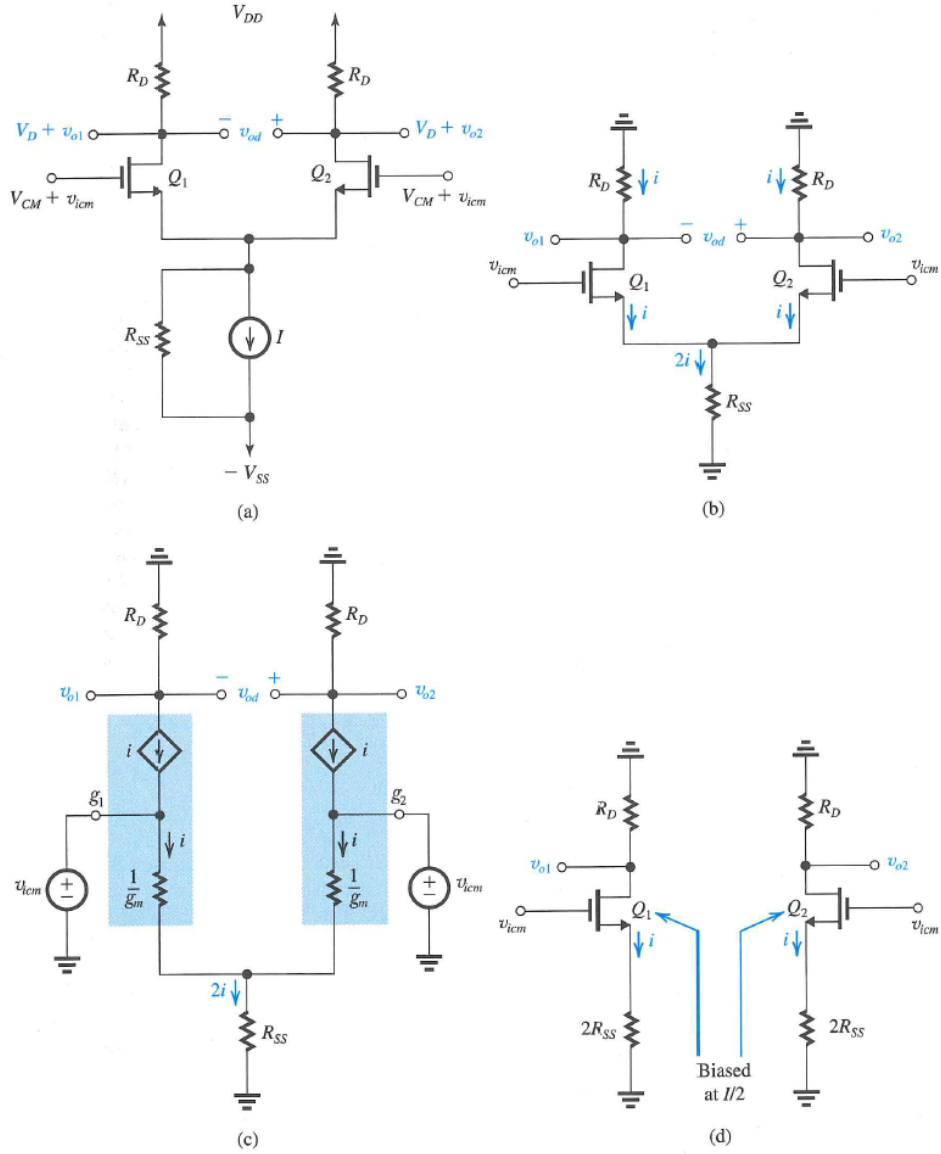


Figure 1: Small-signal analysis of the MOS differential amplifier: (a) The circuit with DC biases in place. (b) The small-signal circuit of the differential amplifier with DC biased removed. (c) The T-model equivalent circuit of the differential amplifier (Courtesy of Sedra and Smith).

Thus the differential voltage output now, due to a small common mode signal,  $v_{icm}$ , is

$$v_{od} = v_{o2} - v_{o1} = -\frac{\Delta R_D}{2R_{SS}} v_{icm} \quad (1.4)$$

The **common-mode gain** due to this imperfection is then

$$A_{cm} = \frac{v_{od}}{v_{icm}} = -\frac{\Delta R_D}{2R_{SS}} = -\left(\frac{R_D}{2R_{SS}}\right) \left(\frac{\Delta R_D}{R_D}\right) \quad (1.5)$$

The desirable signal is the output of the differential signal, while the undesirable signal is the output of the common-mode disturbance. The term **common-mode rejection ratio (CMRR)** is defined as

$$\text{CMRR} = \frac{|A_d|}{|A_{cm}|} \quad (1.6)$$

and when expressed in decibel, it is

$$\text{CMRR(dB)} = 20 \log_{10} \frac{|A_d|}{|A_{cm}|} \quad (1.7)$$

Recall that the differential mode voltage gain is  $g_m R_D$ , then the common-mode rejection ratio can be written as

$$\text{CMRR} = (2g_m R_{SS}) \left/ \left(\frac{\Delta R_D}{R_D}\right)\right. \quad (1.8)$$

It is seen that a source with large  $R_{SS}$  will increase this ratio, as well as a design with small  $\Delta R_D$  or small mismatched.

### 1.1.2 Effect of $g_m$ Mismatch on CMRR

If the transconductance of the two transistors are not matched, it can be shown that the gain for the common-mode disturbance is

$$A_{cm} \approx \left(\frac{R_D}{2R_{SS}}\right) \left(\frac{\Delta g_m}{g_m}\right) \quad (1.9)$$

and the corresponding CMRR will be

$$\text{CMRR} = (2g_m R_{SS}) \left/ \left(\frac{\Delta g_m}{g_m}\right)\right. \quad (1.10)$$

## 1.2 The BJT Case

The BJT differential amplifier is shown in Figure 2. It can be shown that

$$v_{o1} = v_{o2} = -\frac{\alpha R_C}{r_e + 2R_{EE}} v_{icm} \quad (1.11)$$

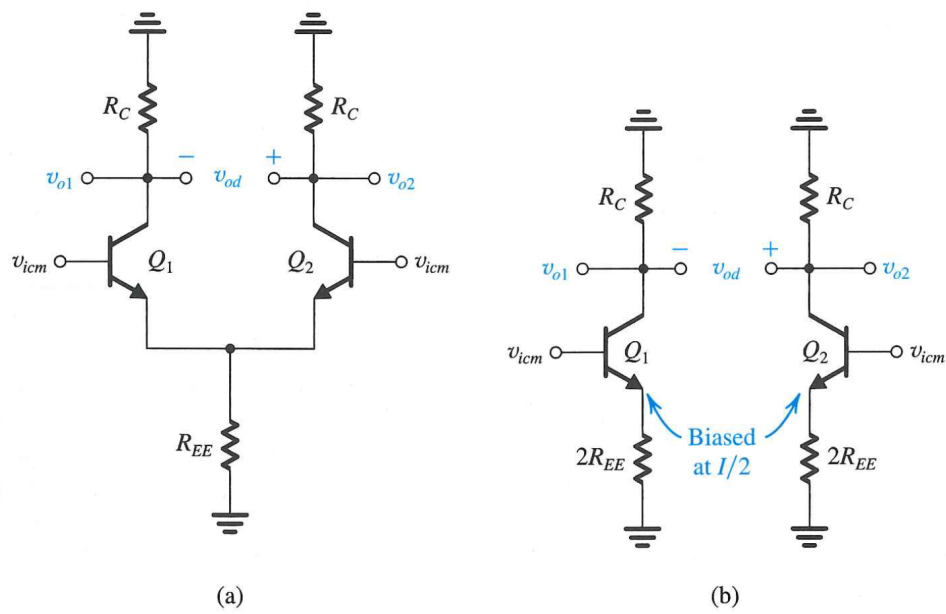


Figure 2: Small-signal analysis of the MOS differential amplifier: (a) The circuit with DC biases in place. (b) The small-signal circuit of the differential amplifier with DC biases removed. (c) The T-model equivalent circuit of the differential amplifier (Courtesy of Sedra and Smith).

Hence, the common mode signal is completely rejected when a differential signal is taken at the output. However, when the two circuits are not perfectly matched, for instance, having a slightly mismatched  $R_C$ , then the differential output is not zero, and one gets

$$A_{cm} = \frac{v_{od}}{v_{icm}} = -\frac{\alpha \Delta R_C}{2R_{EE} + r_e} \quad (1.12)$$

With  $\alpha \approx 1$ , the above becomes

$$A_{cm} \approx -\left(\frac{R_C}{2R_{EE}}\right) \left(\frac{\Delta R_C}{R_C}\right) \quad (1.13)$$

Using the fact that the differential gain is

$$A_d = \frac{\alpha(2R_C)}{2r_e + 2R_{EE}} \approx \frac{R_C}{R_{EE}} \quad (1.14)$$

then the CMRR is<sup>1</sup>

$$\text{CMRR} = 2 / \left(\frac{\Delta R_C}{R_C}\right) \quad (1.15)$$

## 2 Making Sense out of Formulas

Since there are numerous formulas to remember for this course, it may be taxing for your memory bank. Hence, it is best to distill the knowledge in these formulas and look at them from a different light. Often time, with a new look angle, one can cut through the chaste, and arrive at these formulas using the back-of-the-envelope calculations.

The formula for transconductance,  $g_m = \frac{I_C}{V_T}$ , is derived by perturbation expansion. We shall not question its deeper physical meaning. However, the other formulas in Table 7.3 can be derived quite easily. For instance, the formula

$$r_\pi = \frac{\beta}{g_m} \quad (2.1)$$

can be gotten by comparing the controlled current sources in the two hybrid- $\pi$  models in the Table. The equivalence of the models imply that

$$\beta i_b = g_m v_\pi \quad (2.2)$$

Dividing the above  $i_b$ , and using the definition that  $r_\pi = \frac{v_\pi}{i_b}$ , we get formula in (2.1).

To get the formula

$$r_e = \frac{\alpha}{g_m} \quad (2.3)$$

---

<sup>1</sup>There seems to be an error with the textbook formula (9.95).

we compare the current sources in the T models. From this comparison, one gets

$$g_m v_\pi = \alpha i \quad (2.4)$$

but from the figures,  $v_\pi/i = r_e$ , and hence, we get formula (2.3).

With these basic formulas, the derivation of the other formulas are quite straightforward. For instance, using the previous two formulas, one can show that


$$r_\pi = (\beta + 1)r_e \quad (2.5)$$

On the other hand, the above is just the resistance reflection formula for the input impedance when the T model is used, or one can get it by comparing the input impedance of the hybrid- $\pi$  model and the T model.


**Table 7.3** Small-Signal Models of the BJT

Hybrid- $\pi$  Model

■ ( $g_m v_\pi$ ) Version

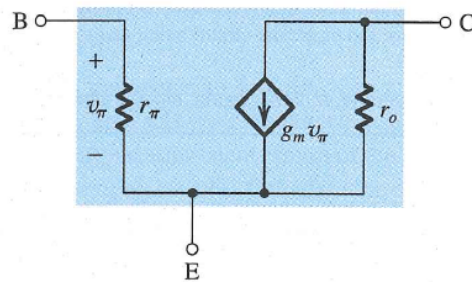


■ ( $\beta i_b$ ) Version

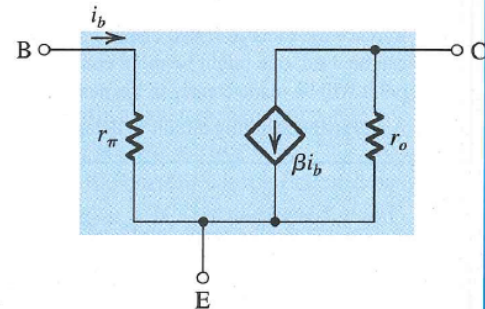


T Model

■ ( $g_m v_\pi$ ) Version

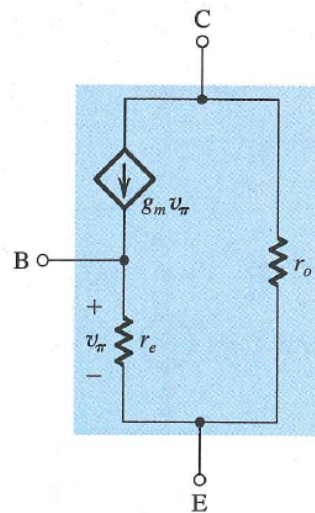

■ ( $\alpha i$ ) Version

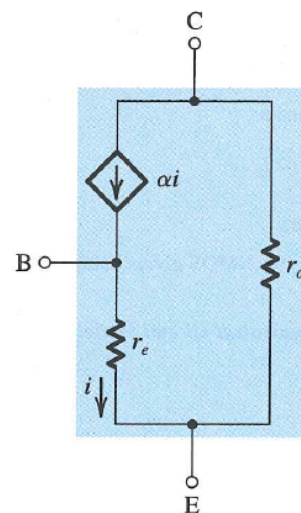

Model Parameters in Terms of DC Bias Currents

$$g_m = \frac{I_C}{V_T} \quad r_e = \frac{V_T}{I_E} = \alpha \frac{V_T}{I_C} \quad r_\pi = \frac{V_T}{I_B} = \beta \frac{V_T}{I_C} \quad r_o = \frac{|V_A|}{I_C}$$

In Terms of  $g_m$

$$r_e = \frac{\alpha}{g_m} \quad r_\pi = \frac{\beta}{g_m}$$

In Terms of  $r_e$

$$g_m = \frac{\alpha}{r_e} \quad r_\pi = (\beta + 1)r_e \quad g_m + \frac{1}{r_\pi} = \frac{1}{r_e}$$

Relationships between  $\alpha$  and  $\beta$

$$\beta = \frac{\alpha}{1 - \alpha} \quad \alpha = \frac{\beta}{\beta + 1} \quad \beta + 1 = \frac{1}{1 - \alpha}$$

The formulas in Table 7.5 can also be easily derived. The formulas in the first row of Table 7.5, corresponding to the common emitter case, can be easily derived, except for the last formula in the row for  $G_v$ . The last formula for  $G_v$  is always equal to the voltage divider formula times  $A_v$ , namely, that

$$G_v = \frac{R_{\text{in}}}{R_{\text{sig}} + R_{\text{in}}} A_v \quad (2.6)$$

With a little bit of manipulation, one gets to the last formula in the first row.

For the second row, the common-emitter case with an emitter resistor  $R_e$ , then part of the input voltage  $v_i$  is shared by  $R_e$ . The formula for  $A_{vo}$  in this row is an approximation. Before the approximation, the exact formula is

$$A_{vo} = \frac{v_o}{v_i} = -\frac{i_c R_C}{v_i} = -\frac{\alpha i_e R_C}{v_i} = -\frac{\alpha R_C}{r_e + R_e} \quad (2.7)$$

where one has used the formula that  $i_e = v_i/(r_e + R_e)$  in the last equality. This equation clearly shows that  $R_e$  reduces the emitter current because only a fraction of  $v_i$  is applied across  $v_{be}$  or  $v_\pi$ . The factor in the above

$$\frac{\alpha}{r_e + R_e} = \frac{g_m}{1 + R_e/r_e} \approx \frac{g_m}{1 + g_m R_e} \quad (2.8)$$

as is seen in the formula above.

Using the voltage divider formula to convert  $v_{\text{sig}}$  to  $v_i$ , one can always get the formulas in the last column on the right. Namely,

$$\frac{v_i}{v_{\text{sig}}} = \frac{R_{\text{in}}}{R_{\text{sig}} + R_{\text{in}}} \quad (2.9)$$

and hence,

$$G_v = \frac{v_o}{v_{\text{sig}}} = \frac{v_i}{v_{\text{sig}}} \frac{v_o}{v_i} = \frac{R_{\text{in}}}{R_{\text{sig}} + R_{\text{in}}} A_v \quad (2.10)$$

With

$$A_v = -\alpha \frac{R_C \parallel R_L}{r_e + R_e} \quad (2.11)$$

and  $R_{\text{in}} = (\beta + 1)(r_e + R_e)$ , and substituting into the above, one gets

$$G_v = -\beta \frac{R_C \parallel R_L}{R_{\text{sig}} + (\beta + 1)(r_e + R_e)} \quad (2.12)$$

the formula we have in the right most column of the second row of the table.



**Table 7.5** Characteristics of BJT Amplifiers<sup>a,b</sup>

	$R_{in}$	$A_{vo}$	$R_o$	$A_v$	$G_v$
Common emitter (Fig. 7.36)	$(\beta + 1)r_e$	$-g_m R_C$	$R_C$	$-g_m(R_C \parallel R_L)$ $-\alpha \frac{R_C \parallel R_L}{r_e}$	$-\beta \frac{R_C \parallel R_L}{R_{sig} + (\beta + 1)r_e}$
Common emitter with $R_e$ (Fig. 7.38)	$(\beta + 1)(r_e + R_e)$	$-\frac{g_m R_C}{1 + g_m R_e}$	$R_C$	$\frac{-g_m(R_C \parallel R_L)}{1 + g_m R_e}$ $-\alpha \frac{R_C \parallel R_L}{r_e + R_e}$	$-\beta \frac{R_C \parallel R_L}{R_{sig} + (\beta + 1)(r_e + R_e)}$
Common base (Fig. 7.40)	$r_e$	$g_m R_C$	$R_C$	$g_m(R_C \parallel R_L)$ $\alpha \frac{R_C \parallel R_L}{r_e}$	$\alpha \frac{R_C \parallel R_L}{R_{sig} + r_e}$
Emitter follower (Fig. 7.43)	$(\beta + 1)(r_e + R_L)$	1	$r_e$	$\frac{R_L}{R_L + r_e}$	$\frac{R_L}{R_L + r_e + R_{sig}/(\beta + 1)}$ $G_{vo} = 1$ $R_{out} = r_e + \frac{R_{sig}}{\beta + 1}$

<sup>a</sup> For the interpretation of  $R_{in}$ ,  $A_{vo}$ , and  $R_o$  refer to Fig. 7.34.

<sup>b</sup> Setting  $\beta = \infty$  ( $\alpha = 1$ ) and replacing  $r_e$  with  $1/g_m$ ,  $R_C$  with  $R_D$ , and  $R_e$  with  $R_s$  results in the corresponding formulas for MOSFET amplifiers (Table 7.4).

The same thing can be said of the MOSFET case. In this case,  $\alpha = 1$  and  $r_e = 1/g_m$ . With these concepts in mind, these formulas can be derived easily and quickly.

Table 7.4 Characteristics of MOSFET Amplifiers					
Amplifier type	Characteristics <sup>a</sup>				
	$R_{in}$	$A_{vo}$	$R_o$	$A_v$	$G_v$
Common source (Fig. 7.35)	$\infty$	$-g_m R_D$	$R_D$	$-g_m (R_D \parallel R_L)$	$-g_m (R_D \parallel R_L)$
Common source with $R_s$ (Fig. 7.37)	$\infty$	$-\frac{g_m R_D}{1 + g_m R_s}$	$R_D$	$\frac{-g_m (R_D \parallel R_L)}{1 + g_m R_s}$ $-\frac{R_D \parallel R_L}{1/g_m + R_s}$	$-\frac{g_m (R_D \parallel R_L)}{1 + g_m R_s}$ $-\frac{R_D \parallel R_L}{1/g_m + R_s}$
Common gate (Fig. 7.39)	$\frac{1}{g_m}$	$g_m R_D$	$R_D$	$g_m (R_D \parallel R_L)$	$\frac{R_D \parallel R_L}{R_{sig} + 1/g_m}$
Source follower (Fig. 7.42)	$\infty$	1	$\frac{1}{g_m}$	$\frac{R_L}{R_L + 1/g_m}$	$\frac{R_L}{R_L + 1/g_m}$

<sup>a</sup> For the interpretation of  $R_{in}$ ,  $A_{vo}$ , and  $R_o$ , refer to Fig. 7.34(b).