

ECE 255

24 October 2017

In this lecture, we will introduce small-signal analysis, operation, and models from Section 7.2 of Sedra and Smith. Since the BJT case has been discussed, we will now focus on the MOSFET case. In the small-signal analysis, one assumes that the device is biased at a DC operating point (also called the Q point or the quiescent point), and then, a small signal is super-imposed on the DC biasing point.

1 The DC Bias Point and Linearization—The MOSFET Case

Before one starts, it will be prudent to refresh our memory on the salient features of the MOSFET from Table 5.1 of Sedra and Smith. Also, Figure 1 is included to remind one of the definition of the relationship between V_{GS} , V_{OV} , V_{GD} , and V_{DS} . When $V_{DS} > V_{OV}$, the channel region is not continuous, and pinching occurs. The device is in the saturation region.

Printed on October 24, 2017 at 15:51: W.C. Chew and Z.H. Chen.

Table 5.1 Regions of Operation of the Enhancement NMOS Transistor

 


Figure 2 illustrates an NMOS operating as an amplifier. It is being biased with a DC voltage, and a small signal is superimposed on top of the DC voltage.

Before proceeding further, one is also reminded of the i - v characteristics of a MOSFET. Namely, that in the saturation region

$$i_D = \frac{1}{2} k_n (v_{GS} - V_t)^2 = \frac{1}{2} k_n v_{OV}^2 \quad (1.1)$$

where

$$v_{GS} = V_{GS} + v_{gs}, \quad v_{OV} = V_{OV} + v_{ov} \quad (1.2)$$

 


Figure 1: A figure to remind us of the definition of v_{GS} , v_{OV} , v_{DS} , and v_{GD} (Courtesy of Sedra and Smith).

 


Figure 2: Circuit diagram of a transistor MOSFET (NMOS) amplifier with a small time-varying signal superimposed on top of a DC voltage bias source (Courtesy of Sedra and Smith).

where $v_{OV} = v_{GS} - V_t$. Again, the notation will be that the total value is denoted by a lower-case letter with upper-case subscript, the DC value or the Q point is denoted by an upper-case letter with upper-case subscript. The small signal is denoted by a lower-case letter with lower-case subscript. However, the threshold voltage, which is a DC value is denoted as V_t in order not to be confused with V_T the thermal voltage.

It is noted that the overdrive voltage v_{OV} is defined as

$$v_{OV} = v_{GS} - V_t = V_{GS} + v_{gs} - V_t \quad (1.3)$$

If we further define that $v_{OV} = V_{OV} + v_{ov}$, equating the time varying and DC parts, one gets

$$V_{OV} = V_{GS} - V_t, \quad v_{ov} = v_{gs} \quad (1.4)$$

If the time-varying signals are turned off, then (1.1) becomes

$$I_D = \frac{1}{2}k_n(V_{GS} - V_t)^2 = \frac{1}{2}k_nV_{OV}^2 \quad (1.5)$$

the i - v relation obtained at the Q point, or the operating point.

In (1.1), by letting

$$v_{GS} = V_{GS} + v_{gs} \quad (1.6)$$

then

$$i_D = \frac{1}{2}k_n(V_{GS} + v_{gs} - V_t)^2 = \frac{1}{2}k_n(V_{GS} - V_t)^2 + k_n(V_{GS} - V_t)v_{gs} + \frac{1}{2}k_nv_{gs}^2 \quad (1.7)$$

For small signal analysis, v_{gs} is assumed to be small. Then v_{gs}^2 is even smaller; and hence, the last term can be ignored in the above. By letting $i_D = I_D + i_d$, a DC term plus a time-varying term, then from the above, one can see that the time-varying term is given by

$$i_d \approx k_n(V_{GS} - V_t)v_{gs} = g_m v_{gs} \quad (1.8)$$

where

$$g_m = k_n(V_{GS} - V_t) = k_nV_{OV} = \frac{i_d}{v_{gs}} = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}} \quad (1.9)$$

The above has the unit of conductance, and it is called the **MOSFET transconductance**. The last equality follows from that the transconductance is the ratio between two incrementally small quantities at the operating point. This incremental relationship is shown in Figure 3.

A more detail analysis by comparing the last two terms on the right-hand side, one can show that the last term can be ignored if

$$v_{gs} \ll 2(V_{GS} - V_t) = 2V_{OV} \quad (1.10)$$

Also, it is seen from the Figure 3 that in order for the small signal analysis to be valid, it is required that $v_{gs} \ll 2V_{OV}$.

 


Figure 3: Graphical depiction of the small signal analysis for MOSFET (Courtesy of Sedra and Smith).

Furthermore, it is seen that at the DC operating point, by KVL

$$V_{DS} = V_{DD} - R_D I_D \quad (1.11)$$

If V_{DD} is held fixed, then by KVL again

$$v_{DS} = V_{DD} - R_D i_D = V_{DD} - R_D (I_D + i_d) = V_{DD} - R_D I_D - R_D i_d \quad (1.12)$$

From the above, by equating the time-varying terms and the DC terms, one concludes that the time varying part of v_{DS} , or v_{ds} , is given by

$$v_{ds} = -i_d R_D = -g_m v_{gs} R_D \quad (1.13)$$

One can define a voltage gain as

$$A_v = \frac{v_{ds}}{v_{gs}} = -g_m R_D \quad (1.14)$$

The negative sign comes about because an increase in v_{gs} causes an increase in i_d , causing the rise in the voltage drop across R_D , and hence, a drop in the voltage v_{ds} . This sign reversal is indicated in Figure 4.

2 Small Signal Equivalent-Circuit Models

By looking at the i - v characteristic curve of the MOSFET as shown in Table 5.1, it is seen for incremental v_{ds} , the current i_d does not change. This relationship can be modeled by a current source. Moreover, the gate of the MOSFET is essentially an open circuit at DC. Hence, the **small-signal equivalent-circuit model** is presented in Figure 5(a).

When the Early effect has to be accounted for, an output resistor r_o can be added as shown in Figure 5(b). The value of r_o is given as

$$r_o = \frac{|V_A|}{I_D}, \text{ where } I_D = \frac{1}{2} k_n V_{OV}^2 \quad (2.1)$$

where $V_A = 1/\lambda$, and $-V_A$ is the negative intercept of the i - v curve.

Here, r_o is typically 10 k Ω to 1000 k Ω . When r_o is included, then the voltage gain becomes

$$A_v = \frac{v_{ds}}{v_{gs}} = -g_m (R_D || r_o) \quad (2.2)$$

In other words, the inclusion of r_o reduces the voltage gain.

The above analysis can be used for PMOS by noting for the sign change in PMOS, and by using $|V_{GS}|$, $|V_t|$, $|V_{OV}|$, and $|V_A|$ in the formulas, and replacing k_n with k_p .

 


Figure 4: Total instantaneous voltage v_{GS} and v_{DS} for the circuit in Figure 2. Note the sign reversal of the amplified signal (Courtesy of Sedra and Smith).

 


Figure 5: The small-signal model for a MOSFET: (a) no Early effect (channel-length modulation effect); (b) Early effect is included by adding $r_o = |V_A|/I_D$ (Courtesy of Sedra and Smith).

3 Transconductance g_m

The transconductance can be looked at with more details by using $k_n = k'_n(W/L)$, giving

$$g_m = k'_n(W/L)(V_{GS} - V_t) = k'_n(W/L)V_{OV} = \mu_n C_{ox}(W/L)V_{OV} \quad (3.1)$$

The transconductance can be increased by increasing the W/L ratio, and also increasing the overdrive voltage V_{OV} . But increasing V_{OV} implies that the operating point for V_{DS} has to increase in order for the MOSFET to be in the saturation region.

Also, by using the fact that

$$I_D = \frac{1}{2}k_n V_{OV}^2 = \frac{1}{2}k'_n(W/L)V_{OV}^2 \quad (3.2)$$

then g_m in (3.1) can be alternatively rewritten as

$$g_m = \sqrt{2k'_n(W/L)I_D} \quad (3.3)$$

implying that g_m is proportional to the square roots of the drain current I_D , and W/L . At this point, note that

1. The transconductance g_m of a MOSFET is geometry dependent whereas that of the BJT is not.
2. The transconductance of a BJT is much larger than that of a MOSFET.

For example, with biasing point of $I_D = 50$ mA, with $k'_n = 120 \mu\text{A}/\text{V}^2$, with $W/L = 1$, $g_m = 0.35$ mA/V, whereas when $W/L = 100$, $g_m = 3.5$ mA/V. But typically, the $g_m = 20$ mA/V for BJT when $I_C = 0.5$ mA.

 


Figure 6: The relationship between I_D , V_{OV} , and g_m as shown in the i_D versus v_{OV} curve (Courtesy of Sedra and Smith).

Alternatively, by letting $k'_n(W/L) = 2I_D/(V_{GS} - V_t)^2$, it can be shown that

$$g_m = \frac{2I_D}{V_{GS} - V_t} = \frac{2I_D}{V_{OV}} \quad (3.4)$$

Since g_m is an incremental relationship, this relationship can be shown graphically as in Figure 6.

The above equations indicate that a designer can change g_m by altering W/L , V_{OV} , and I_D .

4 The T Equivalent-Circuit Model

The hybrid- π equivalent-circuit model can be replaced by the T equivalent-circuit model. The morphing of a hybrid- π model to the T model is shown in Figure 7.

1. The current source in the hybrid- π model can be split into two without affecting the branch current. This is seen from the morphing of Figure 7(a) to Figure 7(b).
2. Note that the gate current is zero. The point X can be connected to the gate input, and yet the gate current is zero because of KCL at X. This is indicated in Figure 7(c).

 


Figure 7: The morphing of the hybrid- π equivalent circuit model in (a) to the T equivalent circuit model in (d) (Courtesy of Sedra and Smith).

3. But the second voltage-controlled current source is just the voltage and current relation in a resistor. Hence, it can be replaced by a resistor as shown in Figure 7(d).

Notice that in the T equivalent-circuit model, due to its construction, and KCL, the gate current is always zero, implying that its resistance is infinite.

Also as the morphing of the hybrid- π equivalent-circuit model to the T equivalent-circuit model is unaffected by connecting a resistor between D and S, an r_o can be thus connected to account for the Early effect or the channel-modulation effect as shown in Figure 8(a). Figure 8(b) is an alternative way of representing the T equivalent-circuit model, so that the gate current is always zero by KCL.

 


Figure 8: The morphing of the π equivalent-circuit model to the T equivalent circuit model is still valid if a resistor is connected between the drain D and the source S. Hence, in (a), r_o can be connected to account for the Early effect. (b) shows an alternative T model that is equivalent (Courtesy of Sedra and Smith).

Example 7.4

Figure 7.18(a) shows a MOSFET amplifier biased by a constant-current source I . Assume that the values of I and R_D are such that the MOSFET operates in the saturation region. The input signal v_i is coupled to the source terminal by utilizing a large capacitor C_{C1} . Similarly, the output signal at the drain is taken through a large coupling capacitor C_{C2} . Find the input resistance R_{in} and the voltage gain v_o/v_i . Neglect channel-length modulation.

 


Figure 7.18 (a) Amplifier circuit for Example 7.4. (b) Small-signal equivalent circuit of the amplifier in (a).

Solution

Replacing the MOSFET with its T equivalent-circuit model results in the amplifier equivalent circuit shown in Fig. 7.18(b). Observe that the dc current source I is replaced with an open circuit and the dc voltage source V_{DD} is replaced by a short circuit. The large coupling capacitors have been replaced by short circuits. From the equivalent-circuit model we determine

$$R_{in} = \frac{v_i}{-i} = 1/g_m$$

and

$$v_o = -iR_D = \left(\frac{v_i}{1/g_m} \right) R_D = g_m R_D v_i$$

Thus,

$$A_v \equiv \frac{v_o}{v_i} = g_m R_D$$

We note that this amplifier, known as the common-gate amplifier because the gate at ground potential is common to both the input and output ports, has a low input resistance ($1/g_m$) and a noninverting gain. We shall study this amplifier type in Section 7.3.5.

5 Common-Source (CS) Amplifier

The common-source amplifier for MOSFET is the analogue of the common-emitter amplifier for BJT.

5.1 Characteristic Parameters of the CS Amplifier

Figure 9(a) shows the small-signal model for the common-source amplifier. Here, R_D is considered part of the amplifier and is the resistance that one measures between the drain and the ground. Then

$$v_o = -g_m v_{gs} R_D \quad (5.1)$$

The small-signal model can be replaced by its hybrid- π model as shown in Figure 9(b). By inspection, one sees that

$$R_{in} = \infty, \quad v_i = v_{sig}, \quad v_{gs} = v_i \quad (5.2)$$

Thus the open-circuit voltage gain is

$$A_{vo} = \frac{v_o}{v_i} = -g_m R_D \quad (5.3)$$

Then from the equivalent-circuit model in Figure 9(b) and the test-current method,


$$R_o = R_D \quad (5.4)$$

If now, a load resistor, R_L is connected to the output across R_D , then the voltage gain proper (also called terminal voltage gain) is


$$A_v = A_{vo} \frac{R_L}{R_L + R_o} = -g_m \frac{R_D R_L}{R_L + R_D} = -g_m (R_D || R_L) \quad (5.5)$$

From the fact that $R_{in} = \infty$, then $v_i = v_{sig}$. The overall voltage gain is the same as the voltage gain proper, namely

$$G_v = \frac{v_o}{v_{sig}} = -g_m (R_D || R_L) \quad (5.6)$$

 

(a)

 

(b)

Figure 9: (a) Small-signal model for a common-source amplifier. (b) The hybrid- π model for the common-source amplifier (Courtesy of Sedra and Smith).