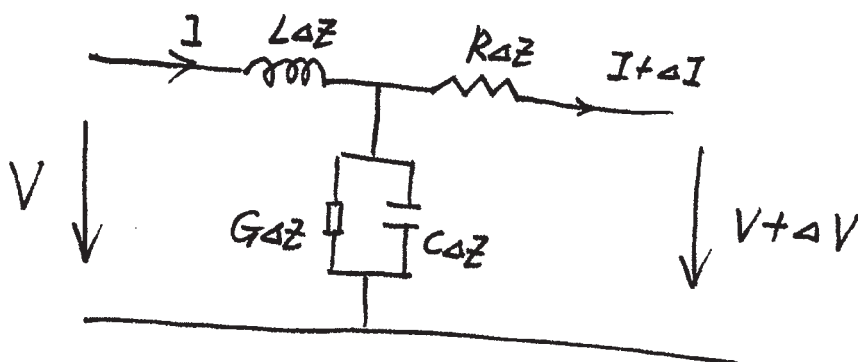


Chapter IV

Review of Transmission Line



Kirchhoff's voltage law:

$$V = j\omega L\Delta z I + R\Delta z (I + \Delta I) + V + \Delta V$$

$$\rightarrow \boxed{\frac{dV}{dz} + (j\omega L + R) I = 0}$$

$$I = G\Delta z V + j\omega C\Delta z V + I + \Delta I$$

$$\rightarrow \boxed{\frac{dI}{dz} + (j\omega C + G) V = 0}$$

$$\frac{d^2 V}{dz^2} + (j\omega L + R) \frac{dI}{dz} = 0$$

$$\frac{d^2 V}{dz^2} - (j\omega L + R)(j\omega C + G) V = 0$$

$$\boxed{\frac{d^2 V}{dz^2} - \gamma^2 V = 0} \quad \gamma^2 = (j\omega L + R)(j\omega C + G)$$

Consider a lossless line,

$$R=0, G=0 \Rightarrow \gamma = j\omega\sqrt{LC}$$

$$\text{or } \gamma = j\beta \quad \beta = \omega\sqrt{LC}$$

$$\frac{d^2 V}{dz^2} + \beta^2 V = 0$$

$$\Rightarrow V(z) = a_+ e^{-j\beta z} + a_- e^{j\beta z}$$

$$\text{Consider } V_+(z) = a_+ e^{-j\beta z}$$

$$\begin{aligned} V_+(z, t) &= \text{Re}[V_+(z) e^{j\omega t}] = \text{Re}[a_+ e^{j\omega t - j\beta z}] \\ &= |a_+| \cos(\omega t - \beta z + \angle a_+) \end{aligned}$$

Consider phase

$$\omega t - \beta z_p = \text{constant}$$

$$\omega - \beta \frac{dz_p}{dt} = 0 \Rightarrow \frac{dz_p}{dt} = \frac{\omega}{\beta} \leftarrow \begin{array}{l} \text{phase velocity} \\ \text{propagation constant} \end{array}$$

Hence. $e^{-j\beta z}$: wave traveling toward +z direction

Similarly, $e^{j\beta z}$: wave traveling toward $-z$ direction

Consider a lossy line:

$$\gamma = \sqrt{(j\omega L + R)(j\omega C + G)} = \alpha + j\beta$$

$$\frac{d^2 V}{dz^2} - \gamma^2 V = 0$$

$$\Rightarrow V(z) = a_+ e^{-\gamma z} + a_- e^{\gamma z}$$

$$\text{Consider } V_+(z) = a_+ e^{-\gamma z} = a_+ e^{-(\alpha + j\beta)z}$$

$$V_+(z, t) = \text{Re} [V_+(z) e^{j\omega t}]$$

$$= \text{Re} [a_+ e^{j\omega t - j\beta z - \alpha z}]$$

$$= |a_+| e^{-\alpha z} \cos(\omega t - \beta z + \angle a_+)$$

α : attenuation constant, β : propagation constant

$$V(z) = a_+ e^{-\gamma z} + a_- e^{\gamma z}$$

$$\text{Define } \Gamma = \frac{V(-l_0)}{V(+l_0)} = \frac{a_-}{a_+}$$

$$V(z) = a_+ e^{-\gamma z} + a_+ \Gamma e^{\gamma z}$$

$$\frac{dV}{dz} = -\gamma a_+ e^{-\gamma z} + \gamma a_+ \gamma e^{\gamma z}$$

$$= -(j\omega L + R)I$$

$$I(z) = \frac{\gamma}{j\omega L + R} a_+ e^{-\gamma z} - \frac{\gamma}{j\omega L + R} a_+ \gamma e^{\gamma z}$$

$$= \frac{\gamma}{j\omega L + R} a_+ (e^{-\gamma z} - \gamma e^{\gamma z})$$

Define the characteristic impedance

$$Z_0 = \frac{V_+}{I_+} = \frac{j\omega L + R}{\gamma} = \sqrt{\frac{j\omega L + R}{j\omega C + G}}$$

$$I(z) = \frac{1}{Z_0} a_+ (e^{-\gamma z} - \gamma e^{\gamma z})$$

Reflection coefficient:

$$P(z) = \frac{V_-(z)}{V_+(z)} = \frac{a_- e^{\gamma z}}{a_+ e^{-\gamma z}} = \gamma e^{2\gamma z}$$

$$P(z_1) = \gamma e^{2\gamma z_1}, \quad P(z_2) = \gamma e^{2\gamma z_2}$$

$$\Rightarrow \boxed{P(z_1) = P(z_2) e^{2\gamma(z_1 - z_2)}}$$

- Review of Transmission Line (continued)

Interested Readers

- Chapter 5, textbook

(43)

Impedance at z :

$$Z(z) = \frac{V(z)}{I(z)} = \frac{a_+ e^{-\gamma z} + a_+ \Gamma e^{\gamma z}}{\frac{1}{Z_0} a_+ (e^{-\gamma z} - \Gamma e^{\gamma z})}$$

$$= Z_0 \frac{1 + \Gamma e^{2\gamma z}}{1 - \Gamma e^{2\gamma z}} = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

$$\Gamma(z) = \frac{Z(z) - Z_0}{Z(z) + Z_0}$$


$$Z(z) = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

Note that:

1. Z_0 is independent of z
2. $Z(z)$ depends on z
3. $\Gamma(z)$ depends on z
4. For a lossless line, $\gamma = j\beta$
 $|\Gamma(z)| = |\Gamma e^{2j\beta z}| = |\Gamma|$ is invariant along z .

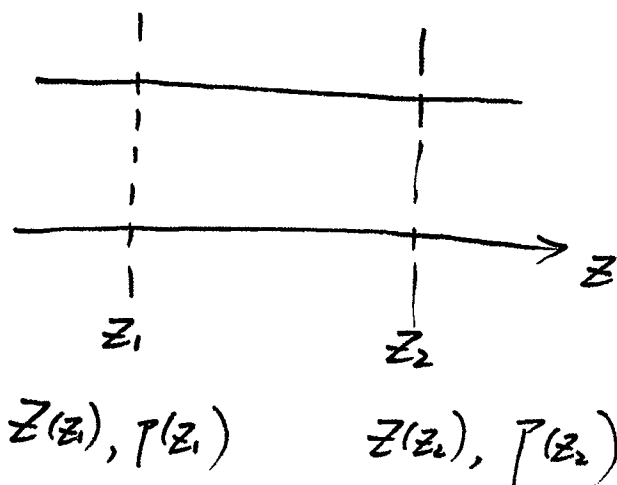(44)

Given information at z_1 , find information at z_2 :



$$\Gamma(z) = \Gamma e^{2\gamma z} \Rightarrow \Gamma(z_2) = \Gamma(z_1) e^{2\gamma(z_2 - z_1)}$$

$$V(z_2) = a_+ e^{-\gamma z_2} + \Gamma a_+ e^{\gamma z_2}$$

$$= a_+ e^{-\gamma z_2} (1 + \Gamma e^{2\gamma z_2})$$

$$= a_+ e^{-\gamma z_2} (1 + \Gamma(z_2))$$

$$I(z_2) = \frac{1}{z_0} a_+ (e^{-\gamma z_2} - \Gamma e^{\gamma z_2}) = \frac{1}{z_0} a_+ e^{-\gamma z_2} (1 - \Gamma e^{2\gamma z_2})$$

$$= \frac{1}{z_0} a_+ e^{-\gamma z_2} (1 - \Gamma(z_2))$$

$$Z(z_2) = \frac{V(z_2)}{I(z_2)} = z_0 \frac{1 + \Gamma(z_2)}{1 - \Gamma(z_2)}$$

$$= z_0 \frac{1 + \Gamma(z_1) e^{2\gamma(z_2 - z_1)}}{1 - \Gamma(z_1) e^{2\gamma(z_2 - z_1)}}$$

(45)

Since

$$Z(z_1) = Z_0 \frac{1 + \Gamma(z_1)}{1 - \Gamma(z_1)} \Rightarrow \Gamma(z_1) = \frac{Z(z_1) - Z_0}{Z(z_1) + Z_0}$$

$$Z(z_2) = Z_0 \frac{1 + \frac{Z(z_1) - Z_0}{Z(z_1) + Z_0} e^{2\gamma(z_2 - z_1)}}{1 - \frac{Z(z_1) - Z_0}{Z(z_1) + Z_0} e^{2\gamma(z_2 - z_1)}}$$

$$= Z_0 \frac{Z_1 + Z_0 + (Z_1 - Z_0)e^{2\gamma(z_2 - z_1)}}{Z_1 + Z_0 - (Z_1 - Z_0)e^{2\gamma(z_2 - z_1)}}$$

$$= Z_0 \frac{Z_1(e^{\gamma l} + e^{-\gamma l}) - Z_0(e^{\gamma l} - e^{-\gamma l})}{Z_1(e^{-\gamma l} - e^{\gamma l}) + Z_0(e^{\gamma l} + e^{-\gamma l})}$$

$$Z(z_2) = Z_0 \frac{Z_1 \cosh \gamma l - Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l - Z_1 \sinh \gamma l}$$

For a lossless line, $\gamma = j\beta$

$$Z_2 = Z_0 \frac{Z_1 \cos \beta l - j Z_0 \sin \beta l}{Z_0 \cos \beta l - j Z_1 \sin \beta l}$$

$$Z_1 = Z_0 \frac{Z_2 \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_2 \sin \beta l}$$



$$Z_{in} = Z_0 \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l}$$

If $Z_L = 0$, $Z_{in} = j Z_0 \tan \beta l$

If $Z_L = \infty$, $Z_{in} = -j Z_0 \cot \beta l$