

Terminated Transmission Lines

For an infinitely long transmission line, the solution consists of the linear superposition of a wave travelling to the right plus a wave travelling to the left. If the transmission line is terminated by a load as shown in the figure, a right-travelling wave will be reflected by the load, and in general, the wave on the transmission line will be

$$V(z) = a_+ e^{-\gamma z} + a_- e^{\gamma z} = V_+(z) + \underbrace{V_-(z)}_{\text{left-going}} \quad (1)$$

At $z=0$, we can define the amplitude of the reflected wave a_- to be related to the amplitude of the right-going or incident wave. In other words, at $z=0$,

$$a_- = \Gamma_L a_+ \quad (2)$$

where Γ_L is the reflection coefficient. Hence,

$$V(z) = a_+ e^{-\gamma z} + \Gamma_L a_+ e^{\gamma z} = a_+ (e^{-\gamma z} + \Gamma_L e^{\gamma z}) \quad (3)$$

The corresponding current $I(z)$ on the transmission line is given by

$$I(z) = -\frac{1}{Z_0} \frac{dV}{dz} = -\frac{a_+}{Z_0} \gamma (e^{-\gamma z} - \Gamma_L e^{\gamma z}) \quad (4)$$

where $\gamma = \sqrt{(j\omega L + R)(j\omega C + G)}$, and $Z_0 = j\omega L + R$.

Hence, $Z/\gamma = \sqrt{Z/\gamma} = Z_0$, and

$$I(z) = \frac{a_+}{Z_0} (e^{-\gamma z} - \Gamma_L e^{\gamma z}) \quad (5)$$

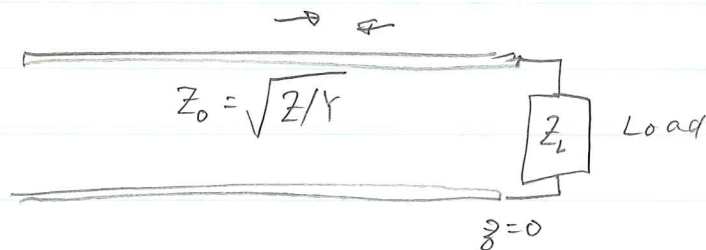


Fig. 1.

A general reflection coefficient ^{at z} can be derived such that

$$\Gamma(z) = \frac{V_-(z)}{V_+(z)} = \frac{a_- e^{\gamma z}}{a_+ e^{-\gamma z}} = \Gamma_L e^{2\gamma z} \quad (6)$$

Of course, $\Gamma(z=0) = \Gamma_L$. Furthermore, we must have

$$\frac{V(z=0)}{I(z=0)} = Z_L \quad (7)$$

or that using (3) and (4) with $z=0$, we have

$$\frac{1 + \Gamma_L}{1 - \Gamma_L} Z_0 = Z_L \quad (8)$$

From the above,

$$\Gamma_L = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (9)$$

$\Gamma_L = 0$ if $Z_L = Z_0$.

Hence, given the termination load Z_L , the reflection coefficient

Γ_L can be found, or vice versa.

In general, we can define the ^{generalized} impedance at z to be

$$\begin{aligned} Z(z) &= \frac{V(z)}{I(z)} = \frac{a_+ (e^{-\gamma z} + \Gamma_L e^{\gamma z})}{\frac{1}{Z_0} a_+ (e^{-\gamma z} - \Gamma_L e^{\gamma z})} \\ &= Z_0 \left(\frac{1 + \Gamma_L e^{2\gamma z}}{1 - \Gamma_L e^{2\gamma z}} \right) = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \quad (10) \end{aligned}$$

Conversely, one can write

$$\Gamma(z) = \frac{Z(z) - Z_0}{Z(z) + Z_0} \quad (11)$$

Usually, a transmission is lossless, and $\gamma = j\beta$. In this case,

$$Z(z) = Z_0 \frac{1 + \Gamma_L e^{2j\beta z}}{1 - \Gamma_L e^{2j\beta z}} \quad (12)$$

From the above, one can show that

$$Z(-l) = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \quad (13)$$

Shorted Terminations

From the above, when we have a short such that $Z_L = 0$, then

$$Z(-l) = jZ_0 \tan(\beta l) = jX \quad (14)$$

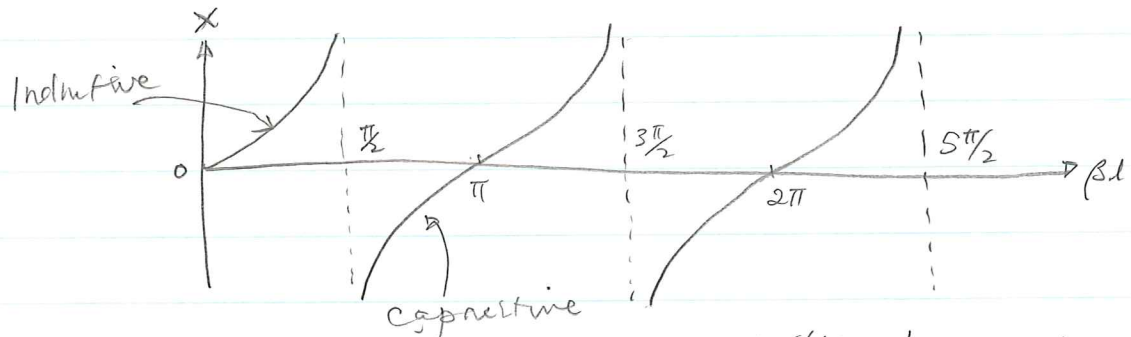


Fig. 2

When $\beta l \ll 1$, then $\tan \beta l \approx \beta l$, and (14) becomes, after using $\beta = \omega \sqrt{LC}$, $Z_0 = \sqrt{L/C}$,

$$Z(-l) \approx jZ_0 \beta l = j\omega L l \quad (15)$$

The above implies that a short length of transmission line connected to a short looks like an inductor as much current will pass through this short producing a strong magnetic field.

Open Terminations

When we have an open circuit such that $Z_L = \infty$, then,

$$Z(-l) = -jZ_0 \cot(\beta l) \quad (15)$$

when $\beta l \ll 1$, $\cot(\beta l) \approx 1/\beta l$, and using $\beta = \omega \sqrt{LC}$, $Z_0 = \sqrt{L/C}$

$$Z(-l) \approx -j \frac{Z_0}{\beta l} = \frac{1}{j\omega C l} \quad (16)$$

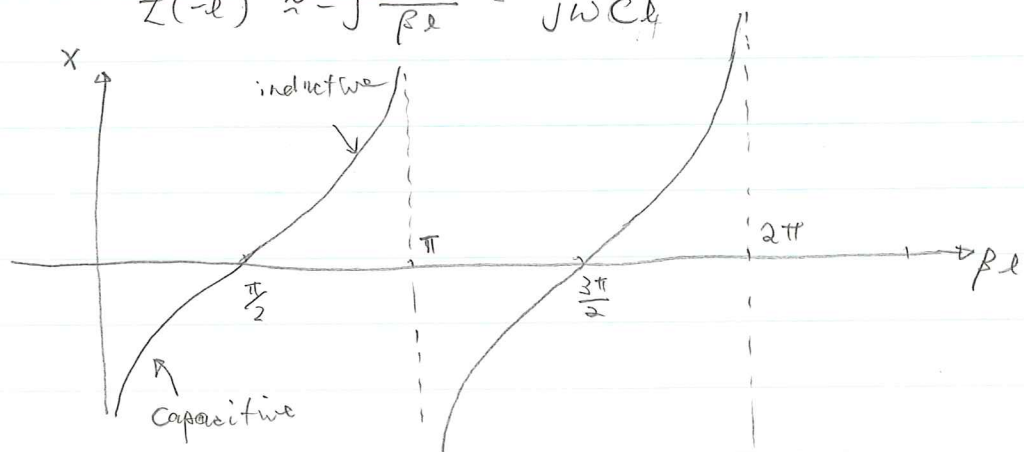



Fig 3

Hence, an open-circuited terminated transmission line ^{short} appears like a capacitor.

But the changing length of l can make a short or an open line look both inductive and capacitive.

In general, a length of transmission line can transform a load Z_L to a range of possible values $Z(-l)$. To understand this range of values, we need to understand the Smith chart (1939). The Smith chart is essentially a graphical calculator for solving transmission line problems. Equation (11) indicates that there is a unique map between the impedance $Z(z)$ and the reflection coefficient $\Gamma(z)$. In the normalized impedance form,
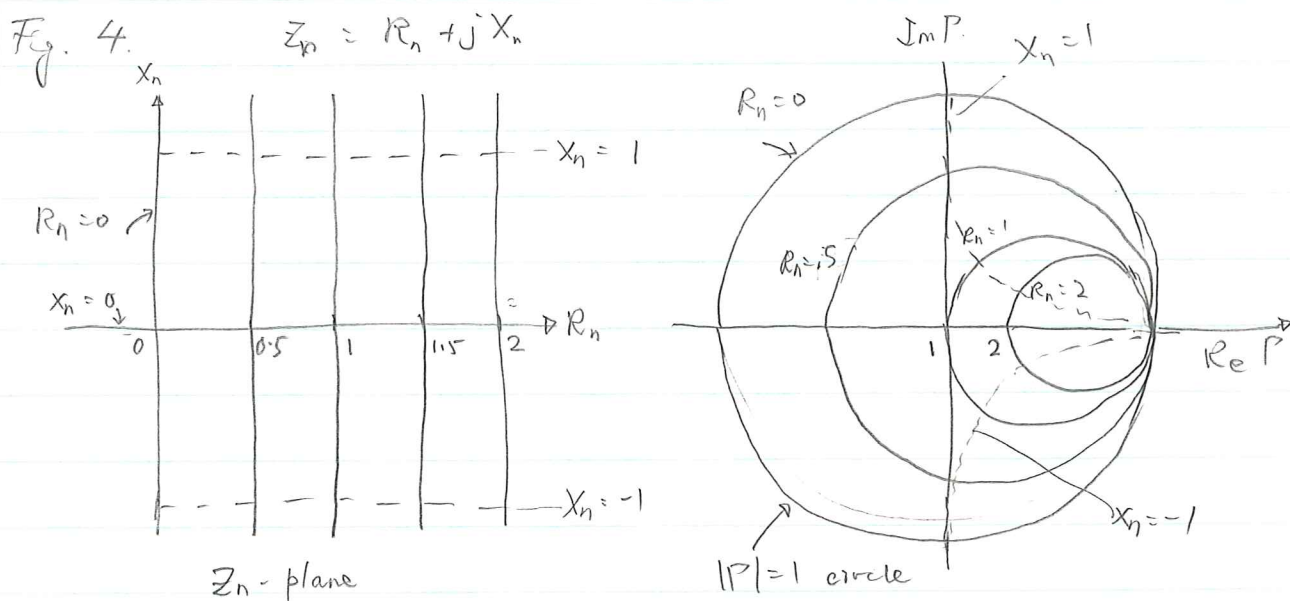
$$\Gamma = \frac{Z_n - 1}{Z_n + 1}, \quad Z_n = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + \Gamma_L e^{-2j\beta l}}{1 - \Gamma_L e^{-j\beta l}} \quad (17)$$



Equation (17) is a bilinear transform in complex variable, a kind of conformal map that maps circles to circles.

VSWR (Voltage Standing Wave Ratio)

The general reflection coefficient for a lossless transmission line at z is given as



$$\Gamma(z) = \frac{V_-(z)}{V_+(z)} = \Gamma_L e^{2j\beta z} \quad (18)$$

The standing wave on a terminated transmission line is given as

$$\begin{aligned} V(z) &= V_0 e^{-j\beta z} + V_0 e^{j\beta z} \Gamma_L \\ &= V_0 e^{-j\beta z} [1 + \Gamma_L e^{2j\beta z}] \\ &= V_0 e^{-j\beta z} (1 + \Gamma(z)) \end{aligned} \quad (19)$$

Hence, $|V(z)|$ is not a constant of z , but

$$|V(z)| = |V_0| |1 + \Gamma(z)| \quad (20)$$

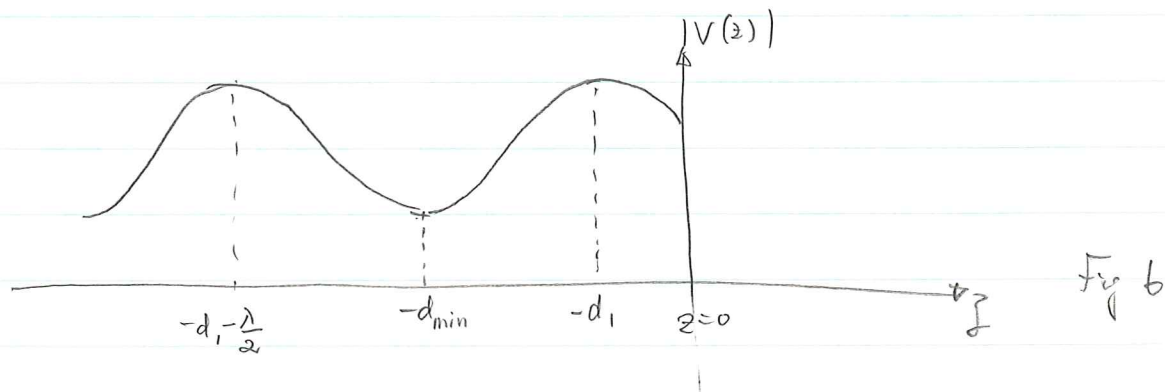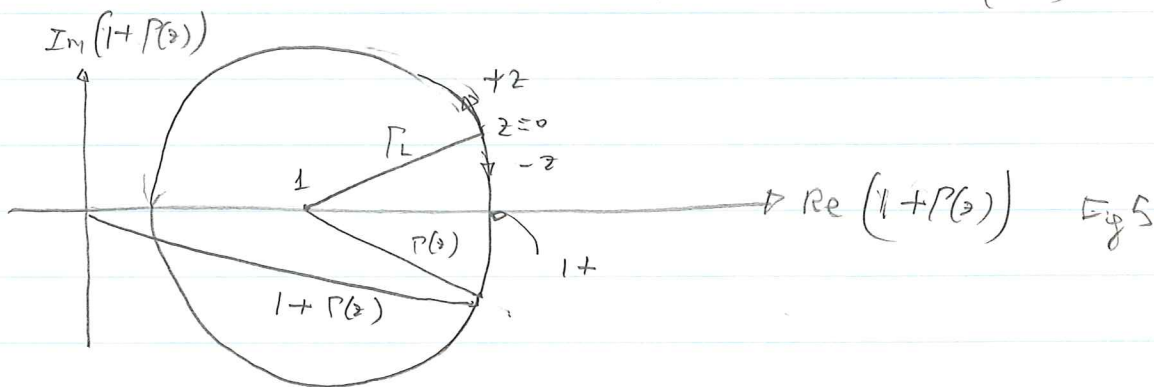

Using the triangular inequality,

$$|V_0| (1 - |\Gamma(z)|) \leq |V(z)| \leq |V_0| (1 + |\Gamma(z)|) \quad (21)$$

But $|\Gamma(z)| = |\Gamma_L|$; hence

$$|V_0| (1 - |\Gamma_L|) \leq |V(z)| \leq |V_0| (1 + |\Gamma_L|) \quad (22)$$

The voltage standing wave ratio, VSWR is

$$VSWR = \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad (23)$$

Conversely,

$$|\Gamma_L| = \frac{VSWR - 1}{VSWR + 1} \quad (24)$$

Hence, the knowledge of VSWR yields the knowledge of $|\Gamma_L|$.

The location of Γ_L in Fig. 5 is determined by the phase of Γ_L .

Hence, the value of d , in Fig 6 is determined by the phase of Γ_L as well. Thus, by measuring the voltage standing wave pattern, one deduces the amplitude and phase of Γ_L .