

Lecture 31

- Phasors: KVL, KCL, & Ohm's phasor law
§ 10.5-10.6

Phasors

Today, we are going to introduce "Phasor" representation of voltage and current for efficient sinusoidal steady state analysis.

Consider a sinusoidal voltage $V(t)$, it can be written as

$$V(t) = V_0 \cos(\omega t + \theta)$$

↓ magnitude ↓ initial phase

From Euler's identity: $e^{j\alpha} = \cos\alpha + j\sin\alpha$
thus, $\cos\alpha = \operatorname{Re}[e^{j\alpha}]$

We have

$$V(t) = \operatorname{Re}[V_0 e^{j(\omega t + \theta)}]$$

$$= \operatorname{Re}[(V_0 e^{j\theta}) e^{j\omega t}]$$

↑

$V(t)$'s phasor representation.

it is complex valued, and it does not depend on time.

Denote $v(t)$'s phasor representation by \tilde{V} , then it is defined as

Phasor: $\tilde{V} = V_0 e^{j\theta}$

a complex quantity having V_0 as magnitude and θ as phase.

From ①, we also see the relationship between $v(t)$ and its phasor

$v(t) = \text{Re}[\tilde{V} e^{j\omega t}]$


So if we can find \tilde{V} , we multiply it by $e^{j\omega t}$, then take real part, we can get its time-domain real-valued form $v(t)$.

Similarly, any sinusoidal current $i(t)$ can be written as $I \cos(\omega t + \theta)$

$i(t) = \text{Re}[\tilde{I} e^{j\omega t}]$

where phasor $\tilde{I} = I e^{j\theta}$.

kcl for phasors

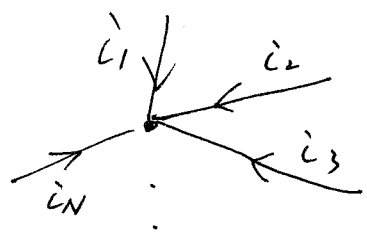

kcl: $i_1 + i_2 + i_3 + \dots + i_N = 0$

For sinusoidal currents,

$$I_1 \cos(\omega t + \theta_1) + I_2 \cos(\omega t + \theta_2) + \dots + I_N \cos(\omega t + \theta_N) = 0$$

$$\text{Re}[\underbrace{I_1 e^{j\theta_1}}_{\uparrow} e^{j\omega t}] + \text{Re}[\underbrace{I_2 e^{j\theta_2}}_{\uparrow} e^{j\omega t}] + \dots + \text{Re}[\underbrace{I_N e^{j\theta_N}}_{\uparrow} e^{j\omega t}] = 0$$

$i_1(t)$'s phasor $i_2(t)$'s phasor $i_N(t)$'s phasor

$$\text{Re}[\tilde{I}_1 e^{j\omega t}] + \text{Re}[\tilde{I}_2 e^{j\omega t}] + \dots + \text{Re}[\tilde{I}_N e^{j\omega t}] = 0$$

$$\text{Re}[(\tilde{I}_1 + \tilde{I}_2 + \dots + \tilde{I}_N) e^{j\omega t}] = 0$$


the above is true for any time t,

$\therefore \tilde{I}_1 + \tilde{I}_2 + \dots + \tilde{I}_N = 0$ (*)

kcl holds true for phasors!

Proof: choose t such that $\omega t = 0$, then $\text{Re}[(\tilde{I}_1 + \tilde{I}_2 + \dots + \tilde{I}_N)] = 0$ (a)
choose another t such that $\omega t = \frac{\pi}{2}$, then $\text{Re}[(\tilde{I}_1 + \tilde{I}_2 + \dots + \tilde{I}_N)j] = 0$ (b)
(b) means the $\text{Im}[\tilde{I}_1 + \tilde{I}_2 + \dots + \tilde{I}_N] = 0$
so (a) and (b) yields (*)

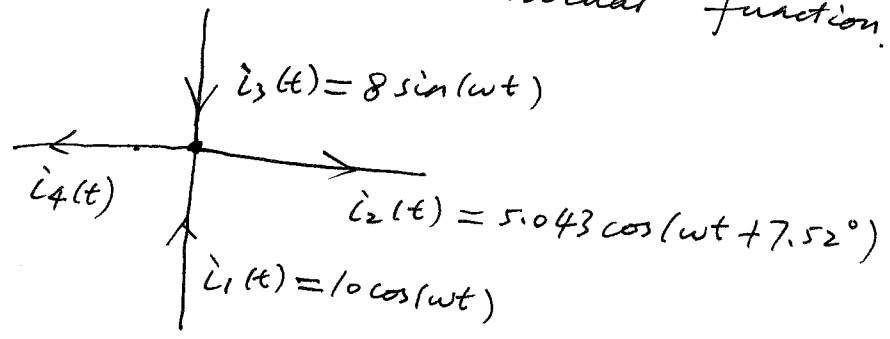Example 1 Find $i_4(t)$ and write it as a single sinusoidal function.



Solution We can use traditional method

$i_4 = i_3 - i_2 + i_1$ to find the answer.

We can also use phasor method.

- $i_1(t) = 10 \cos(\omega t)$

Its phasor $\tilde{I}_1 = 10 e^{j0^\circ} = 10$

- $i_2(t) = 5.043 \cos(\omega t + 7.52^\circ)$

Its phasor $\tilde{I}_2 = 5.043 e^{j7.52^\circ} = 5.043 (\cos 7.52^\circ + j \sin 7.52^\circ) \doteq 5 + j0.66$

- $i_3(t) = 8 \sin(\omega t) = 8 \cos(\omega t - 90^\circ)$

$\tilde{I}_3 = 8 e^{-j90^\circ} = -j8$

Use phasor kcl, we have

$\tilde{I}_4 = \tilde{I}_3 - \tilde{I}_2 + \tilde{I}_1 = -j8 - 5 - j0.66 + 10 = \boxed{5 - j8.66}$


~~$$= 10 e^{-j60^\circ}$$~~

$$= 10 e^{-j60^\circ}$$

- back to real-valued $i_4(t)$,

$$\begin{aligned} i_4(t) &= \operatorname{Re}[\hat{I}_4 e^{j\omega t}] = \operatorname{Re}[10 e^{-j60^\circ} e^{j\omega t}] \\ &= \boxed{10 \cos(\omega t - 60^\circ)} \end{aligned}$$

KVL for phasors

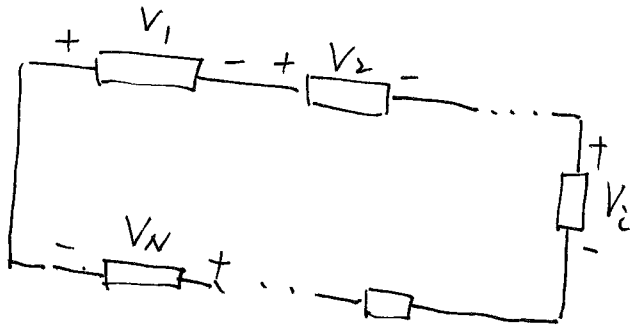

$$\text{KVL: } V_1(t) + V_2(t) + \dots + V_N(t) = 0$$

For sinusoidal voltages,


$$\text{Re}[\tilde{V}_1 e^{j\omega t} + \tilde{V}_2 e^{j\omega t} + \dots + \tilde{V}_N e^{j\omega t}] = 0$$

$$\Rightarrow \text{Re}[(\tilde{V}_1 + \tilde{V}_2 + \dots + \tilde{V}_N) e^{j\omega t}] = 0$$

$$\Rightarrow \boxed{\tilde{V}_1 + \tilde{V}_2 + \dots + \tilde{V}_N = 0}$$

KVL also holds true for phasors.

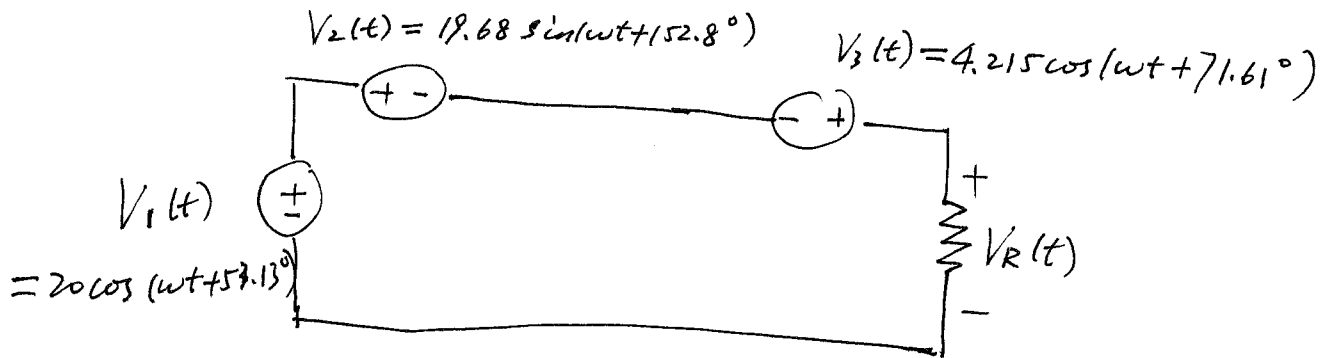Example 2 Find $V_R(t)$ and write it as a single sinusoidal function



Solution Use phasor representation,

$$\tilde{V}_1 = 20 e^{j53.13^\circ} \doteq 12 + j16$$


$$\tilde{V}_2 = 19.68 e^{j(152.8^\circ - 90^\circ)} \doteq 9 + j17.5$$

$$\tilde{V}_3 = 4.215 e^{j71.61^\circ} \doteq 1.33 + j4$$

$$\tilde{V}_R = \tilde{V}_3 - \tilde{V}_2 + \tilde{V}_1 = 4.33 + j2.5 \doteq 5 e^{j30^\circ}$$

$$V_R(t) = \text{Re}[\tilde{V}_R e^{j\omega t}] = \boxed{5 \cos(\omega t + 30^\circ)}$$

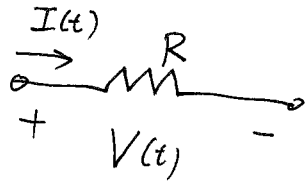Phasor \tilde{V} - \tilde{I} relationship for resistance R



$$V(t) = R I(t)$$


For sinusoidal voltage and current,

$$\text{Re}[\tilde{V}e^{j\omega t}] = R \text{Re}[\tilde{I}e^{j\omega t}] = \text{Re}[\tilde{I}R e^{j\omega t}]$$

True for any time t

$$\Rightarrow \boxed{\tilde{V} = \tilde{I}R}$$

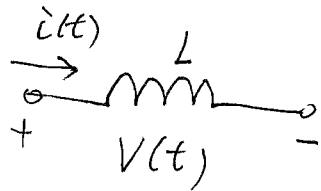Phasor \tilde{V} - \tilde{I} relationship for inductance L



$$V(t) = L \frac{di(t)}{dt}$$

For sinusoidal voltage and current

$$\text{Re}[\tilde{V} e^{j\omega t}] = L \frac{d}{dt} \text{Re}[\tilde{I} e^{j\omega t}]$$

$$= L \text{Re}\left[\frac{d}{dt}(\tilde{I} e^{j\omega t})\right]$$

$$= L \text{Re}[\tilde{I} (j\omega e^{j\omega t})]$$


$$= \text{Re}[\tilde{I} j\omega L (e^{j\omega t})]$$

$$\Rightarrow \boxed{\tilde{V} = j\omega L \tilde{I}}$$

Important Advantage:

Using phasors, the \tilde{V} - \tilde{I} relationship for the inductor becomes a simple "algebraic" relation instead of "differential" relation! This will help us avoid "differential equations" when analyzing circuits involving L .

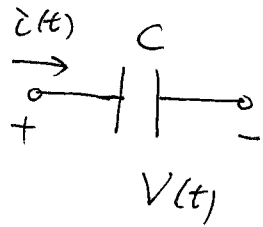Phasor \tilde{V} - \tilde{I} relationship for capacitance C



$$i(t) = C \frac{dV(t)}{dt}$$

$$\begin{aligned} \operatorname{Re}[\tilde{I} e^{j\omega t}] &= C \frac{d}{dt} \operatorname{Re}[\tilde{V} e^{j\omega t}] \\ &= C \operatorname{Re}\left[\frac{d}{dt} (\tilde{V} e^{j\omega t})\right] \\ &= C \operatorname{Re}[j\omega \tilde{V} e^{j\omega t}] \\ &= \operatorname{Re}[j\omega C \tilde{V} e^{j\omega t}] \end{aligned}$$

$$\Rightarrow \tilde{I} = j\omega C \tilde{V}$$

$$\Rightarrow \boxed{\tilde{V} = \frac{\tilde{I}}{j\omega C}}$$

Summary Phasor ohm's Law:


$$\tilde{V} = Z \tilde{I}$$

Where impedance $Z = \begin{cases} R & \text{resistance} \\ j\omega L & \text{inductance} \\ \frac{1}{j\omega C} & \text{capacitance} \end{cases}$

The reciprocal of Z is called Y (admittance)

$$\therefore Y = \frac{1}{Z} = \begin{cases} \frac{1}{R} & \text{resistance} \\ \frac{1}{j\omega L} & \text{inductance} \\ j\omega C & \text{Capacitance} \end{cases}$$

Example

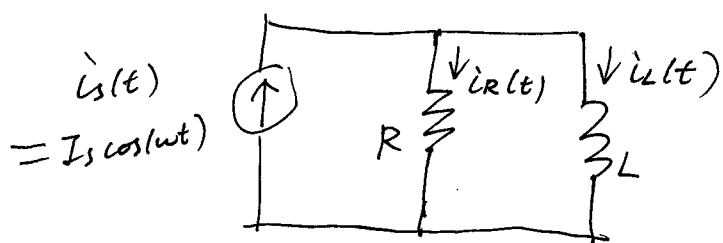

Compute the SSS response $i_L(t)$.

Solution We solved this problem in last lecture using time-domain differential equation, Let's see whether we can use "phasor method" to simplify the analysis.

We can first find $i_L(t)$'s phasor, denoted by \tilde{I}_L , then $i_L(t) = \text{Re}[\tilde{I}_L e^{j\omega t}]$

$$\tilde{I}_s = I_s e^{j0^\circ} = I_s$$

$$\begin{aligned} \tilde{I}_s \oplus &= \tilde{I}_R + \tilde{I}_L && \text{(KCL for phasors)} \\ &= \frac{\tilde{V}_L}{R} + \tilde{I}_L && (\tilde{V}_R = \tilde{I}_R R, \text{ and } \tilde{V}_R = \tilde{V}_L) \end{aligned}$$

$$= \frac{j\omega L}{R} \tilde{I}_L + \tilde{I}_L$$

$$\Rightarrow \tilde{I}_L = \frac{R}{R + j\omega L} \tilde{I}_s = \frac{R}{R + j\omega L} I_s$$

$$\therefore \tilde{I}_L = \frac{R I_s}{\sqrt{R^2 + \omega^2 L^2}} e^{j(-\tan^{-1} \frac{\omega L}{R})}$$

$$\therefore i_L(t) = \text{Re}[\tilde{I}_L e^{j\omega t}] = \frac{R I_s}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t - \tan^{-1} \frac{\omega L}{R})$$

the same as we obtained before!