

ID# \_\_\_\_\_

Name \_\_\_\_\_

**EE255          Exam 3          November 8<sup>th</sup>, 2000**


Instructor (circle one)          Bashir          Furgason

The exam consists of 16 multiple choice questions and 3 workout problems. Record the answers to the multiple choice on this page. Return the entire exam. There will be no partial credit for the multiple choice portion. There may be partial credit for the workout problems and hence show all your work.

**DO NOT BEGIN UNTIL INSTRUCTED TO DO SO**


- |     |   |   |   |   |   |
|-----|---|---|---|---|---|
| 1)  | a | b | c | d | e |
| 2)  | a | b | c | d | e |
| 3)  | a | b | c | d | e |
| 4)  | a | b | c | d | e |
| 5)  | a | b | c | d | e |
| 6)  | a | b | c | d | e |
| 7)  | a | b | c | d | e |
| 8)  | a | b | c | d | e |
| 9)  | a | b | c | d | e |
| 10) | a | b | c | d | e |
| 11) | a | b | c | d | e |
| 12) | a | b | c | d | e |
| 13) | a | b | c | d | e |
| 14) | a | b | c | d | e |
| 15) | a | b | c | d | e |
| 16) | a | b | c | d | e |

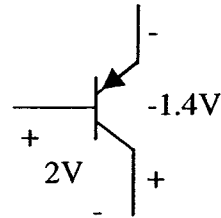1. Given the transistor below, in which region will it operate ?




- (a) Saturation      (b) active      (c) Cut-off      (d) linear      (e) inverse active
- 

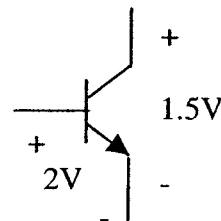2. Given the transistor below, in which region will it operate ?



- (a) Saturation      (b) Active      (c) Cut-off      (d) Linear      (e) Inverse active
- 

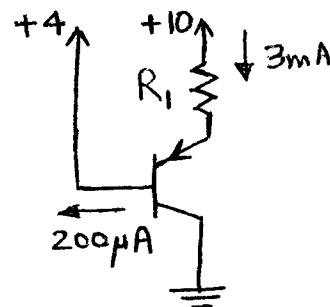3. Given the circuit below as biased below and  $V_{BE_{on}} = -0.6$ , what is the value of  $R_1$  ?




- (a)  $1.1k\Omega$       (b)  $1.8k\Omega$       (c)  $3.3k\Omega$       (d)  $4.6k\Omega$       (e)  $5.8k\Omega$
- 

4. What is the value of  $\beta$  for the transistor in problem 3 ?

- (a) 11      (b) 12      (c) 13      (d) 14      (e) 15
-

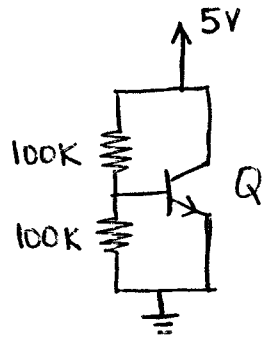5. For the circuit shown below, find the value of  $I_C$  ? Use  $V_{BE_{on}} = 0.7$   $\beta = 100$




- (a) 2mA    (b) 3mA    (c) 3.6mA    (d) 4.5mA    (e) 6mA
- 
6. Given an NPN transistor which has  $I_{C1}=1.1mA @ V_{CE1}=4V$  and  $I_{C2}=1.2mA @ V_{CE2}=14V$  (both for the same  $I_B$ ), then  $V_A$  is closest to which of the following answers ?
- (a) 110    (b) 150    (c) 200    (d) 250    (e) 310
- 
7. If a transistor is biased at room temperature,  $I_C=2mA$ , and  $r_{\pi}=5k\Omega$ , then  $\beta$  is closest to which of the following options ?

- (a) 185    (b) 300    (c) 385    (d) 425    (e) 500

8. If a PNP device is operating at room temperature,  $V_A=50$  and  $r_o=100k\Omega$ , then  $g_m$  is closest to which of the following answers below ?


- (a) 10 millimhos, (b) 20 millimhos, (c) 30 millimhos,  
(d) 40 millimhos, (e) 10 millimhos,

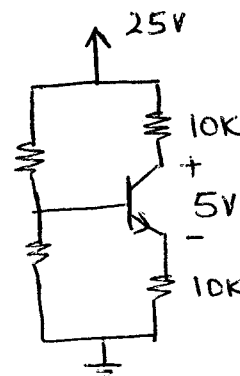9. If the transistor below is biased such that  $I_C=1mA$ . Now suppose that  $R_E$  is doubled, which one of the following will happen.




- (a) Q forced into cut-off (b) Q forced into saturation  
(c)  $V_{CE}$  almost doubles (d)  $V_{BE}$  almost doubles  
(e) the temperature doubles

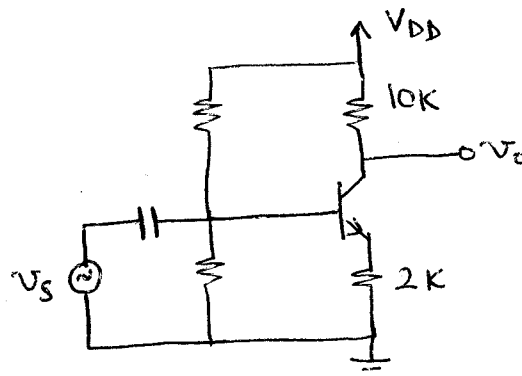10. Given the transistor shown, the transistor is biased in forward active region. If  $\beta$  is quite large, and  $V_A = \infty$ , then the small signal voltage gain is about ;




- (a) +2 (b) -2 (c) +5 (d) -5 (e) +10

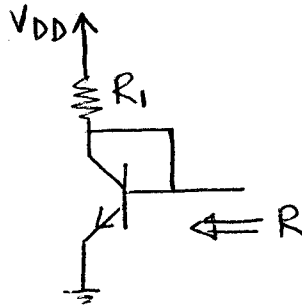11. Given the circuit as shown below, what is the impedance  $R$  as indicated;




- (a)  $R1 \parallel r_{\pi} \parallel r_o \parallel 1/g_m$       (b)  $R1 \parallel r_{\pi}$       (c)  $R1 \parallel r_o \parallel g_m$   
 (d)  $r_{\pi} + r_o$       (e)  $r_{\pi}$

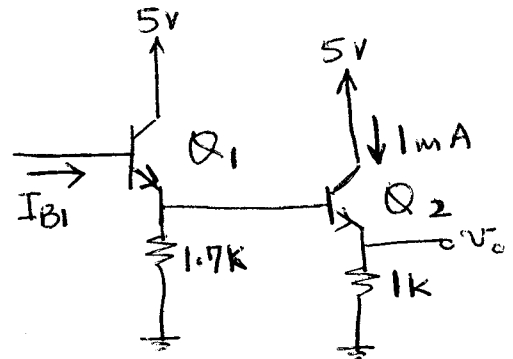12. For the circuit shown below, if  $\beta_1 = \beta_2 = 100$ , and  $V_{BE_{on}} = 0.7$ , find the value of  $I_{B1}$  ?



- (a)  $5\mu A$       (b)  $10\mu A$       (c)  $15\mu A$       (d)  $20\mu A$       (e)  $25\mu A$

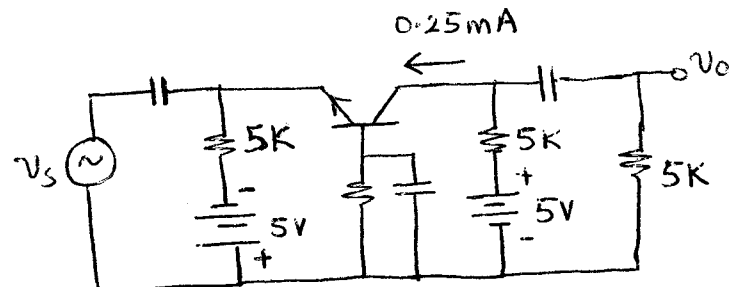13. For the common base amplifier shown below at room temperature,  $V_A = \infty$ , the ac small signal gain is closest to;



- (a) 15      (b) 25      (c) 35      (d) 45      (e) 55


14. What type of amplifier has the lowest output impedance ?

- (a) Common Source,                      (b) Common Base,  
(c) Common Collector,                (d) Common Emitter,  
(d) Common Ground
- 

15. A power NPN transistor is biased such that  $I_C=100\text{mA}$ , and  $V_{CE}=20\text{V}$ .  $\theta_{jc}=10^\circ\text{C/W}$  and  $\theta_{cs}=5^\circ\text{C/W}$ . If the ambient temperature is  $25^\circ\text{C}$  and the device temperature was measured to be  $75^\circ\text{C}$ , find  $\theta_{sa}=?$


- (a)  $10^\circ\text{C/W}$             (b)  $15^\circ\text{C/W}$     (c)  $20^\circ\text{C/W}$     (d)  $25^\circ\text{C/W}$     (e)  $30^\circ\text{C/W}$
- 

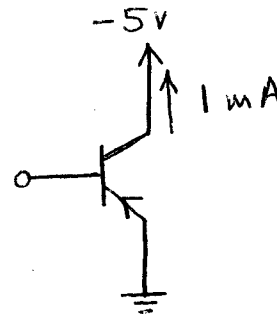16. Given the PNP transistor below at room temperature, if  $I_S=10^{-13}\text{ A}$ , and  $V_A=10\text{V}$ , find the value of  $V_{EB}?$



- (a) 0.455            (b) 0.586            (c) 0.689            (d) 0.799            (e) 100
-

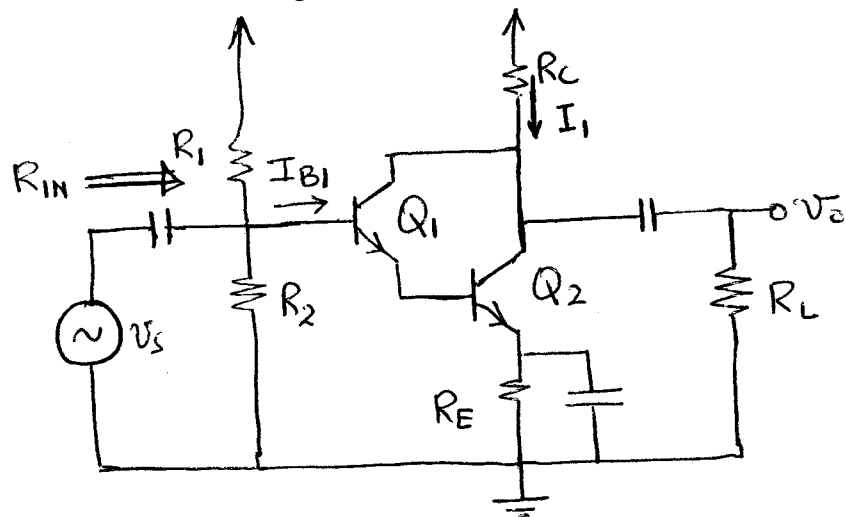17-19 pertain to the circuit diagram below.



$\beta_1 = \beta_2, V_A = \text{infinite}$

17. Draw and label the ac equivalent circuit for the amplifier above. (6 points)

18. Find the expression for the input impedance  $R_{in}$  ? ( $R_{in}$  is indicated in the figure)  
(7 points)

---

19. Derive the expression for  $I_1/I_{B1}$ ? ( $I_1$  and  $I_{B1}$  are shown in the circuit)  
(7 points)



## EE-255 Formula Sheet: Exam 3

### Data:

At 25 °C (R.T.)  $V_T = kT/q = 0.026$  volts

$$k = 1.3806 \times 10^{-23} \text{ J/K} = 8.618 \times 10^{-5} \text{ eV/K} \quad q = 1.6022 \times 10^{-19} \text{ C} \quad 0^\circ\text{C} = 273.16 \text{ K}$$

**Formulas:**  $e^x = 1 + x + x^2/2 + \dots$

### Bipolar Transistors:

$$I_C = \beta I_B \equiv I_S e^{\frac{V_{BE}}{V_T}} \left( 1 + \frac{V_{CE}}{V_A} \right) \quad (\text{active})$$

$$\beta = \frac{\alpha}{1-\alpha} \quad \alpha = \frac{\beta}{1+\beta}$$

$$I_C = \frac{\beta[V_{Th} - V_{BE(on)}]}{R_{Th} + (\beta+1)R_E}$$

### Thermal Effects:

$$T_{dev} - T_{amb} = \theta P_D$$

$$P_D = I_B V_{BE} + I_C V_{CE}$$

$$P_D = I_D V_{DS}$$

7

### Bipolar Amplifiers:

$$g_m = \frac{I_C}{V_T} \quad g_m r_\pi = \beta \quad r_o = \frac{V_A}{I_C}$$

**CE:**  $A_{vi} = -g_m(R_C \parallel r_o \parallel R_L)$   $R_{is} = r_\pi \parallel (R_1 \parallel R_2)$   $R_o = R_C \parallel r_o$

### CE with emitter degeneration:

$$A_{vi} = \frac{-\beta(R_C \parallel R_L)}{r_\pi + (1+\beta)R_E} \quad R_{is} = (R_1 \parallel R_2) \parallel [r_\pi + (\beta+1)R_E] \quad R_o = R_C$$

**CB:**  $A_{vi} = +g_m(R_C \parallel R_L)$   $R_{is} = R_E \parallel \frac{r_\pi}{\beta+1}$   $R_o = R_C$

**CC:**  $A_{vi} = \frac{(1+\beta)(r_o \parallel R_E \parallel R_L)}{r_\pi + (1+\beta)(r_o \parallel R_E \parallel R_L)}$

$$R_{is} = (R_1 \parallel R_2) \parallel [r_\pi + (\beta+1)r_o \parallel R_E \parallel R_L] \quad R_o = r_o \parallel R_E \parallel \left[ \frac{r_\pi + (R_1 \parallel R_2) \parallel R_S}{\beta+1} \right]$$