

Three-stage Common Emitter Amplifier Design

Transistor Parameters: $300 < \beta_{bc} = \beta_0 < 1000$ $V_0 = 0.7 \text{ V}$

Design Objective: $|A_{Vs}| > 10,000$

