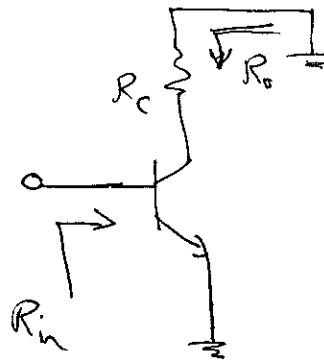


Common emitter


$$R_{in} = r_{\pi}$$

$$A_{v_o} = -g_m (R_c \parallel r_o) \approx -g_m R_c$$

$$R_o = R_c \parallel r_o$$



Common emitter with source resistance

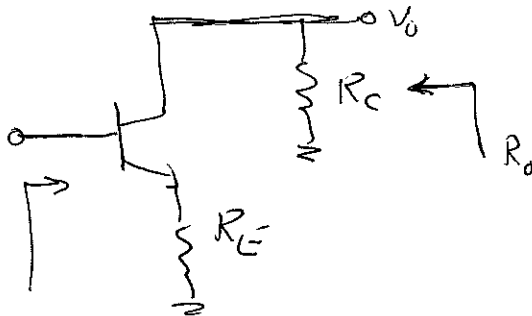

$$R_{in} = r_{\pi} + (\beta + 1) R_E = (1 + \beta) (r_e + R_E) = r_{\pi} (1 + g_m R_E)$$

$$A_{v_o} = - \frac{g_m R_c}{1 + g_m R_E}$$


$$R_o = R_c \text{ (if } r_o = \infty) \text{ or } R_o = R_c \parallel [r_o (1 + g_m R_E)]$$

if r_o is taken into account

Common Source

$$R_{in} = \infty \quad A_{v0} = -g_m (R_D \parallel r_o) \approx -g_m R_D$$

$$R_o = R_D \parallel r_o \approx R_D$$

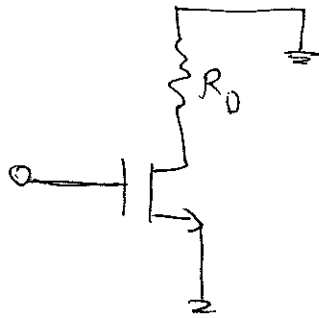


Common source with source resistance


$$A_{v0} = - \frac{g_m R_D}{1 + g_m R_S} \approx - \frac{R_D}{R_S} \quad R_{in} = \infty$$

$$R_o = R_D \quad \text{if } r_o = \infty$$
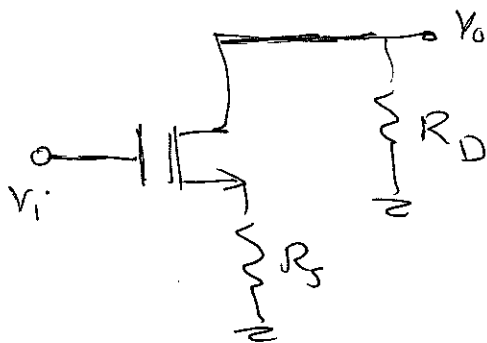
$$\text{if not } R_o = R_D \parallel [r_o (1 + g_m R_S)]$$



Common Gate

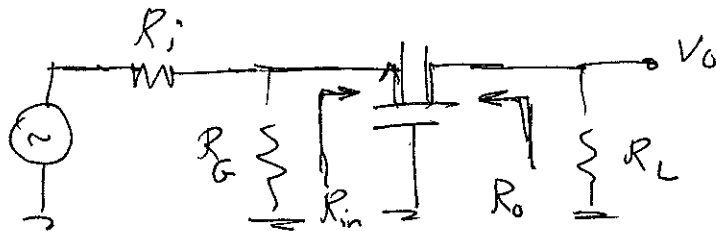


$$R_{in} = \frac{1}{g_m} \quad A_{vo} = g_m R_D \quad (r_o = \infty)$$

$$R_o = R_D \quad (r_o = \infty) \quad \text{or} \quad R_L \parallel r_o \left[1 + g_m (R_i \parallel R_G) \right]$$

Common Base is similar
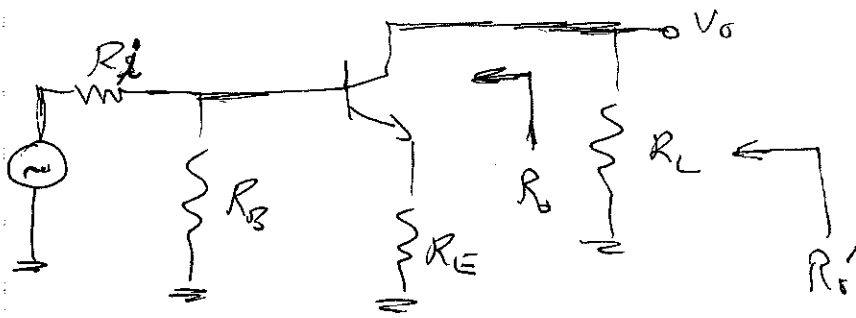
$$R_{in} = \frac{1}{g_m} \quad A_{vo} = g_m R_D \quad R_o = R_L \parallel r_o \left[1 + g_m (R_i \parallel R_B) \right]$$




Common emitter

$$R_o = r_o (1 + g_m R_E) \quad \text{if } R_E \gg r_e$$


$$R_o' = R_o \parallel R_L \quad \text{if ignore } r_o \Rightarrow R_o' = R_L$$

Similar for Common source with source resistance

$$R_o = r_o (1 + g_m R_S)$$

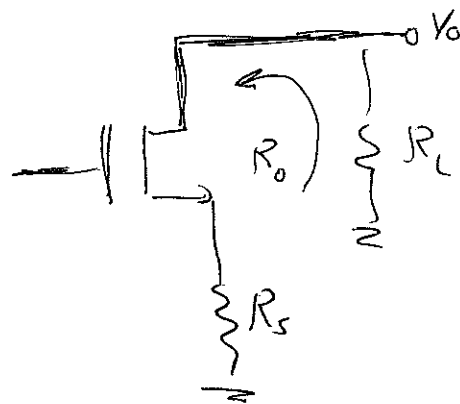

Common Base & Common Gate

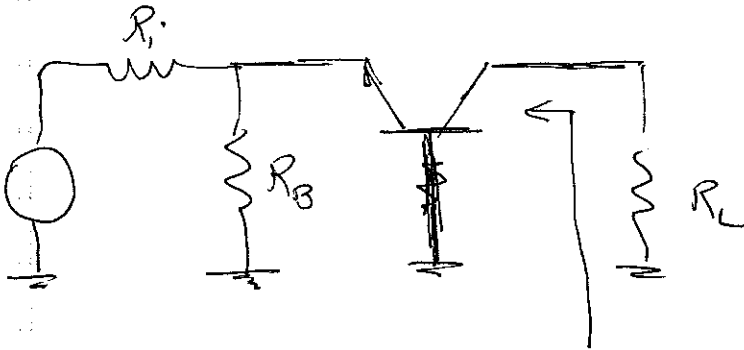


$$R_o = r_o [1 + g_m (R_i \parallel R_B)]$$

For common gate $R_o = r_o [1 + g_m (R_i \parallel R_G)]$


Similar to CB

Common Collector

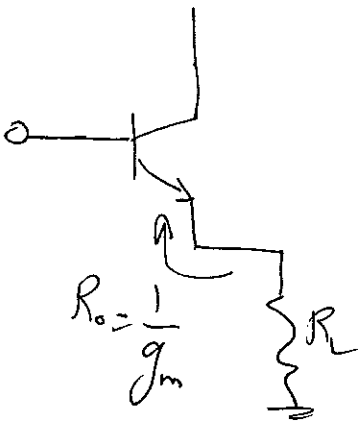


$$R_o = \frac{1}{g_m}$$

Common Drain

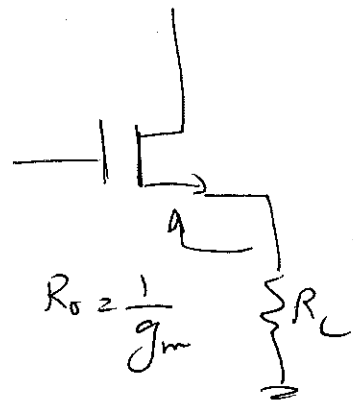

$$R_o = \frac{1}{g_m}$$

BJT Cascode

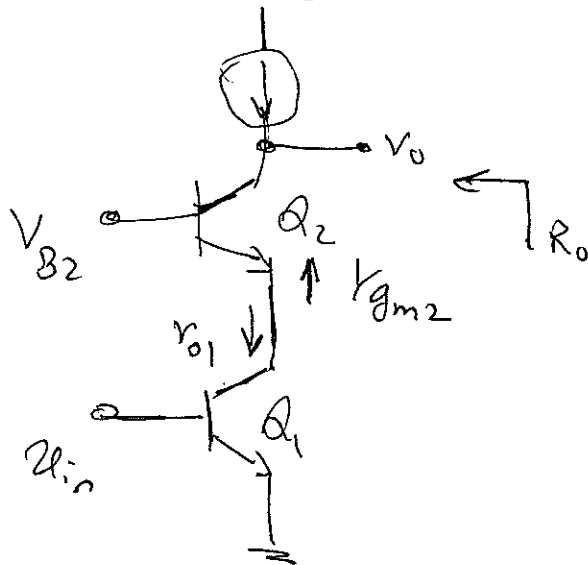

$$R_o = r_{o2} [1 + g_{m2} (r_{o1} \parallel r_{\pi 2})] \approx g_{m2} r_{o2} (r_{o1} \parallel r_{\pi 2}) \\ \approx g_{m2} r_{o2} r_{\pi 2}$$


$$R_o \approx g_{m2} r_{o2} r_{\pi 2}$$

$$\text{Total Gain} = -g_{m1} (r_{o1} \parallel r_{\pi 2}) \cdot g_{m2} r_{o2}$$

if ignoring r_{o1}

$$A_v = -g_{m1} \cdot \frac{1}{g_{m2}} \times g_{m2} \cdot R_L = -g_{m1} R_L$$

MOS Cascode

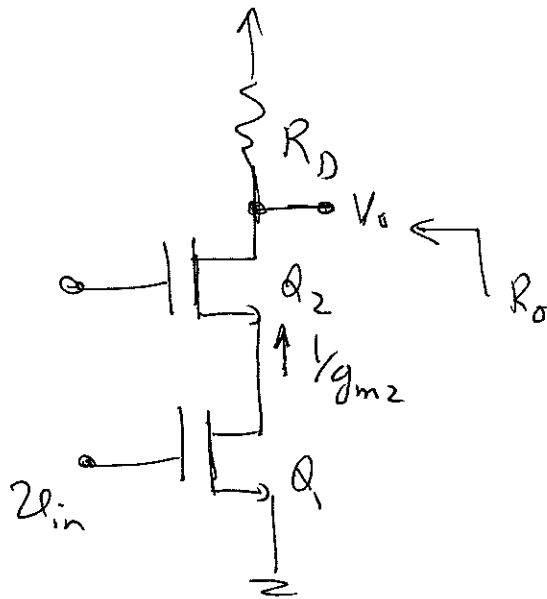

$$R_o = r_{o2}(1 + g_{m2}r_{o1}) \approx g_{m2}r_{o1}r_{o2}$$

$$\text{Gain ignoring } r_{o's} = \left(-g_{m1} \cdot \frac{1}{g_{m2}} \right) \times \left(g_{m2} \cdot R_D \right)$$

$$= -g_{m1}R_D$$