

# ECE-255 Final Exam

## December 13, 2013







Name: \_\_\_\_\_  
(Please print clearly)

Student ID: \_\_\_\_\_

### INSTRUCTIONS

- This is a closed book, closed notes exam.
- Clearly mark your multiple choice answers in the scantron.
- When the exam ends, all writing is to stop. This is not negotiable. No writing while turning in the exam/scantron or risk an F in the exam.
- All students are expected to abide by the customary ethical standards of the university, i.e., your answers must reflect only your own knowledge and reasoning ability. As a reminder, at the very minimum, cheating will result in a zero on the exam and possibly an F in the course.
- Communicating with any of your classmates, in any language, by any means, for any reason, at any time between the official start of the exam and the official end of the exam is grounds for immediate ejection from the exam site and loss of all credit for this exercise.

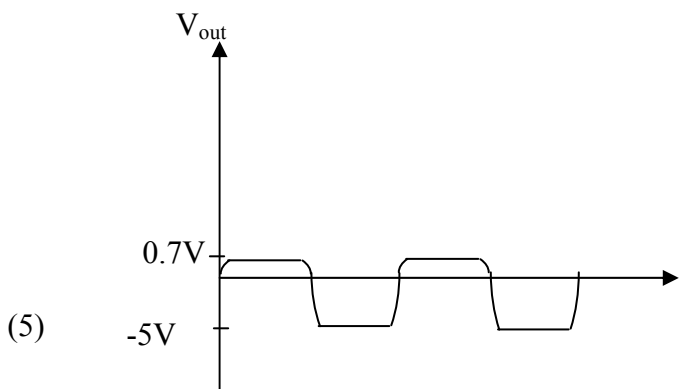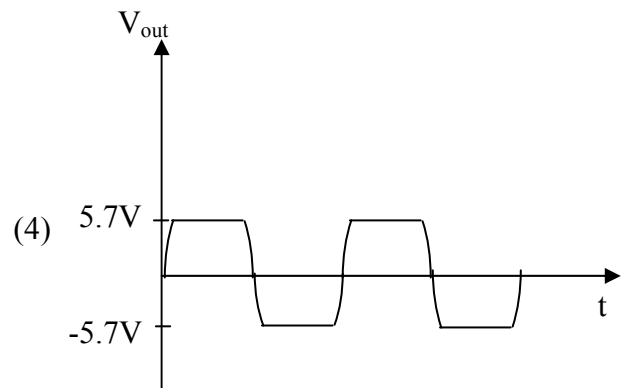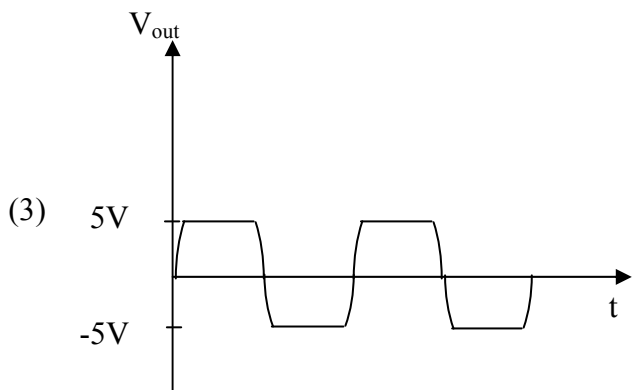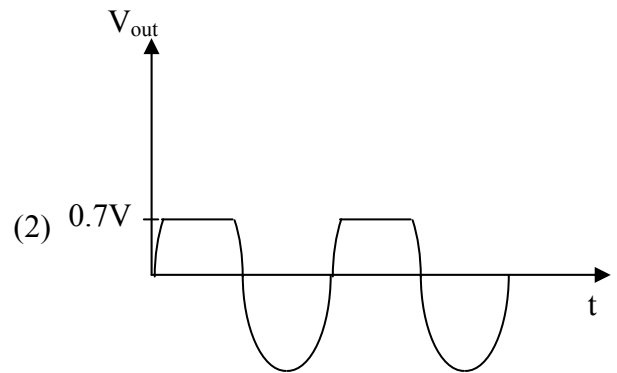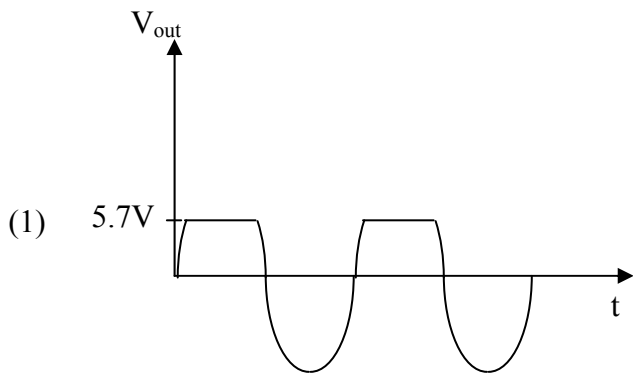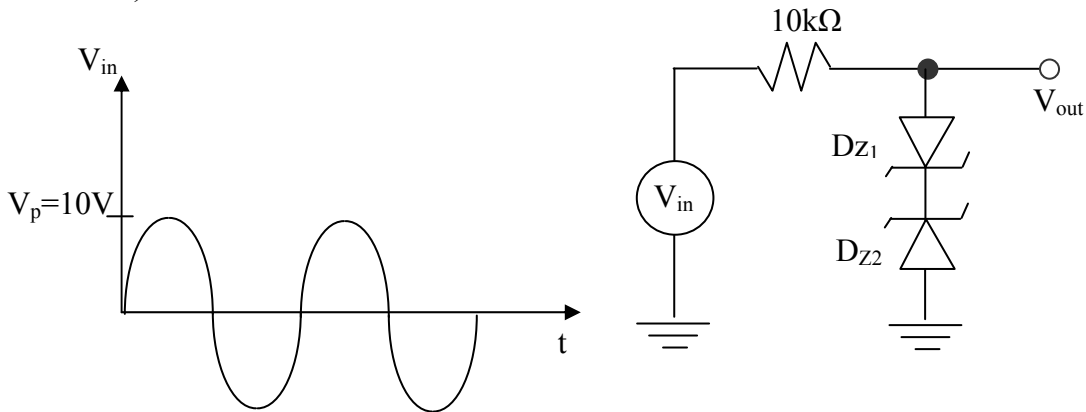
1) For the circuit shown below, if a sinusoidal wave with a peak voltage of 10 V is applied to the input, which one of the curves represent the output voltage? ( $V_{on}=0.7V$ ,  $V_Z=5V$ )



(6) None of these


2) The Zener diode in the circuit has an equivalent resistance  $R_Z = 20 \Omega$ . From the diode data sheet we find that if the voltage across the Zener diode is 6.4 V at  $I_Z = 20 \text{ mA}$ . Determine the output voltage  $V_{\text{out}}$ .

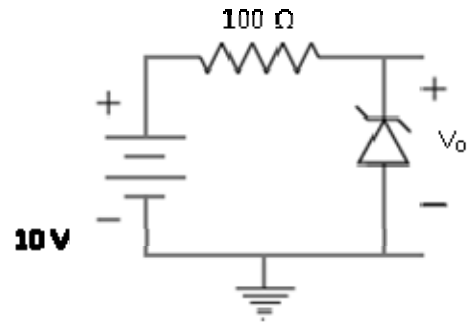- (1)  $V_{\text{out}} = 6.4 \text{ V}$       (2)  $V_{\text{out}} = 6.0 \text{ V}$
- (3)  $V_{\text{out}} = 6.67 \text{ V}$     (4)  $V_{\text{out}} = 5.33 \text{ V}$
- (5)  $V_{\text{out}} = 10 \text{ V}$       (6) None of the above




3) For the three bipolar transistors shown below, identify which one or two devices are operated at “Forward Active” region.


(A)

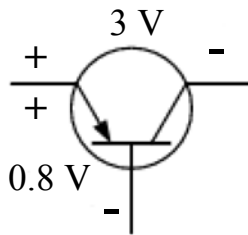

(B)

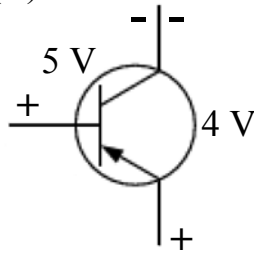


(C)

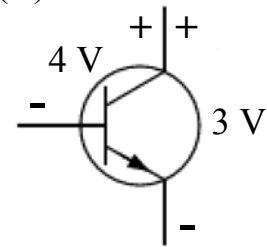

Which device or devices are operated at “Forward active regions”?

- (1) A
- (2) C
- (3) B
- (4) A and B
- (5) B and C
- (6) None of the above.

4) MOSFET circuit:

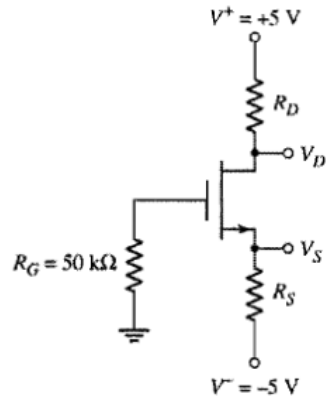

Circuit Values:

$I_D = 2.5 \text{ mA}$

$R_D = 1 \text{ k}\Omega$

$R_S = 1 \text{ k}\Omega$

MOSFET Values:

$V_{TN} = 1.5 \text{ V}$

$k_n' = 1 \text{ mA/V}^2$

$\lambda = 0 \text{ V}^{-1}$

(a) Determine the MOSFET's DC drain-to-source voltage,  $V_{DS}$ . (b) What is the (W/L) ratio required for the MOSFET to satisfy the above biasing conditions?

(1) -4V;10.0

(2) 5V;2.5

(3) 3V;2.5


(4) 4V;2.0

(5) 5V;5.0

(6) None of the above

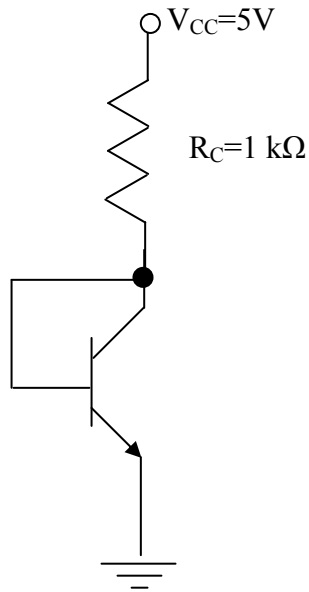5) For the bipolar circuit shown below,  $I_C$ ?

$\beta=80$ ,  $V_{BE(on)}=0.7$ ,  $V_T=25$  mV



(1) 4.3mA

(2) 28.7 $\mu$ A


(3) 2.87mA

(4) 4.25mA

(5) 0.425mA

(6) None of the above

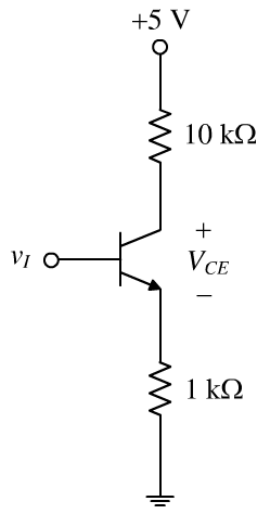6) Find the value of  $V_{CE}$  in the BJT circuit shown below for  $v_I = 0V$ .



BJT Values:

$$\beta = 200$$

$$V_{BE\ ON} = 0.7\ V$$

$$V_{CE\ SAT} = 0.1\ V$$

$$V_A = \infty\ V$$

$$V_T = 26\ mV$$

(1) 0V

(2) 0.1V


(3) 0.7V

(4) 1.3V

(5) 5V

(6) None of the above

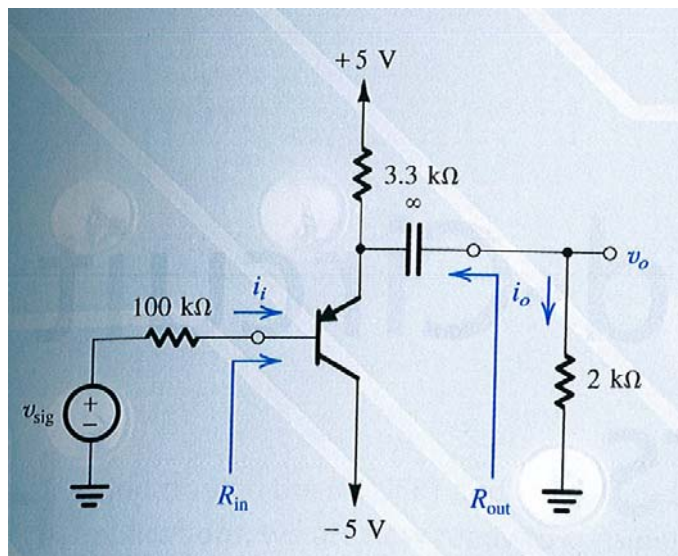7) The value of  $g_m$  in the BJT transistor shown below is? Assume  $\beta=50$ ,  $V_{BE(on)}=0.7$ ,  $V_T=25$  mV.




- (1) 16 mA/V
- (4) 25 mA/V

- (2) 8 mA/V
- (5) 64 mA/V

- (3) 32 mA/V
- (6) None of the above



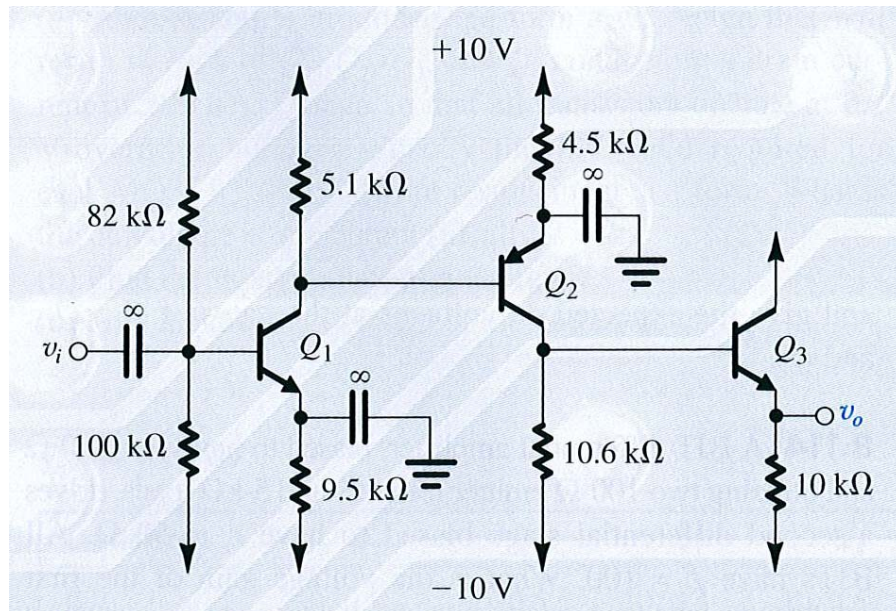8) The multistage amplifier shown below has which of the following configuration:



(1) CC-CE-CE

(2) CC-CE-CC


(3) CE-CE-CC

(4) CE-CE-CE

(5) CB-CE-CC

(6) None of the above

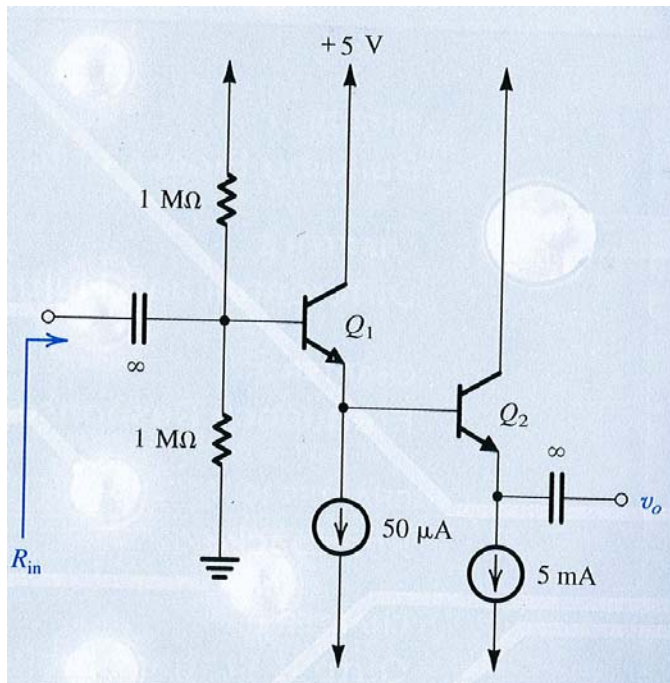9) What is the input impedance of the two stage amplifier shown below? Assume  $\beta=100$ ,  $V_{BE(on)}=0.7$ ,  $V_T=25$  mV.



(1)  $\approx 500\text{k}\Omega$   
 (5)  $\approx 25\text{ k}\Omega$


(2)  $\approx 75\text{k}\Omega$

(6) None of the above

(3)  $\approx 250\text{k}\Omega$

(4)  $\approx 65\text{ k}\Omega$

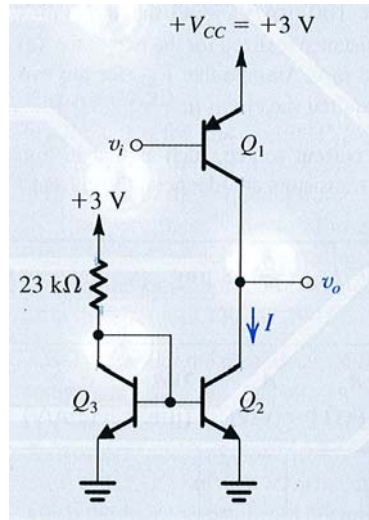10) What is the gain ( $v_o/v_i$ ) of the CE amplifier shown below, assume  $\beta=100$   
 $V_{BE(on)}=0.7$ ,  $V_T=25$  mV, and  $V_A=100$ V for all transistors (Hint:  $R_L$  is the total load resistance seen at the output node)




- (1)  $\approx -2000$       (2)  $\approx -4000$       (3)  $\approx 1$       (4)  $\approx -1000$   
 (5)  $\approx -500$       (6) None of the above

11) For the amplifier shown below known as double cascode, what is the gain  $|A_v|$ ?  $Q_2$  and  $Q_3$  both have twice the Early voltage as that of  $Q_1$ . But they all have the same  $\beta$ .

Note:  $I_{c1}=I_{c2}=I_{c3}$ ,  $g_m=g_{m1}=g_{m2}=g_{m3}$ ,  $2r_{o1}=r_{o2}=r_{o3}$ ,  $r_{\pi1}=r_{\pi2}=r_{\pi3}$


Assume  $r_o \gg 1/g_m$  for all three

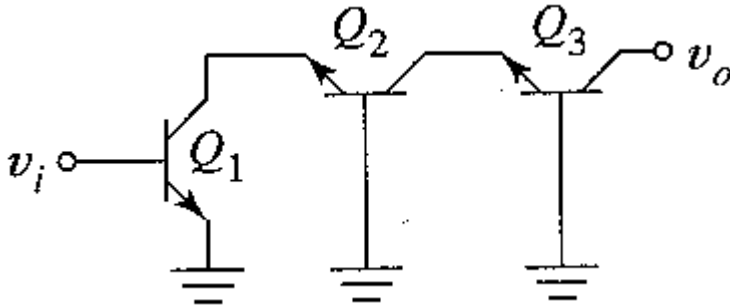

- (1)  $g_m r_{o1}$       (2)  $g_m^3 r_{o1}^3$       (3)  $2g_m r_{o1}$       (4)  $g_m^2 r_{o1}^2$   
 (5)  $4g_m r_{o1}$       (6) None of the above


12) What is the common-mode gain ( $|A_{v_c}|$ ) for the circuit shown below? Assuming  $\beta_0 \gg 1$  and  $r_o \gg 1$ . (hint: use the half circuit model; draw small signal model of BJT to calculate  $v_{oc}/v_{ic}$  at  $v_{id}=0$ ; 2 k $\Omega$  resistor can be regarded as part of transistor or it's much smaller than 50 k $\Omega$ .)

What is the differential mode gain ( $|A_{v_d}|$ ) for the circuit shown below?  
[Answers: first common-mode gain; second differential mode gain]

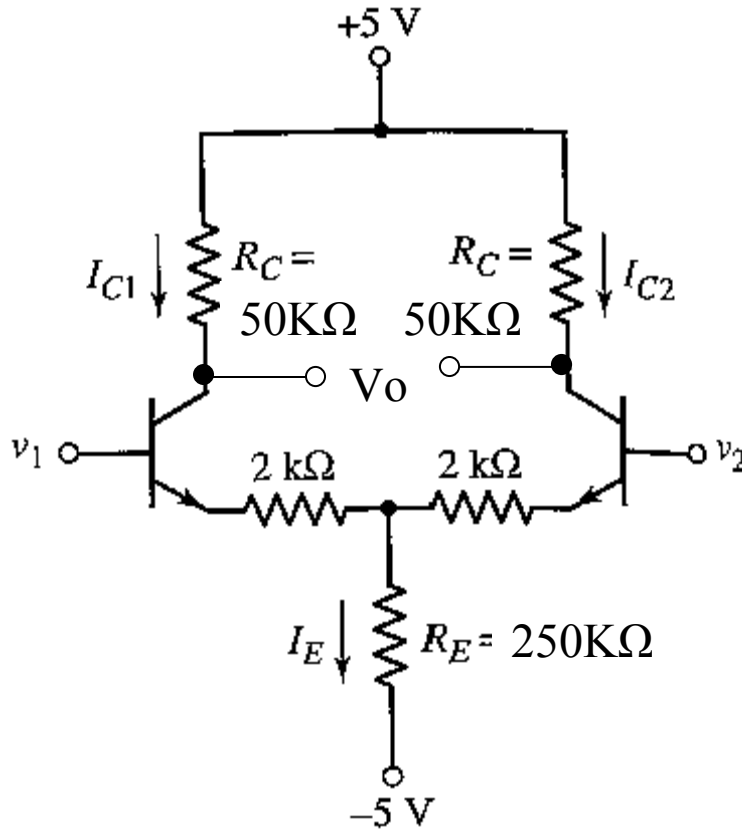


- (1)  $\approx 0.1$  ;  $\approx 25$       (2)  $\approx 0.1$ ;  $\approx 50$       (3)  $\approx 0.2$ ;  $\approx 50$       (4)  $\approx 0.2$ ;  $\approx 25$   
 (5)  $\approx 25$ ;  $\approx 0.1$       (6) None of the below

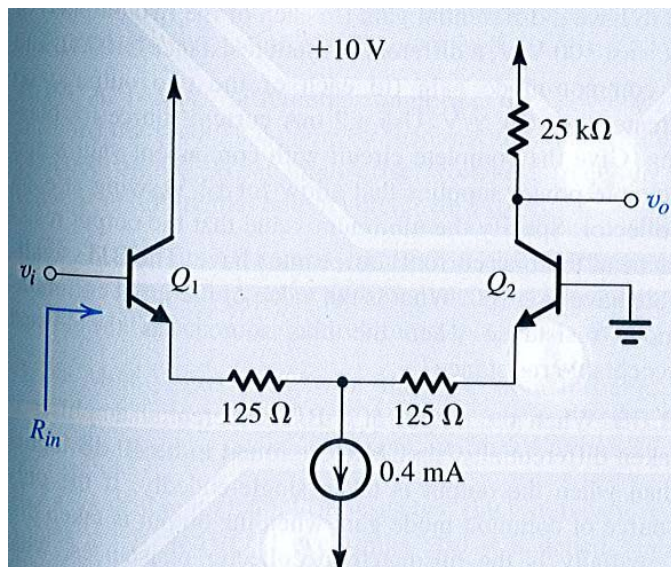13) What is the differential mode input impedance of the amplifier shown below? assume  $\beta=100$ ,  $V_{BE(on)}=0.7$ ,  $V_T=25$  mV, and  $V_A=100$ V.



- (1) 50 kΩ
- (2) 250 Ω
- (3) 25 kΩ
- (4) 25.25 kΩ
- (5) 12.625 kΩ
- (6) None of the above

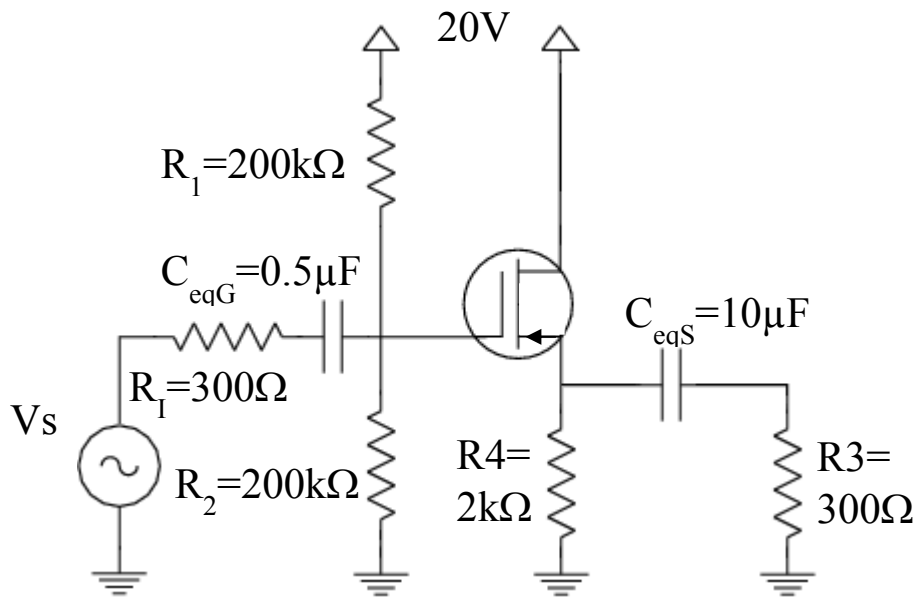14) For the common drain amplifier shown below, the transconductance of the MOSFET is  $g_m = 10\text{mS}$ . Due to the high impedance at the output, the low cut-off frequency,  $\omega_L$ , is dominated by the output pole:  $\omega_L \approx \omega_{out} \approx \frac{1}{R_{eqs}C_{eqs}}$



$R_{eqs}$  is the equivalent resistance “looking into” the output capacitor,  $C_{eqs}$ . What is the value of  $R_{eqs}$ ?

- (1)  $R_{eqs} = 395.2\Omega$                       (2)  $R_{eqs} = 300.0\Omega$                       (3)  $R_{eqs} = 260.9\Omega$
- (4)  $R_{eqs} = 75.0\Omega$                       (5)  $R_{eqs} = 360.9\Omega$                       (6) None of the above


15) Find  $A_{\text{mid}}$  for this transfer function.

$$A_v(s) = \frac{10^{10} s^2 (s+1)(s+200)}{(s+3)(s+5)(s+7)(s+100)^2 (s+300)}$$

- (1) 1
- (2)  $10^{10}$
- (3)  $2 \times 10^{12}$
- (4)  $3.33 \times 10^5$
- (5)  $6.67 \times 10^5$
- (6) None of the above



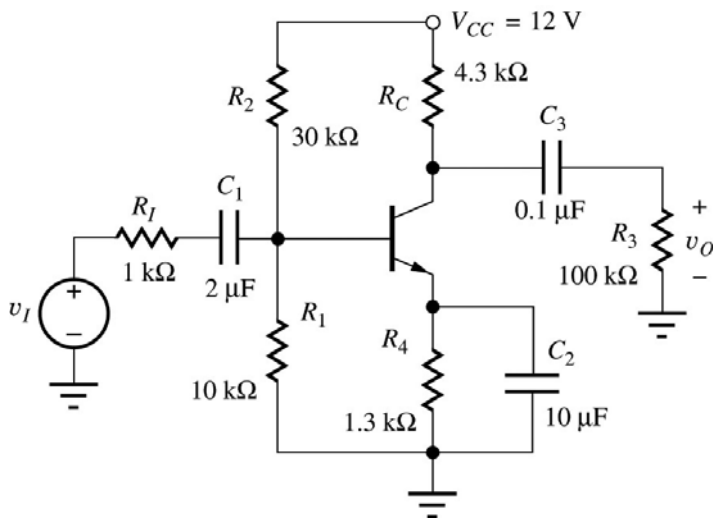
16) Short circuit time constant method is an important technique to determine the low cut-off frequency using equation:  $\omega_L \cong \sum_{i=1}^3 \frac{1}{R_{iS} C_i}$ . For the circuit below, what is the  $R_{1S}$  for the BJT base related loop? Here  $r_{\pi}=1.51 \text{ k}\Omega$  and  $\beta_0=99$  and  $r_0=46.8 \text{ k}\Omega$ .



- 
- (1) 4.88 kΩ
  - (2) 3.044 kΩ
  - (3) 7.095 kΩ
  - (4) 8.095 kΩ
  - (5) 2.26 kΩ
  - (6) None of the above

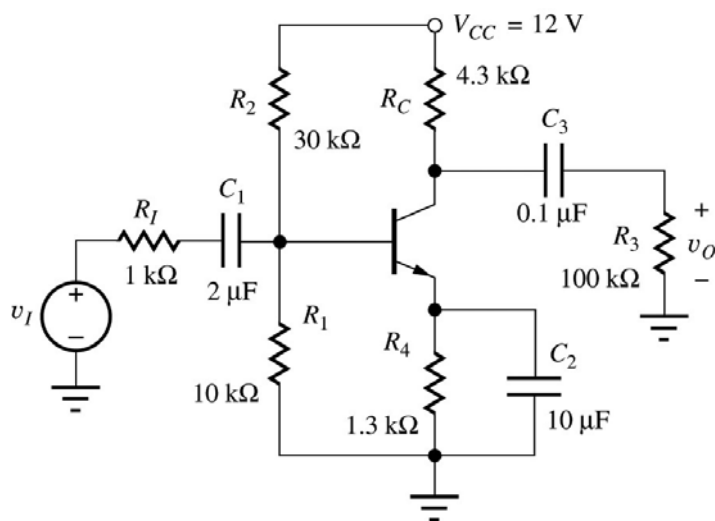17) Short circuit time constant method is an important technique to determine the low cut-off frequency using equation:  $\omega_L \cong \sum_{i=1}^3 \frac{1}{R_i S C_i}$ . For the circuit below (the same


as in Problem 16), what is the time constant for the BJT collector related loop? Here  $r_{\pi}=1.51 \text{ k}\Omega$ ,  $\beta_0=99$ , and  $r_0=46.8 \text{ k}\Omega$ .



- 
- (1) 96.1 rad/s
  - (2) ~ 0.01 s
  - (3) 0.96 rad/s
  - (4) ~ 1.0 s
  - (5) ~ 0.1 s
  - (6) None of the above

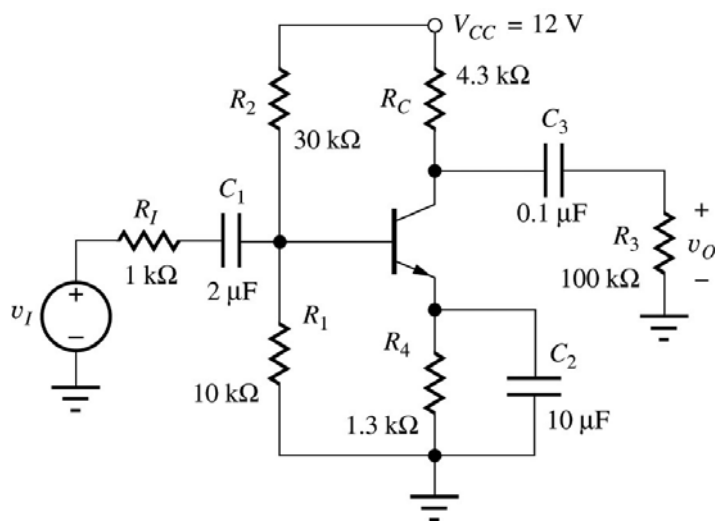
18) Short circuit time constant method is an important technique to determine the low cut-off frequency using equation:  $\omega_L \cong \sum_{i=1}^3 \frac{1}{R_{iS} C_i}$ . For the circuit below (the same

as in Problems 16 and 17), what is  $\omega_L$  for the whole BJT related circuit if  $R_{2S}$  in the emitter loop is known as  $23.3\Omega$ ? Here  $r_{\pi}=1.51 \text{ k}\Omega$ ,  $\beta_0=99$ , and  $r_0=46.8 \text{ k}\Omega$ .




- 
- (1) 2300 rad/s
  - (2) 222 rad/s
  - (3) 96.1 rad/s
  - (4) 4513 rad/s
  - (5)  $2.16 \times 10^{-4}$  rad/s
  - (6) None of the above

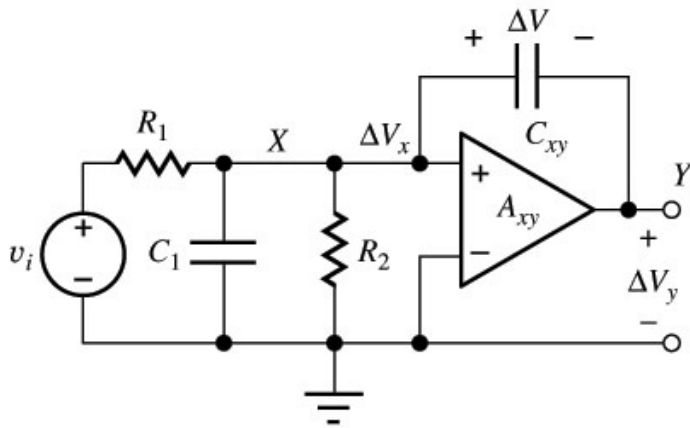19) The circuit below highlights the so-called “Miller Effect”. Determine the equivalent capacitance at the input and the output of this operational amplifier! Assuming  $C_{xy}=1\mu\text{F}$ ,  $C_1=1\mu\text{F}$  and  $A_{xy}=-50$ .



- 1)  $C_{eq}(\text{input})=1\mu\text{F}$  and  $C_{eq}(\text{output})=1\mu\text{F}$
- 2)  $C_{eq}(\text{input})=52\mu\text{F}$  and  $C_{eq}(\text{output})=1\mu\text{F}$
- 3)  $C_{eq}(\text{input})=50\mu\text{F}$  and  $C_{eq}(\text{output})=1\mu\text{F}$
- 4)  $C_{eq}(\text{input})=51\mu\text{F}$  and  $C_{eq}(\text{output})=51\mu\text{F}$
- 5)  $C_{eq}(\text{input})=52\mu\text{F}$  and  $C_{eq}(\text{output})=50\mu\text{F}$
- 6) None of the above

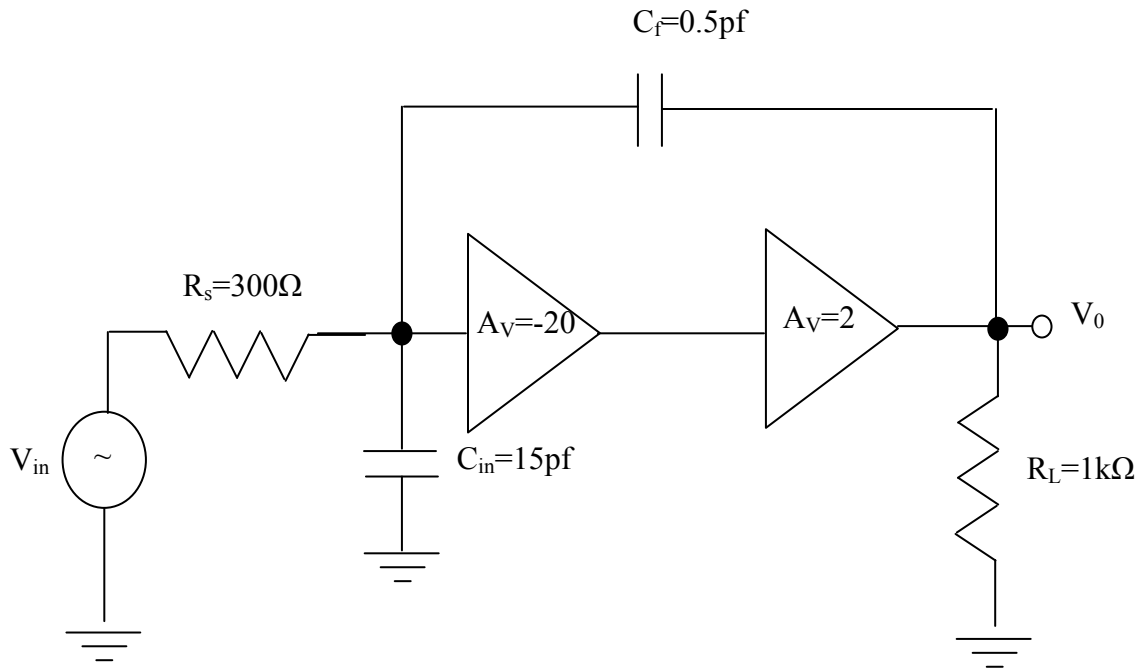20) For the amplifier circuit shown below what is the high cutoff frequency  $f_H$ ?



- (1) ~94MHz
- (2) ~5MHz
- (3) ~35MHz
- (4) ~15 MHz
- (5) ~10MHz
- (6) None of the above