

---


# Chapter 4

## Field-Effect Transistors

### Microelectronic Circuit Design

Richard C. Jaeger

Travis N. Blalock

 


# Chapter Goals

---


- Describe operation of MOSFETs.
- Define FET characteristics in operation regions of cutoff, triode and saturation.
- Develop mathematical models for  $i$ - $v$  characteristics of MOSFETs.
- Introduce graphical representations for output and transfer characteristic descriptions of electron devices.
- Define and contrast characteristics of enhancement-mode and depletion-mode FETs.
- Define symbols to represent FETs in circuit schematics.
- Investigate circuits that bias transistors into different operating regions.
- Learn basic structure and mask layout for MOS transistors and circuits.
- Explore MOS device scaling
- Contrast 3 and 4 terminal device behavior.
- Describe sources of capacitance in MOSFETs.
- Explore FET modeling in SPICE.

# MOS Capacitor Structure

 

- First electrode - Gate: Consists of low-resistivity material such as metal or doped polycrystalline silicon
- Second electrode - Substrate or Body: *n*- or *p*-type semiconductor
- Dielectric - Silicon dioxide: stable high-quality electrical insulator between gate and substrate.
 
# Substrate Conditions for Different Biases



## Accumulation

- $V_G \ll V_{TN}$

## Depletion


- $V_G < V_{TN}$

## Inversion

- $V_G > V_{TN}$


# Low-frequency C-V Characteristics for an MOS Capacitor on p-type Substrate

---

 

- MOS capacitance is a non-linear function of voltage.
- Total capacitance in any region is dictated by the separation between capacitor plates.
- Total capacitance modeled as series combination of fixed oxide capacitance and voltage-dependent depletion-layer capacitance.


# NMOS Transistor: Structure

 

- 4 device terminals: Gate(G), Drain(D), Source(S) and Body(B).
- Source and drain regions form *pn* junctions with substrate.
- $v_{SB}$ ,  $v_{DS}$  and  $v_{GS}$  always positive during normal operation.
- $v_{SB}$  always  $< v_{DS}$  and  $v_{GS}$  to reverse bias *pn* junctions

# NMOS Transistor:

## Qualitative I-V Behavior

 


- $V_{GS} \ll V_{TN}$  : Only small leakage current flows.
- $V_{GS} < V_{TN}$ : Depletion region formed under gate merges with source and drain depletion regions. No current flows between source and drain.
- $V_{GS} > V_{TN}$ : Channel formed between source and drain. If  $v_{DS} > 0$ , finite  $i_D$  flows from drain to source.
- $i_B = 0$  and  $i_G = 0$ .

# NMOS Transistor:

## Triode Region Characteristics

---

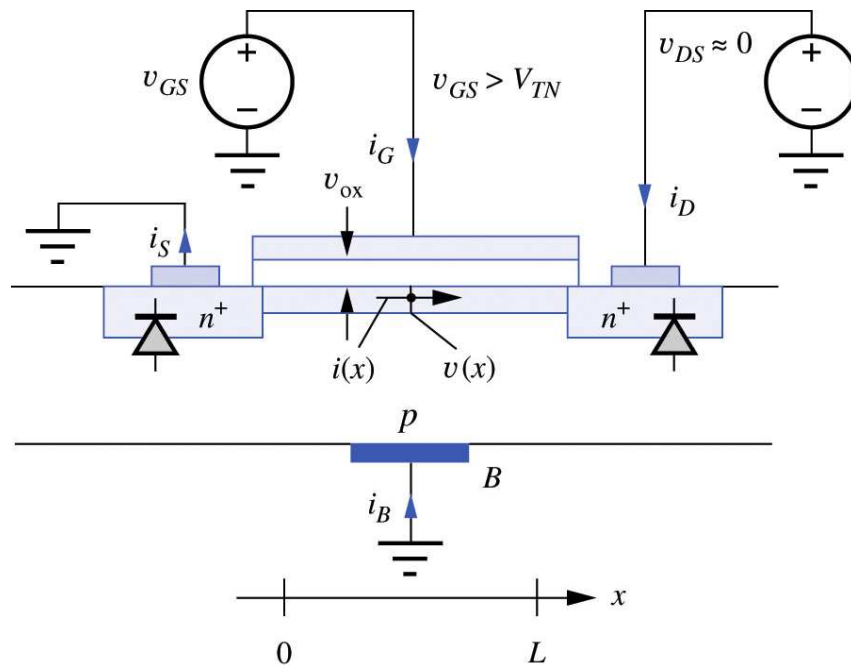

$$i_D = K_n \left( v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS}$$

$$\text{for } v_{GS} - V_{TN} \geq v_{DS} \geq 0$$

$$K_n = K'_n W/L$$

$$K'_n = \mu_n C''_{ox} \quad (\text{A/V}^2)$$

$$C''_{ox} = \epsilon_{ox}/T_{ox}$$


$$\epsilon_{ox} = \text{oxide permittivity (F/cm)}$$

$$T_{ox} = \text{oxide thickness (cm)}$$



# NMOS Transistor:


## Triode Region Characteristics (cont.)

 


- Output characteristics appear to be linear.
- FET behaves like a gate-source voltage-controlled resistor between source and drain with

$$R_{on} = \left[ \frac{\partial i_D}{\partial v_{DS}} \bigg|_{v_{DS} \rightarrow 0} \right]_{Q-Pt}^{-1} = \frac{1}{K'_n \frac{W}{L} (V_{GS} - V_{TN} - V_{DS})} \bigg|_{V_{DS} \rightarrow 0} = \frac{1}{K'_n \frac{W}{L} (V_{GS} - V_{TN})}$$
 
# MOSFET as a Voltage-Controlled Resistor



(a)

 

(b)

## Example 1: Voltage-Controlled Attenuator

$$\frac{v_O}{v_S} = \frac{R_{on}}{R_{on} + R} = \frac{1}{1 + K_n R (V_{GG} - V_{TN})}$$

If  $K_n = 500 \mu\text{A}/\text{V}^2$ ,  $V_{TN} = 1\text{V}$ ,  $R = 2\text{k}\Omega$  and  $V_{GG} = 1.5\text{V}$ , then,


$$\frac{v_O}{v_S} = \frac{1}{1 + 500 \frac{\mu\text{A}}{\text{V}^2} (2000\Omega)(1.5 - 1)\text{V}} = 0.667$$

To maintain triode region operation,


$$v_{DS} \leq v_{GS} - V_{TN} \quad \text{or} \quad v_O \leq V_{GG} - V_{TN}$$

$$0.667v_S \leq (1.5 - 1)\text{V} \quad \text{or} \quad v_S \leq 0.750\text{V}$$
 
# MOSFET as a Voltage-Controlled Resistor (cont.)



(c)

 

(d)

## Example 2: Voltage-Controlled High-Pass Filter

Voltage Transfer function,  $T(s) = \frac{V_o(s)}{V_s(s)} = \frac{s}{s + \omega_o}$   
 where, cut-off frequency

$$\omega_o = \frac{1}{R_{on}C} = \frac{K_n(V_{GS} - V_{TN})}{C}$$



If  $K_n = 500 \mu\text{A}/\text{V}^2$ ,  $V_{TN} = 1\text{V}$ ,  $C = 0.02 \mu\text{F}$   
 and  $V_{GG} = 1.5\text{V}$ , then,

$$f_o = \frac{500 \frac{\mu\text{A}}{\text{V}^2} (1.5 - 1)\text{V}}{2\pi(0.02 \mu\text{F})} = 1.99 \text{ kHz}$$

To maintain triode region operation,

$$v_S \leq V_{GG} - V_{TN} = 0.5 \text{ V}$$

# NMOS Transistor: Saturation Region

  


- If  $v_{DS}$  increases above triode region limit, the channel region disappears and is said to be pinched-off.
- Current saturates at constant value, independent of  $v_{DS}$ .
- Saturation region operation mostly used for analog amplification.

# NMOS Transistor:

## Saturation Region (cont.)

---

 

$$i_D = \frac{K'_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2 \quad \text{for} \quad v_{DS} \geq v_{GS} - V_{TN}$$

$v_{DSAT} = v_{GS} - V_{TN}$  is termed the saturation or pinch - off voltage

---

# Transconductance of an MOS Device

---


- Transconductance relates the change in drain current to a change in gate-source voltage

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{Q-pt}$$

- Taking the derivative of the expression for the drain current in saturation region,


$$g_m = K'_n \frac{W}{L} (V_{GS} - V_{TN}) = \frac{2I_D}{V_{GS} - V_{TN}}$$

# Channel-Length Modulation

 


- As  $v_{DS}$  increases above  $v_{DSAT}$ , the length of the depleted channel beyond the pinch-off point,  $\Delta L$ , increases and the actual  $L$  decreases.
- $i_D$  increases slightly with  $v_{DS}$  instead of being constant.
 
$$i_D = \frac{K'_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$$



$\lambda$  = channel length modulation parameter

# Depletion-Mode MOSFETS

 


- NMOS transistors with  $V_{TN} < 0$
- Ion implantation process is used to form a built-in *n*-type channel in the device to connect source and drain by a resistive channel
- Non-zero drain current for  $v_{GS} = 0$
- Negative  $v_{GS}$  required to turn device off.



# Transfer Characteristics of MOSFETs


## Enhancement- & Depletion-Mode Devices

---

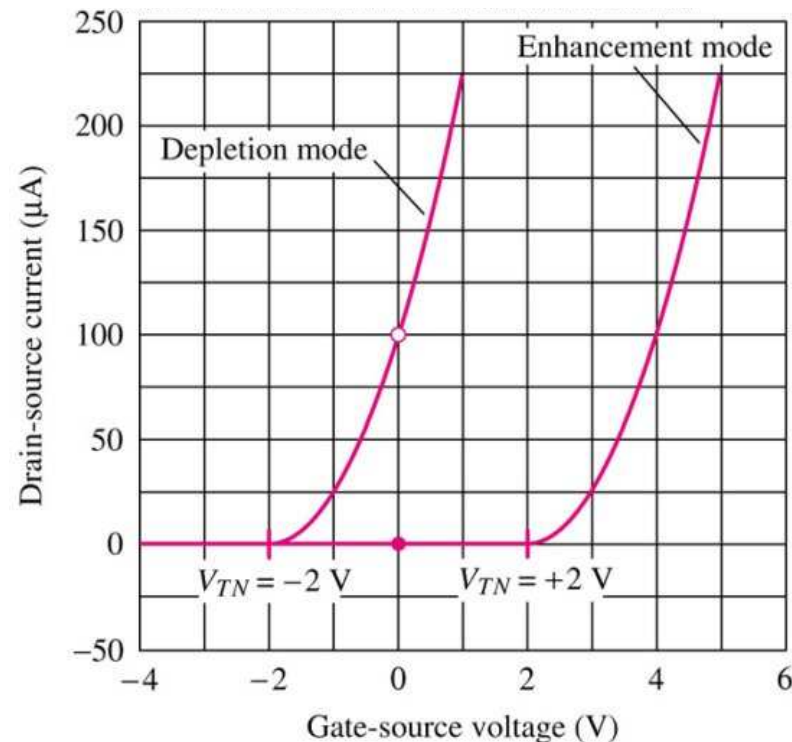

- Transfer Characteristic: Plots drain current versus gate-source voltage for a fixed drain-source voltage

# Body Effect or Substrate Sensitivity

 

- Non-zero  $v_{SB}$  changes threshold voltage, causing substrate sensitivity modeled by

$$V_{TN} = V_{TO} + \gamma \left( \sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right)$$

where

$V_{TO}$  = threshold voltage for  $v_{SB} = 0$

$\gamma$  = body - effect parameter ( $\sqrt{V}$ )


$2\phi_F$  = surface potential (V)

# NMOS Model Summary

---

QuickTime™ and a  
decompressor  
are needed to see this picture.
 
# PMOS Transistors: Enhancement-Mode Structure




PMOS transistor

- $p$ -type source and drain regions in an  $n$ -type substrate.
- $v_{GS} < 0$  required to create  $p$ -type inversion layer in channel region
- For current flow,  $v_{GS} < V_{TP}$
- To maintain reverse bias on source-substrate and drain-substrate junctions,  $v_{SB} < 0$  and  $v_{DB} < 0$
- Positive bulk-source potential causes  $V_{TP}$  to become more negative

# PMOS Transistors: Output Characteristics

---

 


- For  $v_{GS} > V_{TP}$ , transistor is off.
- For more negative  $v_{GS}$ , drain current increases in magnitude.
- PMOS device is in the triode region for small values of  $V_{DS}$  and in saturation for larger values.
- Remember  $V_{TP} < 0$  for an enhancement mode transistor

# PMOS Model Summary


---

QuickTime™ and a  
decompressor  
are needed to see this picture.


# MOSFET Circuit Symbols

 


(a) NMOS enhancement-mode device

 


(b) PMOS enhancement-mode device

 



(c) NMOS depletion-mode device

 



(d) PMOS depletion-mode device

 


(e) Three-terminal NMOS transistors

  


(f) Three-terminal PMOS transistors

  

 
(g) Shorthand notation—NMOS enhancement-mode device



 (h) Shorthand notation—NMOS depletion-mode device



 (i) Shorthand notation—PMOS enhancement-mode device



(j) Shorthand notation—PMOS depletion-mode device

- (g) and (i) are the most commonly used symbols in VLSI logic design.
- MOS devices are symmetric.
- In NMOS,  $n^+$  region at higher voltage is the drain.
- In PMOS  $p^+$  region at lower voltage is the drain


# Internal Capacitances in Electronic Devices

---

- Limit high-frequency performance of the electronic device they are associated with.
- Limit switching speed of circuits in logic applications
- Limit frequency at which useful amplification can be obtained in amplifiers.
- MOSFET capacitances depend on region of operation and are non-linear functions of voltages at device terminals.


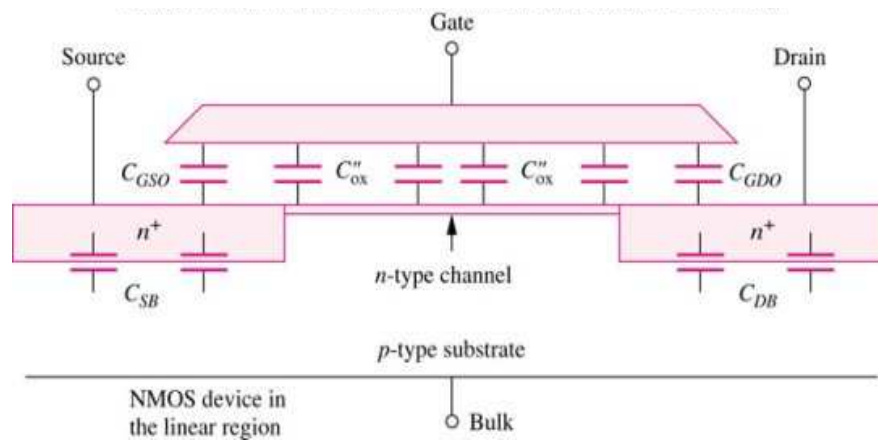
# NMOS Transistor Capacitances: Triode Region



$C_{ox}''$  = Gate-channel capacitance per unit area ( $F/m^2$ ).

$C_{GC}$  = Total gate channel capacitance.

$C_{GS}$  = Gate-source capacitance.

$C_{GD}$  = Gate-drain capacitance.

$C_{GSO}$  and  $C_{GDO}$  = overlap capacitances ( $F/m$ ).

$$C_{GS} = \frac{C_{GC}}{2} + C_{GSO}W = C_{ox}'' \frac{WL}{2} + C_{GSO}W$$

$$C_{GD} = \frac{C_{GC}}{2} + C_{GDO}W = C_{ox}'' \frac{WL}{2} + C_{GDO}W$$

# NMOS Transistor Capacitances: Triode Region (cont.)

---

$$C_{SB} = C_J A_S + C_{JSW} P_S$$

$$C_{DB} = C_J A_D + C_{JSW} P_D$$

$C_{SB}$  = Source-bulk capacitance.


$C_{DB}$  = Drain-bulk capacitance.

$A_S$  and  $A_D$  = Junction bottom area  
capacitance of the source and  
drain regions.

$P_S$  and  $P_D$  = Perimeter of the  
source and drain junction  
regions.

# NMOS Transistor Capacitances: Saturation Region

---

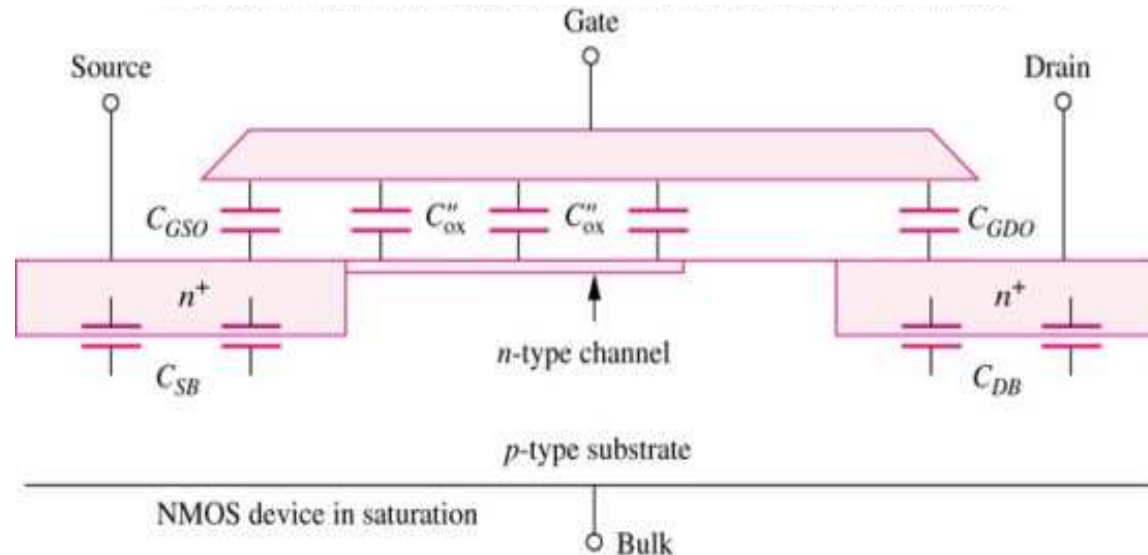


- Drain no longer connected to channel

$$C_{GS} = \frac{2}{3} C_{GC} + C_{GSO} W$$

$$C_{GD} = \frac{2}{3} C_{GDO} W$$
 
# NMOS Transistor Capacitances: Cutoff Region



- Conducting channel region completely gone.

$C_{GB}$  = gate-bulk capacitance

$C_{GBO}$  = gate-bulk capacitance per unit width.


$$C_{GS} = C_{GSO}W$$

$$C_{GD} = C_{GDO}W$$

$$C_{GB} = C_{GBO}W$$

# SPICE Model for NMOS Transistor

Typical default values used by SPICE:

 

$$KP = 50 \text{ or } 20 \mu\text{A/V}^2$$

$$\gamma = 0$$

$$\lambda = 0$$

$$V_{TO} = 1 \text{ V}$$

$$\mu_n \text{ or } \mu_p = 500 \text{ or } 200 \text{ cm}^2/\text{V-s}$$

$$2\Phi_F = 0.6 \text{ V}$$

$$C_{GDO} = C_{GSO} = C_{GBO} = C_{JSW} = 0$$

$$T_{ox} = 100 \text{ nm}$$

# MOS Transistor Scaling

## Scale Factor $\alpha$

---

- Drain current:

$$K_n^* = \mu_n \frac{\epsilon_{ox}}{T_{ox}/\alpha} \frac{W/\alpha}{L/\alpha} = \alpha \mu_n \frac{\epsilon_{ox}}{T_{ox}} \frac{W}{L} = \alpha K_n$$

$$i_D^* = \mu_n \frac{\epsilon_{ox}}{T_{ox}/\alpha} \frac{W/\alpha}{L/\alpha} \left( \frac{v_{GS}}{\alpha} - \frac{V_{TN}}{\alpha} - \frac{v_{DS}}{2\alpha} \right) \frac{v_{DS}}{2\alpha} = \frac{i_D}{\alpha}$$

- Gate Capacitance:

$$C_{GC}^* = (C_{ox}^*) W^* L^* = \frac{\epsilon_{ox}}{T_{ox}/\alpha} \frac{W/\alpha}{L/\alpha} = \frac{C_{GC}}{\alpha}$$

$$\tau^* = C_{GC}^* \frac{\Delta V^*}{i_D^*} = \frac{\tau}{\alpha}$$

where  $\tau$  is the circuit delay in a logic circuit.

# MOS Transistor Scaling

## Scale Factor $\alpha$ (cont.)

---

- Circuit and Power Densities:

$$P^* = V_{DD}^* i_D^* = \frac{V_{DD}}{\alpha} \frac{i_D}{\alpha} = \frac{P}{\alpha^2}$$
$$\frac{P^*}{A^*} = \frac{P^*}{W^* L^*} = \frac{P/\alpha^2}{(W/\alpha)(L/\alpha)} = \frac{P}{A} \quad \text{extremely important result!}$$

- Power-Delay Product:

$$PDP^* = P^* \tau^* = \frac{P}{\alpha^2} \frac{\tau}{\alpha} = \frac{PDP}{\alpha^3}$$

- Cutoff Frequency:

$$\omega_T = \frac{g_m}{C_{GC}} = \frac{\mu_n}{L^2} (V_{GS} - V_{TN})$$

$f_T$  improves with square of channel length reduction

---

# MOS Transistor Scaling (cont.)


---

- High Field Limitations:
  - High electric fields arise if technology is scaled down with supply voltage constant.
  - Causes reduction in mobility of MOS transistor, breakdown of linear relationship between mobility and electric field and carrier velocity saturation.
  - Ultimately results in reduced long-term reliability and breakdown of gate oxide or *pn* junction.
  - Drain current in saturation region is linearized to

$$i_D = \frac{C_{ox}'' W}{2} (v_{GS} - V_{TN}) v_{SAT} \quad \text{where } v_{SAT} \text{ is carrier saturation velocity}$$




# MOS Transistor Scaling (cont.)

 

- Sub-threshold Conduction:
  - $i_D$  decreases exponentially for  $V_{GS} < V_{TN}$ .
  - Reciprocal of the slope in mV/decade gives the turn-off rate for the MOSFET.
  - $V_{TN}$  should be reduced if dimensions are scaled down. However, curve in sub-threshold region shifts horizontally instead of scaling with  $V_{TN}$

# Process-defining Factors

---

 


- **Minimum Feature Size  $F$**  : Width of smallest line or space that can be reliably transferred to the wafer surface using a given generation of lithographic manufacturing tools
- **Alignment Tolerance  $T$** : Maximum misalignment that can occur between two mask levels during fabrication

# Mask Sequence


## Polysilicon-Gate Transistor

---

 

- Mask 1: Defines active area or thin oxide region of transistor
- Mask 2: Defines polysilicon gate of transistor, aligns to mask 1
- Mask 3: Delineates the contact window, aligns to mask 2.
- Mask 4: Delineates the metal pattern, aligns to mask 3.
- Channel region of transistor formed by intersection of first two mask layers. Source and Drain regions formed wherever mask 1 is not covered by mask 2


# Basic Ground Rules for Layout

 

- $F = 2\Lambda$
- $T = F/2 = \Lambda$
- $\Lambda$  could be 1, 0.5, 0.25  $\mu\text{m}$ , etc.
- $W/L = 10\Lambda/2\Lambda = 5/1$
- Transistor Area =  $120\Lambda^2$
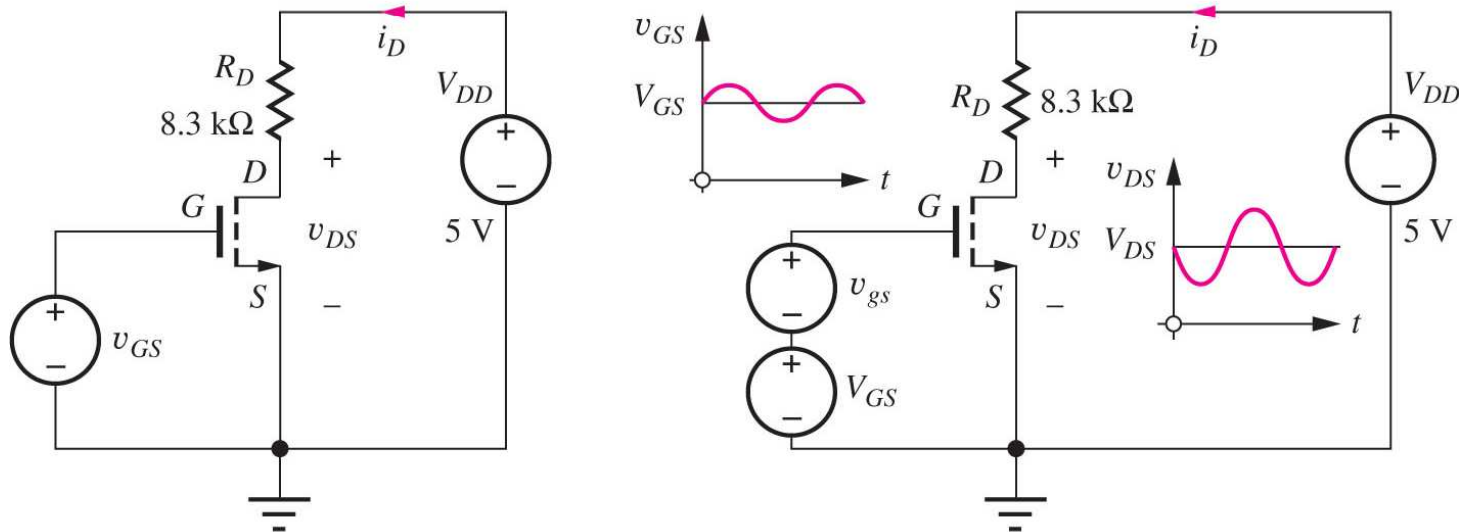
# MOSFET Biasing

- ‘Bias’ sets the dc operating point around which the device operates.
- The ‘signal’ is actually comprised of relatively small changes in the voltages and/or currents.
- Remember (Total = dc + signal):  $v_{GS} = V_{GS} + v_{gs}$  and  $i_D = I_D + i_d$



# Bias Analysis Approach

---

- Assume an operation region (generally the saturation region)
- Use circuit analysis to find  $V_{GS}$
- Use  $V_{GS}$  to calculate  $I_D$ , and  $I_D$  to find  $V_{DS}$
- Check validity of operation region assumptions
- Change assumptions and analyze again if required.

NOTE: An enhancement-mode device with  $V_{DS} = V_{GS}$  is always in saturation

# Four-Resistor and Two-Resistor Biasing



---

- Provide excellent bias for transistors in discrete circuits.
- Stabilize bias point with respect to device parameter and temperature variations using negative feedback.
- Use single voltage source to supply both gate-bias voltage and drain current.
- Generally used to bias transistors in saturation region.
- Two-resistor biasing uses fewer components than four-resistor biasing

# Bias Analysis - Example 1:

## Constant Gate-Source Voltage Biasing

---

  

**Problem:** Find Q-pt ( $I_D$ ,  $V_{DS}$ ,  $V_{GS}$ )

**Approach:** Assume operating region, find Q-point, check to see if result is consistent with assumed region of operation

**Assumption:** Transistor is saturated,  $I_G = I_B = 0$


**Analysis:** Simplify circuit with Thévenin transformation to find  $V_{EQ}$  and  $R_{EQ}$  for gate-bias voltage. Find  $V_{GS}$  and then use this to find  $I_D$ . With  $I_D$ , we can then calculate  $V_{DS}$ .



# Bias Analysis - Example 1:

## Constant Gate-Source Voltage Biasing (cont.)

---

 

$$V_{DD} = I_D R_D + V_{DS}$$

$$V_{DS} = 10V - (50\mu A)(100K) = 5.00 V$$

**Check:**  $V_{DS} > V_{GS} - V_{TN}$ . Hence saturation region assumption is correct.

**Q-pt: (50.0  $\mu A$ , 5.00 V) with  $V_{GS} = 3.00 V$**

**Discussion:** The Q-point of this circuit is quite sensitive to changes in transistor characteristics, so it is not widely used.

Since  $I_G = 0$ ,

$$V_{EQ} = I_G R_{EQ} + V_{GS} = V_{GS}$$



$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2$$

$$I_D = \frac{25 \times 10^{-6}}{2} \frac{A}{V^2} (3 - 1)^2 V^2 = 50.0 \mu A$$

# Bias Analysis - Example 2:

## Load Line Analysis

---

  

**Problem:** Find Q-pt ( $I_D$ ,  $V_{DS}$ ,  $V_{GS}$ )

**Approach:** Find an equation for the load line. Use this to find Q-pt at intersection of load line with device characteristic.

$$V_{DD} = I_D R_D + V_{DS}$$

**Assumption:** Transistor is saturated,  $I_G = I_B = 0$


**Analysis:** For circuit values above, load line becomes

$$10V = I_D (100K) + V_{DS}$$

Use this to find two points on the load line.

# Bias Analysis - Example 2:

## Load Line Analysis (cont.)

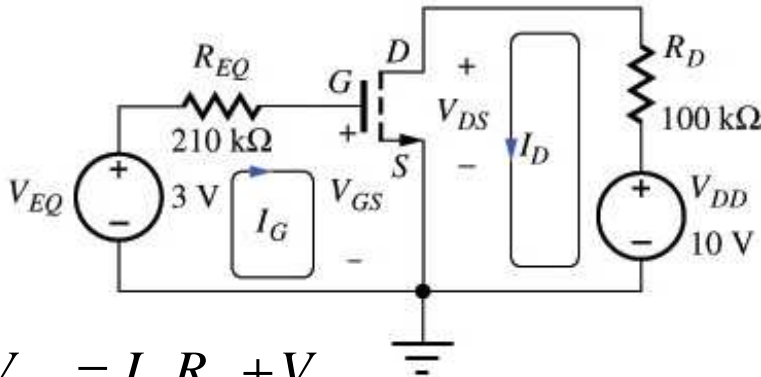


$$V_{DD} = I_D R_D + V_{DS}$$

$$10 = 10^5 I_D + V_{DS}$$

For  $V_{DS} = 0$ ,  $I_D = 100 \mu\text{A}$

For  $I_D = 0$ ,  $V_{DS} = 10 \text{ V}$

 Plotting the line on the transistor output characteristic yields Q-pt at intersection with  $V_{GS} = 3\text{V}$  device curve.



**Check:** The load line approach agrees with previous calculation.



**Q-pt:** (50.0  $\mu\text{A}$ , 5.00 V) with  $V_{GS} = 3.00 \text{ V}$

**Discussion:** Q-pt is clearly in the saturation region. Graphical load line is good visual aid to see device operating region.

# Bias Analysis - Example 3:

## Constant Gate-Source Voltage Biasing with Channel-Length Modulation

---

  

**Problem:** Find Q-pt ( $I_D$ ,  $V_{DS}$ ,  $V_{GS}$ ) of previous example, given  $\lambda = 0.02\text{ V}^{-1}$ .

**Assumption:** Transistor is saturated,  $I_G = I_B = 0$

**Approach:** Assume operation region, find Q-point, check to see if result is consistent with operation region

**Analysis:** Simplify circuit with Thévenin transformation to find  $V_{EQ}$  and  $R_{EQ}$  for gate-bias voltage. Find  $V_{GS}$  and then use this to find  $I_D$ . With  $I_D$ , we can then calculate  $V_{DS}$ .

## Bias Analysis - Example 3:

### Constant Gate-Source Voltage Biasing with Channel-Length Modulation (cont.)

---

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

$$V_{DS} = V_{DD} - I_D R_D$$


$$V_{DS} = 10 - \frac{25 \times 10^{-6}}{2} (10^5) (3 - 1)^2 (1 + 0.02 V_{DS})$$

$$V_{DS} = 4.55 \text{ V}$$

$$I_D = \frac{25 \times 10^{-6}}{2} (3 - 1)^2 [1 + 0.02(4.55)] = 54.5 \mu\text{A}$$

**Check:**  $V_{DS} > V_{GS} - V_{TN}$ . Hence the saturation region assumption is correct.

 
**Q-pt:** (54.5  $\mu\text{A}$ , 4.55 V) with  
 $V_{GS} = 3.00 \text{ V}$



**Discussion:** The bias levels have changed by about 10% (54.5  $\mu\text{A}$  vs 50  $\mu\text{A}$ ). Typically, component values will vary more than this, so there is little value in including  $\lambda$  effects in most circuits.

# Bias Analysis - Example 4:

## Four-Resistor Biasing

 


**Assumption:** Transistor is saturated,  $I_G = I_B = 0$

**Analysis:** First, simplify circuit, split  $V_{DD}$  into two equal-valued sources and apply Thévenin transformation to find  $V_{EQ}$  and  $R_{EQ}$  for gate-bias voltage

 **Problem:** Find Q-pt ( $I_D$ ,  $V_{DS}$ )

**Approach:** Assume operation region, find Q-point, check to see if result is consistent with operation region



# Bias Analysis - Example 4:

## Four-Resistor Biasing (cont.)

$$V_{EQ} = V_{DD} \frac{R_1}{R_1 + R_2} = 10V \frac{1M\Omega}{1M\Omega + 1.5M\Omega} = 4V$$

$$R_{EQ} = R_1 \parallel R_2 = 1M\Omega \parallel 1.5M\Omega = 600k\Omega$$


Since  $I_G = 0$ ,  $V_{EQ} = V_{GS} + I_D R_S$

$$V_{EQ} = V_{GS} + \frac{K_n}{2} (V_{GS} - V_{TN})^2 R_S$$

$$4 = V_{GS} + \frac{25 \times 10^{-6}}{2} (39 \times 10^3) (V_{GS} - 1)^2$$

$$V_{GS} = -2.71V \text{ or } +2.66V$$

 Since  $V_{GS} < V_{TN}$  for  $V_{GS} = -2.71V$ ,  
the MOSFET would be off.



$$\therefore V_{GS} = +2.66V \text{ and } I_D = 34.4 \mu A$$

$$V_{DS} = V_{DD} - I_D R_D = 6.08V$$


$V_{DS} > V_{GS} - V_{TN}$ . Hence the saturation region assumption is correct.

**Q-pt: (34.4  $\mu A$ , 6.08 V) with  $V_{GS} = 2.66V$**

# Bias Analysis - Example 5:
 
## Four-Resistor Biasing with Body Effect

Analysis with body effect using the same assumptions as in example 1:



$$V_{GS} = V_{EQ} - I_D R_S = 6 - 22000 I_D$$

$$V_{SB} = I_D R_S = +22000 I_D$$

$$V_{TN} = V_{TO} + \gamma \left( \sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right)$$

$$V_{TN} = 1 + 0.5 \left( \sqrt{v_{SB} + 0.6} - \sqrt{0.6} \right)$$

$$I_D' = \frac{25 \times 10^{-6}}{2} (V_{GS} - V_{TN})^2$$

Iterative solution can be found using the following steps:

- Estimate value of  $I_D$  and use it to find  $V_{GS}$  and  $V_{SB}$
- Use  $V_{SB}$  to calculate  $V_{TN}$
- Find  $I_D'$  using above 2 steps
- If  $I_D'$  is not same as original  $I_D$  estimate, start again.



# Bias Analysis - Example 5:

## Four-Resistor Biasing (cont.)

---

The iteration sequence leads to  $I_D = 88.0 \mu\text{A}$ ,  $V_{TN} = 1.41 \text{ V}$ ,

$$V_{DS} = V_{DD} - I_D (R_D + R_S) = 10 - 4 \times 10^4 I_D = 6.48 \text{ V}$$

$V_{DS} > V_{GS} - V_{TN}$ . Hence saturation region assumption is correct.

**Q-pt: (88.0  $\mu\text{A}$ , 6.48 V)**


**Check:**  $V_{DS} > V_{GS} - V_{TN}$ , therefore still in active region.

**Discussion:** Body effect has decreased current by 12% and increased threshold voltage by 40%.

# Bias Analysis - Example 6:

## Two-Resistor Feedback Biasing

---

 

**Assumption:**  $I_G = I_B = 0$ , transistor is saturated (since  $V_{DS} = V_{GS}$ )

**Analysis:**  $V_{DS} = V_{DD} - I_D R_D$

$$V_{GS} = V_{DD} - \frac{K_n}{2} (V_{GS} - V_{TN})^2 R_D$$

$$V_{GS} = 3.3 - \frac{2.6 \times 10^{-4}}{2} (10^4) (V_{GS} - 1)^2$$

$$V_{GS} = -0.769 \text{ V or } +2.00 \text{ V}$$

Since  $V_{GS} < V_{TN}$  for  $V_{GS} = -0.769 \text{ V}$ , the MOSFET would be cut-off,

$$\therefore V_{GS} = +2.00 \text{ V and } I_D = 130 \mu\text{A}$$

$V_{DS} > V_{GS} - V_{TN}$ . Hence saturation region assumption is correct.

**Q-pt: (130  $\mu\text{A}$ , 2.00 V)**

# Bias Analysis - Example 7:

## Biasing in Triode Region

**Assumption:** Assume saturation

**Analysis:**  $V_{GS} = V_{DD} = 4 \text{ V}$

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 = \frac{2.5 \times 10^{-4}}{2} (4 - 1)^2$$

$$I_D = 1.13 \text{ mA}$$


$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{DS} = 4 - (1.13 \times 10^{-3}) (1.6 \times 10^3) = 2.19 \text{ V}$$

But  $V_{DS} < V_{GS} - V_{TN}$ . Hence, saturation region operation is incorrect.

Using triode region equation:
 
$$I_D = K_n \left( V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$$



$$4 - V_{DS} = (1.6 \times 10^3) \left( 2.5 \times 10^{-4} \right) \left( 4 - 1 - \frac{V_{DS}}{2} \right) V_{DS}$$

$$V_{DS} = 2.30 \text{ V} \quad \text{and} \quad I_D = 1.06 \text{ mA}$$

$V_{DS} > V_{GS} - V_{TN}$ , transistor is in the triode region

**Q-pt: (1.06 mA, 2.3 V)**

# Bias Analysis - Example 8:

## Two-Resistor biasing for PMOS Transistor

**Assumption:**  $I_G = I_B = 0$ ; transistor is saturated

**Analysis:**

$$V_{GS} - I_G R_G - V_{DS} = 0 \rightarrow V_{DS} = V_{GS}$$

$$V_{DD} + V_{DS} - I_D R_D = 0$$


$$V_{DD} + V_{GS} - \frac{K_p}{2} (V_{GS} - V_{TN})^2 R_D = 0$$

$$15 + V_{GS} - (2.2 \times 10^5) \frac{5 \times 10^{-5}}{2} (V_{GS} + 2)^2 = 0$$

$$V_{GS} = -0.369 \text{ V}, -3.45 \text{ V}$$

$$\text{Since } V_{GS} = -0.369 > V_{TP}, V_{GS} = -3.45 \text{ V}$$
 
$$I_D = 52.5 \mu\text{A} \quad \text{and} \quad V_{DS} = -3.45 \text{ V}$$




$$|V_{DS}| > |V_{GS} - V_{TP}|$$

Hence saturation assumption is correct.

**Q-pt: (52.5 μA, -3.45 V)**

# Junction Field-Effect Transistor Structure

## The JFET

 

- *n*-type semiconductor block houses the channel region in *n*-channel JFET.
- Two *pn* junctions form the gate.
- Current enters channel at the drain and exits at source.

- Much lower input current and much higher input impedance than the BJT.
- In triode region, JFET is a voltage-controlled resistor:

$$R_{CH} = \frac{\rho L}{t W}$$

$\rho$  = resistivity of channel




$L$  = channel length

$W$  = channel width between *pn* junction depletion regions

$t$  = channel depth




- Inherently a depletion-mode device

# JFET with Gate-Source Bias

   


- $v_{GS} = 0$ , gate isolated from channel.
- $V_P < v_{GS} < 0$ ,  $W' < W$ , and channel resistance increases; gate-source junction is reverse-biased,  $i_G$  almost 0.
- $v_{GS} = V_P < 0$ , channel region pinched-off, channel resistance is infinite.

# JFET Channel with Drain-Source Bias

   


- With constant  $v_{GS}$ , depletion region near drain increases with  $v_{DS}$ .
- At  $v_{DSP} = v_{GS} - V_P$ , channel is totally pinched-off;  $i_D$  is saturated.
- JFET also suffers from channel-length modulation like MOSFET at larger values of  $v_{DS}$ .

# *n*-Channel JFET *i-v* Characteristics

 

Transfer Characteristics

 

Output Characteristics



# $n$ -Channel JFET

## $i$ - $v$ Characteristics (cont.)

---

- For all regions :  $i_G = 0$  for  $v_{GS} \leq 0$
- In cutoff region:  $i_D = 0$  for  $v_{GS} \leq V_P$  ( $V_P < 0$ )
- In Triode region:


$$i_D = \frac{2I_{DSS}}{V_P^2} \left( v_{GS} - V_P - \frac{v_{DS}}{2} \right) v_{DS} \quad \text{for } v_{GS} \geq V_P \text{ and } v_{GS} - V_P \geq v_{DS} \geq 0$$

- In pinch-off region:

$$i_D = I_{DSS} \left( 1 - \frac{v_{GS}}{V_P} \right)^2 (1 + \lambda v_{DS}) \quad \text{for } v_{DS} \geq v_{GS} - V_P \geq 0$$

# *p*-Channel JFET


---

 

- Polarities of *n*- and *p*-type regions of the *n*-channel JFET are reversed to get the *p*-channel JFET.
- Channel current direction and operating bias voltages are also reversed.

# JFET Circuit Symbols

---

 

- JFET structures are symmetric like MOSFETs.
- Source and drain determined by circuit voltages.

# JFET n-Channel Model Summary

---

QuickTime™ and a  
decompressor  
are needed to see this picture.


# JFET p-Channel Model Summary

---

QuickTime™ and a  
decompressor  
are needed to see this picture.

# JFET Capacitances and SPICE Modeling

---

 

$C_{GD}$  and  $C_{GS}$  are determined by depletion-layer capacitances of reverse-biased  $pn$  junctions forming gate and are bias dependent.

Typical default values used by SPICE:

$$V_p = -2 \text{ V}$$


$$\lambda = C_{GD} = C_{GS} = 0$$

Transconductance parameter BETA


$$\text{BETA} = I_{DSS}/V_P^2 = 100 \mu\text{A}/\text{V}^2$$

# Example:
 
## Biasing the JFET & Depletion-Mode MOSFET



N-channel JFET

 

Depletion-mode MOSFET

- **Assumptions:** JFET is pinched-off, gate-channel junction is reverse-biased, reverse leakage current of gate,  $I_G = 0$

# Example:

## Biasing JFET & Depletion-Mode MOSFET (cont.)

---

- **Analysis:** Since  $I_S = I_D$ ,  $V_{GS} = -I_D R_S$   
$$V_{GS} = -I_{DSS} R_S \left(1 - \frac{V_{GS}}{V_P}\right)^2 = -(5 \times 10^{-3} \text{ A})(1000 \Omega) \left(1 - \frac{V_{GS}}{-5 \text{ V}}\right)^2$$
$$\therefore V_{GS} = -1.91 \text{ V}, -13.1 \text{ V}$$

Since  $V_{GS} = -13.1 \text{ V}$  is less than  $V_P = -5 \text{ V}$ ,  $V_{GS} = -1.91 \text{ V}$ ,  
and  $I_D = I_S = 1.91 \text{ mA}$ . Also,

$$V_{DS} = V_{DD} - I_D (R_D + R_S) = 12 - (1.91 \text{ mA})(3 \text{ k}\Omega) = 6.27 \text{ V}$$

$V_{DS} > V_{GS} - V_P$ . Hence pinch-off region assumption is correct and gate-source junction is reverse-biased by 1.91 V.

**Q-pt: (1.91 mA, 6.27 V)**



---

# End of Chapter 4

