

---


# Chapter 5

## Bipolar Junction Transistors

### Microelectronic Circuit Design

Richard C. Jaeger

Travis N. Blalock

 


# Chapter Goals

---


- Explore physical structure of bipolar transistor
- Understand bipolar transistor action and importance of carrier transport across base region
- Study terminal characteristics of BJT.
- Explore differences between *npn* and *pnp* transistors.
- Develop the Transport Model for the bipolar device.
- Define four operation regions of BJT.
- Explore model simplifications for each operation region.
- Understand origin and modeling of the Early effect.
- Present SPICE model for bipolar transistor.
- Provide examples of worst-case and Monte Carlo analysis of bias circuits.

# Bipolar Transistor Physical Structure

 

- Consists of 3 alternating layers of  $n$ - and  $p$ -type semiconductor called **emitter (E)**, **base (B)** and **collector (C)**.
- Majority of current enters the collector, crosses the base region and exits through the emitter. A small current also enters the base terminal, crosses the base-emitter junction and exits through the emitter.
- Carrier transport in the the active base region directly beneath the heavily doped ( $n^+$ ) emitter dominates the  $i-v$  characteristics of BJT.

 
# Transport Model for the *npn* Transistor



- Narrow width of the base region causes coupling between the two back-to-back *pn* junctions.
- Emitter injects electrons into base region, almost all travel across narrow base and are removed by collector
- Base-emitter voltage  $v_{BE}$  and base-collector voltage  $v_{BC}$  determine currents in transistor and are said to be positive when they forward-bias their respective *pn* junctions.
- The terminal currents are collector current ( $i_C$ ), base current ( $i_B$ ) and emitter current ( $i_E$ ).
- Primary difference between BJT and FET is that  $i_B$  is significant while  $i_G = 0$ .

# npn Transistor

## Forward Characteristics

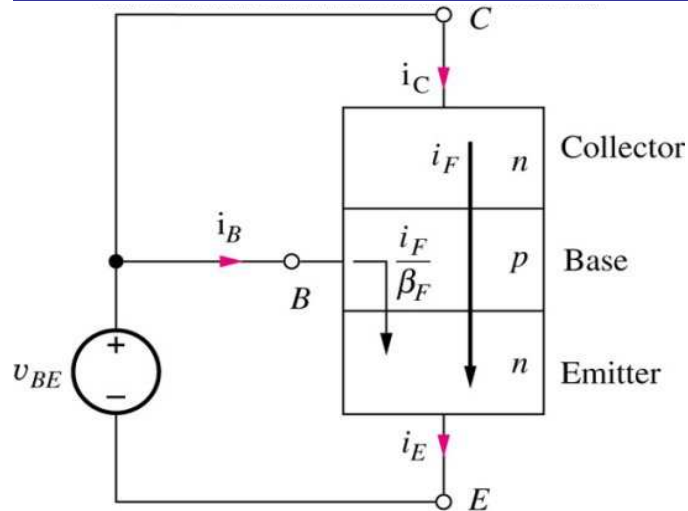

Forward transport current is

$$i_C = i_F = I_S \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$

$I_S$  is the BJT saturation current

$$10^{-18} \text{ A} \leq I_S \leq 10^{-9} \text{ A}$$

$V_T = kT/q = 0.025 \text{ V}$  at room temperature

Base current  $i_B$  is given by

$$i_B = \frac{i_F}{\beta_F} = \frac{I_S}{\beta_F} \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right] \quad 20 \leq \beta_F \leq 500$$

$\beta_F$  is the **forward common-emitter current gain**

Emitter current  $i_E$  is

$$i_E = i_C + i_B = \frac{I_S}{\alpha_F} \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right] \quad \alpha_F = \frac{\beta_F}{\beta_F + 1}$$

$$0.95 \leq \alpha_F \leq 1$$


$\alpha_F$  is the **forward common-base current gain**

In this **forward-active region** of operation

$$\beta_F = \frac{i_C}{i_B} \quad \alpha_F = \frac{i_C}{i_E}$$

# npn Transistor

## Reverse Characteristics

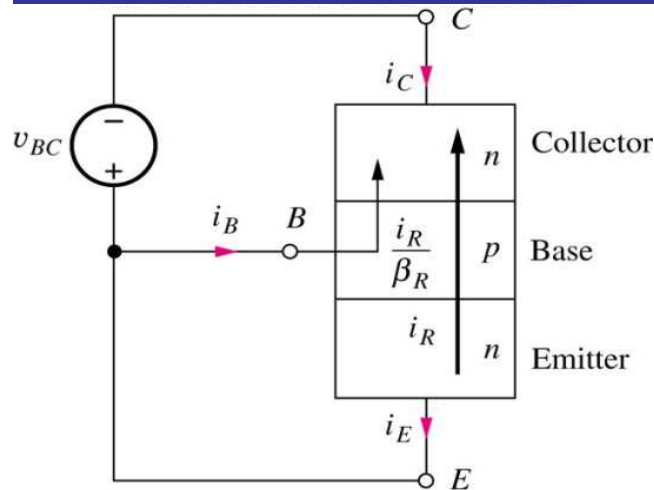

$\beta_R$  is the **reverse common-emitter current gain**

$$0 \leq \beta_R \leq 0.95$$

Base currents in forward and reverse modes are different due to asymmetric doping levels in emitter and collector regions.

Collector current  $i_C$  is given by

Emitter current  $i_E$  is

$$i_E = -i_R = I_S \left[ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$

$$i_C = i_B - i_E = \frac{I_S}{\alpha_R} \left[ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$

Base current  $i_B$  is given by

$$i_B = \frac{i_R}{\beta_R} = \frac{I_S}{\beta_R} \left[ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$

$\alpha_R$  is the **reverse common-base current gain**

$$\alpha_R = \frac{\beta_R}{\beta_R + 1} \quad 0 \leq \alpha_R \leq 0.95$$

# *npn* Transistor

## Complete Transport Model - Valid for Any Bias

---

$$i_C = I_S \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - \exp\left(\frac{v_{BC}}{V_T}\right) \right] - \frac{I_S}{\beta_R} \left[ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$
$$i_E = I_S \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - \exp\left(\frac{v_{BC}}{V_T}\right) \right] + \frac{I_S}{\beta_F} \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$
$$i_B = \frac{I_S}{\beta_F} \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right] - \frac{I_S}{\beta_R} \left[ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$


First term in both emitter and collector current expressions gives current transported completely across base region.

Symmetry exists between base-emitter and base-collector voltages in establishing dominant current in bipolar transistor.

---

# Transport Model Calculations

## Example

 

- **Problem:** Find terminal voltages and currents.
- **Given data:**  $V_{BB} = 0.75 \text{ V}$ ,  $V_{CC} = 5.0 \text{ V}$ ,  $I_S = 10^{-16} \text{ A}$ ,  $\beta_F = 50$ ,  $\beta_R = 1$
- **Assumptions:** Room temperature operation,  $V_T = 25.0 \text{ mV}$ .
- **Analysis:**  $V_{BE} = 0.75 \text{ V}$ ,  
 $V_{BC} = V_{BB} - V_{CC} = 0.75 \text{ V} - 5.00 \text{ V} = -4.25 \text{ V}$

$$I_C = 10^{-16} \left[ \exp\left(\frac{0.75}{0.025}\right) - \exp\left(\frac{-4.25}{0.025}\right) \right] - \frac{10^{-16}}{1} \left[ \exp\left(\frac{-4.25}{0.025}\right) - 1 \right] = 1.07 \text{ mA}$$

$$I_E = 10^{-16} \left[ \exp\left(\frac{0.75}{0.025}\right) - \exp\left(\frac{-4.25}{0.025}\right) \right] + \frac{10^{-16}}{50} \left[ \exp\left(\frac{0.75}{0.025}\right) - 1 \right] = 1.09 \text{ mA}$$

$$I_B = \frac{10^{-16}}{50} \left[ \exp\left(\frac{0.75}{0.025}\right) - 1 \right] - \frac{10^{-16}}{1} \left[ \exp\left(\frac{-4.25}{0.025}\right) - 1 \right] = 21.4 \mu\text{A}$$


$$\beta_F = \frac{I_C}{I_B} = 50.0$$

$$\alpha_F = \frac{I_C}{I_E} = 0.982$$



# *pnp* Transistor Structure


---

 

- Voltages  $v_{EB}$  and  $v_{CB}$  are positive when they forward bias their respective *pn* junctions.
- Collector current and base current exit transistor terminals and emitter current enters the device.

# *pnp* Transistor

## Forward Characteristics

 

Collector current  $i_C$  equals the forward transport current is

$$i_C = i_F = I_S \left[ \exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right]$$

Base current  $i_B$  is given by

$$i_B = \frac{i_F}{\beta_F} = \frac{I_S}{\beta_F} \left[ \exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right]$$

$$i_B = \frac{i_C}{\beta_F}$$


Emitter current  $i_E$  is given by

$$i_E = i_C + i_B = I_S \left( 1 + \frac{1}{\beta_F} \right) \left[ \exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right]$$

$$i_E = i_C + i_B = \frac{I_S}{\alpha_F} \left[ \exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right] = \frac{i_C}{\alpha_F}$$

# *pnp* Transistor

## Reverse Characteristics

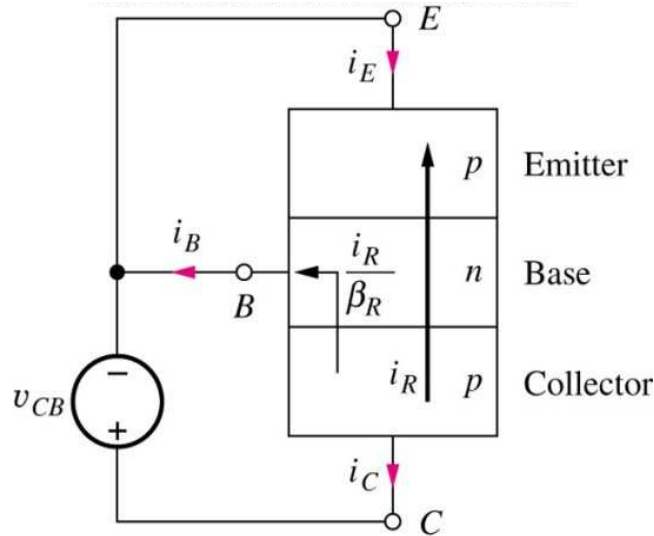

Emitter current  $i_E$  is the negative of the reverse transport current is

$$i_E = -i_R = -I_S \left[ \exp\left(\frac{v_{CB}}{V_T}\right) - 1 \right]$$

Base current  $i_B$  is given by

$$i_B = \frac{i_F}{\beta_R} = \frac{I_S}{\beta_R} \left[ \exp\left(\frac{v_{CB}}{V_T}\right) - 1 \right]$$

$$i_B = \frac{i_E}{\beta_R}$$

Collector current  $i_C$  is given by

$$i_C = i_B - i_E = I_S \left( \frac{1}{\beta_R} + 1 \right) \left[ \exp\left(\frac{v_{CB}}{V_T}\right) - 1 \right]$$

$$i_C = \frac{I_S}{\alpha_R} \left[ \exp\left(\frac{v_{CB}}{V_T}\right) - 1 \right] = \frac{i_E}{\alpha_R}$$

# *pnp* Transistor

## Complete Transport Model Equations for Any Bias

---


$$i_C = I_S \left[ \exp\left(\frac{v_{EB}}{V_T}\right) - \exp\left(\frac{v_{CB}}{V_T}\right) \right] - \frac{I_S}{\beta_R} \left[ \exp\left(\frac{v_{CB}}{V_T}\right) - 1 \right]$$
$$i_E = I_S \left[ \exp\left(\frac{v_{EB}}{V_T}\right) - \exp\left(\frac{v_{CB}}{V_T}\right) \right] + \frac{I_S}{\beta_F} \left[ \exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right]$$
$$i_B = \frac{I_S}{\beta_F} \left[ \exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right] - \frac{I_S}{\beta_R} \left[ \exp\left(\frac{v_{CB}}{V_T}\right) - 1 \right]$$

First term in both emitter and collector current expressions gives current transported completely across base region.

Symmetry exists between base-emitter and base-collector voltages in establishing dominant current in bipolar transistor.

---
 
# Transport Model Circuit Representations



In *npn* transistor (expressions are analogous for *pnp* transistors), the total current traversing base is modeled by a current source given by:

$$i_T = i_F - I_R = I_S \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - \exp\left(\frac{v_{BC}}{V_T}\right) \right]$$

Diode currents correspond directly to the two components of base current.

$$i_B = \frac{I_S}{\beta_F} \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right] - \frac{I_S}{\beta_R} \left[ \exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$


# Operation Regions of Bipolar Transistors

Base-Emitter Junction	Base-Collector Junction	
	Reverse Bias	Forward Bias
Forward Bias	Forward-Active Region (Good Amplifier)	Saturation Region (Closed Switch)
Reverse Bias	Cutoff Region (Open Switch)	Reverse-Active Region (Poor Amplifier)

Binary Logic States

# $i$ - $v$ Characteristics of Bipolar Transistors

## Common-Emitter Output Characteristics

 


For  $i_B = 0$ , the transistor is cutoff. If  $i_B > 0$ ,  $i_C$  also increases.

For  $v_{CE} > v_{BE}$ ,  $npn$  transistor is in forward-active region,  $i_C = \beta_F i_B$  is nearly independent of  $v_{CE}$ .


For  $v_{CE} < v_{BE}$ , transistor is in saturation.

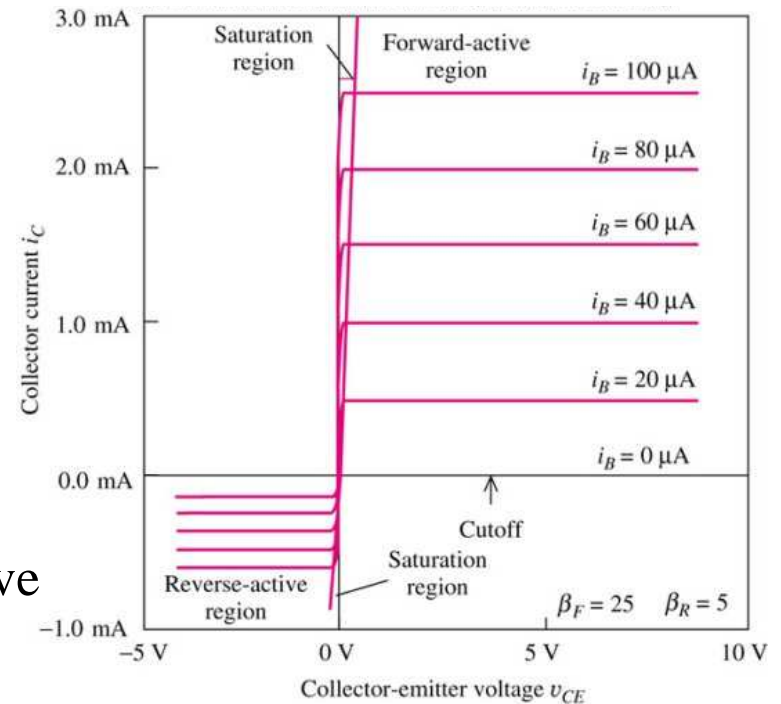For  $v_{CE} < 0$ , roles of collector and emitter reverse.




# $i$ - $v$ Characteristics of Bipolar Transistors

## Common-Base Output Characteristics

 

 For  $v_{CB} > 0$ , *npn* transistor is in the forward-active region.  $i_C \cong i_E$  is nearly independent of  $v_{CB}$  and  $v_{CE}$ .




For  $v_{CB} < 0$ , base-collector diode becomes forward-biased and  $i_C$  grows exponentially (in negative direction) as base-collector diode begins to conduct.



# *i-v* Characteristics of Bipolar Transistors

## Common-Emitter Transfer Characteristic

---

 

Defines relation between collector current and base-emitter voltage of transistor.


Almost identical to transfer characteristic of a *pn* junction diode

Setting  $v_{BC} = 0$  in the collector-current expression yields

$$i_C = I_S \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$

Collector current expression has the same form as that of the diode equation

# Simplified Cutoff Region Model

 

If we assume that

$$v_{BE} \leq -4 \frac{kT}{q} \quad \text{and} \quad v_{BC} \leq -4 \frac{kT}{q}$$

where  $-4kT/q = -0.1$  V, then the transport model terminal current equations simplify to

$$i_C = \frac{I_S}{\beta_R} \quad \text{and} \quad i_E = -\frac{I_S}{\beta_F}$$

$$i_B = -\frac{I_S}{\beta_F} - \frac{I_S}{\beta_F}$$


In the cutoff region, both junctions are reverse-biased; the transistor is said to be in off state

$$v_{BE} < 0, v_{BC} < 0$$

# Simplified Cutoff Region Model

## Example

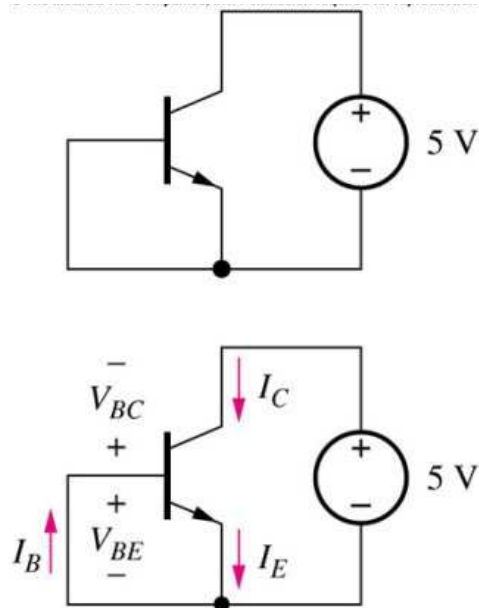- **Problem:** Estimate terminal currents using the transport model
- **Given data:**  $I_S = 10^{-16}$  A,  $\alpha_F = 0.95$ ,  $\alpha_R = 0.25$ ,  $V_{BE} = 0$  V,  $V_{BC} = -5$  V
- **Assumptions:** Simplified transport model assumptions
- **Analysis:** From given voltages, we know that transistor is in cutoff.



$$I_C = I_S \left( 1 + \frac{1}{\beta_R} \right) = \frac{I_S}{\alpha_R} = 4 \times 10^{-16} \text{ A}$$

$$I_E = I_S = 10^{-16} \text{ A}$$

$$I_B = -\frac{I_S}{\beta_R} = -3 \times 10^{-16} \text{ A}$$

For practical purposes, all three currents are essentially zero.

# Simplified Forward-Active Region Model

---

In forward-active region, the emitter-base junction is forward-biased and the collector-base junction is reverse-biased.  $v_{BE} > 0$ ,  $v_{BC} < 0$ . if we assume

$$v_{BE} \geq -4 \frac{kT}{q} \quad \text{and} \quad v_{BC} \leq -4 \frac{kT}{q}$$

then the transport model terminal current equations simplify to

$$\begin{aligned} i_C &\cong I_S \exp\left(\frac{v_{BE}}{V_T}\right) + \frac{I_S}{\beta_R} & i_C &= \alpha_F I_E \\ i_E &\cong I_S \exp\left(\frac{v_{BE}}{V_T}\right) + \frac{I_S}{\beta_F} = \frac{I_S}{\alpha_F} \exp\left(\frac{v_{BE}}{V_T}\right) & i_C &= \beta_F I_B \\ i_B &\cong \frac{I_S}{\beta_F} \exp\left(\frac{v_{BE}}{V_T}\right) + \frac{I_S}{\beta_R} \cong \frac{I_S}{\beta_F} \exp\left(\frac{v_{BE}}{V_T}\right) & i_B &= (\beta_F + 1) I_B \end{aligned}$$


BJT is often considered a current-controlled device, though fundamental forward-active behavior suggests a voltage- controlled current source.

---

# Simplified Forward-Active Region Model

## Example 1

 - **Problem:** Estimate transistor terminal currents and base-emitter voltage
- **Given data:**  $I_S = 10^{-16}$  A,  $\alpha_F = 0.95$ ,  $V_{BC} = V_B - V_C = -5$  V,  $I_E = 100$   $\mu$ A
- **Assumptions:** Simplified transport model assumptions, room temperature operation,  $V_T = 25.0$  mV
- **Analysis:** Current source forward-biases base-emitter diode,  $V_{BE} > 0$ ,  $V_{BC} < 0$ , we know that transistor is in forward-active operation region.



$$I_C = \alpha_F I_E = 0.95(100\mu\text{A}) = 95\ \mu\text{A}$$

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = \frac{0.95}{1 - 0.95} = 19$$


$$I_B = \frac{I_E}{\beta_F + 1} = \frac{100\mu\text{A}}{20} = 5\ \mu\text{A}$$

$$V_{BE} = V_T \ln\left(\alpha_F \frac{I_E}{I_S}\right) = 0.689\ \text{V}$$

# Simplified Forward-Active Region Model

## Example 2

 - **Problem:** Estimate terminal currents, base-emitter and base-collector voltages for the transistor in the given circuit.
- **Given data:**  $I_S = 10^{-16}$  A,  $\alpha_F = 0.95$ ,  $V_C = +5$  V,  $I_B = 100$   $\mu$ A
- **Assumptions:** Simplified transport model assumptions, room temperature operation,  $V_T = 25.0$  mV
- **Analysis:** Current source causes base current to forward-bias base-emitter diode,  $V_{BE} > 0$ ,  $V_{BC} < 0$ , we know that transistor is in forward-active operation region.



$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = \frac{0.95}{1 - 0.95} = 19$$

$$I_C = \beta_F I_B = 19(100 \mu\text{A}) = 1.90 \text{ mA}$$


$$I_E = (\beta_F + 1) I_B = 20(100 \mu\text{A}) = 2.00 \text{ mA}$$

$$V_{BE} = V_T \ln \left( 1 + \frac{I_C}{I_S} \right) = 0.025 \text{ V} \ln \left( 1 + \frac{1.9 \text{ mA}}{0.1 \text{ fA}} \right) = 0.764 \text{ V}$$

$$V_{BC} = V_B - V_C = V_{BE} - V_C = 0.764 - 5 = -4.24 \text{ V}$$

# Simplified Circuit Model

## Forward-Active Region

 


- Current in base-emitter diode is amplified by common-emitter current gain  $\beta_F$  and appears at collector; base and collector currents are exponentially related to base-emitter voltage.
- Base-emitter diode is replaced by constant voltage drop model ( $V_{BE} = 0.7 \text{ V}$ ) since it is forward-biased in forward-active region.
- dc base and emitter voltages differ by 0.7-V diode voltage drop in forward-active region.


# Simplified Forward-Active Region Model

## Example 3

 - **Problem:** Find transistor Q-point
- **Given data:**  $\beta_F = 50$ ,  $\beta_R = 1$
- **Assumptions:** Forward-active region of operation,  $V_{BE} = 0.7 \text{ V}$
- **Analysis:**



(a)

 

(b)

$$V_{BE} + 8200I_E - V_{EE} = 0$$

$$\therefore I_E = \frac{9 - 0.7 \text{ V}}{8200 \text{ } \Omega} = 1.01 \text{ mA}$$

$$I_B = \frac{I_E}{\beta_F + 1} = \frac{1.01 \text{ mA}}{51} = 19.8 \text{ } \mu\text{A}$$

$$I_C = \beta_F I_B = 50(19.8 \text{ } \mu\text{A}) = 0.990 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C - (-V_{BE})$$

$$V_{CE} = 9 - 0.99 \text{ mA}(4.3 \text{ K}) + 0.7 = 5.44 \text{ V}$$

Forward-active region is correct.



# Simplified Circuit Model

## Reverse-Active Region

In reverse-active region, base-collector diode is forward-biased and base-emitter diode is reverse-biased.

Simplified equations are:



$$i_E \cong -I_S \exp\left(\frac{v_{BC}}{V_T}\right)$$

$$i_C \cong -\frac{I_S}{\alpha_R} \exp\left(\frac{v_{BC}}{V_T}\right)$$

$$i_B \cong \frac{I_S}{B_R} \exp\left(\frac{v_{BC}}{V_T}\right)$$

$$i_E = \alpha_R i_C$$


$$i_E = -\beta_R i_B$$

  

# Simplified Reverse-Active Region Model

## Example

 - **Problem:** Find transistor Q-point
- **Given data:**  $\beta_F = 50$ ,  $\beta_R = 1$   $V_{BE} = V_B - V_E = -9$  V. Combination of  $R$  and the voltage source forward biases base-collector junction.
- **Assumptions:** Reverse-active region of operation,  $V_{BC} = 0.7$  V
- **Analysis:**



$$-I_C = \frac{-0.7V - (-9V)}{8200\Omega} = 1.01 \text{ mA}$$

$$I_B = \frac{-I_C}{\beta_R + 1} = \frac{1.01 \text{ mA}}{2} = 0.505 \text{ mA}$$

$$-I_E = \beta_R I_B = 0.505 \text{ mA}$$

Current directions are consistent with reverse-active region operation.

# Simplified Circuit Model


## Saturation Region

- In the saturation region, both junctions are forward-biased, and the transistor operates with a small voltage between collector and emitter.  
 $v_{CESAT}$  is the saturation voltage for the *npn* BJT.


$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) - \frac{I_S}{\alpha_R} \exp\left(\frac{V_{BC}}{V_T}\right) \quad I_B = \frac{I_S}{\beta_F} \exp\left(\frac{V_{BE}}{V_T}\right) + \frac{I_S}{\beta_R} \exp\left(\frac{V_{BC}}{V_T}\right)$$

$$V_{CESAT} = V_{BE} - V_{BC} = V_T \ln \left[ \left( \frac{1}{\alpha_R} \right) \frac{1 + \frac{I_C}{(\beta_R + 1)I_B}}{1 - \frac{I_C}{\beta_F I_B}} \right] \quad \text{for } I_B \geq \frac{I_C}{\beta_F}$$

 No simplified expressions exist for terminal currents other than  $i_C + i_B = i_E$ .



Simplified Model

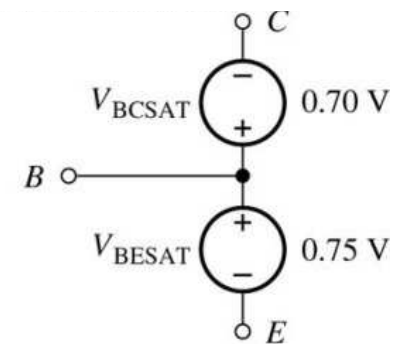

# Non Ideal BJT Behavior

## Junction Breakdown Voltages

---

- If reverse voltage across either of the two  $pn$  junctions in the transistor is too large, the corresponding diode will break down.
- The emitter is the most heavily-doped region, and the collector is the most lightly doped region.
- Due to doping differences, the base-emitter diode has a relatively low breakdown voltage (3 to 10 V). The collector-base diode can be designed to break down at much larger voltages.
- Transistors must be selected in accordance with possible reverse voltages in circuit.


# Non Ideal BJT Behavior

## Minority Carrier Transport in the Base Region

- BJT current dominated by diffusion of minority carriers (electrons in *npn* and holes in *pnp* transistors) across base region.
- Base current consists of hole injection back into emitter and collector and a small additional current to replenish holes lost to recombination with electrons in base.
- Minority carrier concentrations at the two ends of the base region are:

$$n(0) = n_{bo} \exp\left(\frac{v_{BE}}{V_T}\right) \quad \text{and} \quad n(W_B) = n_{bo} \exp\left(\frac{v_{BC}}{V_T}\right)$$

 $n_{bo}$  is equilibrium electron density in the *p*-type base region.



# Minority Carrier Transport in the Base Region (cont.)

---

- For narrow base devices, minority carrier density decreases linearly across the base, and the diffusion current in the base is:

$$I_S = qAD_n \frac{n_{bo}}{W_B} = \frac{qAD_n}{W_B} \frac{n_i^2}{N_{AB}}$$

$N_{AB}$  = doping concentration in base


$n_i^2$  = intrinsic carrier concentration ( $10^{10}/\text{cm}^3$ )

$$n_{bo} = n_i^2 / N_{AB}$$

- Saturation current for the *pn*p transistor is  $I_S = qAD_p \frac{p_{bo}}{W_B} = \frac{qAD_p}{W_B} \frac{n_i^2}{N_{DB}}$
- Due to higher mobility of electrons than holes, the *n*pn transistor conducts higher current than the *pn*p for a given set of applied voltages.

# Non Ideal BJT Behavior

## Base Transit Time

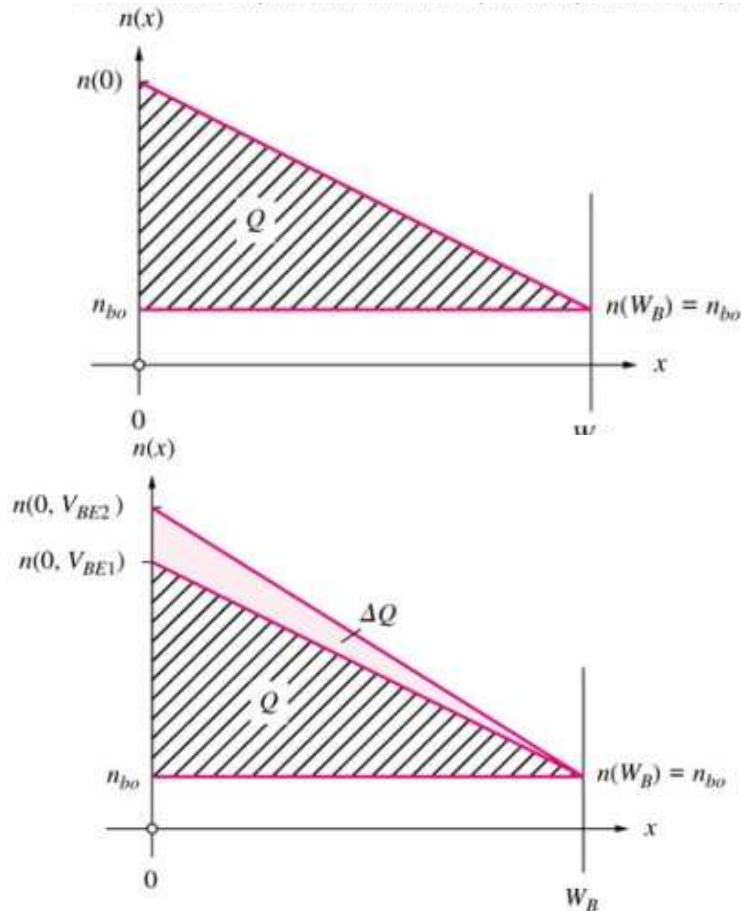

Forward transit time  $\tau_F$  is the time constant associated with storing minority-carrier charge  $Q$  required to establish carrier gradient in base region.

$$Q = qAn_{bo} \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right] \frac{W_B}{2}$$

$$i_T = \frac{qAD_n}{W_B} n_{bo} \left[ \exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$

$$\tau_F = \frac{Q}{i_T} = \frac{W_B^2}{2D_n} = \frac{W_B^2}{2\mu_n V_T}$$

Transit time places upper limit on useful operating frequency of transistor.

# Non Ideal BJT Behavior

## Diffusion Capacitance

---

- For  $v_{BE}$  and hence  $i_C$  to change, charge stored in base region must also change.
- Diffusion capacitance in parallel with forward-biased base-emitter diode models the change in charge with  $v_{BE}$ .

$$C_D = \left. \frac{dQ}{dv_{BE}} \right|_{Q-pt} = \frac{1}{V_T} \frac{qAn_{bo}W_B}{2} \exp\left(\frac{V_{BE}}{V_T}\right) = \frac{I_T}{V_T} \tau_F$$

- Since transport current normally represents collector current in forward-active region,

$$C_D = \frac{I_C}{V_T} \tau_F$$



# $\beta$ Cutoff-Frequency, Transconductance and Transit Time

---

- Forward-biased diffusion and reverse-biased  $pn$  junction capacitances of the BJT cause current gain to be frequency-dependent.
- Unity gain frequency  $f_T$  is frequency at which the current gain is unity

$$\beta(f) = \frac{\beta_F}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}} \quad \text{where} \quad f_B = \frac{f_T}{\beta_F} \quad \text{is the } \beta \text{ cutoff-frequency}$$

- Transconductance is defined by:

$$g_m = \left. \frac{di_C}{dv_{BE}} \right|_{Q-Pt} = \left. \frac{d}{dv_{BE}} \left[ I_S \exp\left(\frac{v_{BE}}{V_T}\right) \right] \right|_{Q-Pt} = \frac{I_C}{V_T}$$

- Transit time is given by:  $\tau_F = \frac{C_D}{g_m}$  with  $g_m = \frac{I_C}{V_T}$


# Early Effect and Early Voltage

---

- As reverse-bias across the collector-base junction increases, width of the collector-base depletion layer increases and width of the base decreases (termed “base-width modulation”).
- In a practical BJT, the output characteristics have a positive slope in forward-active region; collector current is not independent of  $v_{CE}$ .
- Early effect: When the output characteristics are extrapolated back to point of zero  $i_C$ , the curves intersect (approximately) at a common point  $v_{CE} = -V_A$  which lies between 15 V and 150 V. ( $V_A$  is named the Early voltage)
- Simplified equations (including Early effect):

$$i_C = I_S \exp\left(\frac{v_{BE}}{V_T}\right) \left[1 + \frac{v_{CE}}{V_A}\right] \quad \beta_F = \beta_{FO} \left[1 + \frac{v_{CE}}{V_A}\right] \quad i_B = \frac{I_S}{\beta_{FO}} \exp\left(\frac{v_{BE}}{V_T}\right)$$

# BJT SPICE Model

 

- Besides capacitances associated with the physical structure, additional components are: diode current  $i_S$  and substrate capacitance  $C_{JS}$  related to the large area  $pn$  junction that isolates the collector from the substrate and one transistor from the next.
- $R_B$  is resistance between the external base contact and the intrinsic base region.
- Collector current must pass through  $R_C$  on its way to the active region of the collector-base junction.
- $R_E$  models any extrinsic emitter resistance in device.

# BJT SPICE Model Parameters

## Typical Values

---

Saturation Current  $I_S = 3 \times 10^{-17} \text{ A}$

Forward current gain  $BF = 100$

Reverse current gain  $BR = 0.5$

Forward Early voltage  $V_{AF} = 75 \text{ V}$

Base resistance  $R_B = 250 \text{ } \Omega$

Collector Resistance  $R_C = 50 \text{ } \Omega$


Emitter Resistance  $R_E = 1 \text{ } \Omega$

Forward transit time  $TT = 0.15 \text{ ns}$


Reverse transit time  $TR = 15 \text{ ns}$

# High Performance BJTs

---

 

(a)

 

(b)

- Modern BJTs use a combination of shallow and deep trench isolation processes to reduce device capacitances and transit times.
- Devices have polysilicon emitters, narrow bases, and/or SiGe base regions.
- SiGe transistors exhibit cutoff frequencies  $> 100$  GHz.

# Biasing for the BJT


## Overview

---

- The goal of biasing is to establish known Q-point which in turn establishes initial operating region of the transistor.
- For a BJT, the Q-point is represented by  $(I_C, V_{CE})$  for an *npn* transistor or  $(I_C, V_{EC})$  for a *pnp* transistor.
- The Q-point controls values of diffusion capacitance, transconductance, input and output resistances.
- In general, during circuit analysis, we use simplified mathematical relationships derived for a specified operation region, and the Early voltage is assumed to be infinite.
- Two practical biasing circuits used for a BJT are:
  - Four-Resistor Bias Network
  - Two-Resistor Bias Network

# BJT Biasing

## Four-Resistor Bias Network

 


Thevenin Equivalent of  
Base Bias Network

$$V_{EQ} = V_{CC} \frac{R_2}{R_1 + R_2} = 4 \text{ V}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = 12 \text{ k}\Omega$$

$$\beta_F = 75$$

 

$$V_{EQ} = I_B R_{EQ} + V_{BE} + I_E R_E$$

$$I_B = \frac{V_{EQ} - V_{BE}}{R_{EQ} + (\beta_F + 1) R_E}$$

$$I_B = \frac{4 \text{ V} - 0.7 \text{ V}}{12 \text{ k}\Omega + (76) 16 \text{ k}\Omega} = 2.69 \text{ }\mu\text{A}$$

$$I_C = \beta_F I_B = 202 \text{ }\mu\text{A}$$

$$I_E = (\beta_F + 1) I_B = 204 \text{ }\mu\text{A}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 4.29 \text{ V}$$

**Forward active region is correct**


**Q-point is (202  $\mu\text{A}$ , 4.29 V)**

# BJT Biasing
 
## Four-Resistor Bias Network (cont.)

- All calculated currents  $> 0$ ,  $V_{BC} = V_{BE} - V_{CE} = 0.7 - 4.32 = -3.62$  V
- Hence, base-collector junction is reverse-biased, and assumption of forward-active region operation is correct.
- Load-line for the circuit is:

$$V_{CE} = V_{CC} - \left( R_C + \frac{R_E}{\alpha_F} \right) I_C = 12 - 38200 I_C$$



The two points needed to plot the load line are (0, 12 V) and (314  $\mu\text{A}$ , 0). The resulting load line is plotted on the common-emitter output characteristics.

$I_B = 2.7 \mu\text{A}$  - the intersection of the corresponding characteristic with load line gives the Q-point: (200  $\mu\text{A}$ , 4.3 V)



# BJT Biasing

## Four-Resistor Bias Design Objectives

---

- We know that

$$I_C \cong I_E = \frac{V_{EQ} - V_{BE} - I_B R_{EQ}}{R_E} \cong \frac{V_{EQ} - V_{BE}}{R_E} \quad \text{for} \quad I_B R_{EQ} \ll (V_{EQ} - V_{BE})$$

- We desire  $I_B \ll I_{R2}$  that  $I_{R1} = I_{R2}$ . In this case, base current doesn't disturb the voltage divider action of  $R_1$  and  $R_2$ . Thus, the Q-point is independent of base current as well as current gain!
- Also,  $V_{EQ}$  is designed to be large enough that small variations in the assumed value of  $V_{BE}$  won't affect  $I_E$  and  $I_C$ .
- Current in the base voltage divider network is set by choosing  $I_2 \leq I_C/5$ . This ensures that power dissipation in bias resistors is  $< 17\%$  of the total quiescent power consumed by circuit, and  $I_2 \gg I_B$  for  $\beta > 50$ .

# BJT Biasing

## Four-Resistor Bias Design Guidelines

---

- Choose Thévenin equivalent base voltage  $\frac{V_{CC}}{4} \leq V_{EQ} \leq \frac{V_{CC}}{2}$
  - Select  $R_1$  to set  $I_1 = 9I_B$ .  $R_1 = \frac{V_{EQ}}{9I_B}$
  - Select  $R_2$  to set  $I_2 = 10I_B$ .  $R_2 = \frac{V_{CC} - V_{EQ}}{10I_B}$
  - $R_E$  is determined by  $V_{EQ}$  and the desired  $I_C$ .  $R_E \cong \frac{V_{EQ} - V_{BE}}{I_C}$
  - $R_C$  is determined by desired  $V_{CE}$ .  $R_C \cong \frac{V_{EQ} - V_{BE}}{I_C} - R_E$
-

# Four-Resistor Bias for BJT

## Design Example

---

- **Problem:** Design 4-resistor bias circuit with given parameters.
- **Given data:**  $I_C = 750 \mu\text{A}$ ,  $\beta_F = 100$ ,  $V_{CC} = 15 \text{ V}$ ,  $V_{CE} = 5 \text{ V}$
- **Assumptions:** Forward-active operation region,  $V_{BE} = 0.7 \text{ V}$
- **Analysis:** Divide  $(V_{CC} - V_{CE})$  equally between  $R_E$  and  $R_C$ . Thus,  $V_E = 5 \text{ V}$  and  $V_C = 10 \text{ V}$ ; Choose nearest 5% resistor values.

$$R_C = \frac{V_{CC} - V_C}{I_C} = 6.67 \text{ k}\Omega \rightarrow 6.8 \text{ k}\Omega \quad I_2 = 10I_B = 75.0 \mu\text{A}$$

$$R_E = \frac{V_E}{I_E} = 6.60 \text{ k}\Omega \rightarrow 6.8 \text{ k}\Omega \quad I_2 = 9I_B = 67.5 \mu\text{A}$$

$$V_B = V_E + V_{BE} = 5.7 \text{ V}$$

$$R_1 = \frac{V_B}{9I_B} = 84.4 \text{ k}\Omega \rightarrow 82 \text{ k}\Omega$$


$$I_B = \frac{I_C}{\beta_F} = 7.5 \mu\text{A}$$

$$R_2 = \frac{V_{CC} - V_B}{10I_B} = 124 \text{ k}\Omega \rightarrow 120 \text{ k}\Omega$$

# BJT Biasing

## Two-Resistor Bias Example

 - **Problem:** Find the Q-point a for *npn* transistor in a 2-resistor bias circuit with given parameters.
- **Given data:**  $\beta_F = 50$ ,  $V_{CC} = 9\text{ V}$
- **Assumptions:** Forward-active operation region,  $V_{EB} = 0.7\text{ V}$
- **Analysis:**



$$9 = V_{EB} + 18000I_B + 1000(I_C + I_B)$$

$$9 = V_{EB} + 18000I_B + 1000(51I_B)$$

$$I_B = \frac{9 - 0.7\text{ V}}{69000\ \Omega} = 120\ \mu\text{A} \quad I_C = 50I_B = 6.01\text{ mA}$$

$$V_{EC} = 9 - 1000(I_C + I_B) = 2.88\text{ V} \quad V_{EC} > V_{BE}$$

**Forward-active region operation is correct Q-point is : (6.01 mA, 2.88 V)**


# Tolerances & Worst-Case Analysis

## Example

 - **Problem:** Find worst-case values of  $I_C$  and  $V_{CE}$  in the circuit below.
- **Given data:**  $\beta_{FO} = 75$  with 50% tolerance,  $V_A = 50$  V, 5 % tolerance on  $V_{CC}$ , 10% tolerance for each resistor.  $R_1 = 18$  k $\Omega$ ,  $R_2 = 36$  k $\Omega$ .
- **Simplified Analysis:**

$$I_C \cong I_E \cong \frac{V_{EQ} - V_{BE}}{R_E}$$

To maximize  $I_C$ ,  $V_{EQ}$  should be maximized,  $R_E$  should be minimized and the opposite for minimizing  $I_C$ . Extremes of  $R_E$  are: 14.4 k $\Omega$  and 17.6 k $\Omega$ .



$$V_{EQ} = V_{CC} \frac{R_1}{R_1 + R_2} = \frac{V_{CC}}{1 + (R_2/R_1)}$$

To maximize  $V_{EQ}$ ,  $V_{CC}$  and  $R_1$  should be maximized,  $R_2$  should be minimized and opposite for minimizing  $V_{EQ}$ .

# Tolerances & Worst-Case Analysis

## Example (cont.)


$$V_{CC} = 12V \pm 5\%$$

$$R_1 = 18k\Omega \pm 10\%$$

$$R_2 = 36k\Omega \pm 10\%$$

$$V_{EQ} = V_{CC} \frac{R_1}{R_1 + R_2} = \frac{V_{CC}}{1 + (R_2/R_1)}$$
 
$$R_{EQ} = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2$$



$$V_{EQ}^{\max} = \frac{12V(1.05)}{1 + [36k\Omega(0.9)/18k\Omega(1.1)]} = 4.78 V$$

$$V_{EQ}^{\min} = \frac{12V(0.95)}{1 + [36k\Omega(1.1)/18k\Omega(0.9)]} = 3.31 V$$

$$I_C^{\max} \cong \frac{4.78V - 0.7V}{16k\Omega(0.90)} = 283 \mu A$$

$$I_C^{\min} \cong \frac{3.31V - 0.7V}{16k\Omega(1.1)} = 148 \mu A$$

# Tolerances & Worst-Case Analysis

## Example (cont.)

---

Extremes of  $V_{EQ}$  are: 4.78 V and 3.31 V.

Extremes for  $I_C$  are: 283  $\mu$ A and 148  $\mu$ A.

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E \cong V_{CC} - I_C R_C - \frac{V_{EQ} - V_{BE}}{R_E} R_E$$

$$V_{CE} \cong V_{CC} - I_C R_C - V_{EQ} + V_{BE}$$

$$V_{CE}^{\max} = 12V(1.05) - 0.148mA(22k\Omega)(.9) - 3.31 + 0.7 = 6.73 V$$

$$V_{CE}^{\min} = 12V(0.95) - 0.283mA(22k\Omega)(1.1) - 4.78 + 0.7 = 0.471 V \quad \times$$

To maximize  $V_{CE}$ ,  $I_C$  and  $R_C$  should be minimized, and opposite for minimizing  $V_{EQ}$ .

Extremes of  $V_{CE}$  are: 7.06 V (forward-active region) and

0.471 V (saturated, hence calculated values for

$V_{CE}$  and  $I_C$  actually not correct).

# Tolerances - Monte Carlo Analysis

---

- In real circuits, it is unlikely that various components will reach their extremes at the same time, instead they will have some statistical distribution. Hence worst-case analysis over-estimates extremes of circuit behavior.
- In Monte Carlo analysis, values of each circuit parameter are randomly selected from possible distributions of parameters and used to analyze the circuit.
- Random parameter sets are generated, and the statistical behavior of circuit is built up from the analysis of many test cases.



# Tolerances - Monte Carlo Analysis

## Example

---

For each Case: Assign random values to all circuit elements

$$V_{CC} = 12 \left[ 1 + 0.1 (\text{Rand}(\ ) - 0.5) \right]$$

$$R_1 = 18000 \left[ 1 + 0.2 (\text{Rand}(\ ) - 0.5) \right]$$

$$R_2 = 36000 \left[ 1 + 0.2 (\text{Rand}(\ ) - 0.5) \right]$$

$$R_E = 16000 \left[ 1 + 0.2 (\text{Rand}(\ ) - 0.5) \right]$$

$$R_C = 22000 \left[ 1 + 0.2 (\text{Rand}(\ ) - 0.5) \right]$$

$$\beta_F = 75 \left[ 1 + (\text{Rand}(\ ) - 0.5) \right]$$

Then calculate resulting currents and voltages

$$V_{EQ} = V_{CC} \frac{R_1}{R_1 + R_2}$$

$$R_{EQ} = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_B = \frac{V_{EQ} - V_{BE}}{R_{EQ} + (\beta_F + 1) R_E}$$

$$I_C = \beta_F I_B$$

$$I_E = (\beta_F + 1) I_B$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$


Note: Assume constant  $V_{BE} = 0.7$  for simplicity.

---

# Tolerances - Monte Carlo Analysis

## Example (cont.)

---

 

- Full results of Monte Carlo analysis of 500 cases of the 4-resistor bias circuit yields mean values of 207  $\mu\text{A}$  and 4.06 V for  $I_C$  and  $V_{CE}$  respectively which are close to values originally estimated from nominal circuit elements. Standard deviations are 19.6  $\mu\text{A}$  and 0.64 V respectively.
  - The worst-case calculations lie well beyond the extremes of the distributions
    - Note that circuit never saturates in the Monte Carlo Analyses
-

---

# End of Chapter 5

