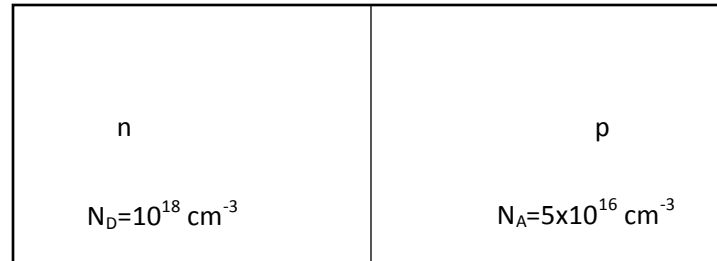



- 1) A pn junction diode is shown below with the doping levels on each side indicated in the figure. What is the majority and minority carrier densities in the n and p sides of the diode? Assume $n_i = 10^{10} \text{ cm}^{-3}$



- 1) N-side ($n=10^{18}$, $p= 5 \times 10^{16}$) P-side ($n=2000$, $p= 5 \times 10^{16}$)
- 2) N-side ($n=10^{18}$, $p= 100$) P-side ($n=2000$, $p= 5 \times 10^{16}$)
- 3) N-side ($n=100$, $p= 5 \times 10^{16}$) P-side ($n=10^{18}$, $p= 5 \times 10^{16}$)
- 4) N-side ($n=10^{18}$, $p= 10^{10}$) P-side ($n=2000$, $p= 5 \times 10^{16}$)
- 5) N-side ($n=10^{18}$, $p= 100$) P-side ($n=2000$, $p= 10^{10}$)
- 6) None of the above

$$\begin{array}{ll}
 n\text{-side} & n = N_D = 10^{18} \text{ cm}^{-3} & p = \frac{n_i^2}{N_D} = \frac{10^{20}}{10^{18}} = 100 \text{ cm}^{-3} \\
 p\text{-side} & p = N_A = 5 \times 10^{16} \text{ cm}^{-3} & n = \frac{n_i^2}{N_A} = \frac{10^{20}}{5 \times 10^{16}} = 2000 \text{ cm}^{-3}
 \end{array}$$

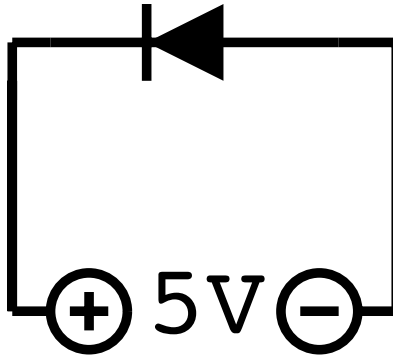- 2) Assuming a reverse bias voltage of 5 V is applied to the above diode, what is the depletion layer width? On which side of the junction is the depletion layer penetrating more? Dielectric constant of silicon is 11.7 and $\epsilon_0 = 8.85 \times 10^{-14}$ F/cm, thermal voltage at room temperature is 25 mV.



- 1) $W=40\mu\text{m}$ and mostly in the p region
- 2) $W=0.4\mu\text{m}$ and mostly in the n region
- 3) $W=0.4\mu\text{m}$ and mostly in the p region
- 4) $W= 0.2\mu\text{m}$ and mostly in the p region
- 5) $W=40\mu\text{m}$ and mostly in the n region
- 6) None of the above


$$V_0 = V_T \ln \left(\frac{N_D N_A}{n_i^2} \right) = 0.025 \ln \left(\frac{10^{18} \times 5 \times 10^{16}}{10^{20}} \right) = 0.846 (141) V$$

$$W = \sqrt{\frac{2 \times \epsilon_0 \times \epsilon \left(\frac{1}{N_D} + \frac{1}{N_A} \right)}{q}} = \sqrt{\frac{2 \times 11.7 \times 8.85 \times 10^{-14} \left(\frac{1}{10^{18}} + \frac{1}{5 \times 10^{16}} \right)}{1.6 \times 10^{-19}}} = 0.0000399 (075) \text{ cm} = 0.4 \mu\text{m}$$

Since $N_D > N_A \Rightarrow$ mostly in p -region

$W = 0.4 \mu\text{m}$ and mostly in p -region


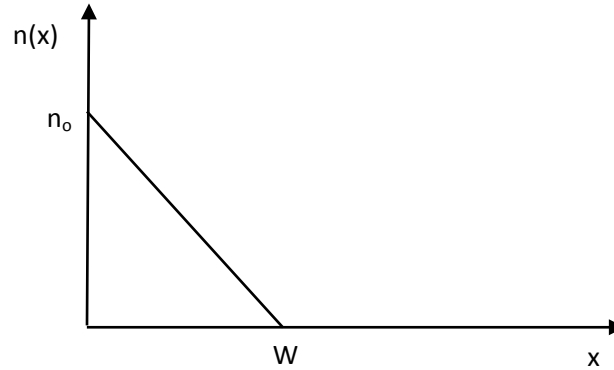
- 3) The linear electron concentration profile shown in figure below has been established in a piece of silicon, if $n_0 = 10^{17} \text{ cm}^{-3}$ and $W=1 \mu\text{m}$, what is the electron current density? Assume room temperature operation ($V_T = 25 \text{ mV}$) and an electron mobility of $1250 \text{ cm}^2/\text{V}\cdot\text{s}$. ($q = 1.6 \times 10^{-19} \text{ C}$)



- 1) $J_n = -5000 \text{ A/cm}^2$
- 2) $J_n = 500,000 \text{ A/cm}^2$
- 3) $J_n = 5000 \text{ A/cm}^2$
- 4) $J_n = -200,000 \text{ A/cm}^2$
- 5) $J_n = -250 \text{ A/cm}^2$
- 6) None of the above

$$J_n = q \underbrace{D_n}_{\mu_n V_T} \frac{dn}{dx} = 1.6 \times 10^{-19} [\text{C}] (1250 [\text{cm}^2 / (\text{Vs})]) \times 0.025 [\text{V}] \times \left(\frac{-10^{17} [\text{cm}^{-3}]}{10^{-4} [\text{cm}]} \right) = -5000 [\text{A/cm}^2]$$

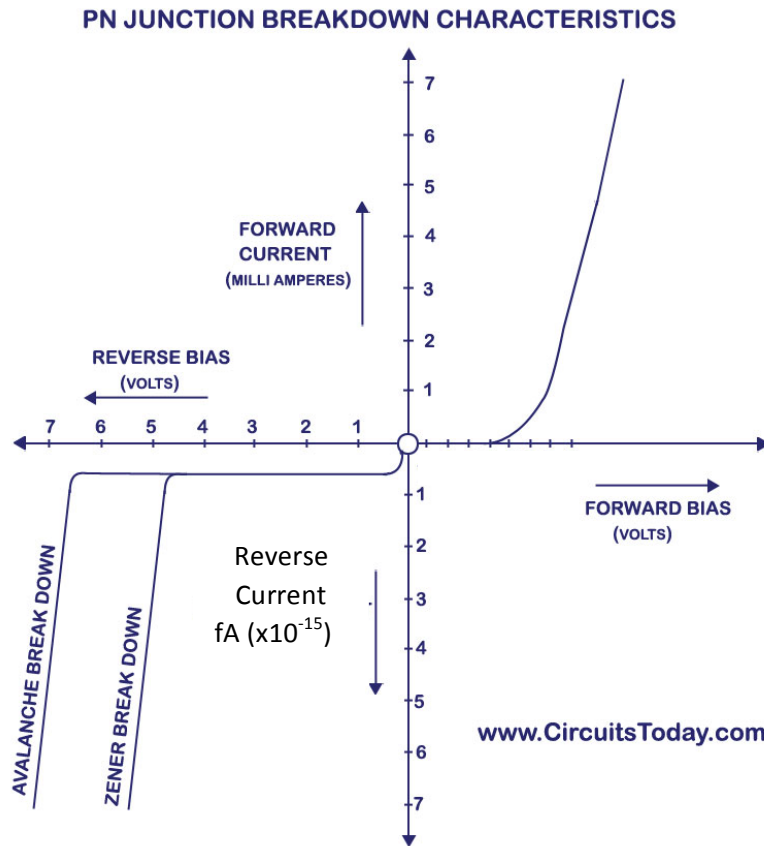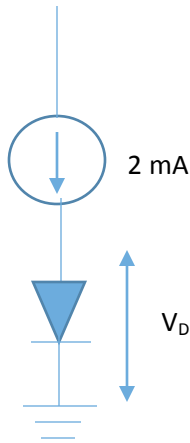- 4) The circuit below shows a diode forward biased using a current source of 2 mA in magnitude what is the voltage drop across the diode (V_D)? The iv characteristics of the diode is also shown below. Assume room temperature operation $V_T = 25$ mV




- 1) $V_D = 0.725$ V
- 2) $V_D = 0.710$ V
- 3) $V_D = 0.825$ V
- 4) $V_D = 0.65$ V
- 5) $V_D = 0.8$ V
- 6) None of the above

$$V_D = V_T \ln\left(\frac{I}{I_S}\right) = 0.025 \ln\left(\frac{2 \times 10^{-3}}{0.5 \times 10^{-15}}\right) = 0.725(433) \text{ V}$$

$$V_D = 0.725 \text{ V}$$

- 5) Find the value of R such that the output voltage will be 2.4 V. Assume that all diodes are the same and have 0.7 voltage drop at 1mA. $V_T=0.025V$

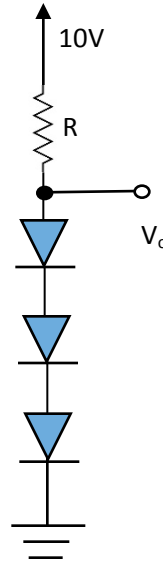- 1) $R=7.6k\Omega$
- 2) $R=1.4k\Omega$
- 3) $R=7.9k\Omega$
- 4) $R=140\Omega$
- 5) $R=44\Omega$
- 6) None of the above



$$\text{Individual Diode } V_D = 0.8[V]$$


$$I_D = I_S \exp(V_D/V_T)$$

$$\begin{cases} I_D = I_S \exp(0.8/0.025) \\ \frac{10^{-3}}{\exp(0.7/0.025)} = I_S \end{cases} \Rightarrow I_D = \frac{10^{-3} \exp(0.8/0.025)}{\exp(0.7/0.025)} = 0.0545(982) = 54.6[\text{mA}]$$

$$R = \frac{10[V] - V_O}{I_D} = \frac{(10 - 2.4)[V]}{0.0546[A]} = 139.(19)[\Omega]$$

$$R = 139[\Omega]$$

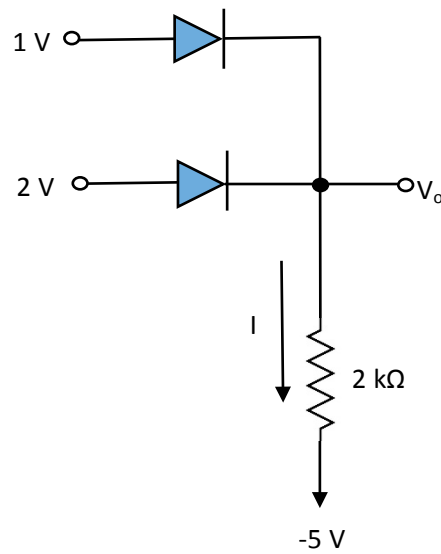
6) In figure shown below what is the current I assuming both diodes are ideal?



- 1) $I=3\text{mA}$
- 2) $I=3.5\text{mA}$
- 3) $I=0$
- 4) $I=2.5\text{mA}$
- 5) $I=2\text{mA}$
- 6) None of the above

$$I = \frac{(V_o - (-5)) [V]}{2 \times 10^3 [\Omega]} = \frac{2 + 5}{2} [mA] = 3.5 [mA]$$

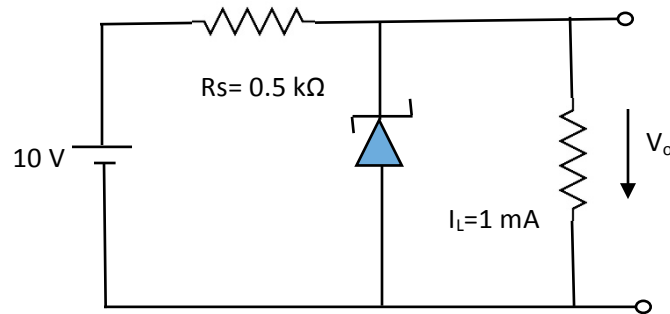- 7) The figure below shows a Zener shunt voltage regulator. From Zener data sheet we have ($V_Z=6.8V$ at $I_Z=5mA$ and $r_Z=20\Omega$), what is the voltage across the load (V_o) if $I_L=1mA$?



- 1) $V_o=6.83V$
- 2) $V_o=6.7V$
- 3) $V_o=6.8V$
- 4) $V_o=3.2V$
- 5) $V_o=6.807V$
- 6) None of the above

First find V_{zo}

$$V_Z = V_{ZO} + r_Z I_Z$$

$$V_Z - r_Z I_Z = V_{ZO} = 6.8[V] - 20[\Omega]5 \times 10^{-3}[A] = 6.7[V]$$


$$V_{ZO} = 6.7[V]$$

$$I_{OC} = \frac{(10[V] - V_{ZO})}{R_s + r_Z} = \frac{(10 - 6.7)[V]}{520[\Omega]} = 6.34(615)[mA] = 6.35[mA]$$






$$I_L = 1[mA] \Rightarrow I_Z = 5.35[mA]$$

$$V_o = 6.7[V] + 20[\Omega]5.35 \times 10^{-3}[A] = 6.807[V]$$

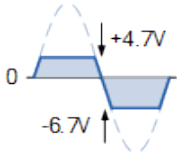
8) Which one of the clipping circuits below produce the following output



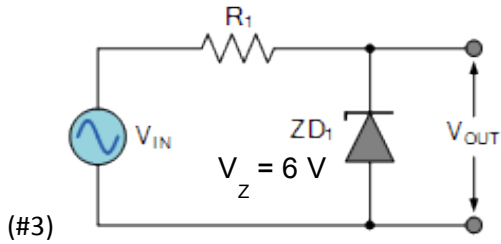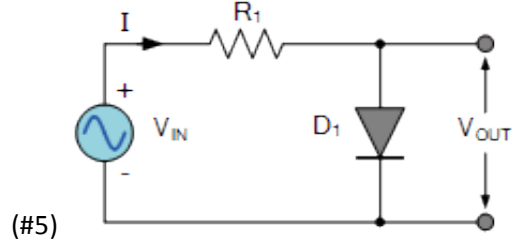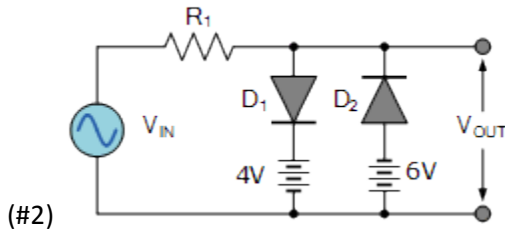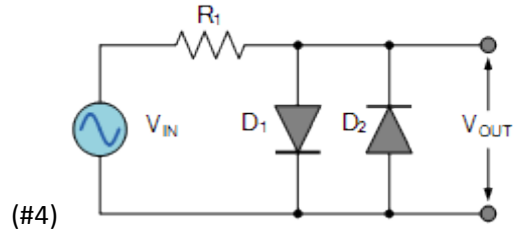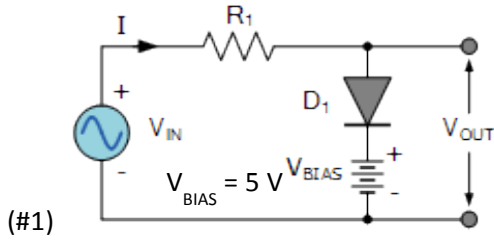
in response to the input signal, $V_{in} = (10V)\sin\omega t$? Assume $V_{ON} = 0.7 V$ for all diodes.



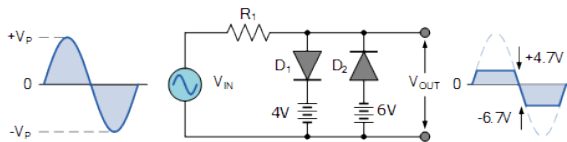- 1) Clipping circuit #1
- 2) Clipping circuit #2
- 3) Clipping circuit #3
- 4) Clipping circuit #4
- 5) Clipping circuit #5
- 6) None of the above



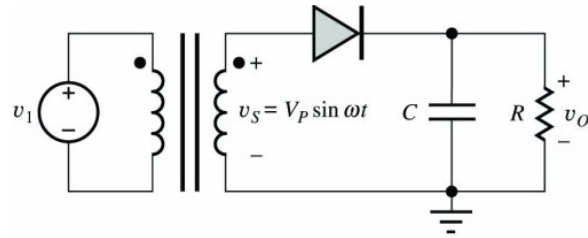- 9) Find the value of the conduction angle for a half-wave rectifier driven from a transformer having a secondary voltage of 12.6 Vrms (60 Hz) with $R = 15 \Omega$ and $C = 25,000 \mu\text{F}$. Assume the diode on-voltage $V_{on} = 0 \text{ V}$, and that for small Δt $\cos(\omega\Delta t) \approx 1 - \frac{1}{2}(\omega\Delta t)^2$.



- 1) 1.0 rad
- 2) 0.7 rad
- 3) 0.1 rad
- 4) 0.3 rad
- 5) 0.6 rad
- 6) None of the above

$$V_P = 12.6\sqrt{2} [V] = 17.8 [V]$$

$$V_r = \frac{V_P}{fCR} =$$

$$\frac{17.8 [V]}{60 [Hz] \times 15 [\Omega] \times 25 \times 10^{-3} [F]} = 0.791 (111) [V]$$

$$V_P \cos\left(\frac{\omega\Delta t}{\theta}\right) = V_P - V_r$$

$$\cos \theta \approx 1 - \frac{1}{2}\theta^2$$

$$\theta = \sqrt{\frac{2V_r}{V_P}} = \sqrt{\frac{2 \times 0.791}{17.8}} =$$


$$0.298 (142) \approx 0.3 [rad] = 17^\circ$$

$$\text{Exact Value } \theta = \arccos \frac{V_P - V_r}{V_P}$$

$$= 0.299237 \approx 0.3 [rad] = 17^\circ$$

10) Select a minimal capacitor sufficient for a bridge rectifier (60 Hz) with given specifications, $V_{dc} = 15\text{ V}$, $V_r < 0.15\text{ V}$, $I_{dc} = 2\text{ A}$.

Assume $V_{on} = 1\text{ V}$.

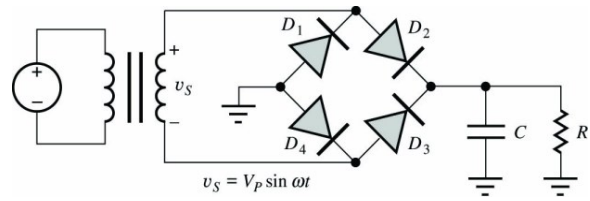

- 1) 0.111 F
- 2) 3.62 μF
- 3) 0.412 F
- 4) 19.1 pF
- 5) 0.337 F
- 6) None of the above

$$C = I_{dc} \left(\frac{T/2}{V_r} \right) = 2\text{ A} \left(\frac{1}{120\text{ s}} \right) \left(\frac{1}{0.15\text{ V}} \right) = 0.111\text{ F}$$