

ECE 5984: Power Distribution System Analysis


## Lecture 15: Center-Tapped Transformers and Secondaries

Reference: Textbook, Chapter 11

*Instructor: V. Kekatos*


# Center-tapped and three-winding transformers

terminology: 240/120 V

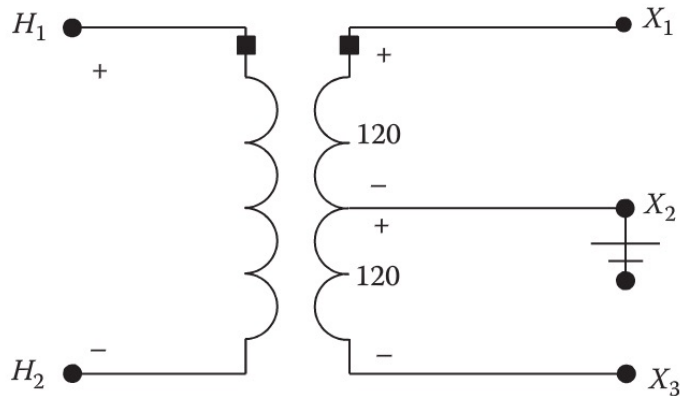

*center-tapped (two-winding)  
transformer*


terminology: 120/240 V

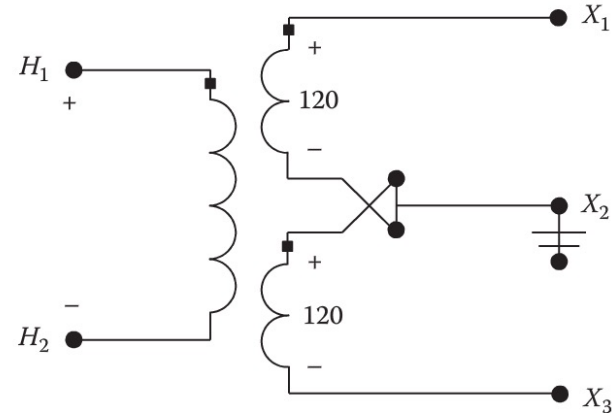

*three-winding transformer*


- Either known as *split-phase*
- Oven, washing machine, dryer connected on 240V; else on 120V
- Secondary windings in 120/240 can be connected in series or parallel

# Autotransformer implementation

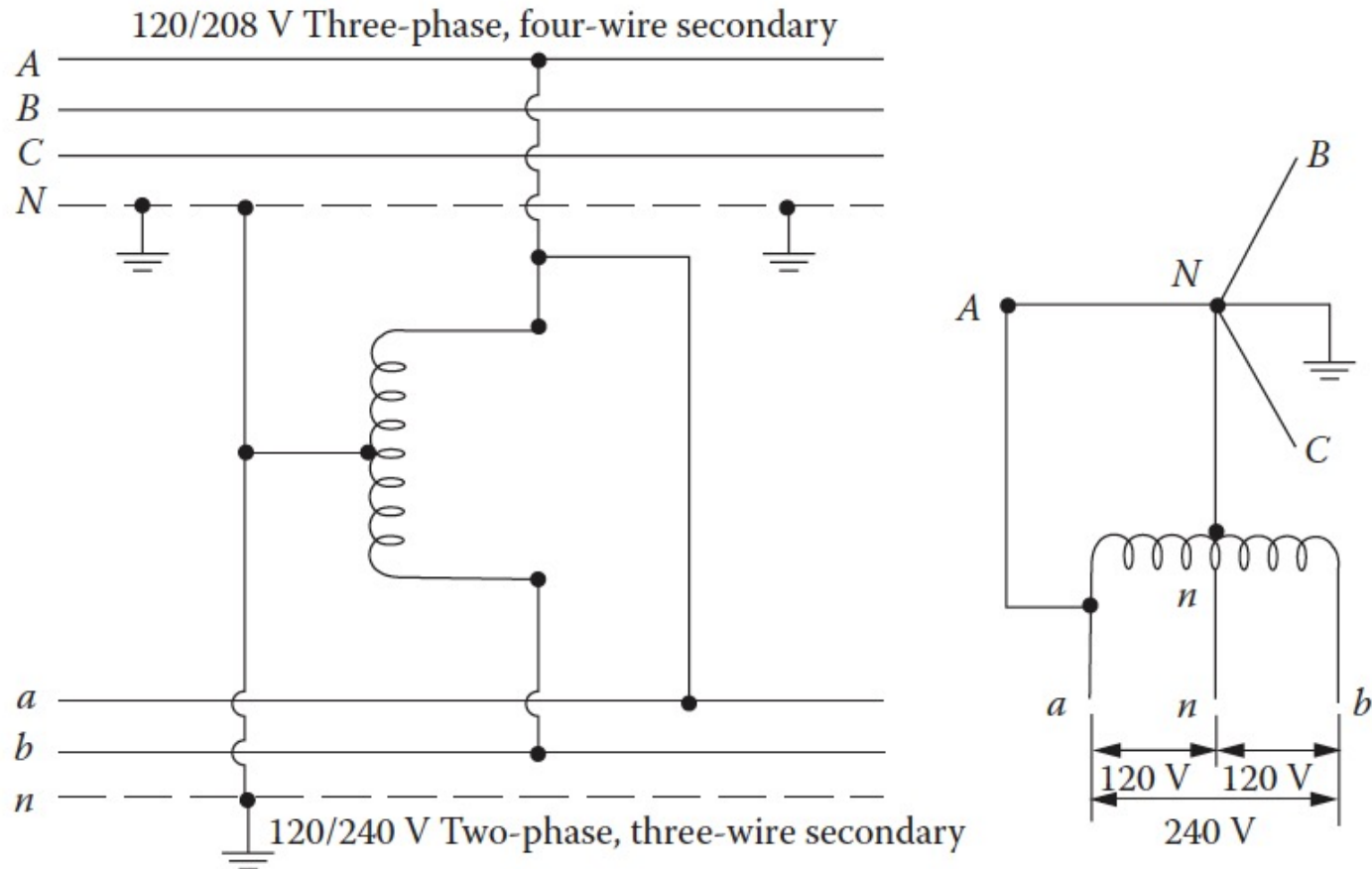

[Gonen: Electric Power Distribution Engineering]

# Center-tapped transformer model

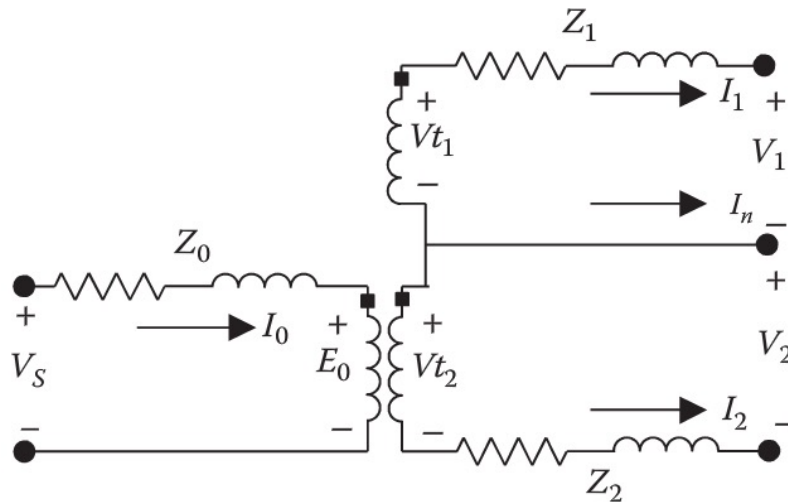


$$n_t = \frac{\text{primary voltage}}{\text{secondary (full) voltage}}$$

- Backward model  $\mathbf{D} = \frac{1}{2n_t} [+1 \quad -1]$

- Forward model  $\mathbf{E} = \frac{1}{2n_t} \mathbf{1}, \quad \mathbf{F} = \begin{bmatrix} Z_1 + \frac{Z_0}{4n_t^2} & -\frac{Z_0}{4n_t^2} \\ +\frac{Z_0}{4n_t^2} & -\left(Z_2 + \frac{Z_0}{4n_t^2}\right) \end{bmatrix}$

# Finding impedances

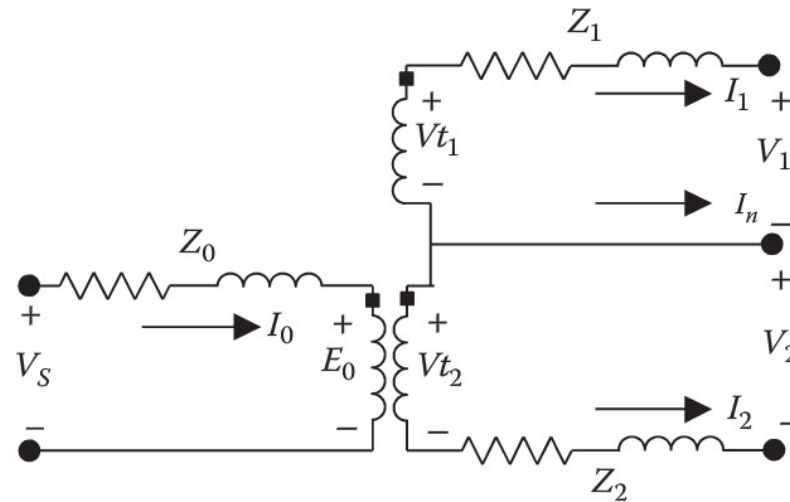


- Typically given the per-unit transformer impedance; found via a short-circuit test
- It is empirically partitioned across windings as

$$Z_0 = 0.5R_M + j0.8X_M \text{ pu}$$

$$Z_1 = Z_2 = R_M + j0.4X_M \text{ pu}$$

# Example

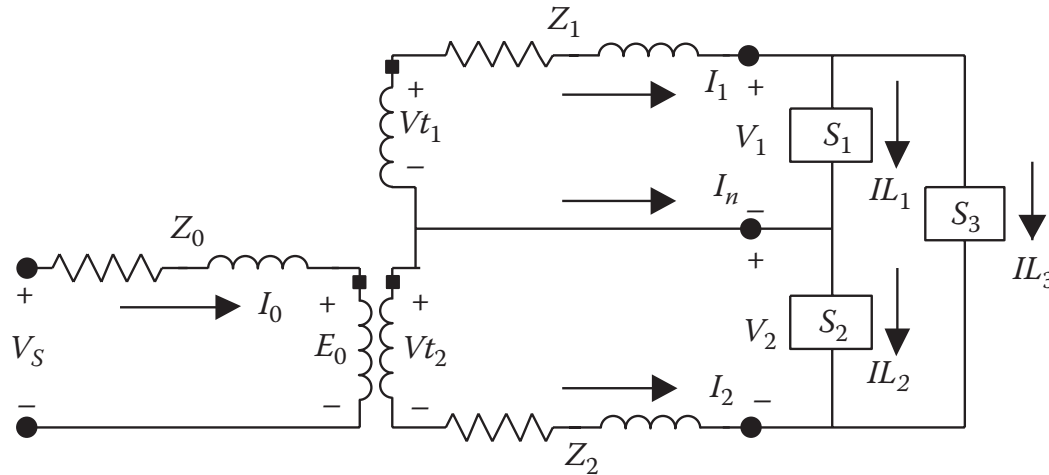

- Constant-power loads

$S_1 = 10 \text{ kVA}$  at 95% lagging

$S_2 = 15 \text{ kVA}$  at 90% lagging

$S_3 = 25 \text{ kVA}$  at 85% lagging

Source voltage:  $7200/0 \text{ V}$

- 50 kVA, 7200-240/120 V center-tapped transformer  $R_M + jX_M = 0.011 + j0.018 \text{ pu}$

- Split impedances  $Z_{pu_0} = 0.5 \cdot R_A + j0.8 \cdot X_A = 0.0055 + j0.0144 \text{ pu}$

$$Z_{pu_1} = R_A + j0.4 \cdot X_A = 0.011 + j0.0072 \text{ pu}$$

- Convert to ohms

$$Z_{\text{base,hi}} = \frac{7,200^2}{50,000} = 1,036.8$$


$$Z_0 = Z_{pu_0} \cdot Z_{\text{base}_{hi}} = 5.7024 + j14.9299 \Omega$$

$$Z_{\text{base,lo}} = \frac{120^2}{50,000} = 0.288$$

$$Z_1 = Z_2 = Z_{pu_1} \cdot Z_{\text{base}_{lo}} = 0.0032 + j0.0024 \Omega$$

- Construct matrices using above and turns ratio  $n_t = \frac{7,200}{240} = 30$

## Example (cont'd)

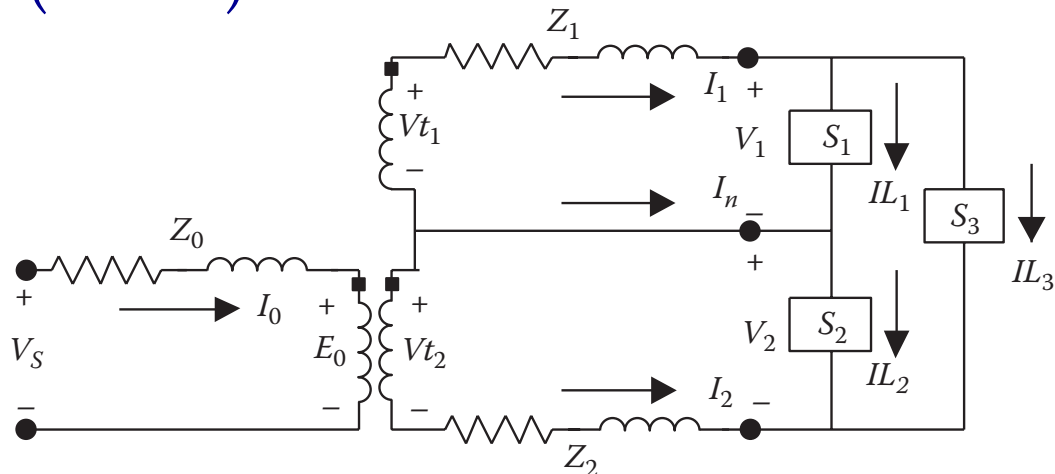


- Initialize load voltages (unloaded system)  $[V_{ld}] = \begin{bmatrix} V_1 \\ V_2 \\ V_1 + V_2 \end{bmatrix} = \begin{bmatrix} \underline{120/0} \\ \underline{120/0} \\ \underline{240/0} \end{bmatrix}$

- Update load currents  $I_{ld_i} = \left( \frac{SL_i \cdot 1000}{V_{ld_i}} \right)^* = \begin{bmatrix} \underline{83.3/-18.2} \\ \underline{125.0/-25.8} \\ \underline{104.2/-31.8} \end{bmatrix}$

- Update secondary line currents  $[I_{12}] = \begin{bmatrix} 1 & 0 & 1 \\ 0 & -1 & -1 \end{bmatrix} \cdot \begin{bmatrix} I_{L1} \\ I_{L2} \\ I_{L3} \end{bmatrix} = \begin{bmatrix} \underline{186.2/-25.8} \\ \underline{228.9/151.5} \end{bmatrix}$

- Forward/backward sweep converged within four iterations  $[V_{ld}] = \begin{bmatrix} \underline{117.88/-0.64} \\ \underline{117.71/-0.63} \\ \underline{235.60/-0.64} \end{bmatrix}$

# Triplex secondary

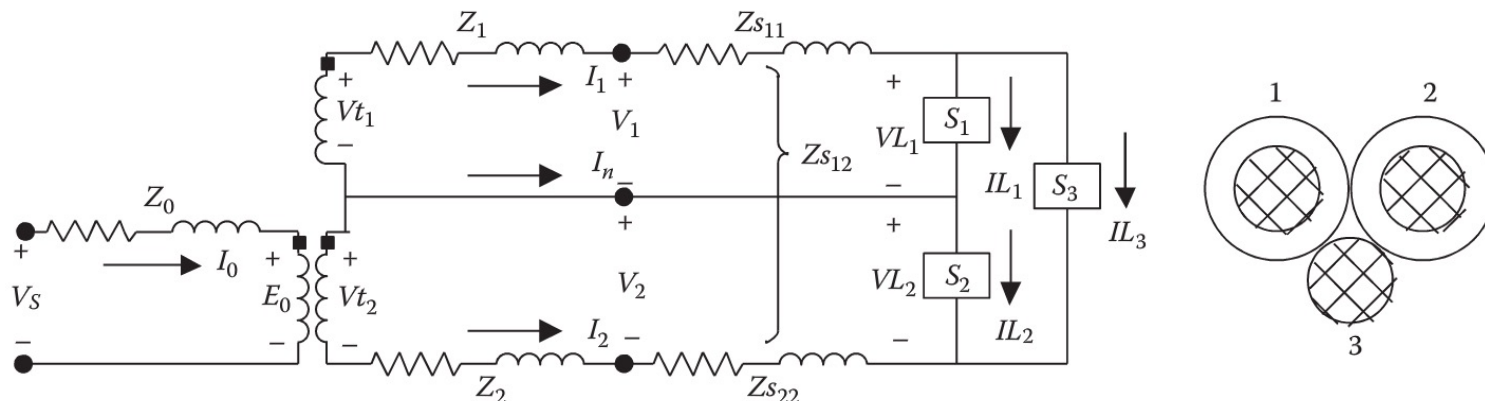

- Two insulated phase conductors and one ungrounded neutral conductor
- Apply Carson's equations to get a 3x3 primitive impedance matrix

$$D_{12} = D + 2T \quad D : \text{conductor diameter}$$

$$D_{13} = D_{23} = D + T \quad T : \text{insulation thickness}$$

- Kron reduction (grounded neutral) to get a 2x2 phase impedance matrix  $\mathbf{Z}$

- Backward/forward updates  $\mathbf{v}_n := \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}, \mathbf{v}_m := \begin{bmatrix} V_{L1} \\ V_{L2} \end{bmatrix}, V_{L3} = V_{L1} + V_{L2}$




$$\mathbf{i}_n = \mathbf{i}_m$$

$$\mathbf{v}_m = \mathbf{v}_n - \mathbf{Z}\mathbf{i}_m$$



# Example with triplex secondary

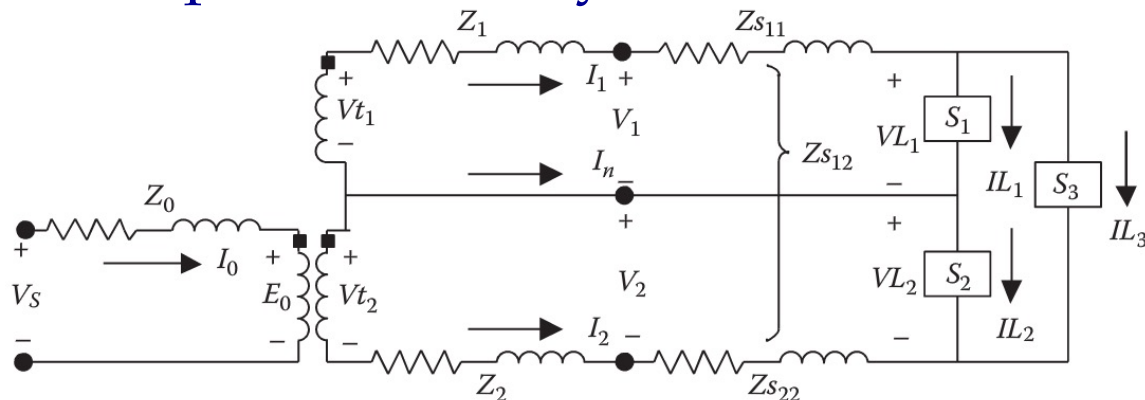

- Phase impedance matrix of triplex  $[Z_s] = \begin{bmatrix} 0.0271 + j0.0146 & 0.0087 + j0.0081 \\ 0.0087 + j0.0081 & 0.0271 + j0.0146 \end{bmatrix} \Omega$

- Secondary voltages  $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 117.89 / -0.64 \\ 117.75 / -0.62 \end{bmatrix}$

- Load voltages  $\begin{bmatrix} VL_1 \\ VL_2 \\ VL_3 \end{bmatrix} = \begin{bmatrix} 114.63 / -0.45 \\ 122.58 / -0.96 \\ 237.21 / -0.72 \end{bmatrix}$

- Line currents  $\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 190.2 / -26.2 \\ 227.5 / 150.6 \end{bmatrix}$

*voltage rise!*


- Primary current  $I_0 = 6.98 / -28.0$

- Neutral current  $I_n = [t_n] \cdot [I_{12}] = 25.4 / -15.0$

- Ground current  $I_g = -(I_n + I_1 + I_2) = 20.8 / -84.5$


*So far, considered 3W 1-phase service. How about 4W 3-phase service?*

# Wye-delta center-tapped transformer

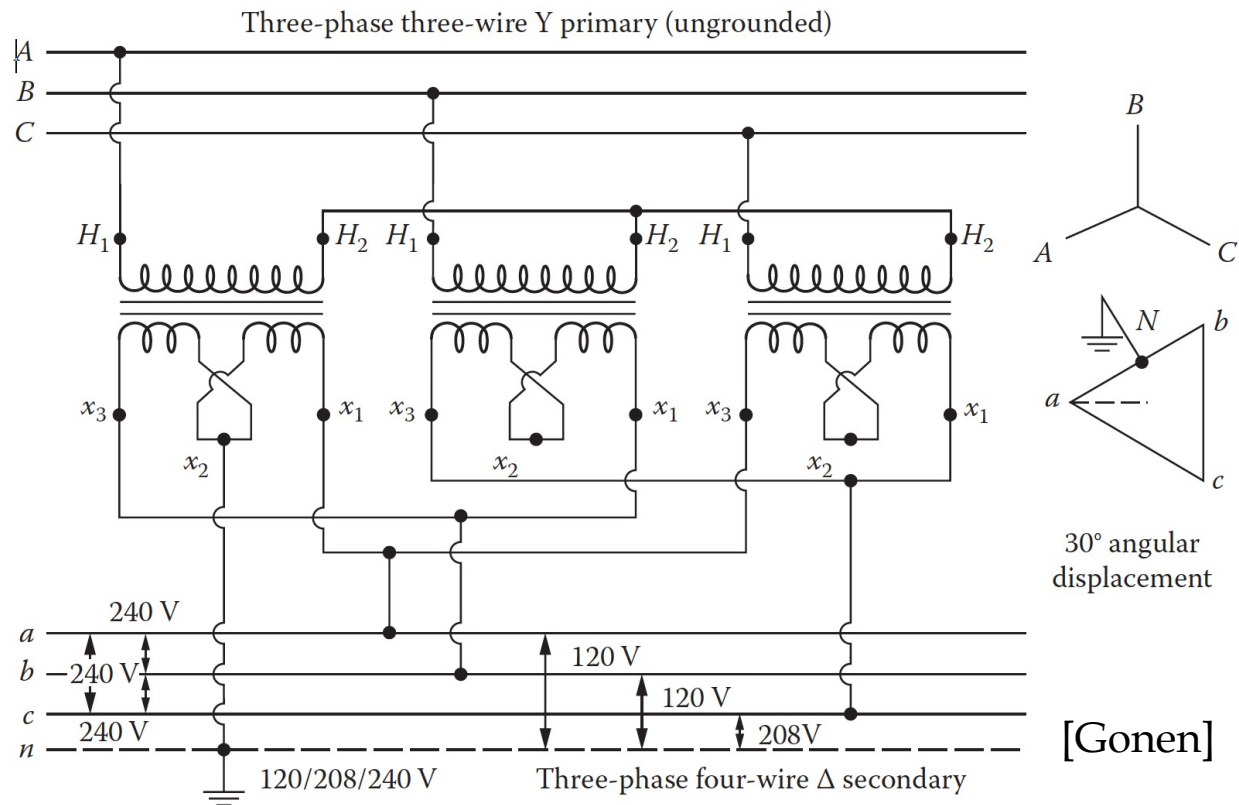

- Common connection for combination of single- and three-phase loads
- One center-tapped '*lighting*' transformer for three-wire service to single-phase loads
- Two regular '*power*' transformers for three-phase loads

# Wye-delta center-tapped transformer

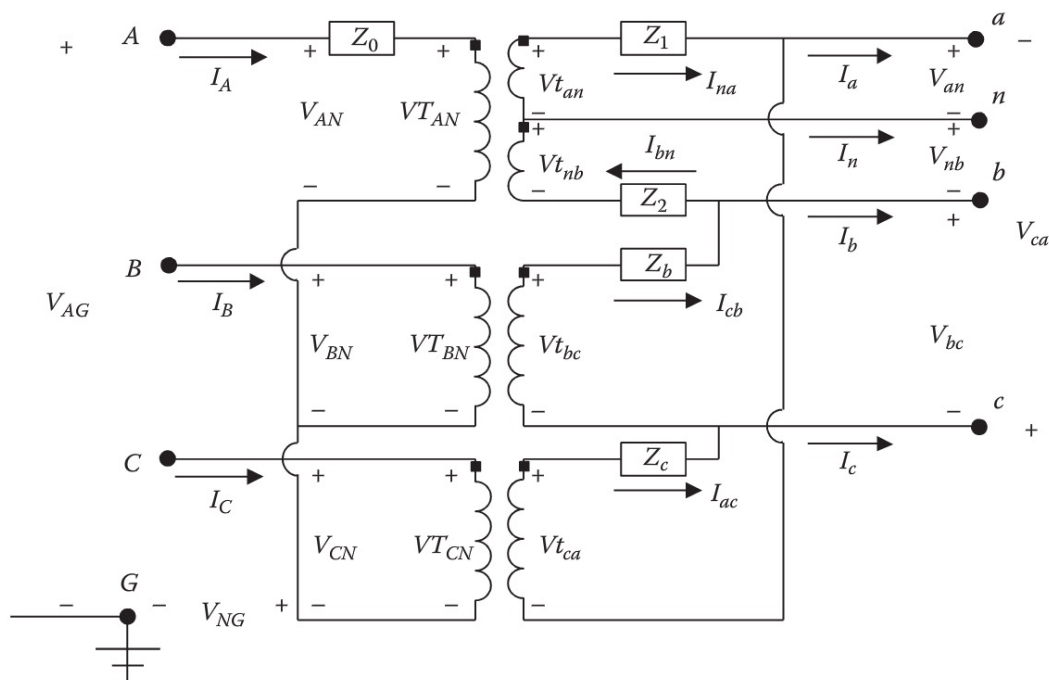

- Use zero-sum primary currents to convert secondary delta to line currents


- Backward sweep 
$$\mathbf{D} = \frac{1}{6n_t} \begin{bmatrix} 2 & -2 & 0 & 0 \\ -1 & 1 & -3 & 0 \\ -1 & 1 & 3 & 0 \end{bmatrix}$$

*neutral current can be ignored*

- Forward sweep 
$$\mathbf{E} = \frac{1}{2n_t} \begin{bmatrix} 1 & 0 & 0 \\ 1 & 0 & 0 \\ 0 & 2 & 0 \\ 0 & 0 & 2 \end{bmatrix}, \quad \mathbf{F} = \frac{1}{6} \begin{bmatrix} 5z_1 + \frac{z_0}{n_t^2} & z_1 - \frac{z_0}{n_t^2} & 3z_1 & 0 \\ -z_2 + \frac{z_0}{n_t^2} & -5z_2 - \frac{z_0}{n_t^2} & -3z_2 & 0 \\ -z_b & z_b & -3z_b & 0 \\ -z_c & z_c & 3z_c & 0 \end{bmatrix}$$

$$\tilde{\mathbf{v}}_m = \mathbf{E}\mathbf{v}_n - \mathbf{F}\mathbf{i}_m$$
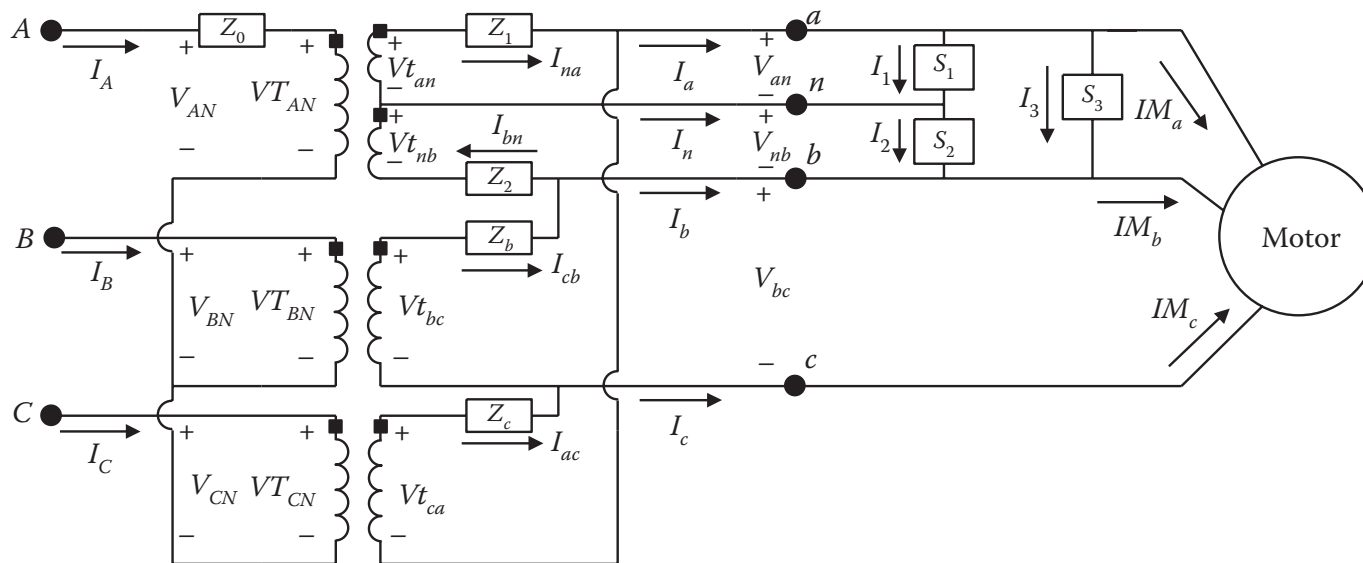
# Example with wye-delta center-tapped transformer



## single-phase loads

$SL_1 = 3 \text{ kVA}, 120 \text{ V}, 0.95 \text{ lagging power factor}$

$SL_2 = 5 \text{ kVA}, 120 \text{ V}, 0.90 \text{ lagging power factor}$

$SL_3 = 8 \text{ kVA}, 240 \text{ V}, 0.85 \text{ lagging power factor}$

## induction motor

$Z_s = 0.0774 + j0.1843 \Omega$

$Z_r = 0.0908 + j0.1843 \Omega$

$Z_m = 0 + j4.8385 \Omega$

slip = 0.035


## transformers and source

Lighting transformer: 25 kVA, 7200–240/120 V,  $Z_{L_{pu}} = 0.012 + j0.017$

Power transformers: 10 kVA, 7200–240 V,  $Z_{P_{pu}} = 0.016 + j0.014$

Source voltage: Balanced line-to-neutral 7200 V

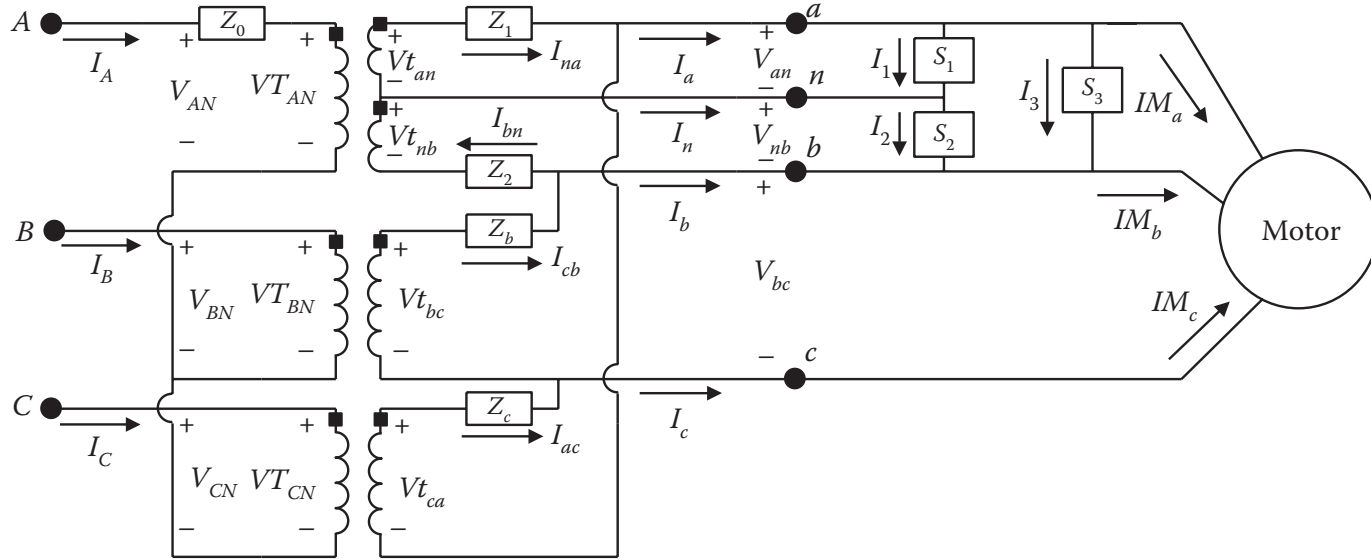
# Example with wye-delta center-tapped transformer (cont'd)



*motor*



$$[VM] = \begin{bmatrix} 234.7/\underline{-0.39} \\ 235.1/\underline{-120.1} \\ 236.1/\underline{119.7} \end{bmatrix} \quad V_{unbalance} = 0.3382\% \quad [I_M] = \begin{bmatrix} 56.3/\underline{-65.6} \\ 56.1/\underline{176.6} \\ 58.1/\underline{54.6} \end{bmatrix}$$

# Open Wye - open Delta

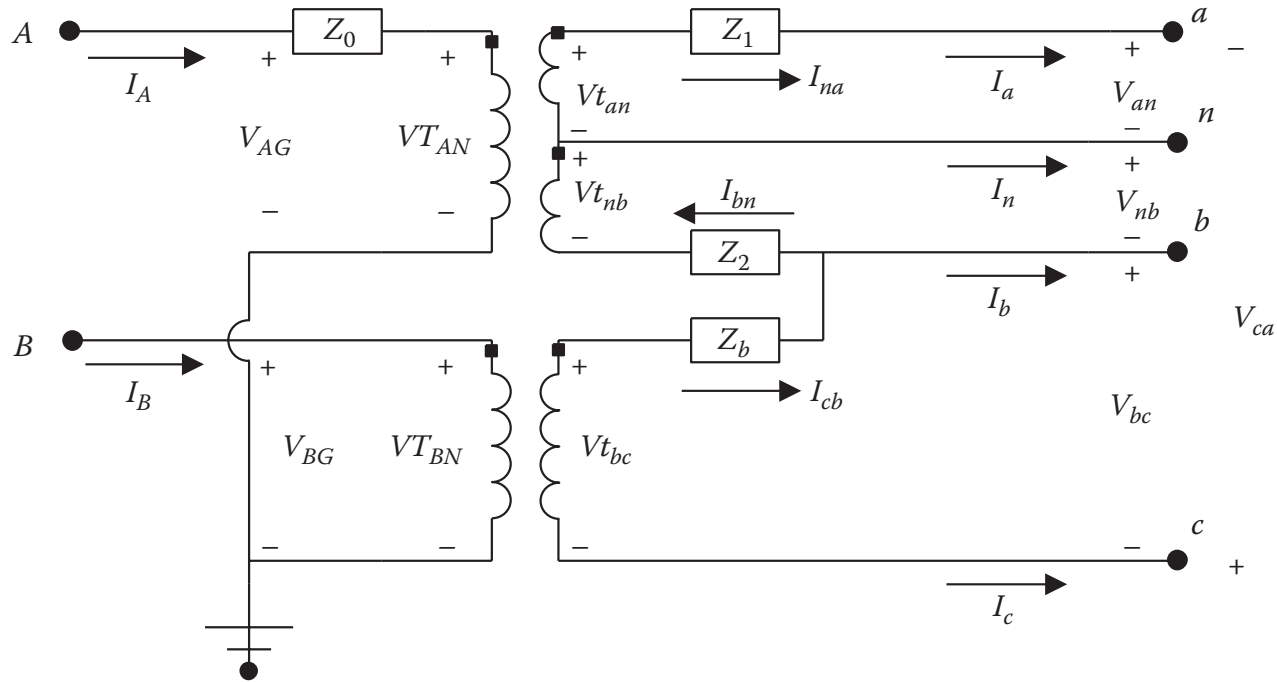


- Two sending currents and two sending voltages
- Four receiving currents and three receiving voltages
- *Leading*: lighting transformer on A; power transformer on B
- *Lagging*: lighting transformer on A; power transformer on C

# Leading open Wye - open Delta

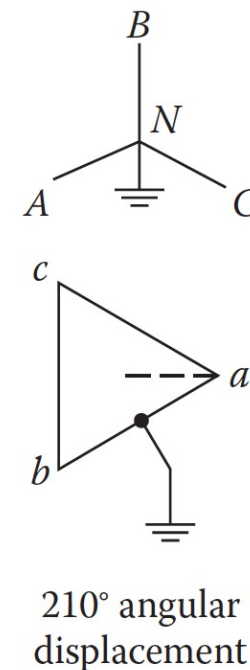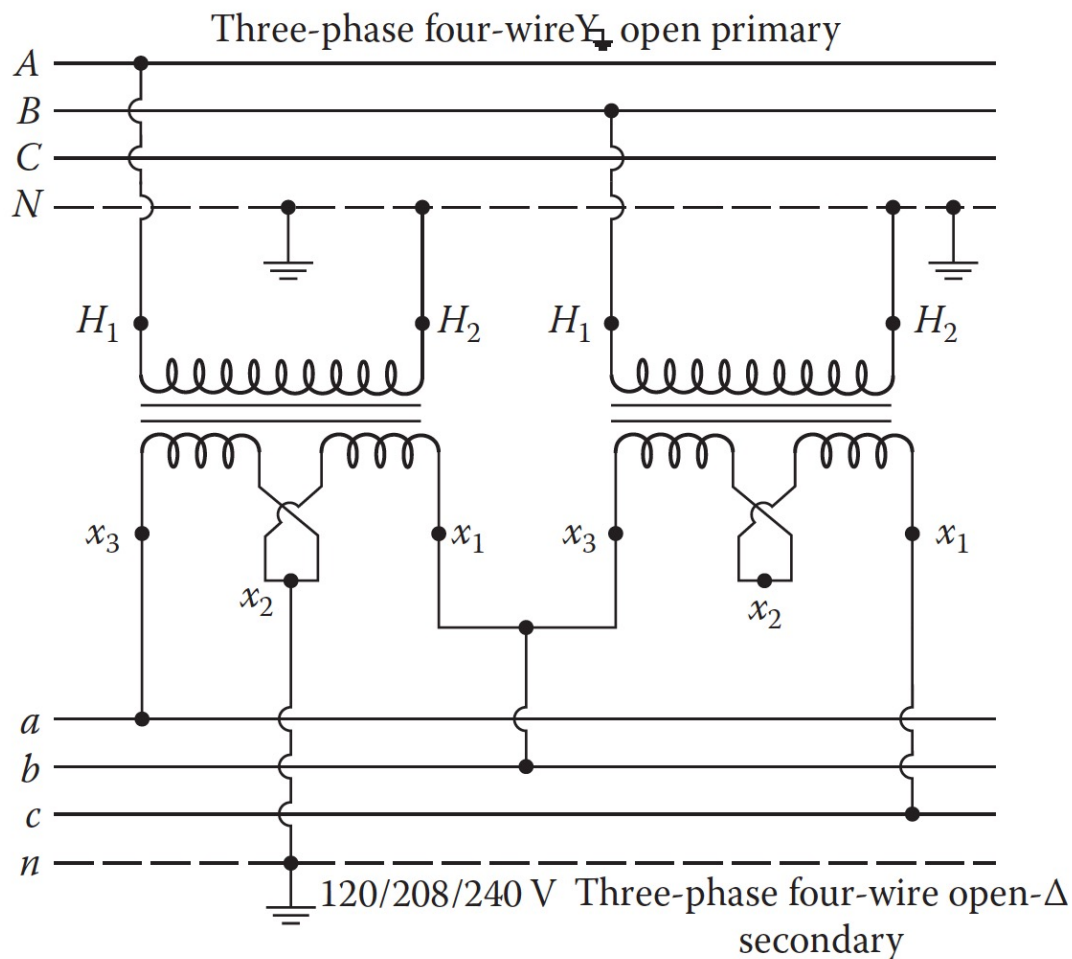

- Leading because lighting (resp. power) transformer is connected on A (resp. B)

# Lagging open Wye - open Delta

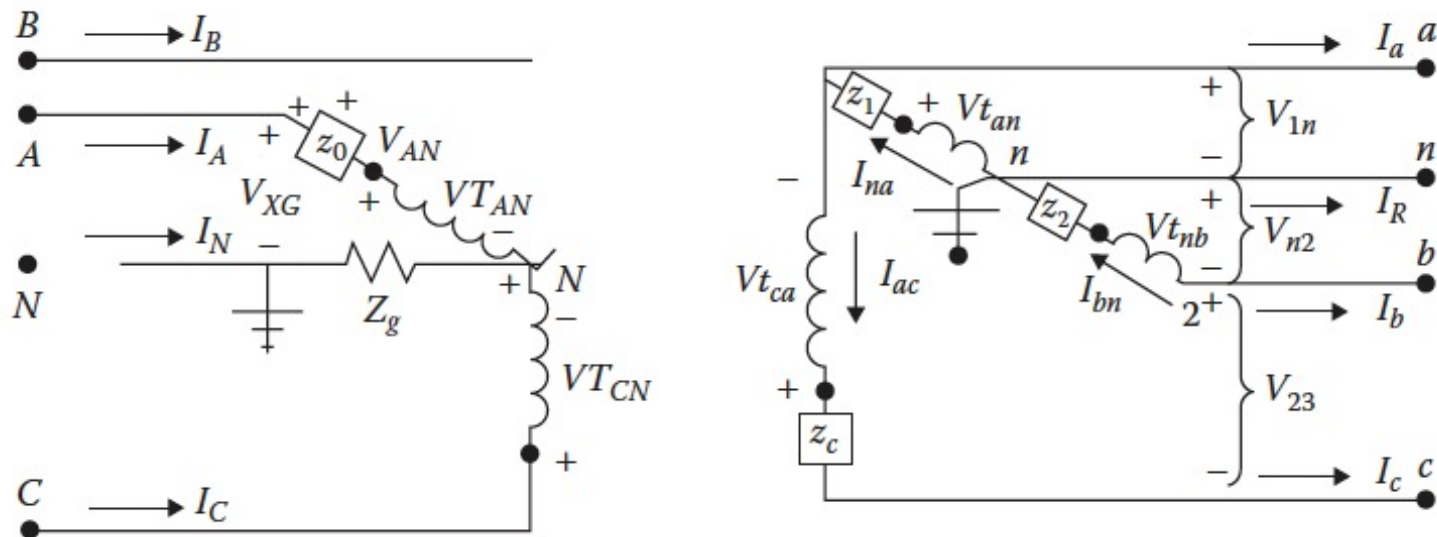

- No trick in deriving the CDEF model; similar model for leading connections


- Backward model 
$$\mathbf{D} = \frac{1}{2n_t} \begin{bmatrix} 1 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 2 & 0 \end{bmatrix}$$

- Forward model

$$\mathbf{E} = \frac{1}{2n_t} \begin{bmatrix} 1 & 0 & 0 \\ 1 & 0 & 0 \\ 0 & 0 & 1 \end{bmatrix}, \mathbf{F} = \begin{bmatrix} z_1 + \frac{z_0+z_g}{4n_t^2} & -\frac{z_0+z_g}{4n_t^2} & z_1 + \frac{z_0+3z_g}{4n_t^2} & 0 \\ \frac{z_0+z_g}{4n_t^2} & -z_2 - \frac{z_0+z_g}{4n_t^2} & \frac{z_0+3z_g}{4n_t^2} & 0 \\ \frac{z_g}{2n_t^2} & -\frac{z_g}{2n_t^2} & z_c + \frac{3z_g}{2n_t^2} & 0 \end{bmatrix}$$




# Quadruplex secondary

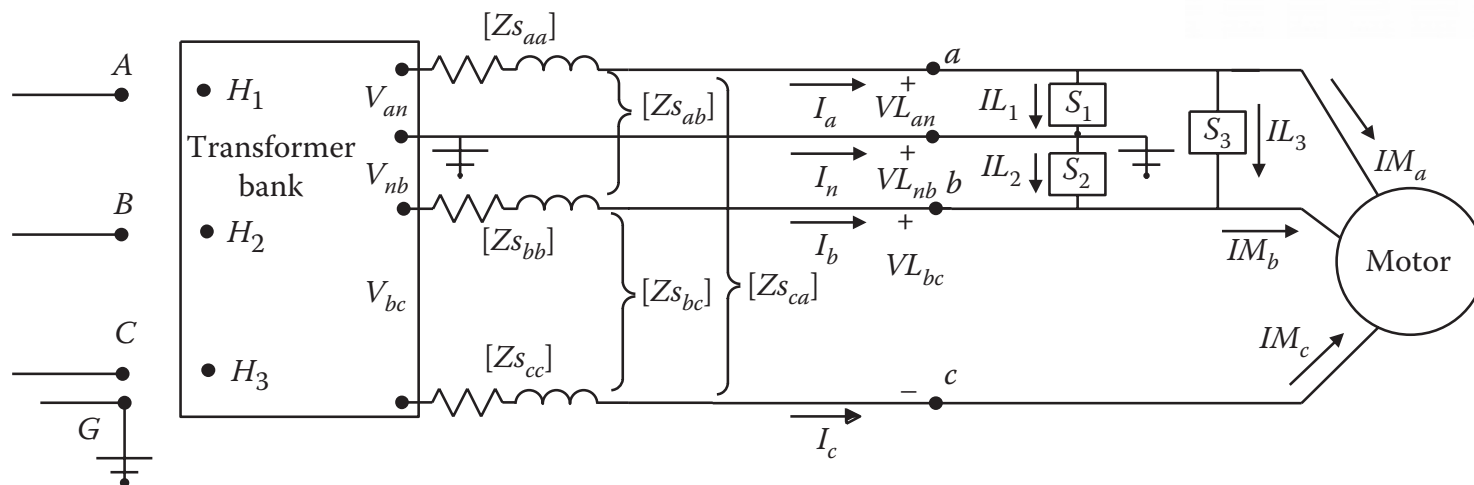


- Kron reduction on primitive (4x4) to get the 3x3 phase impedance matrix  $\mathbf{Z}$
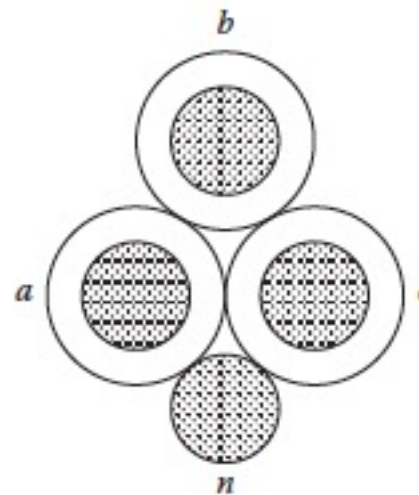
$$\begin{bmatrix} \tilde{v}_a \\ \tilde{v}_b \\ \tilde{v}_c \end{bmatrix} = \begin{bmatrix} v_{an} - v_{L,an} \\ v_{bn} - v_{L,bn} \\ v_{cn} - v_{L,cn} \end{bmatrix} = \mathbf{Z} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix}$$



# Incorporating line drop

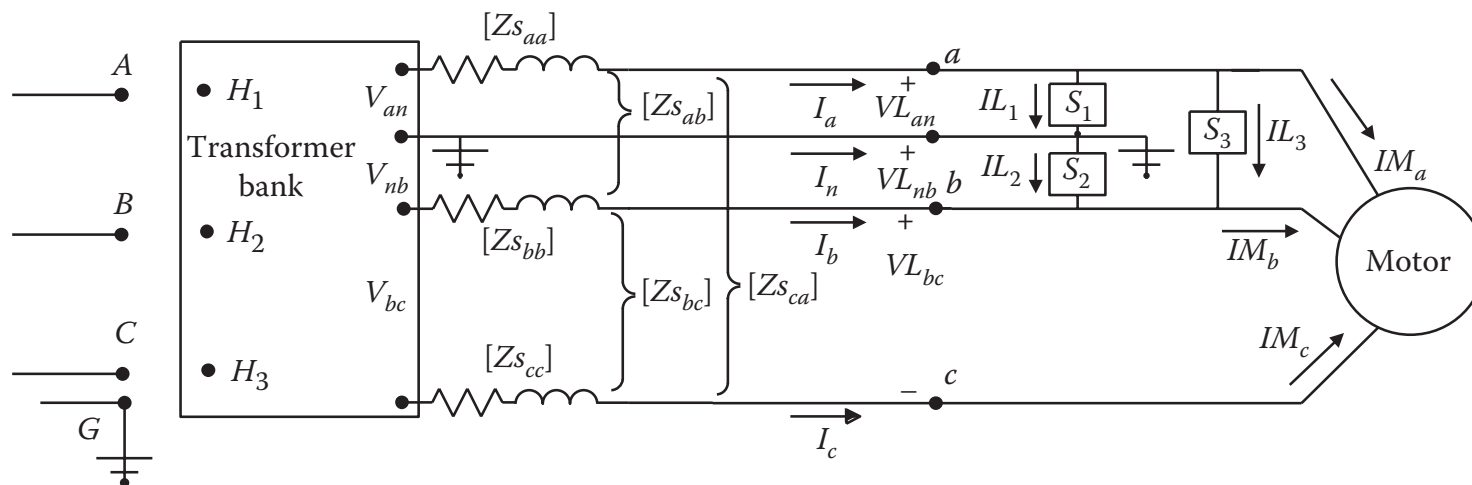

- Relate transformer-load voltage drops to line voltage drops

$$\begin{bmatrix} v_{an} \\ v_{nb} \\ v_{bc} \\ v_{ca} \end{bmatrix} - \begin{bmatrix} v_{L,an} \\ v_{L,nb} \\ v_{L,bc} \\ v_{L,ca} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} \tilde{v}_a \\ \tilde{v}_b \\ \tilde{v}_c \end{bmatrix}$$

$\downarrow$   $\mathbf{V}_n$                        $\downarrow$   $\mathbf{V}_m$



- Forward update

$$\mathbf{V}_m = \mathbf{V}_n - \begin{bmatrix} z_{aa} & z_{ab} & z_{ac} \\ -z_{ab} & -z_{bb} & -z_{bc} \\ z_{ab} - z_{ac} & z_{bb} - z_{bc} & z_{bc} - z_{cc} \\ z_{ac} - z_{aa} & z_{bc} - z_{ab} & z_{cc} - z_{ac} \end{bmatrix} \mathbf{i}_m$$

# Summary
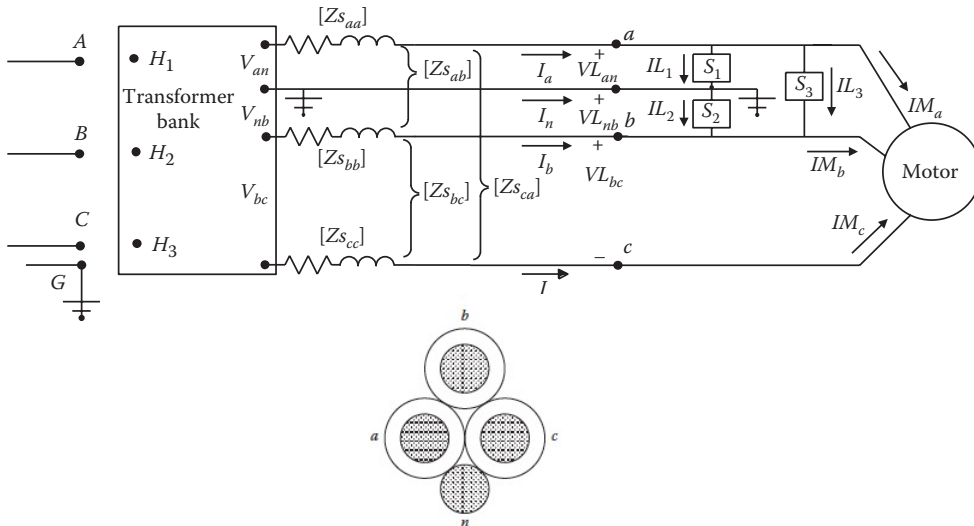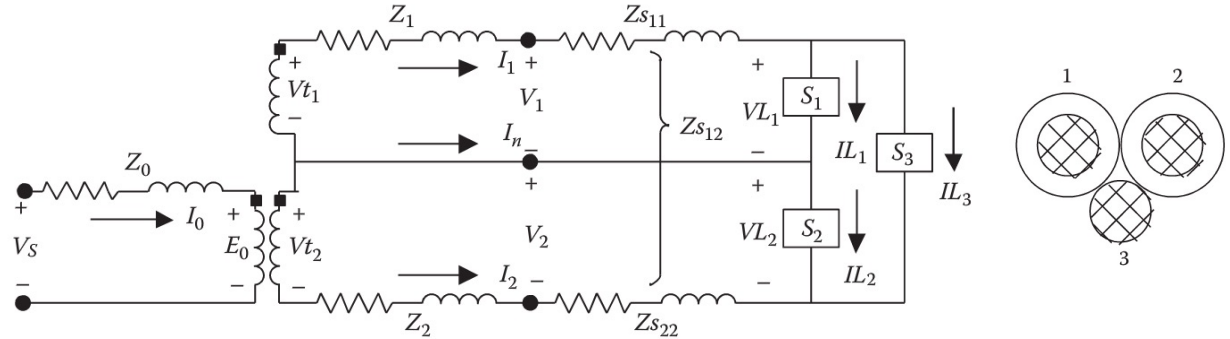
## 3W single-phase service

- split-phase transformer
- triplex cable



## 4W three-phase service

- Wye-Delta transformer
- open Wye-open delta transformer
- quadruplex cable