

ECE 5984: Power Distribution System Analysis


## Lecture 3: Approximate Feeder Analysis

Reference: Textbook, Chapter 3

*Instructor: V. Kekatos*
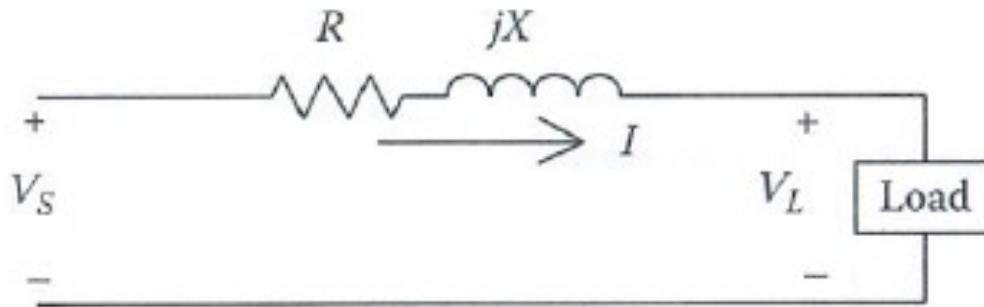
# Approximate analysis

- Develop *approximate* methods for determining **voltage drops** and **power losses**
- *Assumptions*
  - loads are balanced three-phase
  - loads are constant-current (if constant-power, assume negligible voltage drop)
  - lines are transposed and three-phase
- Single-phase (line-to-neutral) equivalent



$$V_S = ZI + V_L$$

[Kersting]

Voltage drop:  $\Delta V := |V_S| - |V_L|$

Power losses:  $P_\ell := 3R|I|^2$


# Line impedance

- Due to transposition and balanced loads, *positive-sequence impedance* suffices


$$z_1 = r + j\omega \cdot 2 \cdot 10^{-7} \cdot \ln \left( \frac{\bar{D}}{\bar{R}} \right) \Omega/\text{m}$$
$$= r + j \cdot 0.1213 \cdot \ln \left( \frac{\bar{D}}{\bar{R}} \right) \Omega/\text{mile}$$

$$\text{GMD: } \bar{D} := (D_{ab}D_{bc}D_{ca})^{1/3}$$

$$\text{GMR: } \bar{R}$$

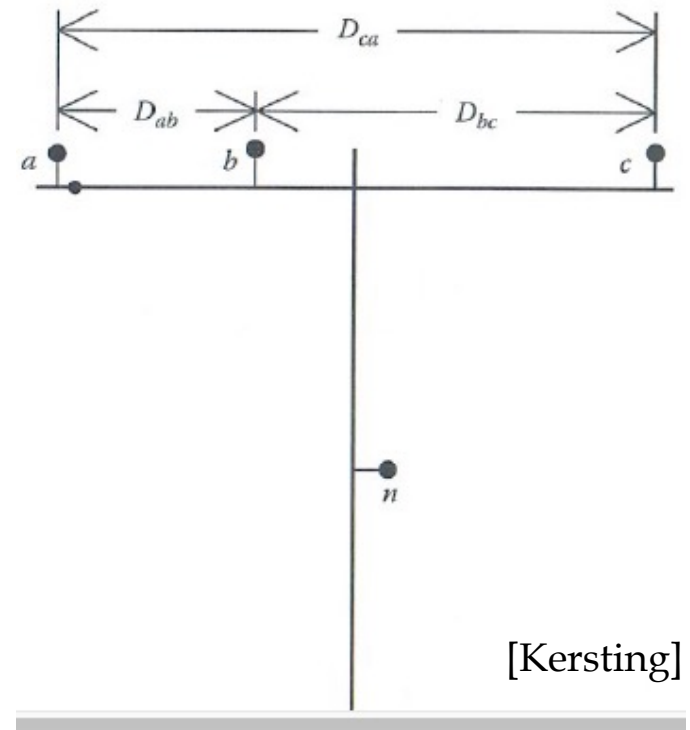

# Voltage drop

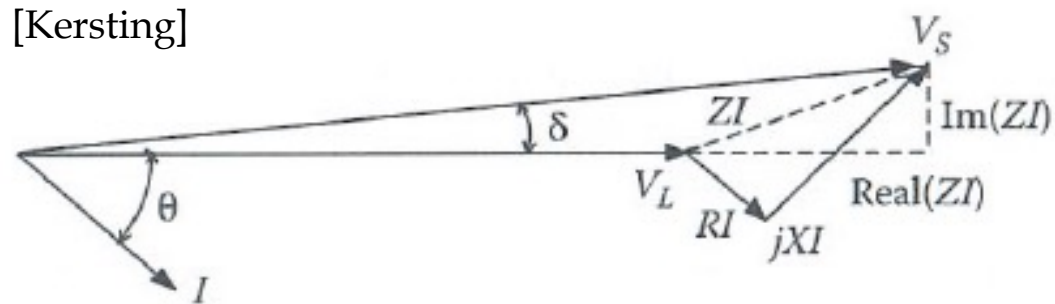

- Because  $\delta$  is small, approximate

$$\Delta V \simeq \text{Re}(ZI)$$

[Why?]

**Example:**  $V_S = 2400 \text{ V}$ ,  $Z = 0.284 + j0.568 \ \Omega$ ,  $I = 43 \angle -25^\circ \text{ A} \Rightarrow$   
 $V_L = 2378.41 \angle -0.40^\circ \text{ V}$

exact voltage drop:  $\Delta V = 21.59 \text{ V} = 0.9\%$

approx. voltage drop:  $\Delta V = 21.65 \text{ V} = 0.9\%$

# 'Voltage-square law'

*Both relative voltage drop and power losses are (approximately) inversely proportional to the LL voltage level*

$$\Delta V \simeq \operatorname{Re}(ZI) \simeq \operatorname{Re}\left(Z \frac{S^*}{\sqrt{3}V_{LL}}\right) \Rightarrow \frac{\Delta V}{V_{LN}} = \operatorname{Re}\left(\frac{ZS^*}{V_{LL}^2}\right)$$

If you double the voltage level, you can transfer four times more power for the same relative voltage drop (or the same power for four times the distance)

$$P_\ell = 3R|I|^2 \simeq 3R \left| \frac{S}{\sqrt{3}V_{LL}} \right|^2 \Rightarrow P_\ell = \frac{R|S|^2}{V_{LL}^2}$$

If you double the voltage level, you can transfer two times more power for the same copper losses (or the same power for four times the distance)

# $K_{drop}$ factor

- Factors used for fast and approximate voltage drop calculations

**Definition:** Voltage drop relative to nominal *phase (not LL) voltage* for serving 1 kVA load with given power factor located 1 mile away

$$K_{drop} := \frac{\Delta V [\%]}{\text{kVA} \cdot \text{mile}}$$

- From previous approximation  $\Delta V \simeq \text{Re}(ZI)$
- Impedance over a mile  $Z = z [\Omega/\text{mile}]$
- Current for 1 kVA @ given PF  $S = |S|e^{j\theta}$ ,  $\theta = \pm \cos^{-1}(\text{PF})$  : +/- for lagging/leading

typical: lagging PF 0.9  
 $\theta = +25.84^\circ$

$$I \simeq \frac{S^*}{\sqrt{3}V_{LL}} = \frac{1000 \cdot e^{-j\theta}}{\sqrt{3}V_{LL}}$$

- Simplified expression  $K_{drop} = \frac{\Delta V}{V_{LN}} \times 100 = \frac{\text{Re}(z \cdot e^{-j\theta})}{V_{LL}^2} \times 10^5$

*voltage-square law*

## $K_{drop}$ factor (cont'd)

- Simplified expression  $K_{drop} = \frac{\text{Re}(z \cdot e^{-j\theta})}{V_{LL}^2} \times 10^5$  [% voltage drop (LN)/mile/kVA]

- Utilities compute  $K$  factors for all combinations of voltage levels and line types

**Example:** For a line with  $z = 0.306 + j0.627 \Omega/\text{mile}$ , compute  $K_{drop}$  assuming lagging PF 0.9 and nominal voltage of 12.47 kV

$$K_{drop} = 3.53 \cdot 10^{-4}$$

- Questions that can be easily answered with  $K$  factors:

*How far can I serve a 7500 kVA load within the 3% voltage drop?*


$$K_{drop} \cdot 7,500 \cdot d = 3 \Rightarrow d = 1.13 \text{ miles}$$

*What is the maximum load I can serve within 1.5 miles from the substation?*

$$K_{drop} \cdot L \cdot 1.5 = 3 \Rightarrow L = 5,668 \text{ kVA}$$
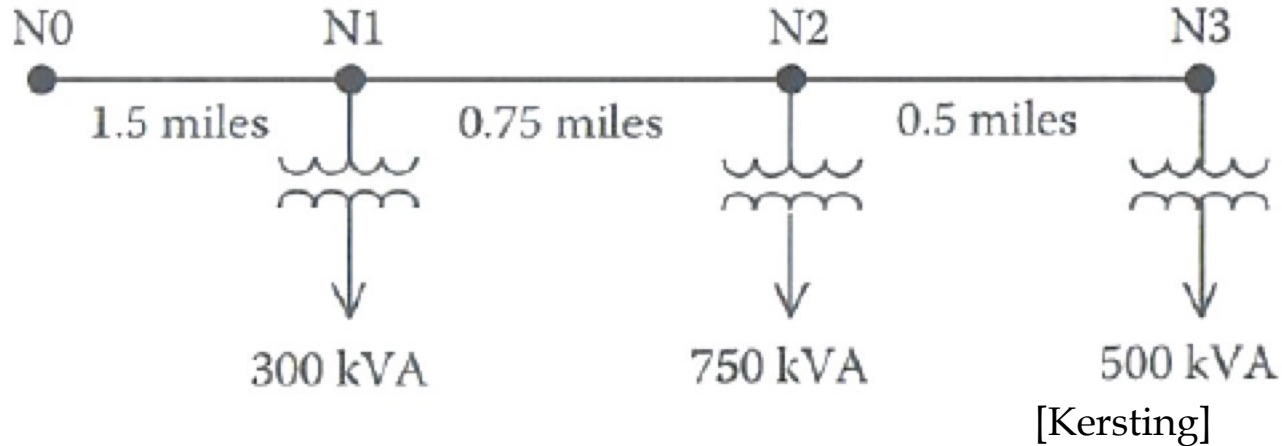
# Line segments in series

- Voltage drops calculated through  $K$  factors apply additively



## Example

$$\Delta V_{01} = \frac{|V_0| - |V_1|}{V_{LN}} \% = K_{\text{drop}} \cdot (300 + 750 + 500) \cdot 1.5 = 0.82$$

$$\Delta V_{12} = \frac{|V_1| - |V_2|}{V_{LN}} \% = K_{\text{drop}} \cdot (750 + 500) \cdot 0.75 = 0.33$$

$$\Delta V_2 = \Delta V_{01} + \Delta V_{12} = 1.15$$




# $K_{rise}$ factor

- Factors for approximately calculating voltage rise incurred by capacitors

$$K_{rise} := \frac{\Delta V_{rise} [\%]}{\text{kVAR} \cdot \text{mile}}$$

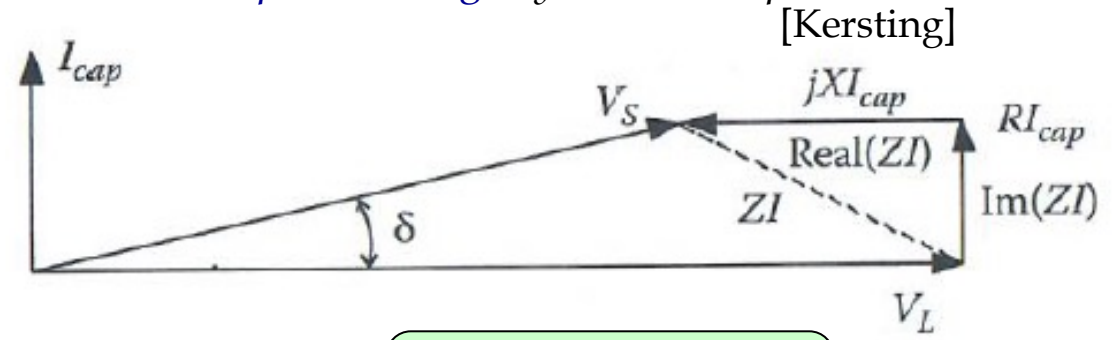**Definition:** Voltage rise relative to nominal phase voltage by 1 kVAR capacitor located 1 mile away



$$\Delta V_{rise} \simeq |\text{Re}(ZI_c)| = X|I_c|$$




$$K_{rise} = \frac{x}{V_{LL}^2} \times 10^5$$

**Example:** For the previous line, find the  $K_{rise}$  and the capacitor rating needed to fix a voltage drop of 3.5% to 2.5% located 1.5 miles away

$$K_{rise} = 4.03 \cdot 10^{-4}$$

$$K_{rise} \cdot Q_c \cdot 1.5 = 1 \Rightarrow Q_c = 1,653 \text{ kVAR}$$

# Uniformly distributed discrete loads

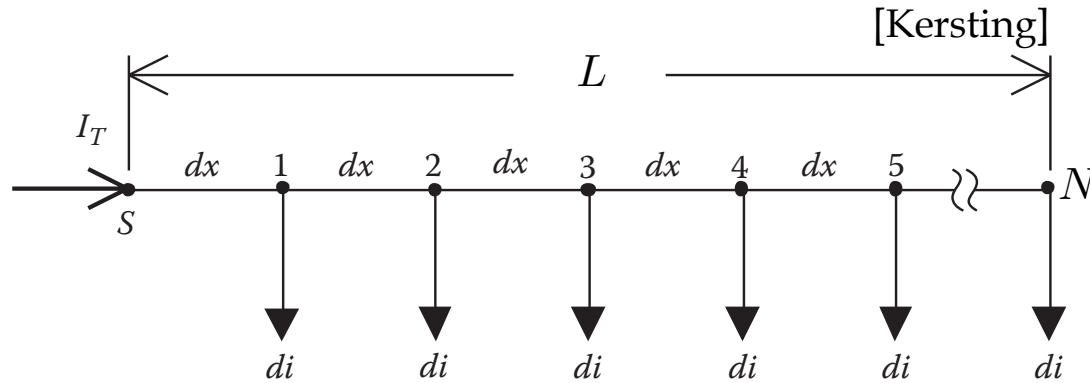


- $N$  loads uniformly distributed over a line segment of length  $L$
- Current loads drawing equal current
- Analyze voltage drop at *end of segment* and total power losses

# Uniformly distributed discrete loads (cont'd)
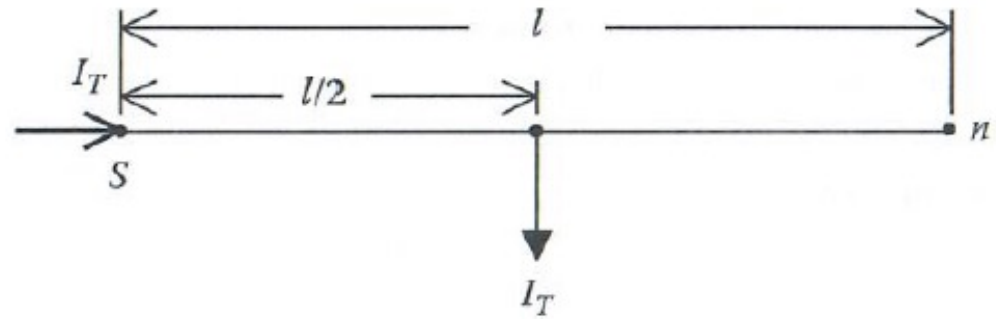
## Voltage drop

$$\Delta V = \operatorname{Re} \left\{ \frac{1}{2} Z I \left( 1 + \frac{1}{N} \right) \right\}$$


$$\stackrel{N \rightarrow \infty}{\equiv} \operatorname{Re} \left\{ \frac{1}{2} Z I \right\}$$



## Power losses

$$P_\ell = 3R|I|^2 \left[ \frac{1}{3} + \frac{1}{2N} + \frac{1}{6N^2} \right]$$


$$\stackrel{N \rightarrow \infty}{\equiv} 3\frac{R}{3}|I|^2$$

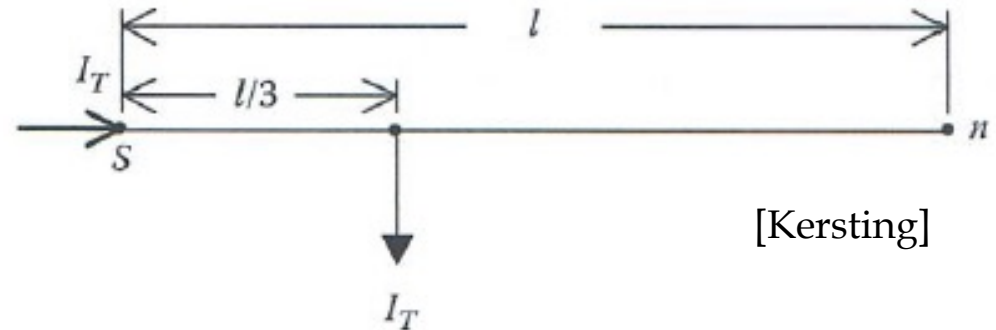

[Kersting]
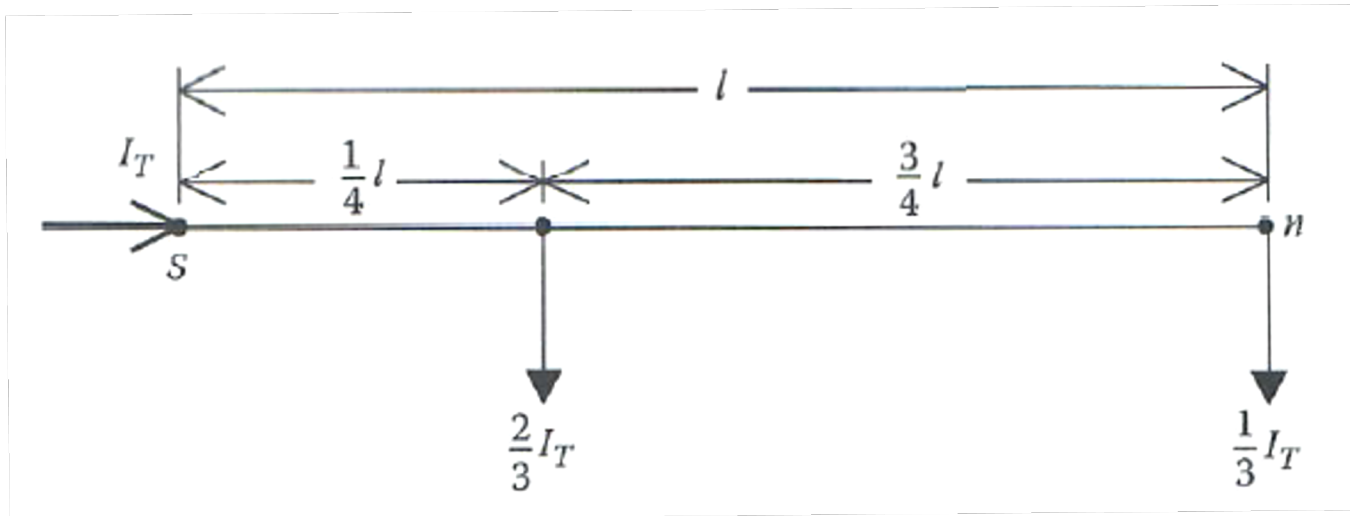
## Uniformly distributed discrete loads (cont'd)

*Can you replace all loads with two loads rather than one that agrees both in voltage drop and power losses?*



[Kersting]

# Loads uniformly distributed over areas


- Assume constant-current loads uniformly distributed over a geographic area
- A primary distribution line runs across and serves the area
- Given
  - load density  $D$  [kVA/mile<sup>2</sup>]
  - area shape and dimensions
  - geographical area  $A$  [mile<sup>2</sup>]
  - load PF (assumed constant)
  - per-mile impedance of main line
  - nominal voltage  $V_{LL}$
- Wanted: Find voltage drop at the end of the primary and total power losses
- Total current at the substation entering the primary

$$I \simeq \frac{D \cdot A \cdot e^{-j\theta}}{\sqrt{3} \cdot V_{LL}}$$

# Rectangular area

Voltage drop  $\Delta V = \operatorname{Re} \left\{ \frac{1}{2} Z I \right\}$

Power losses  $P_\ell = 3 \left( \frac{1}{3} R |I|^2 \right)$

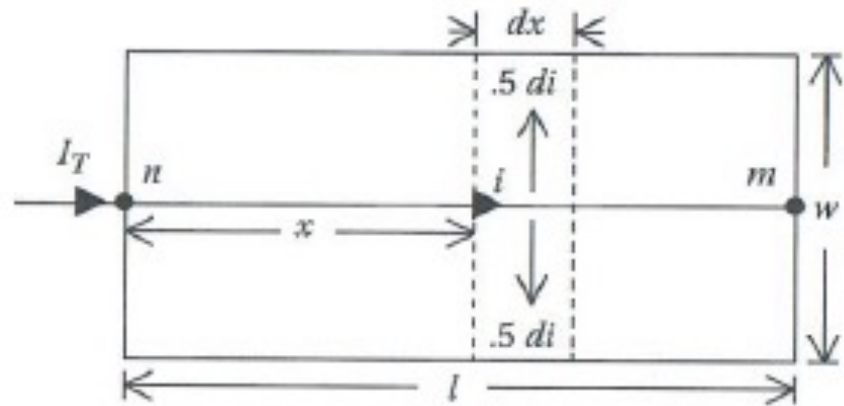

- Compare to uniformly distributed loads

[Kersting]

**Example:** Find power losses and choose voltage level between 4.16 and 12.47 kV for rectangular area with

$\ell = 10,000$  ft;  $w = 6,000$  ft;  $D = 2500$  kVA/mile<sup>2</sup>; PF = 0.9;  $z = 0.306 + j0.627$   $\Omega$ /mile


1 mile = 5280 feet

# Triangular area

- Load increases as moving away from substation

Voltage drop  $\Delta V = \text{Re} \left\{ \frac{2}{3} ZI \right\}$

Power losses  $P_\ell = 3 \left( \frac{8}{15} R |I|^2 \right)$

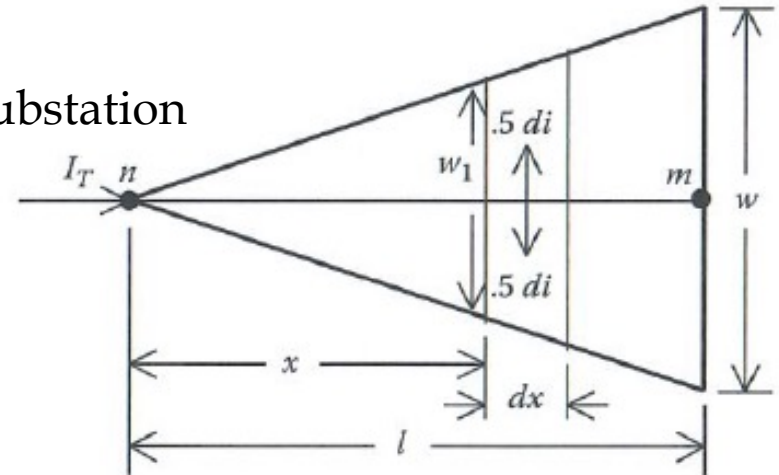

[Kersting]



- $K$  factors can be combined with formulas derived from distributed loads

**Example:** Find voltage drop in triangular area and placement of a 1,800 kVAR capacitor to bring voltage within 3%

$\ell = 15,000 \text{ ft}; w = 6,000 \text{ ft}; D = 3500 \text{ kVA/mile}^2; \text{PF} = 0.9$

$K_{\text{drop}} = 0.00035291 \frac{\Delta V [\%]}{\text{kVA} \cdot \text{mile}}; K_{\text{rise}} = 0.00040331 \frac{\Delta V [\%]}{\text{kVAR} \cdot \text{mile}}$


# Why rectangular and triangle areas?

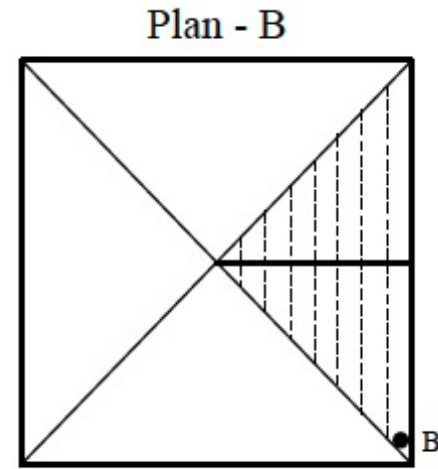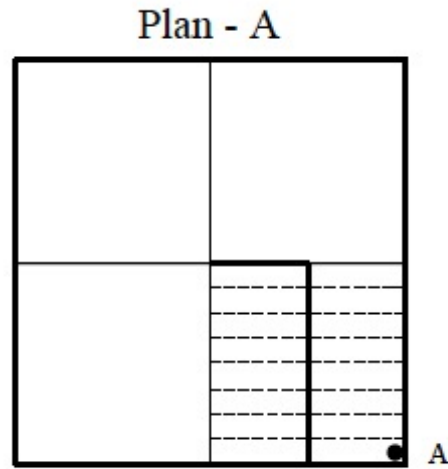

[Kersting]



# Trapezoidal area

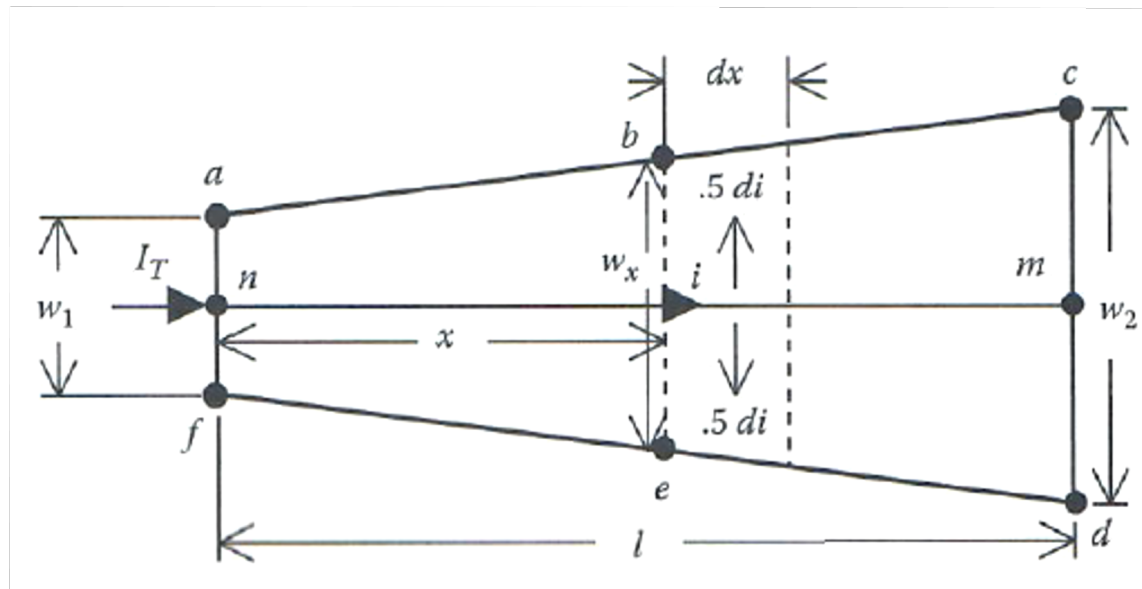

[Kersting]

*Voltage drop*

$$\Delta V = \operatorname{Re} \{ Z I \} \frac{w_1 + 2w_2}{3(w_1 + w_2)}$$

*Power losses*

$$P_\ell = 3R|I|^2 \frac{8w_2^2 + 9w_1w_2 + 3w_1^2}{15(w_1 + w_2)^2}$$

- Square area as special case  $w_1 = w_2 = w$
- Triangular area as special case  $w_1 = 0; w_2 = w$

# Area coverage principle

$$\Delta V = \beta \cdot \text{Re} \{ ZI \} \Rightarrow \frac{\Delta V}{V_{LN}} = \text{Re} \left\{ \frac{\beta z l S^*}{V_{LL}^2} \right\} = \text{Re} \left\{ \frac{\beta z l D A e^{-j\theta}}{V_{LL}^2} \right\}$$

depends on geometry (square, triangle, trapezoid)

- For the same line, geometry, and power factor  $\frac{\Delta V}{V_{LN}} \propto \frac{\ell D A}{V_{LL}^2}$
- Assume constant load density  $D$
- For the same % voltage drop, service area can change as

$$\left. \begin{array}{l} \ell' = \alpha \ell \\ w' = \alpha w \end{array} \right\} \Rightarrow A' = \alpha^2 A \quad \text{where} \quad \alpha = \left( \frac{V'_{LN}}{V_{LN}} \right)^{2/3}$$



$$\begin{aligned} \Delta V &= 3\%, V_{LN} = 1 \\ \ell &= 2, w = 0.5, A = 1 \end{aligned}$$



$$\begin{aligned} \alpha &= 2^{2/3} = 1.587 \\ \alpha^2 &= 2^{4/3} = 2.52 \end{aligned}$$



$$\begin{aligned} \Delta V &= 3\%, V_{LN} = 2 \\ \ell &= 3.17, w = 0.79, A = 2.52 \end{aligned}$$

# Summary

- Approximated voltage drop as  $|V_1| - |V_2| \simeq \text{Re}\{ZI_{12}\}$
- Introduced  $K_{drop}/K_{rise}$  for fast calculations of voltage drops
- Replaced uniformly distributed loads with discrete loads to match losses and/or voltage drop
- Derived formulas for voltage drop and power losses for basic area shapes
- Aforementioned tools are useful for planning/design purposes
  - sizing transformers and capacitors
  - deciding voltage levels
  - assigning customers to feeders