

ECE 5984: Power Distribution System Analysis


## Lecture 6: Distribution Line Models

Reference: Textbook, Chapter 6

*Instructor: V. Kekatos*
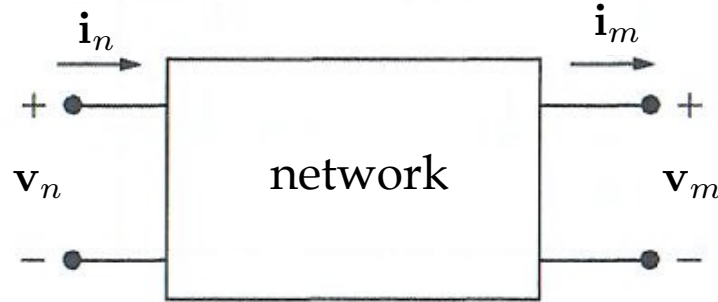
# Outline


- Use line characteristics to obtain a two-port network for distribution lines



- Derive convenient *matrix expressions* for voltages and (line, neutral, ground) currents
- See why expressions are needed in power flow solvers
- Study special cases of transposed and parallel lines
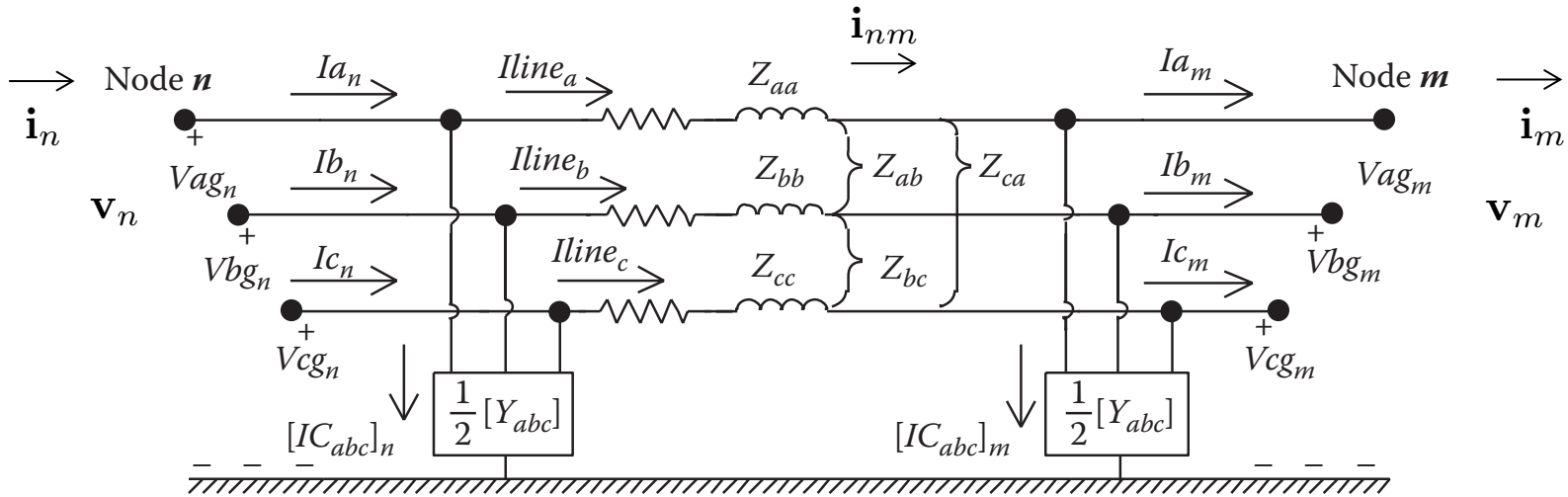
# Multiphase line segment model

- Wave propagation equations to model long, medium, and short lines



KCL at receiving node:

$$\mathbf{i}_{nm} = \mathbf{i}_m + \frac{1}{2} \mathbf{Y}_{nm} \mathbf{v}_m \quad (1)$$

Ohm's law:

$$\mathbf{v}_n - \mathbf{v}_m = \mathbf{Z}_{nm} \mathbf{i}_{nm} \quad (2)$$

KCL at sending node:


$$\mathbf{i}_n = \frac{1}{2} \mathbf{Y}_{nm} \mathbf{v}_n + \mathbf{i}_{nm} \quad (3)$$

- We will express the line as a two-port network
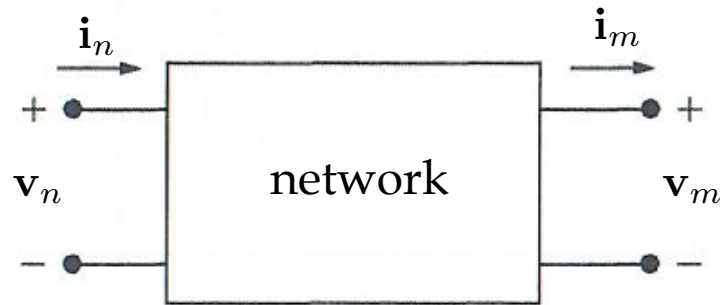
# Two-port network

- Plug (1) in (2) to get  $\mathbf{v}_n = (\mathbf{I} + \frac{1}{2}\mathbf{ZY}) \mathbf{v}_m + \mathbf{Z}\mathbf{i}_m$  (4)

- Plug (2) and (4) in (3)  $\mathbf{i}_n = \mathbf{Y} (\mathbf{I} + \frac{1}{4}\mathbf{ZY}) \mathbf{v}_m + (\mathbf{I} + \frac{1}{2}\mathbf{YZ}) \mathbf{i}_m$  (5)



- Matrix generalization of the transmission line model

$$\mathbf{v}_n = \mathbf{A}\mathbf{v}_m + \mathbf{B}\mathbf{i}_m$$

$$\mathbf{A} = \mathbf{I} + \frac{1}{2}\mathbf{ZY}$$

$$\mathbf{B} = \mathbf{Z}$$

$$\mathbf{i}_n = \mathbf{C}\mathbf{v}_m + \mathbf{D}\mathbf{i}_m$$

$$\mathbf{C} = \mathbf{Y} (\mathbf{I} + \frac{1}{4}\mathbf{ZY})$$


$$\mathbf{D} = \mathbf{I} + \frac{1}{2}\mathbf{YZ} = \mathbf{A}^\top$$

*typo in (6.15):*  $\mathbf{D} \neq \mathbf{I} + \frac{1}{2}\mathbf{ZY}$
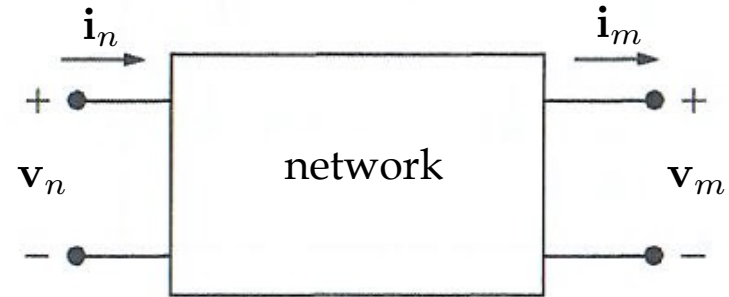
# Reversing network sides

- Previous model expresses sending side in terms of receiving side

$$\begin{bmatrix} \mathbf{v}_n \\ \mathbf{i}_n \end{bmatrix} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{v}_m \\ \mathbf{i}_m \end{bmatrix}$$



- Express receiving side in terms of sending side

$$\begin{bmatrix} \mathbf{v}_m \\ \mathbf{i}_m \end{bmatrix} = \begin{bmatrix} \mathbf{A} & -\mathbf{B} \\ -\mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{v}_n \\ \mathbf{i}_n \end{bmatrix}$$

*argument and formula in (6.21)-(6.22) are not correct*

- Show it either through matrix inversion or exploit circuit symmetry

# Additional line matrices

- Express receiving voltage in terms of its current and sending voltage

$$\mathbf{v}_m = \mathbf{E}\mathbf{v}_n - \mathbf{F}\mathbf{i}_m \quad \text{where} \quad \mathbf{E} := \mathbf{A}^{-1}, \mathbf{F} := \mathbf{A}^{-1}\mathbf{B}$$

follows from top block of ABCD model

- Similar to the expression used in *transmission systems*  $\mathbf{Y}_{\text{series}} := \mathbf{Z}_{\text{series}}^{-1}$

$$\mathbf{i}_n = \left( \mathbf{Y}_{\text{series}} + \frac{1}{2} \mathbf{Y}_{\text{shunt}} \right) \mathbf{v}_n - \mathbf{Y}_{\text{series}} \mathbf{v}_m \quad \text{if you want to build the } Y\text{-bus matrix}$$

- Neutral currents can be found via the *neutral transformation matrix*

$$\begin{bmatrix} \mathbf{v}_\phi - \mathbf{v}'_\phi \\ \mathbf{v}_n - \mathbf{v}'_n \end{bmatrix} = \begin{bmatrix} \mathbf{Z}_{\phi\phi} & \mathbf{Z}_{\phi n} \\ \mathbf{Z}_{\phi n}^\top & \mathbf{Z}_{nn} \end{bmatrix} \begin{bmatrix} \mathbf{i}_{mn,\phi} \\ \mathbf{i}_{mn,\text{neutral}} \end{bmatrix} \Rightarrow \begin{aligned} \mathbf{i}_{nm,\text{neutral}} &= -\mathbf{Z}_{nn}^{-1} \mathbf{Z}_{\phi n}^\top \mathbf{i}_{nm,\phi} \\ \mathbf{v}_\phi - \mathbf{v}'_\phi &= (\mathbf{Z}_{\phi\phi} - \mathbf{Z}_{\phi n} \mathbf{Z}_{nn}^{-1} \mathbf{Z}_{\phi n}^\top) \mathbf{i}_\phi \end{aligned}$$

*phase impedance matrix*

- Ground current  $i_{nm,g} = -\mathbf{1}^\top \mathbf{i}_{nm,\text{neutral}} - \mathbf{1}^\top \mathbf{i}_{nm,\phi}$

# Example

An untransposed distribution line with the given matrices connects unbalanced load to a balanced three-phase 12.47 kV source.

Given sending currents, find receiving voltages, complex load, neutral and ground current.

$$\mathbf{Z}_\phi = \begin{bmatrix} 0.8667 + j2.0417 & 0.2955 + j0.9502 & 0.2907 + j0.7290 \\ 0.2955 + j0.9502 & 0.8837 + j1.9852 & 0.2992 + j0.8023 \\ 0.2907 + j0.7290 & 0.2992 + j0.8023 & 0.8741 + j2.0172 \end{bmatrix} \Omega$$

$$\mathbf{Y}_{\text{sh},\phi} = \begin{bmatrix} j10.7409 & -j3.4777 & -j1.3322 \\ -j3.4777 & j11.3208 & -j2.2140 \\ -j1.3322 & -j2.2140 & j10.2104 \end{bmatrix} \mu\text{S}$$

$$\mathbf{v}_n = \begin{bmatrix} 7199.56 / 0 \\ 7199.56 / -120 \\ 7199.56 / 120 \end{bmatrix} \text{V} \quad \mathbf{i}_n = \begin{bmatrix} 249.97 / -24.5 \\ 277.56 / -145.8 \\ 305.54 / 95.2 \end{bmatrix} \text{A}$$

*balanced source*

# Modified line model


- Modulo long rural lines or underground cables, shunt admittance can be ignored

$$\begin{bmatrix} \mathbf{v}_n \\ \mathbf{i}_n \end{bmatrix} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{v}_m \\ \mathbf{i}_m \end{bmatrix} \quad \longrightarrow \quad \begin{aligned} \mathbf{v}_n - \mathbf{v}_m &= \mathbf{Z}\mathbf{i}_m \\ \mathbf{i}_n &= \mathbf{i}_m \end{aligned}$$

$$\begin{aligned} \mathbf{A} &= \mathbf{I} + \frac{1}{2}\mathbf{Z}\mathbf{Y} \simeq \mathbf{I} & \mathbf{B} &= \mathbf{Z} \\ \mathbf{C} &= \mathbf{Y} \left( \mathbf{I} + \frac{1}{4}\mathbf{Z}\mathbf{Y} \right) \simeq \mathbf{0} & \mathbf{D} &= \mathbf{I} + \frac{1}{2}\mathbf{Y}\mathbf{Z} \simeq \mathbf{I} \end{aligned}$$

- Relating receiving voltage to its current and sending voltage
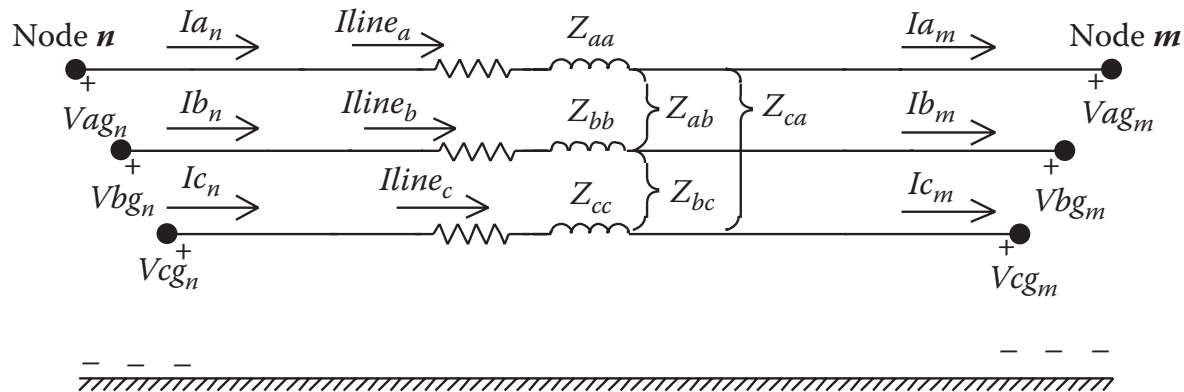
$$\mathbf{v}_m = \mathbf{v}_n - \mathbf{Z}\mathbf{i}_m$$



- Vectorized form of *short* transmission line model



## Example (cont'd)

- Receiving voltage  $\mathbf{v}_m = \mathbf{v}_n - \mathbf{Z}\mathbf{i}_m = \begin{bmatrix} 6942.53 / -1.47 \\ 6918.35 / -121.55 \\ 6887.71 / 117.31 \end{bmatrix} \text{ V}$  *unbalanced!*

- Receiving voltage would be **unbalanced** even if load were balanced! [why?]

- ANSI/NEMA standards for unbalance

$$V_{\text{unbalance}} = \frac{\text{max deviation from average magnitude}}{\text{average magnitude}} \cdot 100\%$$

- Example

$$|V_{\text{average}}| = \frac{6942.53 + 6918.35 + 6887.71}{3} = 6916.20 \text{ V}$$

$$V_{\text{deviation}_{\text{max}}} = |6887.71 - 6916.20| = 28.49$$

$$V_{\text{unbalance}} = \frac{28.49}{6916.20} \cdot 100 = 0.4119\%$$

*imbalance should be lower than 1% for an induction motor*

## Example (cont'd)

- Complex load 
$$\begin{bmatrix} S_a \\ S_b \\ S_c \end{bmatrix} = \begin{bmatrix} V_{ag} \cdot I_a^* \\ V_{bg} \cdot I_b^* \\ V_{cg} \cdot I_c^* \end{bmatrix} = \begin{bmatrix} 1597.2 + j678.8 \\ 1750.8 + j788.7 \\ 1949.7 + j792.0 \end{bmatrix} \text{ kVA}$$

- Neutral transformation matrix

$$-\frac{1}{z_{nn}} \mathbf{z}_{\phi n}^\top = [-0.4292 - j0.1291 \quad -0.4476 - j0.1373 \quad -0.4373 - j0.1327]$$

- Neutral current 
$$i_{n,\text{neutral}} = -\frac{1}{z_{nn}} \mathbf{z}_{\phi n}^\top \mathbf{i}_\phi = \underline{26.2 / -29.5} \text{ A}$$

- Ground current 
$$I_g = -(I_a + I_b + I_c + I_n) = \underline{32.5 / -77.6} \text{ A}$$

# Transposed lines


- Line model (ignoring shunt)  $\mathbf{Z}_\phi = \begin{bmatrix} z_s & z_m & z_m \\ z_m & z_s & z_m \\ z_m & z_m & z_s \end{bmatrix} = (z_s - z_m)\mathbf{I}_3 + z_m\mathbf{1}\mathbf{1}^\top$

- Voltage drop  $\mathbf{v}_n - \mathbf{v}_m = (z_s - z_m)\mathbf{i} + z_m\mathbf{1}(\mathbf{1}^\top \mathbf{i})$

- Relation between sequence and (off)diagonal phase impedances

$$\mathbf{Z}_s = \begin{bmatrix} z_0 & 0 & 0 \\ 0 & z_+ & 0 \\ 0 & 0 & z_+ \end{bmatrix}$$

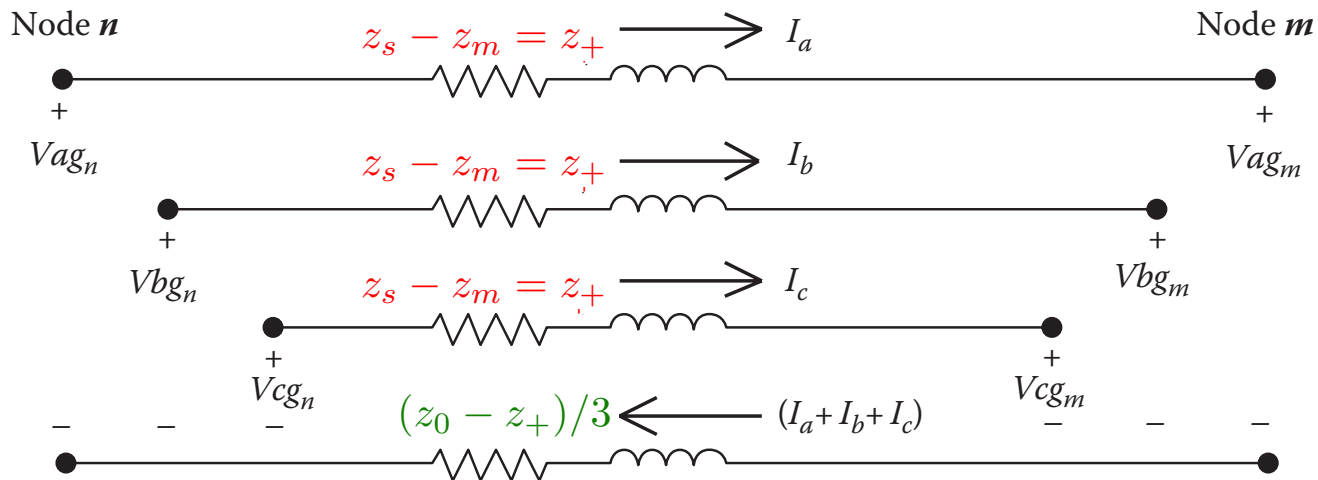(Note: In the original image,  $z_0$  is circled in blue, and  $z_+$  is circled in red. The matrix elements are  $z_s + 2z_m$ ,  $z_s - z_m$ , and  $z_s - z_m$ .)



- Apply KVL to see equivalence of circuit
- What if phase currents are balanced?

# Three-wire Delta lines


- Need to express voltage drop in LL voltages and line currents
- Use 'equivalent' LN voltages so equations derived so far can be used

$$\text{LL voltages } \tilde{\mathbf{v}} = \begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} \quad \text{LN voltages } \mathbf{v} = \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

- LN-to-LL conversion  $\tilde{\mathbf{v}} = \mathbf{D}_f \mathbf{v}$ ,  $\mathbf{D}_f = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix}$


e.g.,  $V_{ab} = V_{an} - V_{bn}$
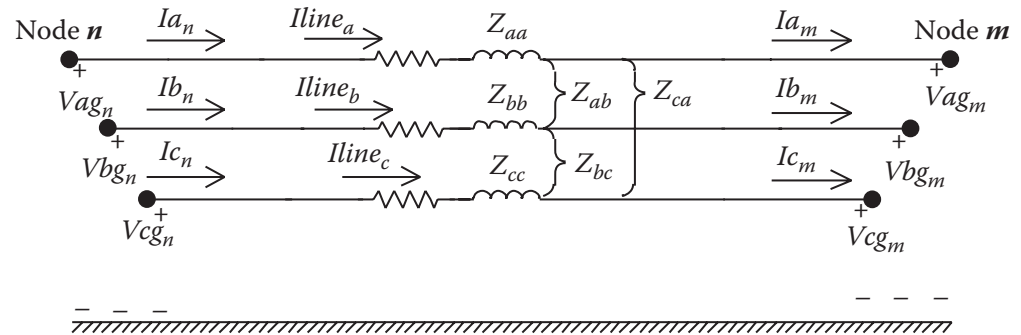
$$\begin{aligned} \tilde{\mathbf{v}}_n - \tilde{\mathbf{v}}_m &= \mathbf{D}_f (\mathbf{v}_n - \mathbf{v}_m) \\ &= \mathbf{D}_f \mathbf{Z}_\phi \mathbf{i}_{\text{line}} \end{aligned}$$



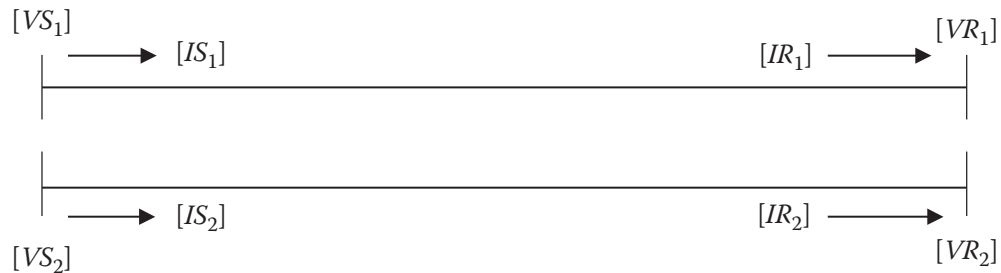
# Parallel lines


- Two-port network model holds for coupled impedance matrices
- Three scenarios can be identified



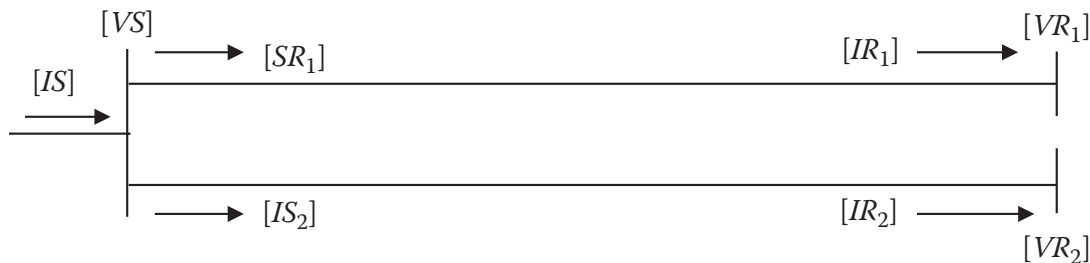*lines sharing no end  
(physically parallel)*



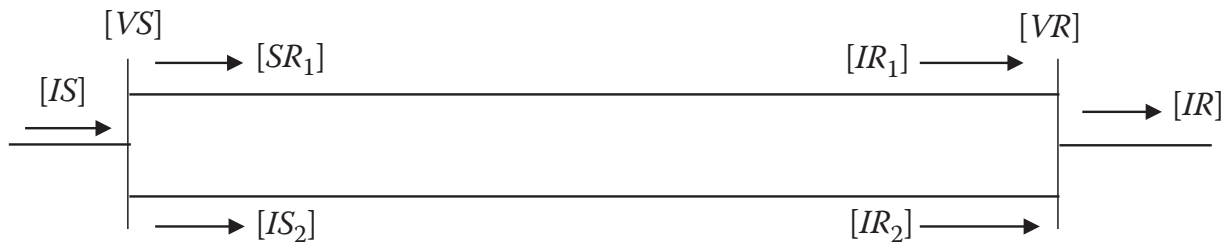*lines sharing one end  
(physically parallel)*




*lines sharing both ends  
(electrically parallel)*
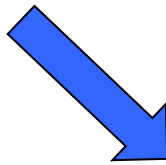
# Lines sharing no end



- Except for having vectors of double dimensions, no other difference

$$\begin{bmatrix} \mathbf{v}_n \\ \mathbf{i}_n \end{bmatrix} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{v}_m \\ \mathbf{i}_m \end{bmatrix}$$




$$\begin{bmatrix} \mathbf{v}_{n1} \\ \mathbf{v}_{n2} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_{11} & \mathbf{A}_{12} \\ \mathbf{A}_{12}^\top & \mathbf{A}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{v}_{m1} \\ \mathbf{v}_{m2} \end{bmatrix} + \begin{bmatrix} \mathbf{B}_{11} & \mathbf{B}_{12} \\ \mathbf{B}_{12}^\top & \mathbf{B}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{i}_1 \\ \mathbf{i}_2 \end{bmatrix}$$

# Lines sharing one end



- Sending voltages coincide


$$\begin{bmatrix} \mathbf{v}_m \\ \mathbf{i}_m \end{bmatrix} = \begin{bmatrix} \mathbf{A} & -\mathbf{B} \\ -\mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{v}_n \\ \mathbf{i}_n \end{bmatrix}$$

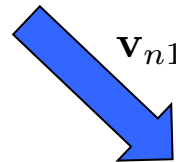
 $\mathbf{v}_{n1} = \mathbf{v}_{n2}$

$$\mathbf{v}_{m1} = (\mathbf{A}_{11} + \mathbf{A}_{12})\mathbf{v}_n - \mathbf{B}_{11}\mathbf{i}_1 - \mathbf{B}_{12}\mathbf{i}_2$$

$$\mathbf{v}_{m2} = (\mathbf{A}_{12}^\top + \mathbf{A}_{22})\mathbf{v}_n - \mathbf{B}_{12}^\top\mathbf{i}_1 - \mathbf{B}_{22}\mathbf{i}_2$$

# Lines sharing both ends

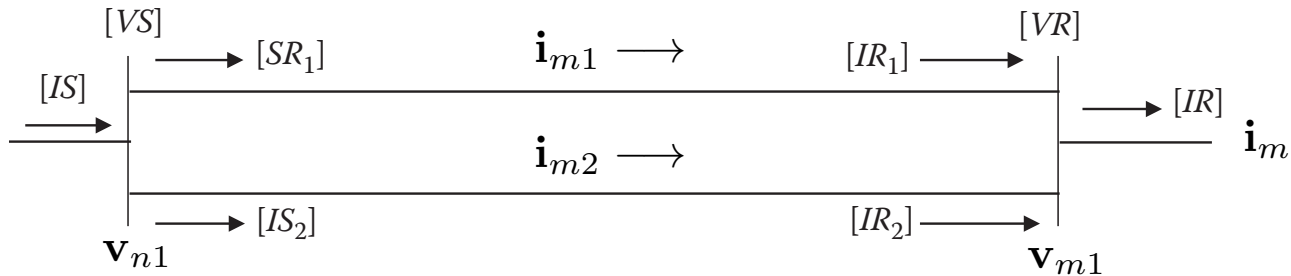

- Sending and receiving voltages coincide
- Given receiving voltage and net current, find per-line currents

$$\begin{bmatrix} \mathbf{v}_n \\ \mathbf{i}_n \end{bmatrix} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{v}_m \\ \mathbf{i}_m \end{bmatrix} \quad \longrightarrow \quad \begin{matrix} \mathbf{v}_{n1} = (\mathbf{A}_{11} + \mathbf{A}_{12})\mathbf{v}_{m1} + \mathbf{B}_{11}\mathbf{i}_{m1} + \mathbf{B}_{12}\mathbf{i}_{m2} \\ \mathbf{v}_{n1} = (\mathbf{A}_{12}^\top + \mathbf{A}_{22})\mathbf{v}_{m1} + \mathbf{B}_{12}^\top\mathbf{i}_{m1} + \mathbf{B}_{22}\mathbf{i}_{m2} \end{matrix}$$

*unknown*

$$\quad \longleftarrow \quad \mathbf{i}_{m2} = \mathbf{i}_m - \mathbf{i}_{m1}$$

$$\mathbf{i}_{m1} = (\mathbf{B}_{12} + \mathbf{B}_{12}^\top - \mathbf{B}_{11} - \mathbf{B}_{22})^{-1} [(\mathbf{A}_{11} + \mathbf{A}_{12} - \mathbf{A}_{12}^\top - \mathbf{A}_{22})\mathbf{v}_{m1} + (\mathbf{B}_{12} - \mathbf{B}_{22})\mathbf{i}_m]$$


- How can you find sending current and voltage?



# Power flow solvers

- Given a feeder and loads, we would like to find the voltages at all buses
- If we know the voltages, we can specify everything else
- Two-port networks relate *linearly* voltages and currents (sending/receiving)
- However, *load currents depend on load voltages* (unless load is an impedance)
- Nonlinear power flow equations are solved by iterative techniques
- *Forward-backward solver*: technique tailored to distribution grids (radial)

# Forward-backward solver

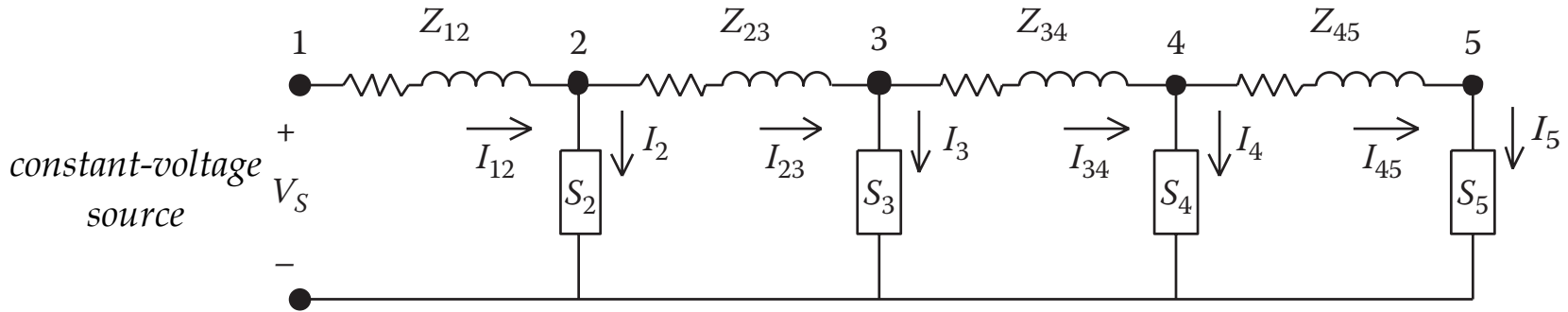

- Toy example on line feeder with constant-power loads
- *Backward sweep* updates currents given voltages

$$I_i^{(t+1)} = \left( \frac{S_i}{V_i^{(t)}} \right)^* \quad \text{[load]}$$

$$I_{i-1,i}^{(t+1)} = I_i^{(t+1)} + I_{i,i+1}^{(t+1)} \quad \text{[line]}$$

*feeder end to feeder head*



- *Forward sweep* updates voltages given currents


$$V_{i+1}^{(t+1)} = V_i^{(t+1)} + Z_{i,i+1} I_{i,i+1}^{(t+1)}$$

*feeder head to feeder end*



- Several iterations needed to converge; initialize voltages at nominal

# Series components

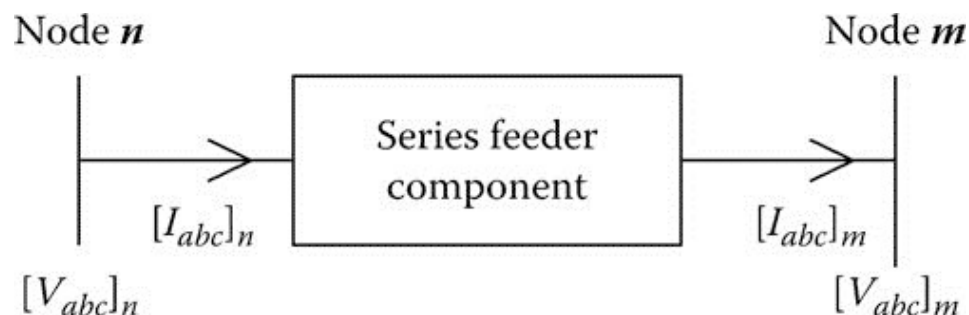


- Distribution lines, voltage regulators (Lecture 8), and transformers (Lecture 9)
- *Backward sweep*  $\mathbf{i}_n^{(t+1)} = \mathbf{C}\mathbf{v}_m^{(t)} + \mathbf{D}\mathbf{i}_m^{(t+1)}$
- *Forward sweep*  $\mathbf{v}_m^{(t+1)} = \mathbf{E}\mathbf{v}_n^{(t+1)} - \mathbf{F}\mathbf{i}_m^{(t+1)}$
- Voltages are *LN* ones
- Matrix  $\mathbf{C} = \mathbf{0}$  except for
  - long underground lines (due to shunt admittance)
  - grounded Wye-Delta transformers

# Shunt components (Lecture 7)

- Spot static loads:  
for ZIP loads, compute currents for each component separately
- Spot induction motors:  
constant-impedance (fixed speed/slip)  
constant-power: compute slip value first
- Capacitor banks:  
constant-impedance loads  
susceptance computed using rated voltage/VAR values
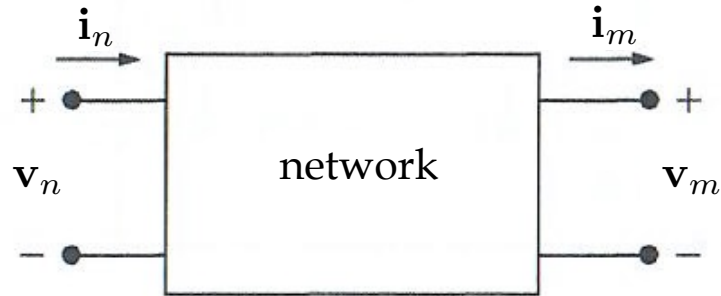
# Summary

- Developed ABCD model for multiphase untransposed distribution lines



- Untransposed lines entail unbalanced currents even for balanced loads
- Model simplifies except for long rural or underground lines
- Studied the special cases of transposed and parallel lines
- Explained how the obtained matrices are used in FB solver