

# ECE 5984: Power Distribution System Analysis

## Lecture 7: Load Models

Reference: Textbook, Chapter 9

*Instructor: V. Kekatos*

# Outline

## *Approximate power flow analysis of Chapter 2*

- Each loads described as a kVA/PF or kW/kVAR duplet
- Given feeder voltage, find voltages at all buses
- Found currents from complex power and assuming nominal voltage at load


## *Load models for detailed power flow analysis*

- Wye or delta-connected loads
- Multiple-phase (V- or 1-phase as special cases)
- Power-voltage relationship (ZIP model) and combinations
- Static or dynamic loads (induction motor loads)
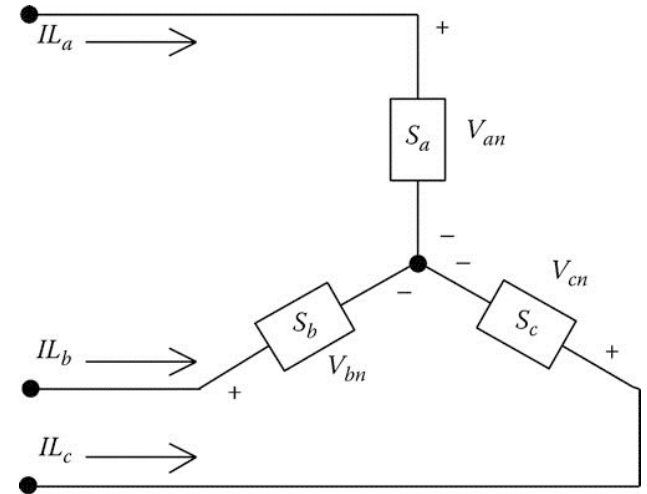
# Constant-power loads

- Common in power flow analysis
- *Given*: complex three-phase power  $\{s_\phi^0\}_\phi$
- *Backward sweep*: given voltages, update current

$$i_\phi = \left( \frac{s_\phi^0}{v_\phi} \right)^* \quad \forall \phi \quad \implies \quad \mathbf{i} = \text{dg}^{-1}(\mathbf{v}^*)(\mathbf{s}^0)^*$$



- *Forward sweep*: given substation voltage and currents, update voltages downstream
- Complex power remains constant at all  $\mathbf{v}$ :  $s_\phi(v_\phi) = s_\phi^0, \quad \forall \phi$
- Single-/two-phase loads modeled by setting missing currents to zero

# Constant-impedance loads

- *Given:* complex rated three-phase power at rated voltage  $|v_\phi^{\text{rated}}|$
- Constant per-phase *impedance* found once as

$$z_\phi^0 = \frac{|v_\phi^{\text{rated}}|^2}{(s_\phi^{\text{rated}})^*}$$

- *Backward sweep:* given voltage, update current as


$$i_\phi = \frac{v_\phi}{z_\phi^0} \quad \forall \phi \quad \Longrightarrow \quad \mathbf{i} = \text{dg}^{-1}(\mathbf{z}^0)\mathbf{v}$$

- Propagate currents upstream; update voltages downstream; and iterate

- Complex power  $s_\phi(v_\phi) = v_\phi i_\phi^* = \frac{|v_\phi|^2}{(z_\phi^0)^*} \quad \forall \phi$

magnitude (apparent power) depends *quadratically* on  $|v_\phi|$


power factor remains *constant*

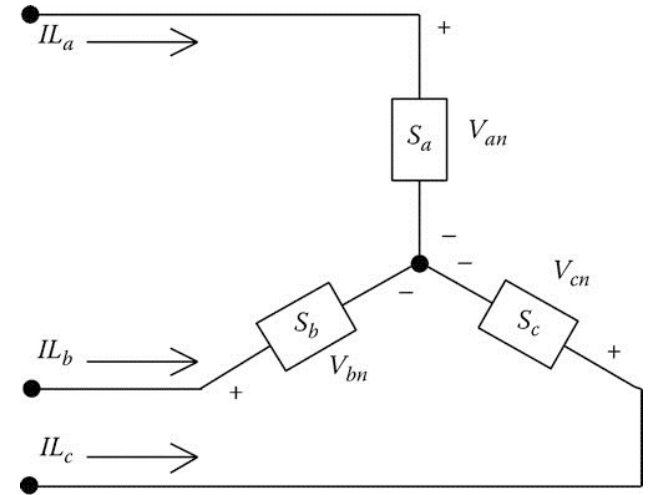


# Constant-current loads

- *Given:* complex rated three-phase power at rated voltage  $|v_\phi^{\text{rated}}|$


- Constant per-phase *current* found once as
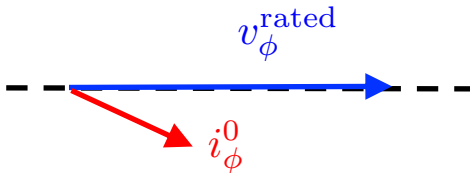
$$i_\phi^0 = \frac{(s_\phi^{\text{rated}})^*}{|v_\phi^{\text{rated}}|}$$

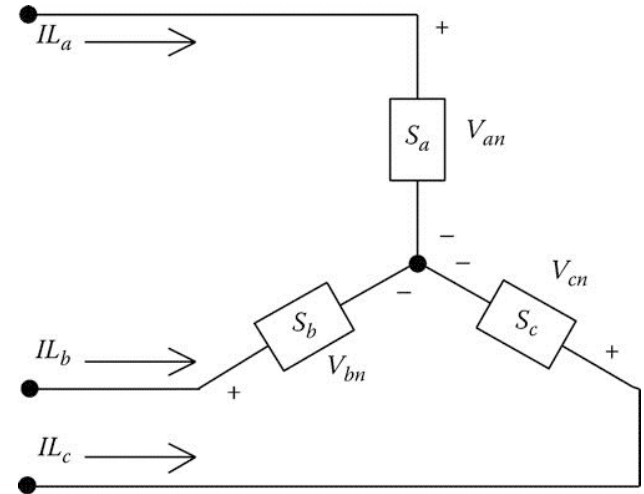


- *Backward sweep:* given voltage  $v_\phi = |v_\phi|e^{j\theta_\phi}$ , update current

$$i_\phi = i_\phi^0 e^{j\theta_\phi} = i_\phi^0 \frac{v_\phi}{|v_\phi|} \quad \forall \phi$$

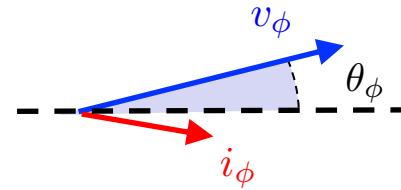


- Propagate currents upstream; update voltages downstream; and iterate
- Complex power  $s_\phi(v_\phi) = |v_\phi| \cdot (i_\phi^0)^* \quad \forall \phi$

magnitude (apparent power) depends *linearly* on  $|v_\phi|$

power factor remains *constant*
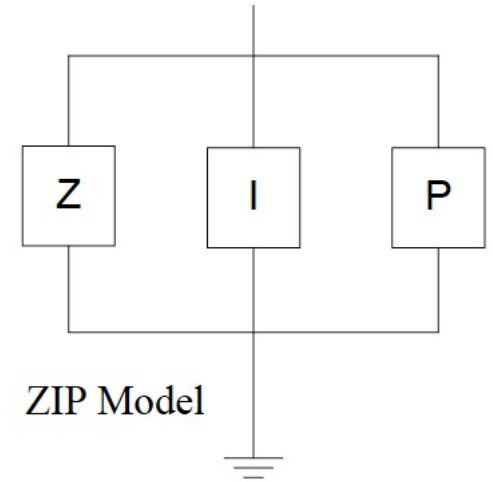
# ZIP model

- Loads typically described as combination of 3 types
- To specify a ZIP load:
  - complex three-phase power  $\{s_\phi\}$
  - percentages for either two or all three of the load types (Z%, I%, P%)
  - percentages refer to *complex power at nominal voltage*
- Line current will be updated as the sum of the three respective currents
- Constant load types are special cases (100% Z, I, or P)
- ZIP is a time-invariant model; recent research on time-variant loads (*water heaters, HVAC, buildings*)



[Kevin Schneider, PNNL]

# Example of ZIP load

Combination load with rated complex power

$$\mathbf{s} = \begin{bmatrix} 1.9 + j1.2 \\ 2.3 + j0.8 \\ 1.8 + j0.8 \end{bmatrix} \text{ MVA at } V_{LL} = 12.47 \text{ kV and } Z : 20\%; I : 30\%; P : 50\%$$

- Constant-impedance component  $\mathbf{s}_Z^{\text{rated}} = 0.2\mathbf{s} \implies z_\phi^0 = \frac{7,200^2}{(s_{Z,\phi}^{\text{rated}})^*}$
- Constant-current component  $\mathbf{s}_I^{\text{rated}} = 0.3\mathbf{s} \implies i_\phi^0 = \frac{(s_{I,\phi}^{\text{rated}})^*}{7,200}$
- Constant-power component  $\mathbf{s}_P^0 = 0.5\mathbf{s}$
- Once constants have been calculated, currents are iteratively updated as

$$\begin{aligned} i_\phi(v_\phi^t) &= i_{Z,\phi}(v_\phi^t) + i_{I,\phi}(v_\phi^t) + i_{P,\phi}(v_\phi^t) \\ &= \frac{v_\phi^t}{z_\phi^0} + \frac{v_\phi^t}{|v_\phi^t|} i_\phi^0 + \left( \frac{s_\phi^0}{v_\phi^t} \right)^* \end{aligned}$$

- Currents are propagated upstream; voltages are updated downstream

# Voltage conversions (LN to LL)


- LN voltages  $\mathbf{v} = \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$       LL voltages  $\tilde{\mathbf{v}} = \begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix}$

- LN-to-LL conversion  $\tilde{\mathbf{v}} = \mathbf{D}_f \mathbf{v}$  where  $\mathbf{D}_f = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix}$  *singular matrix!*

- Difference* matrix  $\mathbf{D}_f$  not to be confused with matrix  $\mathbf{D}$  in ABCD models

- LL voltages are zero-sum  $\mathbf{1}^\top \tilde{\mathbf{v}} = V_{ab} + V_{bc} + V_{ca} = 0$  *even for unbalanced conditions*

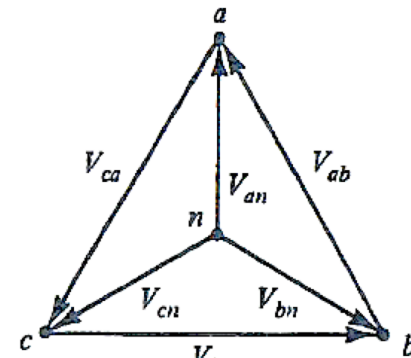- Usual conversion  $\tilde{\mathbf{v}} = \sqrt{3}e^{j\pi/6}\mathbf{v}$  holds only for balanced voltages





# Voltage conversions (LL to LN)

- Without extra info, LN voltages cannot be uniquely recovered from LL voltages

$$\tilde{\mathbf{v}} = \mathbf{D}_f \mathbf{v} \quad \text{where} \quad \mathbf{D}_f = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix} \quad \textit{singular matrix!}$$

- For example, if  $\tilde{\mathbf{v}} = \mathbf{D}_f \mathbf{v} \Rightarrow \tilde{\mathbf{v}} = \mathbf{D}_f (\mathbf{v} + \beta \mathbf{1}) \quad \forall \beta \in \mathbb{C}$
- We can recover a set of 'equivalent' LN voltages by adding the extra info that they are zero sum  $\mathbf{1}^\top \mathbf{v} = 0$

$$\tilde{\mathbf{v}} = \mathbf{D}_f \mathbf{v} = \mathbf{D}_f \mathbf{v} + \frac{1}{3} \mathbf{1} \mathbf{1}^\top \mathbf{v} = \left( \mathbf{D}_f + \frac{1}{3} \mathbf{1} \mathbf{1}^\top \right) \mathbf{v} \Rightarrow$$
$$\mathbf{v} = \mathbf{W} \tilde{\mathbf{v}} \quad \text{where} \quad \mathbf{W} = \left( \mathbf{D}_f + \frac{1}{3} \mathbf{1} \mathbf{1}^\top \right)^{-1} = \frac{1}{3} \begin{bmatrix} 2 & 1 & 0 \\ 0 & 2 & 1 \\ 1 & 0 & 2 \end{bmatrix}$$

## 'Law of cosines'

- *Goal:* Given  $LL$  voltage magnitudes, find  $LL$  voltage phasors
- Determine their phase angles using the *law of cosines*
- Exploit zero-sum property  $V_{ab} + V_{bc} + V_{ca} = 0$  and use  $V_{ab}$  as reference

$$V_{ab} + V_{bc} + V_{ca} = 0 \Rightarrow$$

$$V_{ab} + V_{bc} = -V_{ca} \Rightarrow$$

$$|V_{ab}|^2 + |V_{bc}|^2 + 2\operatorname{Re}\{V_{ab}V_{bc}^*\} = |V_{ca}|^2 \Rightarrow$$


$$|V_{ab}|^2 + |V_{bc}|^2 + 2|V_{ab}| \cdot |V_{bc}| \cos(\theta_{ab} - \theta_{bc}) = |V_{ca}|^2 \Rightarrow$$

$$|V_{ab}|^2 + |V_{bc}|^2 + 2|V_{ab}| \cdot |V_{bc}| \cos(\theta_{bc}) = |V_{ca}|^2$$
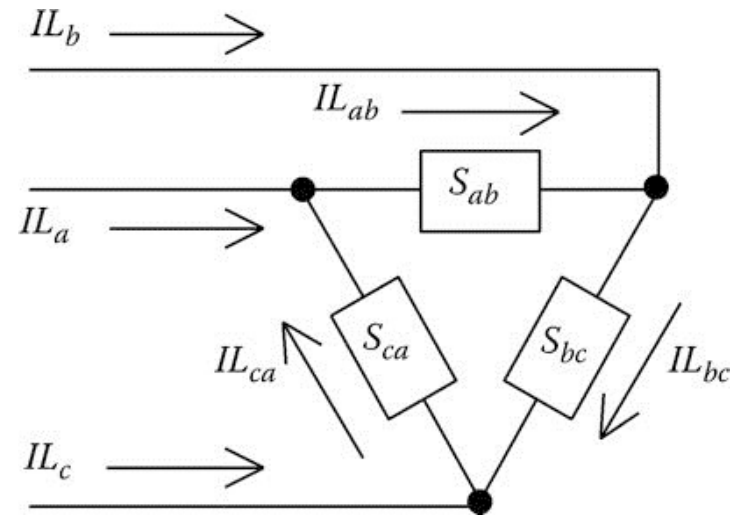
# Delta-connected loads

$$\text{line currents } \mathbf{i} = \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

$$\text{phase (delta) currents } \tilde{\mathbf{i}} = \begin{bmatrix} I_{ab} \\ I_{bc} \\ I_{ca} \end{bmatrix}$$



- We are given voltage and complex power ratings for each delta phase
- Phase (delta) currents are computed as in Y-connection based on ZIP parameters
- Line currents are computed as differences of phase currents

$$\mathbf{i} = \begin{bmatrix} I_{ab} - I_{ca} \\ I_{bc} - I_{ab} \\ I_{ca} - I_{bc} \end{bmatrix} = \begin{bmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \tilde{\mathbf{i}} = \mathbf{D}_f^T \tilde{\mathbf{i}}$$


# Shunt capacitors

- In Ch. 2, capacitors were approximated as constant-current
- To be precise, they are *constant-susceptance* loads
- Calculate susceptance from ratings


$$B_{\phi} = \frac{Q_{\phi}^{\text{rated}}}{|v_{\phi}^{\text{rated}}|^2} \text{ Siemens} > 0$$

- Update line currents as

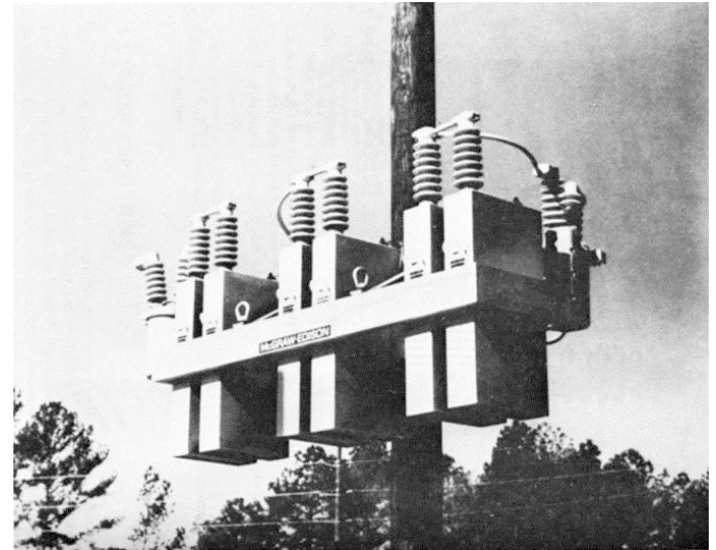
$$i_{\phi} = jB_{\phi}v_{\phi} \quad \forall \phi$$



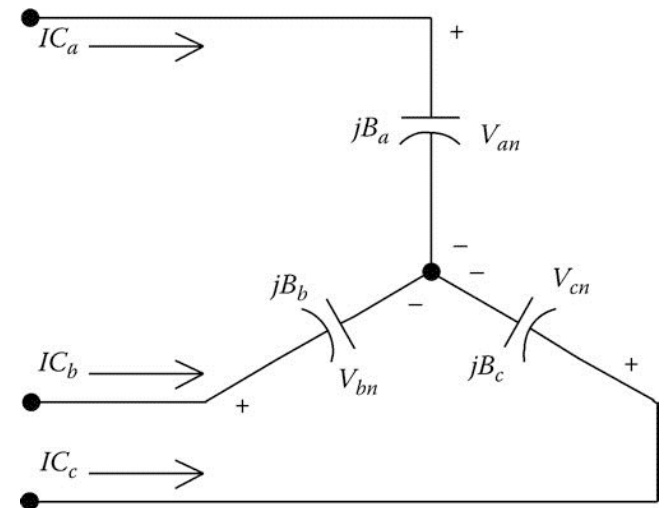capacitors on a switched pole-top rack [Gonen]



# Delta-connected capacitors

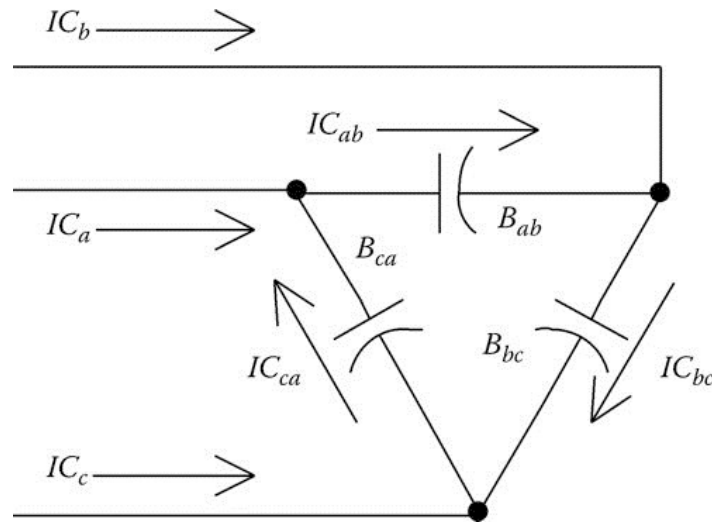


- Phase susceptance  $B_\phi = \frac{Q_\phi^{\text{rated}}}{V_{LL}^2}$  Siemens  $> 0$
- Update phase (delta) currents as  $\tilde{\mathbf{i}} = j\text{dg}(\mathbf{B})\tilde{\mathbf{v}}$
- Update line currents as  $\mathbf{i} = \mathbf{D}_f^\top \tilde{\mathbf{i}}$

# Induction machines under unbalanced conditions

- *Goal*: incorporate induction machines into our power flow analysis
- *Questions* to be answered
  - a) Given terminal (stator) voltages, find currents
  - b) Given stator voltage and current, find rotor voltage/current and losses
  - c) Find the slip that yields a specified value of power
- *Methodology*
  - Step 1*) Use existing sequence model to find a phase impedance model  $\mathbf{v} = \mathbf{Z}\mathbf{i}$
  - Step 2*) Use T-model to propagate voltages/currents from stator to rotor
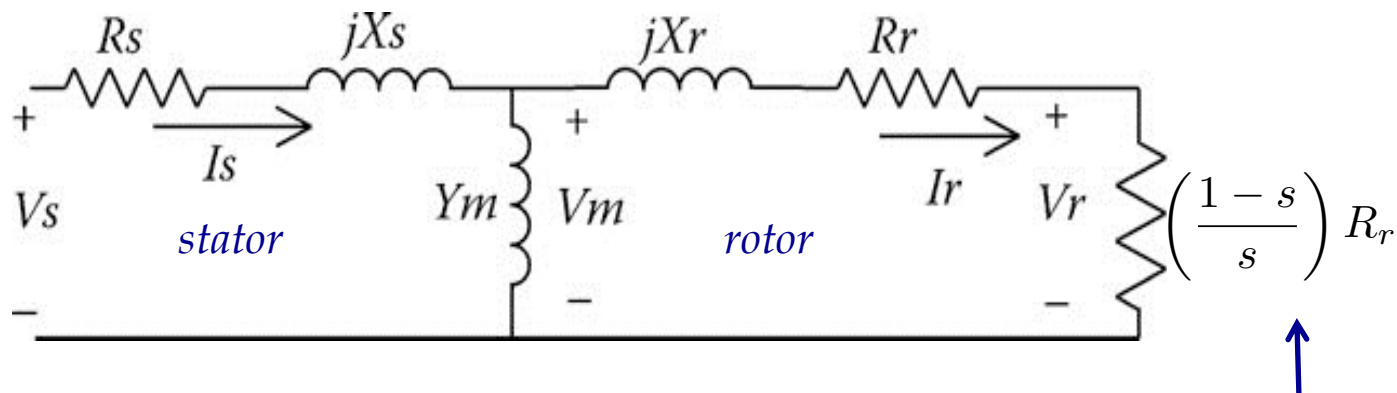
# Induction machine under balanced operation



- Per-phase IM model under balanced conditions

$$n_s = \frac{120f_e}{P} \text{ synchronous speed [rpm]}$$

$f_e$  : electric frequency

$P$  : number of poles

$n_r$  : mechanical (rotor) speed [rpm]


$$s = \frac{n_s - n_r}{n_s}, \quad s \in [0, 1]$$

- Stator windings connected as *ungrounded Wye* or *Delta*

*virtual resistor models power converted from electrical to mechanical*
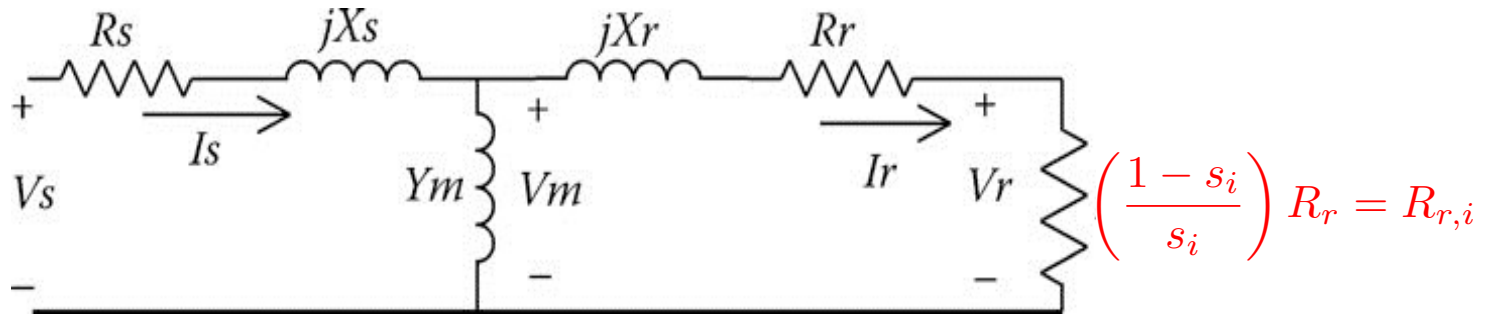
# Sequence-equivalent circuit

- Study unbalanced conditions through sequence domain



- Zero-sequence current and voltage are zero

- Sequence circuits differ only in slip

$$s_1 = s$$

$$s_2 = 2 - s \Rightarrow \left(\frac{1-s_2}{s_2}\right) R_r < 0 \text{ negative!}$$

- Equivalent impedance  $Z_0 = 1$

$$Z_i = Z_s + \frac{(jX_m)(Z_r + R_{r,i})}{jX_m + Z_r + R_{r,i}}, \quad i = 1, 2$$

J. E. Williams, "Operation of 3-phase induction motors on unbalanced voltages," *AIEE Trans. Power App. Syst.*, Apr. 1954.



# Problem setup

- Consider ungrounded Wye, since sequence networks apply for Wye
- If Delta-connected, convert it to ungrounded Wye with  $Z_Y = \frac{Z_\Delta}{3}$
- *Goal:* given **unbalanced**  $LN$  voltages, find line currents; and vice versa
- Line currents are zero-sum
- $LL$  voltages are zero-sum
- $LN$  voltages assumed zero-sum wlog ('equivalent')

## Step 1: phase impedance matrix

- Sequence circuits are decoupled  $\mathbf{i}_s = \mathbf{dg}^{-1}(\mathbf{z})\mathbf{v}_s$  where  $\mathbf{z} := [Z_0 \ Z_1 \ Z_2]^\top$

- Sequence-to-phase transformation

$$\mathbf{i} = \mathbf{A}_s \mathbf{dg}^{-1}(\mathbf{z}) \mathbf{A}_s^{-1} \mathbf{v}$$

voltages used must be zero-sum; not *LG* voltages that may be available

- Phase-frame admittance matrix  $\mathbf{A}_s \mathbf{dg}^{-1}(\mathbf{z}) \mathbf{A}_s^{-1}$  *depends on slip!*

- Relating line currents to *LL* voltages

$$\mathbf{i} = \mathbf{A}_s \mathbf{dg}^{-1}(\mathbf{z}) \mathbf{A}_s^{-1} \mathbf{W} \tilde{\mathbf{v}}$$


- Previous two boxed equations can be inverted

- Per-phase complex power  $\mathbf{s} = \mathbf{dg}(\mathbf{v})\mathbf{i}^*$

- Total power consumed by motor  $S = \mathbf{1}^\top \mathbf{s} = \mathbf{v}^\top \mathbf{i}^*$
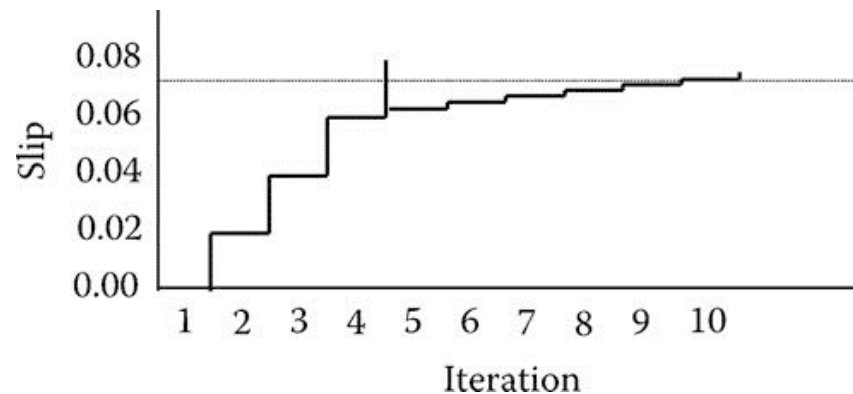
## Step 2: computing the slip


- So far: given input voltage and slip, find line currents to propagate upstream
- Motor has been assumed a *constant-impedance* load depending on given slip
- Usually the input power is specified (*constant-power* load) and the *slip varies*
- Given input voltage, iteratively update slip to match specified power



- Input *active power* is an increasing function of slip (at steady state)
- Use bisection or incremental updates to bring the error in input power to zero
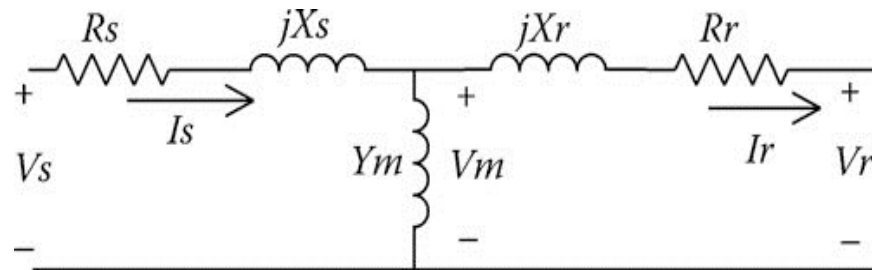
## Step 3: finding rotor voltages/currents

- What if we need to find the internal circuit quantities?



- ABCD model for each sequence circuit

$$\begin{bmatrix} V_s^{\text{st}} \\ I_s^{\text{st}} \end{bmatrix} = \begin{bmatrix} 1 + Z_s Y_m & Z_s + Z_r + Z_s Z_r Y_m \\ Y_m & 1 + Z_r Y_m \end{bmatrix} \begin{bmatrix} V_s^r \\ I_s^r \end{bmatrix}, \quad s = 0, 1, 2$$

- Inverted ABCD model for each sequence circuit

$$\begin{bmatrix} V_s^r \\ I_s^r \end{bmatrix} = \begin{bmatrix} 1 + Z_r Y_m & -(Z_s + Z_r + Z_s Z_r Y_m) \\ -Y_m & 1 + Z_s Y_m \end{bmatrix} \begin{bmatrix} V_s^{\text{st}} \\ I_s^{\text{st}} \end{bmatrix}, \quad s = 0, 1, 2$$

- Sequence circuits are independent; stack together; invert through  $A_s$

$$\begin{bmatrix} \mathbf{v}_s^{\text{st}} \\ \mathbf{i}_s^{\text{st}} \end{bmatrix} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{v}_s^r \\ \mathbf{i}_s^r \end{bmatrix}$$


- Useful to calculate SCL, RCL, converted power, rotor current

# Sequence networks of $T$ model

$$\mathbf{Z}_s = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0.1 + j0.25 & 0 \\ 0 & 0 & 0.1 + j0.25 \end{bmatrix}$$

$$\mathbf{Z}_r = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0.08 + j0.175 & 0 \\ 0 & 0 & 0.08 + j0.175 \end{bmatrix}$$
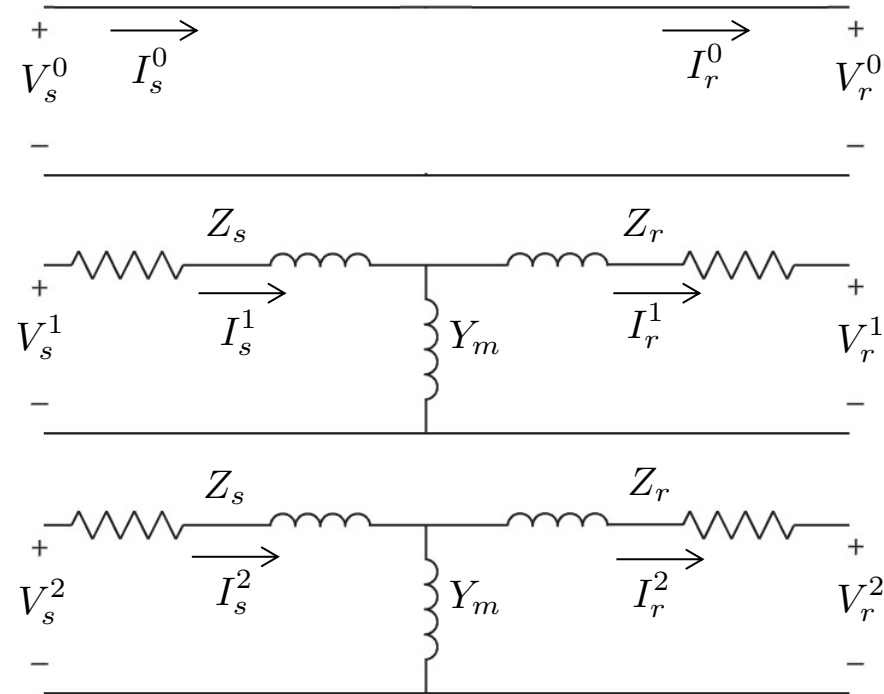
$$\mathbf{Y}_m = \begin{bmatrix} 0 & 0 & 0 \\ 0 & -j0.16 & 0 \\ 0 & 0 & -j0.16 \end{bmatrix}$$



- ABCD model for motor's  $T$  circuit

$$\begin{bmatrix} \mathbf{v}^{\text{st}} \\ \mathbf{i}^{\text{st}} \end{bmatrix} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{v}^r \\ \mathbf{i}^r \end{bmatrix}$$

- Inverse model through matrix inversion or circuit trick
- Zero-sequence can be selected identical to positive sequence to yield identity matrices!

$$\mathbf{A} = \mathbf{I} + \mathbf{A}_s \mathbf{Z}_s \mathbf{Y}_m \mathbf{A}_s^{-1}$$

$$\mathbf{B} = \mathbf{A}_s (\mathbf{Z}_s + \mathbf{Z}_r + \mathbf{Z}_s \mathbf{Y}_m \mathbf{Z}_r) \mathbf{A}_s^{-1}$$

$$\mathbf{C} = \mathbf{A}_s \mathbf{Y}_m \mathbf{A}_s^{-1}$$

$$\mathbf{D} = \mathbf{I} + \mathbf{A}_s \mathbf{Y}_m \mathbf{Z}_r \mathbf{A}_s^{-1}$$

# Summary

- Time-invariant loads through ZIP model
- Induction motor under unbalanced conditions
  - a)* relate stator voltages to currents for a specific slip
  - b)* given stator voltages/currents, find rotor voltages/currents
  - c)* find slip to match power (consumed or generated)
- All models can be readily integrated to Forward-Backward Sweep
- *Not covered*
  - fitting ZIP model parameters
  - time-variant models (water heaters, HVAC, buildings)
  - dynamic modeling (induction machine was assumed in steady-state)