 


**LEARNING OUTCOME #2: “an ability to analyze and design combinational logic circuits.”**


**Multiple Choice – select the single most appropriate response for each question.**

 **Note that “none of the above” MAY be a VALID ANSWER.**

- If the function  $F(X,Y,Z)$  is represented by the **ON SET**  $\sum_{X,Y,Z}(0,3,5,6)$ , then the **complement** of this function  $F'(X,Y,Z)$  is represented by the **ON SET**:
  - $\sum_{X,Y,Z}(0,3,5,6)$
  - $\sum_{X,Y,Z}(1,2,4,7)$
  - $\sum_{X,Y,Z}(1,2,4,6)$
  - $\sum_{X,Y,Z}(1,3,5,7)$
  - none of the above
- If the function  $F(X,Y,Z)$  is represented by the **ON SET**  $\sum_{X,Y,Z}(0,3,5,6)$ , then the **dual** of this function  $F^D(X,Y,Z)$  is represented by the **ON SET**:
  - $\sum_{X,Y,Z}(0,3,5,6)$
  - $\sum_{X,Y,Z}(1,2,4,7)$
  - $\sum_{X,Y,Z}(1,2,4,6)$
  - $\sum_{X,Y,Z}(1,3,5,7)$
  - none of the above
- The **XOR property** listed below that is **NOT** true is:
  - $X \oplus 0 = X$
  - $X \oplus 1 = X'$
  - $X \oplus X = X$
  - $X \oplus X' = 1$
  - none of the above
- A circuit consisting of a level of **NOR gates** followed by a level of **AND gates** is **logically equivalent** to:
  - a multi-input OR gate
  - a multi-input AND gate
  - a multi-input NOR gate
  - a multi-input NAND gate
  - none of the above



- The circuit shown exhibits the **following type of hazard** when its input, X, transitions from **low-to-high**:
  - a static-zero hazard
  - a static-one hazard
  - a dynamic hazard
  - a consensus hazard
  - none of the above



The following K-map applies to questions 6 through 11:

	X'		X	
Z'	0	1	0	0
Z	1	0	d	1
	Y'	Y		Y'

6. The **cost** of a **minimal sum of products** realization of this function (assuming **both true and complemented variables** are available) would be:
 

(A) 10    (B) 11    (C) 12    (D) 13    (E) none of the above
7. The **cost** of a **minimal product of sums** realization of this function (assuming **both true and complemented variables** are available) would be:
 

(A) 10    (B) 11    (C) 12    (D) 13    (E) none of the above
8. Assuming the availability of **only true** input variables, the **fewest number of 2-input NAND gates** that are needed to realize this function is:
 

(A) 5    (B) 6    (C) 7    (D) 8    (E) none of the above
9. Assuming the availability of **only true** input variables, the **fewest number of 2-input NOR gates** that are needed to realize this function is:
 

(A) 5    (B) 6    (C) 7    (D) 8    (E) none of the above
10. Assuming the availability of **only true** input variables, the **fewest number of 2-input open-drain NAND gates** that are needed to realize this function is:
 


(A) 5    (B) 6    (C) 7    (D) 8    (E) none of the above
11. Assuming the availability of **only true** input variables, the **number of pull-up resistors** required to realize this function using **2-input open-drain NAND gates** is:
 

(A) 1    (B) 2    (C) 3    (D) 4    (E) none of the above


The following K-map applies to question 12:

		<b>W'</b>		<b>W</b>		
		<b>0</b>	<b>d</b>	<b>1</b>	<b>0</b>	<b>Z'</b>
<b>Y'</b>		<b>1</b>	<b>0</b>	<b>1</b>	<b>d</b>	<b>Z</b>
<b>Y</b>		<b>d</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>Z</b>
		<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>Z'</b>
		<b>X'</b>	<b>X</b>	<b>X'</b>		

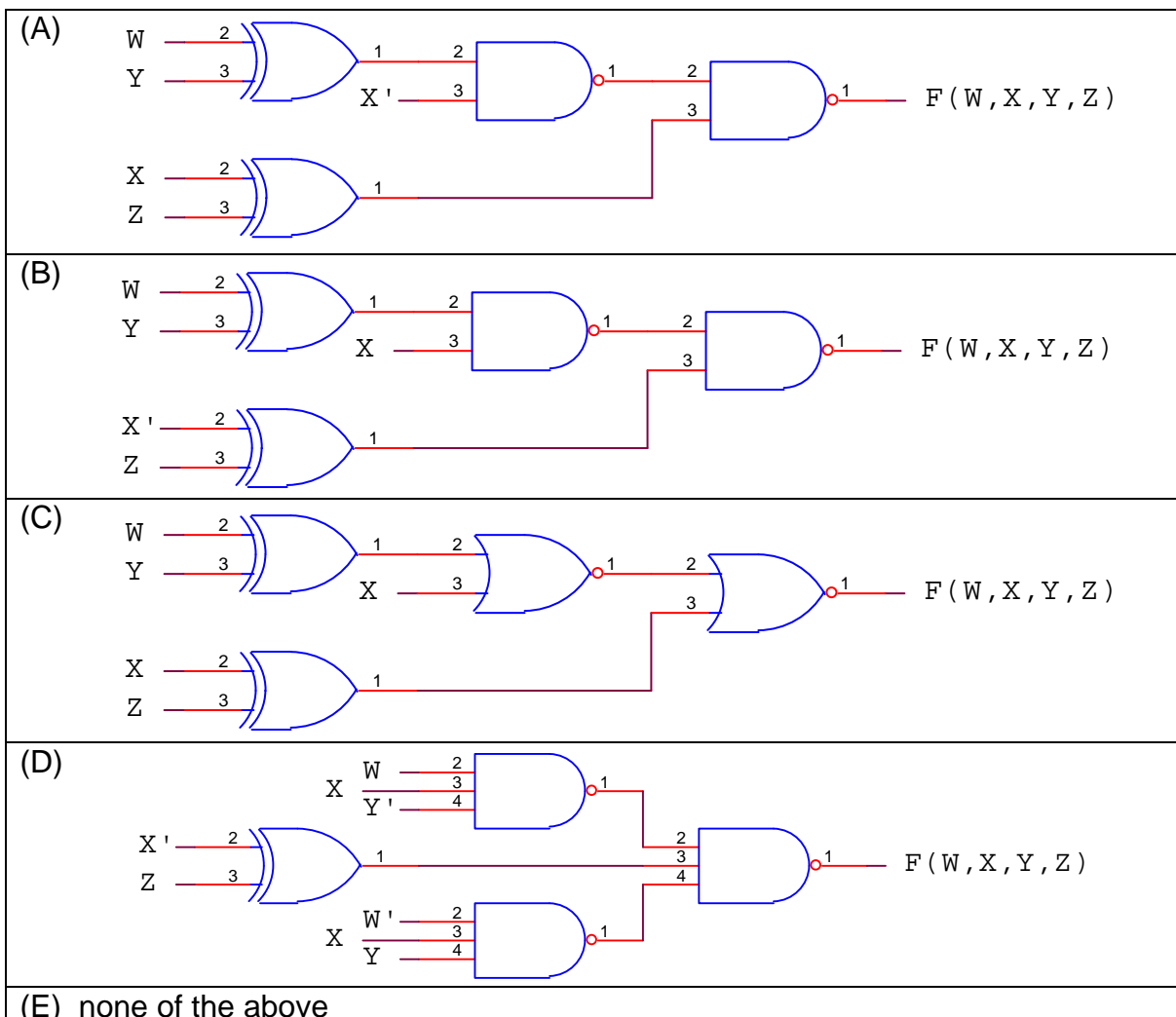12. Assuming the availability of **both true and complemented** variables, the **simplest** (lowest cost) realization of this function is depicted by the following circuit:





 The following circuit applies to questions 13 through 16:



 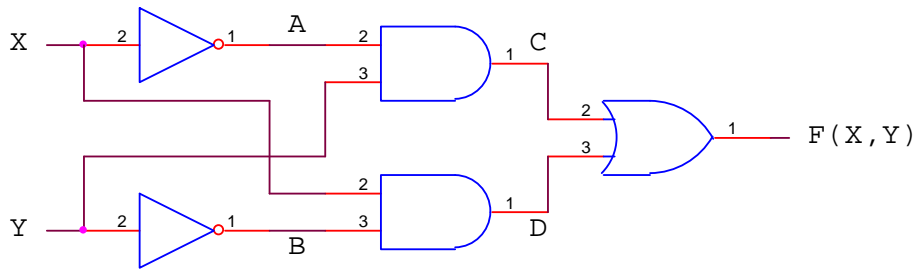13. Expressed in a **minimum sum-of-products** form, the function realized by this circuit is:
- $X \cdot Y + X \cdot Z + X' \cdot Z$
  - $X' \cdot Z' + Y' \cdot Z'$
  - $Y \cdot Z' + Y' \cdot Z' + X' \cdot Y'$
  - $Z + X \cdot Y$
  - none of the above
14. The **ON-SET** of the function realized by this circuit is:
- $\sum_{x,y,z}(0,2,4)$
  - $\sum_{x,y,z}(1,3,5,6,7)$
  - $\sum_{x,y,z}(3,5,7)$
  - $\sum_{x,y,z}(0,1,2,4,6)$
  - none of the above
15. Expressed in a **minimum product-of-sums** form, the function realized by this circuit is:
- $(X+Z) \cdot (Y+Z)$
  - $(X'+Y') \cdot (X+Y) \cdot (Y+Z')$
  - $Z' \cdot (X'+Y')$
  - $(X'+Z') \cdot (Y'+Z')$
  - none of the above
16. Assuming the availability of **only true** variables, realization of this same function using **only 2-input NOR gates** would require:
- two** (2-input NOR) gates
  - three** (2-input NOR) gates
  - four** (2-input NOR) gates
  - five** (2-input NOR) gates
  - none of the above

The following circuit and timing chart apply to questions 17 and 18:



17. Steady-state (static) analysis of the function realized by this circuit predicts that the output  $F(X,Y)$  should:

- (A) always be low
- (B) always be high
- (C) be equal to the input X
- (D) be equal to the input Y
- (E) none of the above

18. The dynamic behavior of the circuit (depicted in the timing chart) does **NOT** match the steady-state analysis of the function because:

- (A) the circuit does not contain a complete sum
- (B) a consensus term needs to be added
- (C) more than one input changes simultaneously
- (D) all of the above
- (E) none of the above

The following excerpt from an **ispLever Reduced Equation Report** applies to questions 19 through 21.

Title: 8-to-3 Priority Encoder				
P-Terms	Fan-in	Fan-out	Type	Name (attributes)
4/4	7	1	Pin	E0
4/3	6	1	Pin	E1
4/1	4	1	Pin	E2
8/1	8	1	Pin	GS
=====				
20/9	Best P-Term Total: 9			
	Total Pins: 12			
	Total Nodes: 0			
	Average P-Term/Output: 2			
Positive-Polarity Equations:				
E0 = (!I6 & !I4 & !I2 & I1 # !I6 & !I4 & I3 # !I6 & I5 # I7);				
E1 = (!I5 & !I4 & I2 # !I5 & !I4 & I3 # I6 # I7);				
E2 = (I4 # I5 # I6 # I7);				
GS = (I1 # I0 # I2 # I3 # I4 # I5 # I6 # I7);				
Reverse-Polarity Equations:				
!E0 = (!I7 & !I5 & !I3 & !I1 # !I7 & !I5 & !I3 & I2 # !I7 & !I5 & I4 # !I7 & I6);				
!E1 = (!I7 & !I6 & !I3 & !I2 # !I7 & !I6 & I4 # !I7 & !I6 & I5);				
!E2 = (!I7 & !I6 & !I5 & !I4);				
!GS = (!I7 & !I6 & !I5 & !I4 & !I3 & !I2 & !I1 & !I0);				

**ispLEVER operators:**  
 AND - &    OR - #  
 NOT - !    XOR - \$

19. The **Best P-Term Total** shown in the report indicates:
- the minimum number of pins needed to implement the logic function
  - the minimum number of macrocells needed to implement the logic function
  - the minimum number of OR gates needed to implement the logic function
  - the minimum number of AND gates needed to implement the logic function
  - none of the above
20. The **number of P-Terms** needed to realize the **!E0** (reverse-polarity) equation is:
- 1
  - 2
  - 4
  - 8
  - none of these
21. The **number of P-Terms** needed to realize the **GS** (positive-polarity) equation is:
- 1
  - 2
  - 4
  - 8
  - none of these

The following Verilog module applies to questions 22 through 24:

```
module diff_pri(A,B,C,D,EN,E0,E1,GS);
  input wire A,B,C,D,EN;
  output wire E0, E1;
  output wire GS;

  reg [2:0] EGS;

  always @ (A,B,C,D) begin
    casez ({A,B,C,D})
      4'b0000: EGS = 3'b000;
      4'b0001: EGS = 3'b111;
      4'b001?: EGS = 3'b101;
      4'b01??: EGS = 3'b011;
      4'b1????: EGS = 3'b001;
    endcase
  end

  assign E1 = EN ? EGS[2]:1'bz;
  assign E0 = EN ? EGS[1]:1'bz;
  assign GS = EGS[0];

endmodule
```

22. The **highest priority input** is:

- (A) A
- (B) B
- (C) C
- (D) D
- (E) none of the above

23. If input **A is asserted** and input **EN is negated**, the outputs will be:

- (A) E1=0, E0=0, GS=0
- (B) E1=0, E0=0, GS=1
- (C) E1=Hi-Z, E0=Hi-Z, GS=1
- (D) E1=Hi-Z, E0=Hi-Z, GS=Hi-Z
- (E) none of the above

24. When inputs **B** and **C** are **asserted simultaneously** (and EN is asserted), the **encoded output** will be:

- (A) 00
- (B) 01
- (C) 10
- (D) 11
- (E) none of the above

The following Verilog module applies to questions 25 through 27:

```
module bigmux(EN,S,A,B,C,D,Y);
  input wire EN;
  input wire [1:0] S;
  input wire [7:0] A,B,C,D;
  output tri [7:0] Y;

  wire [7:0] Ytmp,SEL1,SEL0;

  assign SEL1 = {8{S[1]}};
  assign SEL0 = {8{S[0]}};

  assign Ytmp = (~SEL1 & ~SEL0 & A) | (~SEL1 & SEL0 & B) |
               (SEL1 & ~SEL0 & C) | (SEL1 & SEL0 & D);


  assign Y = EN ? Ytmp : 8'bzzzzzzzz;

endmodule
```

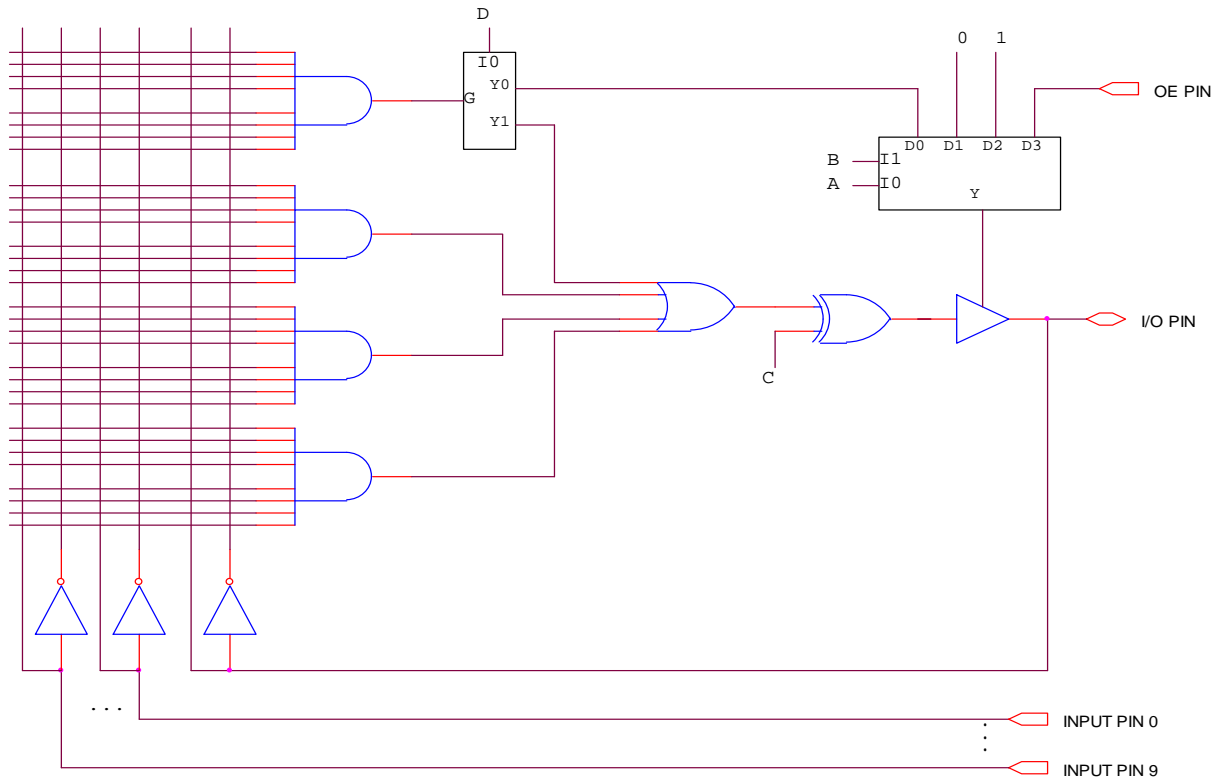25. The **number of equations** generated by this program (that would be burned into a PLD that realized this design) is:
- (A) 2
  - (B) 8
  - (C) 9
  - (D) 16
  - (E) none of the above
26. When **EN=0**, **S1=1**, and **S0=1**, bits 0 through 7 of output **Y** will:
- (A) all be Hi-Z
  - (B) all be zero
  - (C) all be one
  - (D) be equal to bits 0 through 7 of input **D**
  - (E) none of the above
27. When **EN=1**, **S1=1**, and **S0=1**, bits 0 through 7 of output **Y** will:
- (A) all be Hi-Z
  - (B) all be zero
  - (C) all be one
  - (D) be equal to bits 0 through 7 of input **D**
  - (E) none of the above



The **Macrocell Reference Figure** below applies to questions 28 through 30.



28. If  $D=1$ , the **maximum number of product terms** that can be implemented by each macrocell is:  
 (A) 3    (B) 4    (C) 8    (D) 32    (E) none of these
29. To realize the **ON SET** of a function with an **active low** output, the following settings should be used:  
 (A) **C=0, B=0, A=1**  
 (B) **C=0, B=1, A=0**  
 (C) **C=1, B=0, A=1**  
 (D) **C=1, B=1, A=0**  
 (E) none of the above
30. The purpose of setting **B=0** and **A=1** is to:  
 (A) force the macrocell to use the PoS form of the logic equations  
 (B) enable one of the AND gates to be the source for the tri-state output enable  
 (C) make the OE pin the source for the tri-state enable  
 (D) enable the I/O pin to be used as an extra input  
 (E) none of the above