

**LEARNING OUTCOME #2: "an ability to analyze and design combinational logic circuits."**




1. B
2. A
3. C
4. C
5. A
6. A
7. D
8. D
9. E
10. A
11. C
12. B
13. B – see PQ #6
14. A – see PQ #6
15. C – see PQ #6
16. C – see PQ #6
17. B
18. C
19. D
20. C
21. D
22. A
23. C
24. B
25. D
26. A
27. D
28. B
29. D
30. D

K-map for questions 6-11:

	X'	X	
Z'	0	1	0
Z	1	0	1
	Y'	Y	Y'

*non-essential prime implicants - 2 does not matter which one is used -> both yield the same result*  
 $F = X'YZ' + Y'Z$  COST=10

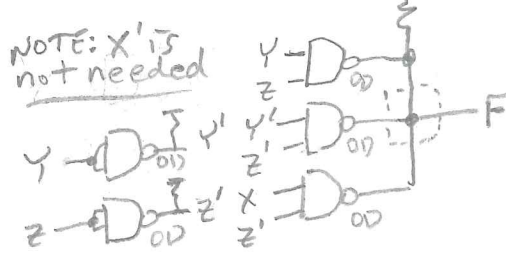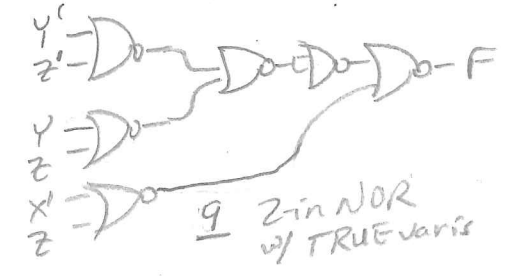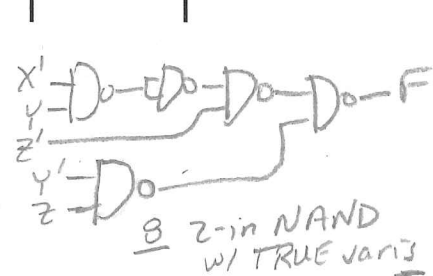$F' = YZ + Y'Z' + XZ'$   
 $\Rightarrow F = (Y'+Z) \cdot (Y+Z) \cdot (X'+Z)$   
 COST=13



K-map for question 12:

	W'	W	
Z'	0	d	1
Z	1	0	1
Y'	d	1	0
Y	0	1	1
	X'	X	X'

$F = XZ' + X'Z + W'XY + WX'Y'$   
 $= (X \oplus Z) + X(W \oplus Y)$

