 


**OUTCOME #2: “an ability to analyze and design combinational logic circuits.”**

**Multiple Choice – select the single most appropriate response for each question. Note that “none of the above” MAY be a VALID ANSWER.**

**Place answers on the supplied BUBBLE SHEET only – nothing written here will be graded.**

- Most **logic minimization methods** are based on a generalization of:
  - the covering theorem
  - the combining theorem
  - the consensus theorem
  - DeMorgan’s Law
  - none of the above
- If the function  $F(X,Y,Z)$  is represented by the **ON set**  $\Sigma_{x,y,z}(0,3,4,7)$ , then the **dual** of this function  $F^D(X,Y,Z)$  is represented by the **ON set**:
  - $\Sigma_{x,y,z}(0,3,4,7)$
  - $\Sigma_{x,y,z}(1,2,4,6)$
  - $\Sigma_{x,y,z}(1,2,5,6)$
  - $\Sigma_{x,y,z}(1,2,4,7)$
  - none of the above
- The **property** listed below that is **NOT** true for **XOR gates** is:
  - Associativity
  - commutivity
  - distributivity
  - idempotency
  - none of the above
- The circuit shown below exhibits the following type of **hazard** when its input, X, transitions from **high-to-low**:
  - a static-0 hazard
  - a static-1 hazard
  - a dynamic low-to-high hazard
  - a dynamic high-to-low hazard
  - none of the above



X																			
A																			
F																			

The following K-map applies to questions 5 through 8:

		$W'$		$W$		
		$1$	$d$	$0$	$1$	$Z'$
$Y'$		$0$	$1$	$1$	$0$	
	$Z$	$0$	$d$	$1$	$0$	
$Y$		$d$	$1$	$0$	$1$	$Z'$
		$X'$	$X$	$X'$		

5. Assuming the availability of **only true** input variables, the **fewest number of 2-input NAND gates** that are needed to realize this function is:
 


(A) 6    (B) 7    (C) 8    (D) 9    (E) none of the above
6. Assuming the availability of **only true** input variables, the **fewest number of 2-input NOR gates** that are needed to realize this function is:
 

(A) 6    (B) 7    (C) 8    (D) 9    (E) none of the above
7. Assuming the availability of **only true** input variables, the **fewest number of 2-input open-drain NAND gates** that are needed to realize this function is:
 

(A) 6    (B) 7    (C) 8    (D) 9    (E) none of the above
8. Assuming the availability of **only true** input variables, the **number of pull-up resistors** required to realize this function using **2-input open-drain NAND gates** is:
 

 
(A) 2    (B) 3    (C) 4    (D) 5    (E) none of the above

The following circuit applies to questions 9 and 10:



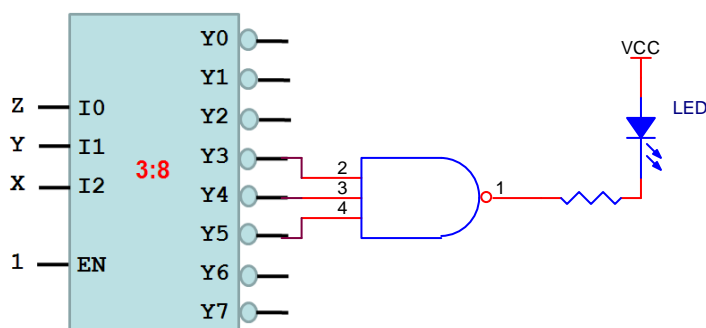
9. The **OFF set** of the function realized by this circuit is:
- (A)  $\Pi_{x,y,z}(3,4)$   
 (B)  $\Pi_{x,y,z}(1,6)$   
 (C)  $\Pi_{x,y,z}(0,2,3,4,5,7)$   
 (D)  $\Pi_{x,y,z}(0,1,2,5,6,7)$   
 (E) none of the above
10. The **cost** of a **minimal product of sums** realization of this function (assuming **both true and complemented variables** are available) would be:
- (A) 10    (B) 11    (C) 12    (D) 13    (E) none of the above

The following circuit applies to question 11:



 11. The **ON set** realized by this circuit, where the LED “on” condition corresponds to  $F(X,Y,Z)=1$ , is:
- (A)  $\Sigma_{x,y,z}(3,4,5)$   
 (B)  $\Sigma_{x,y,z}(0,1,2,6,7)$   
 (C)  $\Sigma_{x,y,z}(0,1,2)$   
 (D)  $\Sigma_{x,y,z}(6,7)$   
 (E) none of the above

The following circuit applies to questions 12 and 13:



12. Expressed in minimum sum-of-products form, the function realized by this circuit is:


- (A)  $W \cdot Y + X \cdot Z$
- (B)  $W' \cdot Y' + X' \cdot Z'$
- (C)  $X \cdot Y + Y \cdot Z + W \cdot Z + W \cdot X$
- (D)  $W' \cdot Y' + X' \cdot Y \cdot Z' + X' \cdot Y' \cdot Z'$
- (E) none of the above

13. Expressed in minimum product-of-sums form, the function realized by this circuit is:


- (A)  $(W+Y) \cdot (X+Z)$
- (B)  $(W'+Y') \cdot (X'+Z')$
- (C)  $(X+Y) \cdot (Y+Z) \cdot (W+Z) \cdot (W+X)$
- (D)  $(X'+Y') \cdot (Y'+Z') \cdot (W'+Z') \cdot (W'+X')$
- (E) none of the above

14. The multiplexer circuit shown realizes the following **OFF set**:

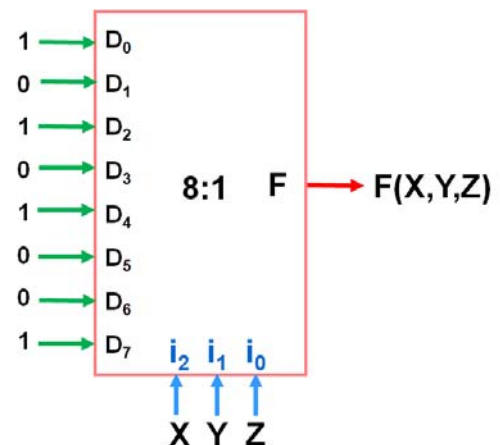- (A)  $\prod_{x,y,z} (0,2,4,7)$
- (B)  $\prod_{x,y,z} (0,1,6,7)$
- (C)  $\prod_{x,y,z} (1,3,4,7)$
- (D)  $\prod_{x,y,z} (1,3,5,6)$
- (E) none of the above



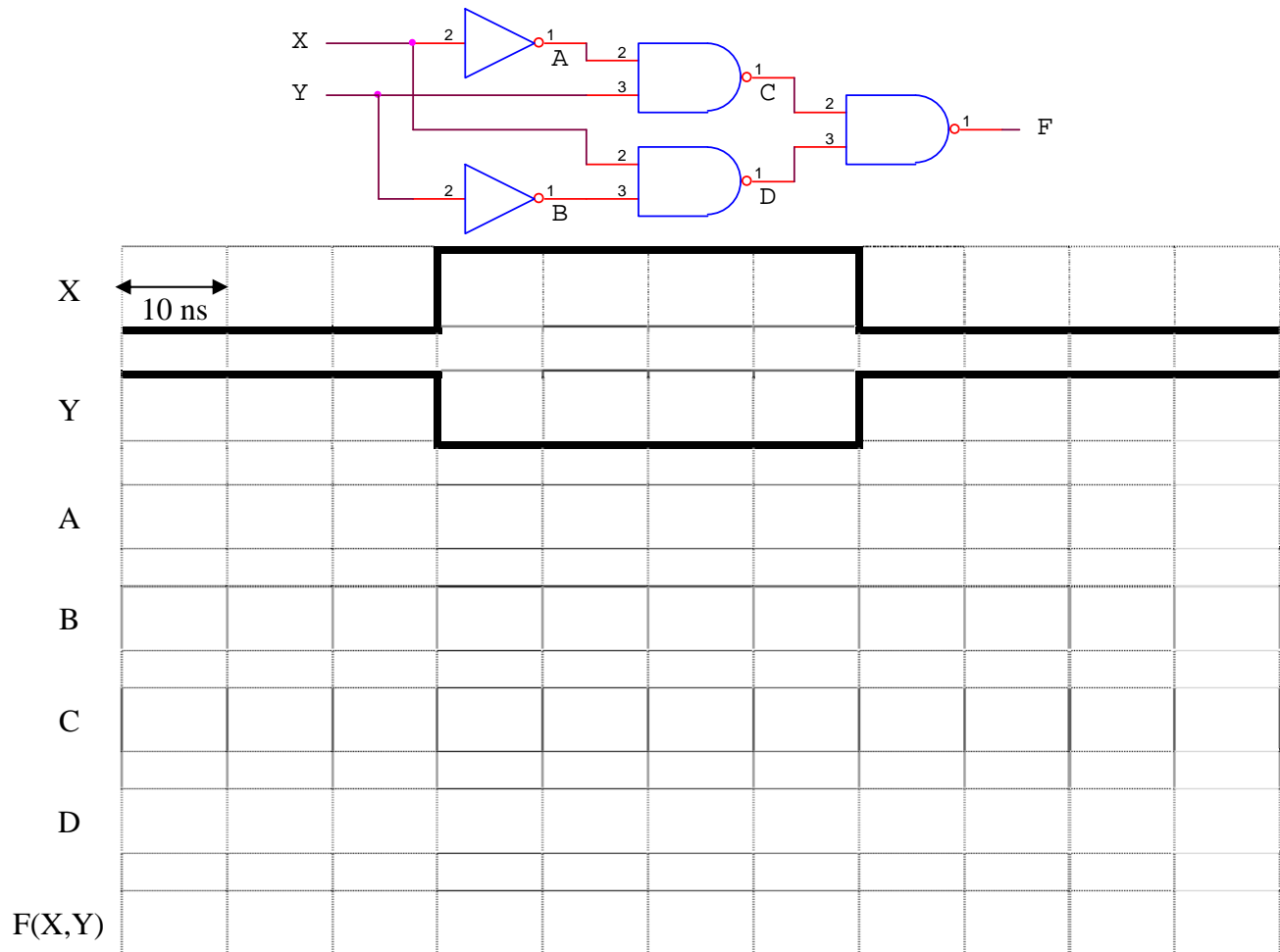The following circuit and timing chart apply to questions 15 and 16. Assume each gate has a propagation delay of 10 ns; use the chart provided as a worksheet.



15. Steady-state (static) analysis of the function realized by this circuit for the inputs provided predicts that the output  $F(X,Y)$  should:
- always be low
  - always be high
  - be equal to the input X
  - be equal to the input Y
  - none of the above
16. Dynamic analysis of the output  $F(X,Y)$  reveals that:
- a static "0" hazard will be produced whenever the inputs X and Y transition simultaneously
  - a static "1" hazard will be produced whenever the inputs X and Y transition simultaneously
  - a static "0" hazard will be produced only when input X transitions from low-to-high and input Y transitions from high-to-low
  - a static "1" hazard will be produced only when input X transitions from high-to-low and input Y transitions from low-to-high
  - none of the above

The **ispLever-Generated Reports** below apply to questions 17 through 19.

REDUCED EQUATION REPORT:					CHIP REPORT:	
P-Terms	Fan-in	Fan-out	Type	Name (attributes)		
4/4	4	1	Pin	X	X = B&D&!A&C # !B&!D&!A&C # B&D&A&!C # !B&!D&A&!C;	
3/4	4	1	Pin	Y	Y = B&D # A&C # !A&!C;	
=====						
7/8	Best P-Term Total: 7					
	Total Pins: 6					
	Total Nodes: 0					
	Average P-Term/Output: 3					
Positive-Polarity Equations:						
X = !B&!D&A&!C # B&D&A&!C # !B&!D&!A&C # B&D&!A&C;						
Y = B&D # !A&!C # A&C;						
Reverse-Polarity Equations:						
!X = B&!D # !B&D # !A&!C # A&C;						
!Y = !D&A&!C # !B&A&!C # !D&!A&C # !B&!A&C;						

ispLEVER operators:					
AND	-	&	OR	-	#
NOT	-	!	XOR	-	\$

P22V10G				
A	1		24	Vcc
B	2		23	Y
C	3		22	
D	4		21	
	5		20	
	6		19	
	7		18	
	8		17	
	9		16	
	10		15	
	11		14	X
GND	12		13	

17. The **total number of P terms** used by this Verilog program is:

- (A) 3
- (B) 4
- (C) 7
- (D) 8
- (E) none of these


18. The **chip report** indicates that the fitter program chose the following forms of the reduced equations to burn into the PLD:

- (A) the positive polarity forms of both X and Y
- (B) the reverse polarity forms of both X and Y
- (C) the positive polarity form of X and the reverse polarity form of Y
- (D) the reverse polarity form of X and the positive polarity form of Y
- (E) none of the above

19. A possible **Verilog source form** of the equation for X is:

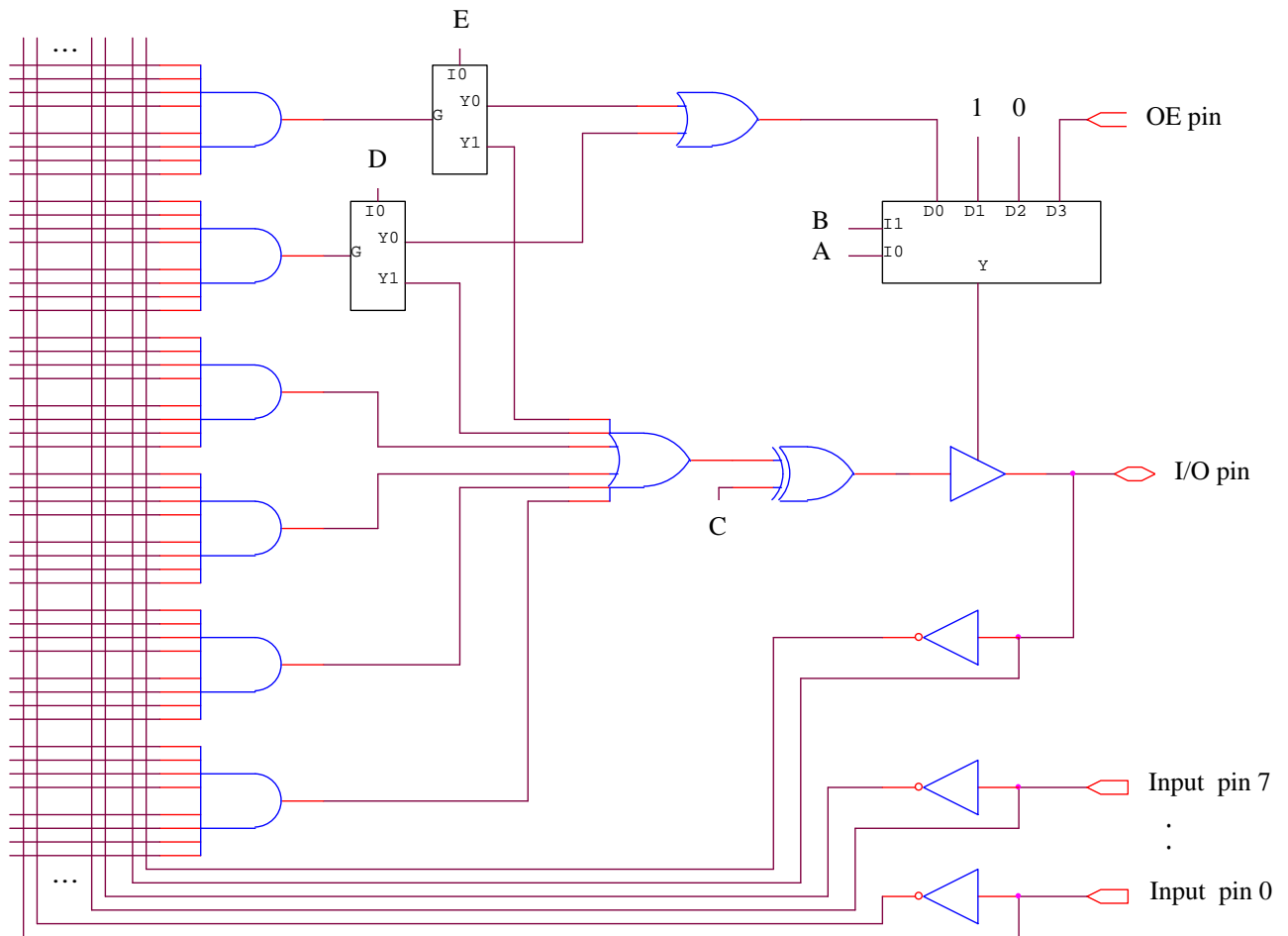- (A)  $X = (B \wedge D) \& (A \sim \wedge C);$
- (B)  $X = (B \wedge D) \mid (A \sim \wedge C);$
- (C)  $X = (B \sim \wedge D) \& (A \wedge C);$
- (D)  $X = (B \sim \wedge D) \mid (A \wedge C);$
- (E) none of the above

The **Macrocell Reference Figure** below applies to questions 20 through 22.



20. The possibilities for controlling the tri-state buffer enable do **not** include:
- (A) always OFF
  - (B) always ON
  - (C) controlled by an expression comprised of one product term
  - (D) controlled by an expression comprised of two product terms
  - (E) none of the above
21. If **D=0** and **E=1**, the **maximum number** of **product terms** that can be utilized by a function realized by the macrocell I/O pin is:
- (A) 2    (B) 4    (C) 5    (D) 6    (E) none of these
22. To realize the **positive polarity equation** of a function with an **active low** output, the following settings should be used:
- (A) **C=0, B=0, A=1**
  - (B) **C=0, B=1, A=0**
  - (C) **C=1, B=0, A=1**
  - (D) **C=1, B=1, A=0**
  - (E) none of the above

The following Verilog program applies to questions 23 through 25:

23. The number of equations generated by this program is:
- (A) 2
  - (B) 4
  - (C) 8
  - (D) 16
  - (E) none of the above
24. When **TEN** is negated, **S[1]=1**, and **S[0]=1**, the outputs **Y\_z[3:0]** will:
- (A) all be zero
  - (B) all be one
  - (C) all be Hi-Z
  - (D) be equal to the inputs **A[3:0]**
  - (E) none of the above
25. When **TEN** is asserted, **S[1]=1**, and **S[0]=0**, the outputs **Y\_z[3:0]** will:
- (A) be equal to the inputs **A[3:0]**
  - (B) be equal to the inputs **B[3:0]**
  - (C) be equal to the inputs **C[3:0]**
  - (D) be equal to the inputs **D[3:0]**
  - (E) none of the above

```

/* Mid-Size Multiplexer */
module midmux(TEN,S,A,B,C,D,Y_z);

    input wire TEN;
    input wire [1:0] S;
    input wire [3:0] A, B, C, D;
    output tri [3:0] Y_z;
    wire [3:0] Y;

    assign Y_z = TEN ? Y : 4'bZZZZ;

    always @ (S) begin
        Y = 4'b0000;
        case (S)
            2'd0: Y = A;
            2'd1: Y = B;
            2'd2: Y = C;
            2'd3: Y = D;
        endcase
    end
endmodule

```

The following Verilog program applies to questions 26 and 27:

26. If input **I[0]** is **asserted** and *all the other inputs* are **negated**, the output produced will be:
- (A) **E\_z[1]=0, E\_z[0]=0, G=0**
  - (B) **E\_z[1]=0, E\_z[0]=0, G=1**
  - (C) **E\_z[1]=Hi-Z, E\_z[0]=Hi-Z, G=Hi-Z**
  - (D) **E\_z[1]=Hi-Z, E\_z[0]=Hi-Z, G=1**
  - (E) none of the above
27. If inputs **I[1]**, **I[2]**, and **TEN** are **asserted** and *all the other inputs* are **negated**, the output produced will be:
- (A) **E\_z[1]=0, E\_z[0]=0, G=0**
  - (B) **E\_z[1]=0, E\_z[0]=1, G=1**
  - (C) **E\_z[1]=1, E\_z[0]=0, G=1**
  - (D) **E\_z[1]=Hi-Z, E\_z[0]=Hi-Z, G=1**
  - (E) none of the above

```

/* Mid-Size Priority Encoder */
module prienc(I, E_z, G, TEN);
    input wire [3:0] I;
    input wire TEN;
    output tri [1:0] E_z;
    output wire G;
    reg [2:0] EG;
    always @ (I) begin
        casez (I)
            4'b0000: EG = 3'b000;
            4'b0001: EG = 3'b001;
            4'b001?: EG = 3'b011;
            4'b01???: EG = 3'b101;
            4'b1????: EG = 3'b111;
        endcase
    end
    assign G = EG[0];
    assign E_z = TEN ? EG[2:1] : 2'bzz;
endmodule

```



The following Verilog program and 22V10 diagram apply to questions 28 through 30.

```

/* Big XOR Attempt on 22V10 */


module bigxor (I, BXOUT);

    input wire [11:0] I;
    output wire BXOUT;

    assign BXOUT = ^I;

endmodule

```

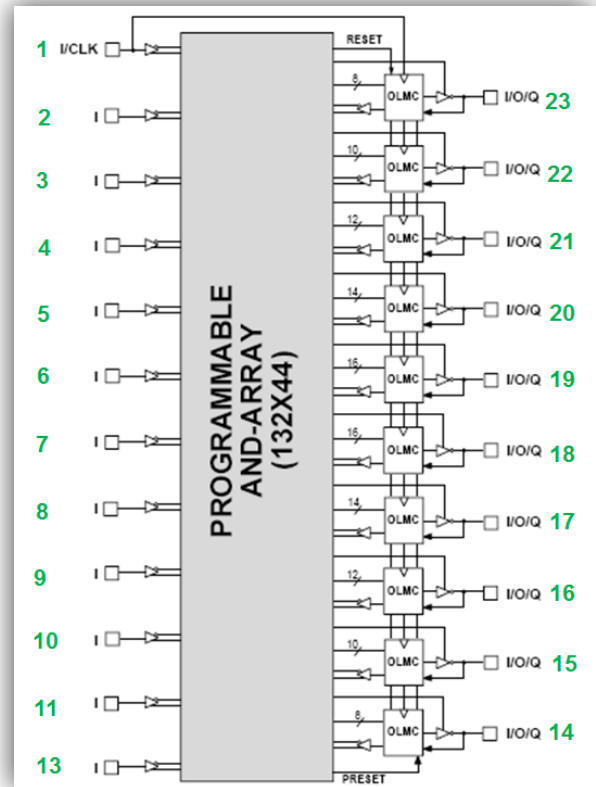

Pins 14 & 23 – 8 P-terms each  
 Pins 15 & 22 – 10 P-terms each  
 Pins 16 & 21 – 12 P-terms each  
 Pins 17 & 20 – 14 P-terms each  
 Pins 18 & 19 – 16 P-terms each

28. Just when you thought the exam was safe from your well-intentioned “best friend from another major” (BFFAM), you discover a Verilog program they have written for a 22V10. It looks like this time your BFFAM is attempting to create a 12-variable XOR function. The **number of product terms** required to realize the equation for **BXOUT**, given the Verilog program **as written**, is:
- 24
  - 1024
  - 2048
  - 4096
  - none of these
29. As expected, the Verilog program targeting a 22V10 **doesn't fit (as written)** because:
- the pin numbers are not specified
  - there are an insufficient number of input pins
  - there are an insufficient number of I/O (macrocell) pins
  - there are an insufficient number of P-terms
  - none of the above
30. The Verilog program shown could be **modified** to successfully realize the “Big XOR” function on a single 22V10 by:
- adding an explicit pin assignment for **BXOUT**
  - adding explicit pin assignments for *all* the input and output variables
  - splitting the equation for BXOUT** into two 5-variable XOR functions (assigned to two specific macrocells), the **outputs of which** could then be XORed with the **other two inputs** using a third macrocell (i.e. using a total of 3 macrocells)
  - changing their degree option*, as there is **no way** to implement a 12-variable XOR function on a 22V10, and consequently there is **no way** to successfully modify the Verilog program!
  - none of the above