

LEARNING OUTCOME #3: “an ability to analyze and design sequential logic circuits.”**Multiple Choice – select the single most appropriate response for each question.****Note that “none of the above” MAY be a VALID ANSWER.**

1. A “new” type of flip-flop, the “PU”, is described by the given PS-NS table. The characteristic equation for this flip-flop is:

- (A) $Q^* = P \cdot Q' + U' \cdot Q$
 (B) $Q^* = P \cdot Q + U' \cdot Q'$
 (C) $Q^* = P' \cdot Q + U \cdot Q'$
 (D) $Q^* = P \cdot U + Q'$
 (E) none of the above

PU Flip-Flop PS-NS Table
for questions 1 and 2


P	U	Q	Q*
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

2. The excitation required to effect a state transition of the PU flip-flop from “0” to “1” is:
- (A) $P=d, U=0$
 (B) $P=d, U=1$
 (C) $P=0, U=d$
 (D) $P=1, U=d$
 (E) none of the above

3. Assuming the state machine depicted in the given state transition diagram is initialized to state **00**, the input sequence **1101000100** will cause the following output sequence to be generated:

 - (A) **0000100000**
 (B) **0100001000**
 (C) **0010000100**
 (D) **0000100010**
 (E) none of the above

State Transition Diagram
for questions 3 and 4




4. The **embedded binary sequence** recognized by this state machine is the pattern:

- (A) **001**
 (B) **010**
 (C) **011**
 (D) **0101**
 (E) none of the above

5. A **D latch** is called a **transparent** because:
- (A) the output “follows” the input when the latch is closed
 - (B) the output “follows” the input when the latch is open
 - (C) the output “freezes” when the latch is closed
 - (D) the output “freezes” when the latch is open
 - (E) none of the above
6. **Metastable** behavior of an edge-triggered D flip-flop can be caused by:
- (A) violating its minimum setup time requirement
 - (B) violating its minimum hold time requirement
 - (C) violating its minimum clock pulse width requirement
 - (D) all of the above
 - (E) none of the above

 7. The next state equation represented by the following state transition diagram is:



- (A) $X^* = A' \cdot X' + A \cdot X$
 - (B) $X^* = A' \cdot X + A \cdot X'$
 - (C) $X^* = A + X$
 - (D) $X^* = A \cdot X$
 - (E) none of the above
8. The initial state (after **START** is asserted) is:
- (A) **000**
 - (B) **010**
 - (C) **110**
 - (D) **111**
 - (E) none of the above
9. The number of states in the **periodic sequence** (after **START** is asserted) is:
- (A) **1**
 - (B) **2**
 - (C) **6**
 - (D) **7**
 - (E) none of the above

Verilog program for questions 8 and 9:


```

module mystery_seq(CLK, START, Q);
  input wire CLK;
  input wire START;
  output reg[2:0] Q;

  always @ (posedge CLK, posedge START)
  begin
    if (START == 1'b1)
      Q <= 3'b111;
    else
      Q <= next_Q;
    end


  always @ (Q) begin
    case(Q)
      3'b000: next_Q = 3'b'000;
      3'b001: next_Q = 3'b'010;
      3'b010: next_Q = 3'b'101;
      3'b011: next_Q = 3'b'110;
      3'b100: next_Q = 3'b'001;
      3'b101: next_Q = 3'b'011;
      3'b110: next_Q = 3'b'100;
      3'b111: next_Q = 3'b'110;
    endcase
  endmodule
  
```

 The following circuit applies to questions 10 through 14:



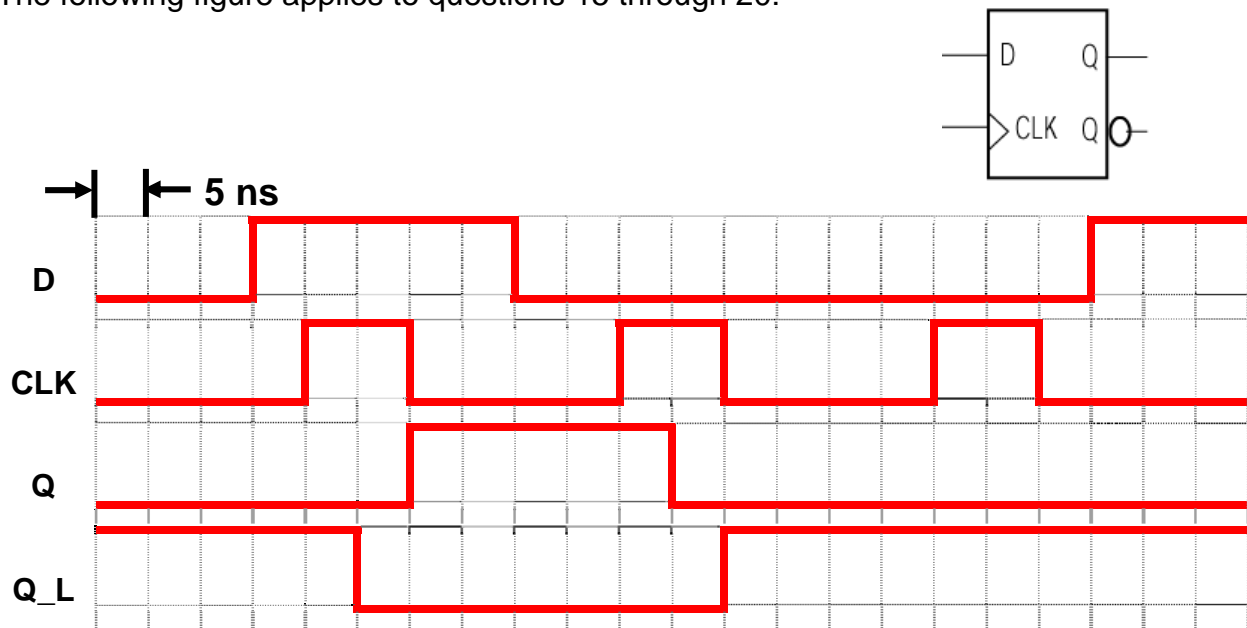
10. If the **input** combination **A=0, B=1** is applied to this circuit, the (steady state) output will be:
- (A) X=0, Y=0
 - (B) X=0, Y=1
 - (C) X=1, Y=0
 - (D) X=1, Y=1
 - (E) unpredictable
11. If the **input** combination **A=0, B=0** is applied to this circuit, **followed immediately** by the **input** combination **A=1, B=0**, the (steady state) output will be:
- (A) X=0, Y=0
 - (B) X=0, Y=1
 - (C) X=1, Y=0
 - (D) X=1, Y=1
 - (E) unpredictable
12. If the **input** combination **A=0, B=0** is applied to this circuit, the (steady state) output will be:
- (A) X=0, Y=0
 - (B) X=0, Y=1
 - (C) X=1, Y=0
 - (D) X=1, Y=1
 - (E) unpredictable
13. If the **input** combination **A=0, B=0** is applied to this circuit, **followed immediately** by the **input** combination **A=1, B=1**, the (steady state) output will be:
- (A) X=0, Y=0
 - (B) X=0, Y=1
 - (C) X=1, Y=0
 - (D) X=1, Y=1
 - (E) unpredictable
14. If the **propagation delay** of each gate is **10 ns**, the **minimum length of time** that (valid) input combinations need to be asserted **in order to prevent metastable behavior** is:
- (A) 10 ns
 - (B) 20 ns
 - (C) 30 ns
 - (D) 40 ns
 - (E) none of the above

The following figure applies to questions 15 through 20:




15. The **duty cycle** of the clocking signal is:
- (A) 20%
 - (B) 33%
 - (C) 40%
 - (D) 67%
 - (E) none of the above
16. The **nominal setup time** provided for the D flip-flop, based on the excitation signals (D and CLK) depicted in the timing chart, is:
- (A) 5 ns (B) 10 ns (C) 15 ns (D) 20 ns (E) none of the above
17. The **nominal hold time** provided for the D flip-flop, based on the excitation signals (D and CLK) depicted in the timing chart, is:
- (A) 5 ns (B) 10 ns (C) 15 ns (D) 20 ns (E) none of the above
18. The **nominal clock pulse width** provided for the D flip-flop, based on the excitation signals (D and CLK) depicted in the timing chart, is:
- (A) 5 ns (B) 10 ns (C) 15 ns (D) 20 ns (E) none of the above
19. The $t_{PLH}(C \rightarrow Q)$ of the D flip-flop is:
- (A) 5 ns (B) 10 ns (C) 15 ns (D) 20 ns (E) none of the above
20. The $t_{PHL}(C \rightarrow Q)$ of the D flip-flop is:
- (A) 5 ns (B) 10 ns (C) 15 ns (D) 20 ns (E) none of the above

 21. The following Verilog program implements the state transition diagram below:



(A)	<pre> /* Program (A) */ module CQ(CLK, M, Q); input wire CLK, M; output reg [2:0] Q; reg [2:0] next_Q; always @ (posedge CLK) begin Q <= next_Q; end always @ (Q, M) begin next_Q[0] = ~Q[0]; next_Q[1] = ~Q[1] ^ (~M&~Q[0] M&Q[0]); next_Q[2] = ~Q[2] ^ (~M&~Q[1]&~Q[0] M& Q[1]& Q[0]); end endmodule </pre>
(B)	<pre> /* Program (B) */ module CQ(CLK, M, Q); input wire CLK, M; output reg [2:0] Q; reg [2:0] next_Q; always @ (posedge CLK) begin Q <= next_Q; end always @ (Q, M) begin next_Q[0] = ~Q[0]; next_Q[1] = Q[1] ^ (~M&Q[0] M&~Q[0]); next_Q[2] = Q[2] ^ (~M& Q[1]& Q[0] M&~Q[1]&~Q[0]); end endmodule </pre>
(C)	<pre> /* Program (C) */ module CQ(CLK, M, Q); input wire CLK, M; output reg [2:0] Q; reg [2:0] next_Q; always @ (posedge CLK) begin Q <= next_Q; end always @ (Q, M) begin next_Q[0] = ~Q[0]; next_Q[1] = Q[1] ^ (~M&~Q[0] M& Q[0]); next_Q[2] = Q[2] ^ (~M&~Q[1]&~Q[0] M& Q[1]& Q[0]) end endmodule </pre>
(D)	all of the above
(E)	none of the above

 22. The following timing diagram depicts the behavior of the circuit shown below:



(A)	
(B)	
(C)	
(D)	
(E)	none of the above

23. As a contestant on the soon-to-be-cancelled TV series *Digital Moment of Truth*, you have been asked to identify which of the following statements concerning **state machine models** is **true**:
- (A) Mealy and Moore models that represent equivalent state machines will **always** have the **same** number of states
 - (B) Mealy and Moore models that represent equivalent state machines will **always** have a **different** number of states
 - (C) **any Mealy model** can be transformed into **an equivalent Moore model**, and *vice-versa*
 - (D) Mealy and Moore models that represent equivalent state machines, when realized, will exhibit the **same observable behavior** (i.e., if placed in a “black box”, their **observable behavior** would be **indistinguishable**)
 - (E) none of the above
24. As a contestant on the TV series *Are You Smarter Than a Website Contractor?*, you have been asked to explain why a “D” latch is called **transparent**. Hoping to forgo an admission before a national television audience to the contrary, you calmly answer that a “D” latch is called **transparent because its output**:
- (A) is equal to its input when the latch enable is high-impedance
 - (B) is equal to its input when the latch enable is asserted
 - (C) is equal to its input when the latch enable is negated
 - (D) changes state as soon as the latch is clocked
 - (E) none of the above
25. The next topic over which you’ve been asked to “Digitally Digress” with the stars of *Dual Dynasty* is the phenomenon of metastability. You confidently explain that **the next state of an edge-triggered D flip-flop will most likely be random if**:
- (A) its minimum setup time requirement is not met
 - (B) its minimum hold time requirement is not met
 - (C) its minimum clock pulse width requirement is not met
 - (D) all of the above
 - (E) none of the above
26. As a contestant on the hit TV series *Digital Survivor – Flips vs. Flops*, you have been asked to implement a **negative edge-triggered D flip-flop** using **only 2-input NAND** gates. The **minimum** number of gates you will need to complete this task is:
- (A) 9 (B) 10 (C) 11 (D) 12 (E) none of these
27. Your next task on *Digital Survivor* is to build a circuit that **divides** the frequency of a clocking signal **by two**. Provided you have successfully completed Problem 26, above, and have a working negative edge-triggered D flip-flop, the number of **additional 2-input NAND gates** you will need to complete this task is:
- (A) 0 (B) 1 (C) 2 (D) 3 (E) none of these
28. Your final task on *Digital Survivor* is to implement a finite state machine that has **212 states** with as few flip-flops as possible. To **reduce** the **number of flip-flops** required in this design **by one** (using either “obvious” or “formal” state minimization procedures), **you would have to identify and eliminate _____ redundant state(s)**.
- (A) 1 (B) 2 (C) 84 (D) 128 (E) none of these

The following Verilog program applies to questions 29 and 30:

```

/* Multi-Color LED Light Machine */
module mcleds(CLK, M, R, G, Y, B);
  input wire CLK;
  input wire M;
  output wire R, G, B, Y;
  reg [1:0] Q, next_Q;
  reg [5:0] nQRGYB;

  always @ (posedge CLK) begin
    Q <= next_Q;
  end

  assign next_Q    = nQRGYB[5:4]
  assign {R,G,Y,B} = nQRGYB[3:0];

  always @ (Q, M) begin
    case ({Q,M})
      3'b000: nQRGYB = {2'b10,4'b1000};
      3'b001: nQRGYB = {2'b11,4'b1000};
      3'b010: nQRGYB = {2'b11,4'b0010};
      3'b011: nQRGYB = {2'b00,4'b1111};
      3'b100: nQRGYB = {2'b01,4'b0100};
      3'b101: nQRGYB = {2'b01,4'b1110};
      3'b110: nQRGYB = {2'b00,4'b0001};
      3'b111: nQRGYB = {2'b10,4'b1100};
    endcase
  end
endmodule

```

29. When **M=0**, the (repeating) colored LED sequence produced will be:

- (A) **R→G→Y→B→...**
- (B) **R→Y→G→B→...**
- (C) **B→Y→G→R→...**
- (D) **B→G→Y→R→...**
- (E) none of the above

30. When **M=1**, the (repeating) colored LED sequence produced will be:

- (A) **R→RGYB→RGY→RG→...**
- (B) **R→RG→RGY→RGYB→...**
- (C) **RGYB→RGY→RG→R→...**
- (D) **R→RGY→RG→RGYB→...**
- (E) none of the above