

## Homework 12

*Due at the beginning of your scheduled lab period*


Last Name (Printed): \_\_\_\_\_ Lab Div: \_\_\_\_\_ Date: \_\_\_\_\_

E-mail: \_\_\_\_\_@purdue.edu Signature: \_\_\_\_\_

Printed copies of these pages along with your original (**hand-annotated**, **not photocopied**) written solution in the space provided (unless otherwise indicated) are required in order to receive credit. NOTE: The purpose of homework is to provide an opportunity for practicing the kinds of problems you will be asked to solve on quizzes and exams – **copying the work of someone else does not accomplish this**.

- [8 pts] Draw a circuit that multiplies a 5-bit unsigned binary number  $X_4 X_3 X_2 X_1 X_0$  by a 3-bit unsigned binary number  $Y_2 Y_1 Y_0$ , using an array of full-adder cells. Determine the *worst case propagation delay* if each full adder takes 10 ns to produce its C and S outputs, and each AND gate (used to generate the product components) has 5 ns of propagation delay.

<b>X4</b>	<b>X3</b>	<b>X2</b>	<b>X1</b>	<b>X0</b>
	<b>x</b>	<b>Y2</b>	<b>Y1</b>	<b>Y0</b>
<hr/>				

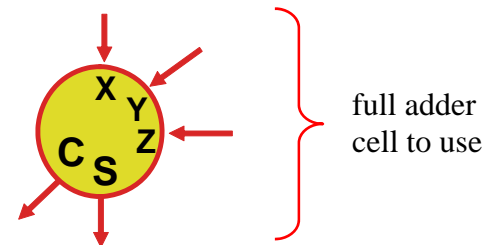

2. [6 pts] Complete the magnitude comparator chart below and derive the function for “A less than or equal to B” (“ALEB”) in its simplest (minimal) form, assuming that A and B are *signed numbers*.

A <sub>1</sub>	A <sub>0</sub>	(A)	B <sub>1</sub>	B <sub>0</sub>	(B)	?	C	Z	N	V
0	0	0	0	0	0	(A) = (B)				
0	0	0	0	1	+1	(A) < (B)				
0	0	0	1	0	-2	(A) > (B)				
0	0	0	1	1	-1	(A) > (B)				
0	1	+1	0	0	0	(A) > (B)				
0	1	+1	0	1	+1	(A) = (B)				
0	1	+1	1	0	-2	(A) > (B)				
0	1	+1	1	1	-1	(A) > (B)				
1	0	-2	0	0	0	(A) < (B)				
1	0	-2	0	1	+1	(A) < (B)				
1	0	-2	1	0	-2	(A) = (B)				
1	0	-2	1	1	-1	(A) < (B)				
1	1	-1	0	0	0	(A) < (B)				
1	1	-1	0	1	+1	(A) < (B)				
1	1	-1	1	0	-2	(A) > (B)				
1	1	-1	1	1	-1	(A) = (B)				

		C'		C		
N'		0	4	12	8	V'
		1	5	13	9	
N		3	7	15	11	V
		2	6	14	10	V'
		Z'		Z		Z'

3. [6 pts] Complete the magnitude comparator chart below and derive the function for “A higher than or same B” (“AHSB”) in its simplest (minimal) form, assuming that A and B are *unsigned numbers*.

A <sub>1</sub>	A <sub>0</sub>	(A)	B <sub>1</sub>	B <sub>0</sub>	(B)	?	C	Z	N	V
0	0	0	0	0	0	(A) = (B)				
0	0	0	0	1	+1	(A) < (B)				
0	0	0	1	0	+2	(A) < (B)				
0	0	0	1	1	+3	(A) < (B)				
0	1	+1	0	0	0	(A) > (B)				
0	1	+1	0	1	+1	(A) = (B)				
0	1	+1	1	0	+2	(A) < (B)				
0	1	+1	1	1	+3	(A) < (B)				
1	0	+2	0	0	0	(A) > (B)				
1	0	+2	0	1	+1	(A) > (B)				
1	0	+2	1	0	+2	(A) = (B)				
1	0	+2	1	1	+3	(A) < (B)				
1	1	+3	0	0	0	(A) > (B)				
1	1	+3	0	1	+1	(A) > (B)				
1	1	+3	1	0	+2	(A) > (B)				
1	1	+3	1	1	+3	(A) = (B)				

		C'		C		
		0	4	12	8	
N'						V'
	1	5	13	9		
						V
N	3	7	15	11		
	2	6	14	10		V'
		Z'	Z	Z'		