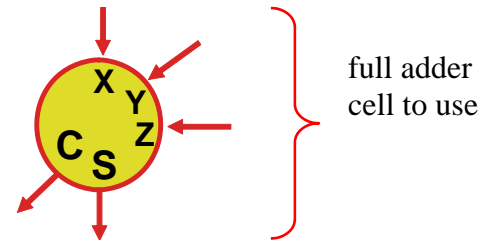



Homework 12 - Solution*Due at the beginning of your scheduled lab period*

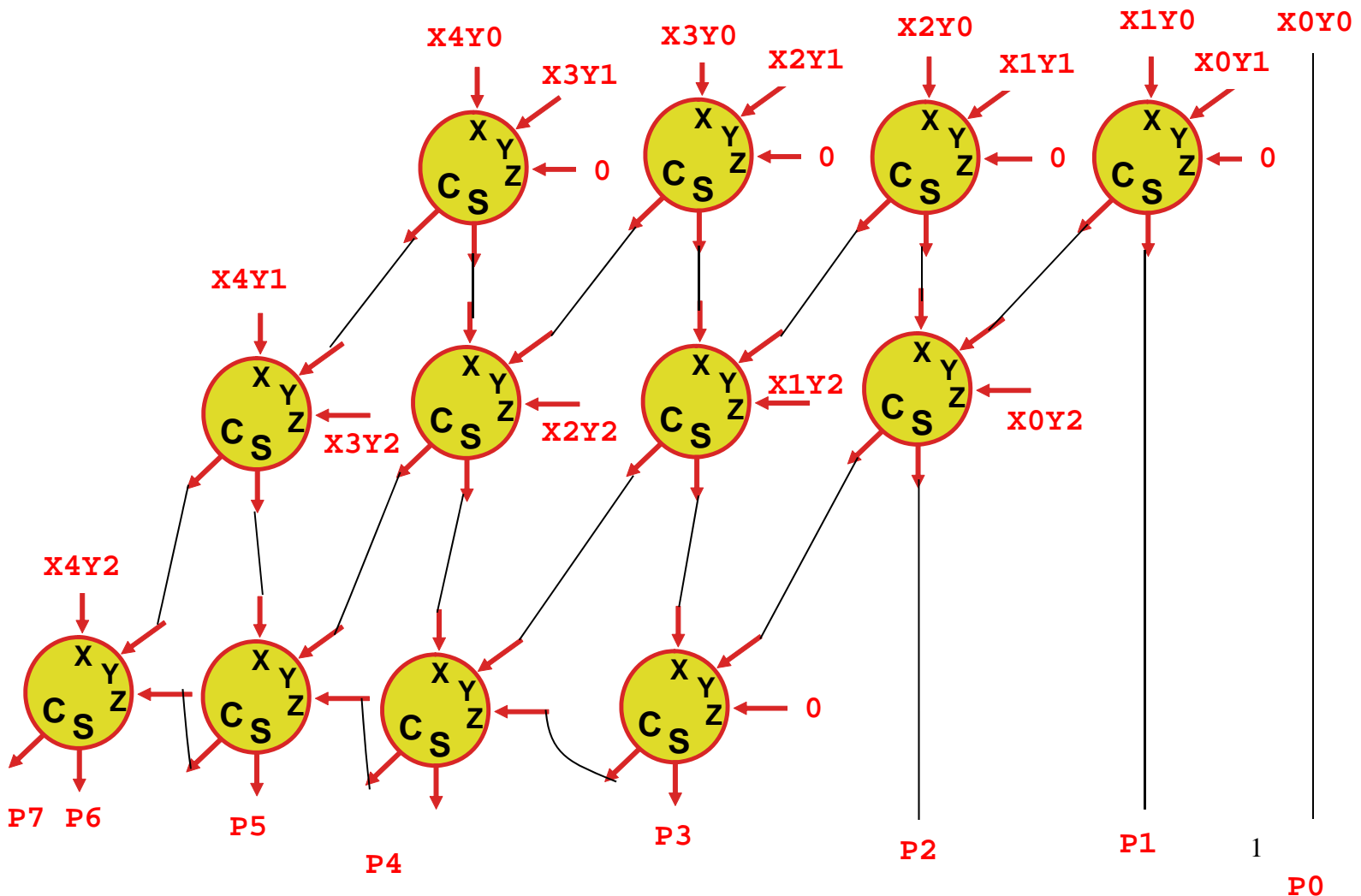1. [8 pts] Draw a circuit that multiplies a 5-bit unsigned binary number $X_4 X_3 X_2 X_1 X_0$ by a 3-bit unsigned binary number $Y_2 Y_1 Y_0$, using an array of full-adder cells. Determine the *worst case propagation delay* if each full adder takes 10 ns to produce its C and S outputs, and each AND gate (used to generate the product components) has 5 ns of propagation delay.

$$\begin{array}{r}
 \begin{array}{ccccc}
 X_4 & X_3 & X_2 & X_1 & X_0 \\
 \times & Y_2 & Y_1 & Y_0 & \\
 \hline
 X_4Y_0 & X_3Y_0 & X_2Y_0 & X_1Y_0 & X_0Y_0 \\
 X_4Y_1 & X_3Y_1 & X_2Y_1 & X_1Y_1 & X_0Y_1 \\
 X_4Y_2 & X_3Y_2 & X_2Y_2 & X_1Y_2 & X_0Y_2 \\
 \hline
 P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0
 \end{array}
 \end{array}$$



Array should have 4 diagonals/3 rows (12 FA cells total, plus 15 AND gates); worst case delay path is 65 ns



2. [6 pts] Complete the magnitude comparator chart below and derive the function for “A *less than or equal to* B” (“ALEB”) in its simplest (minimal) form, assuming that A and B are *signed two’s complement numbers*.

A ₁	A ₀	(A)	B ₁	B ₀	(B)	?	C	Z	N	V
0	0	0	0	0	0	(A) = (B)	1	1	0	0
0	0	0	0	1	+1	(A) < (B)	0	0	1	0
0	0	0	1	0	-2	(A) > (B)	0	0	1	1
0	0	0	1	1	-1	(A) > (B)	0	0	0	0
0	1	+1	0	0	0	(A) > (B)	1	0	0	0
0	1	+1	0	1	+1	(A) = (B)	1	1	0	0
0	1	+1	1	0	-2	(A) > (B)	0	0	1	1
0	1	+1	1	1	-1	(A) > (B)	0	0	1	1
1	0	-2	0	0	0	(A) < (B)	1	0	1	0
1	0	-2	0	1	+1	(A) < (B)	1	0	0	1
1	0	-2	1	0	-2	(A) = (B)	1	1	0	0
1	0	-2	1	1	-1	(A) < (B)	0	0	1	0
1	1	-1	0	0	0	(A) < (B)	1	0	1	0
1	1	-1	0	1	+1	(A) < (B)	1	0	1	0
1	1	-1	1	0	-2	(A) > (B)	1	0	0	0
1	1	-1	1	1	-1	(A) = (B)	1	1	0	0

	C'		C		
N'	0 0	4 d	12 1	8 0	V'
	1 d	5 d	13 d	9 1	
N	3 0	7 d	15 d	11 d	V
	2 1	6 d	14 d	10 1	V'
	Z'	Z	Z'		

$$\text{ALEB} = Z + N' \bullet V + N \bullet V'$$

3. [6 pts] Complete the magnitude comparator chart below and derive the function for “A higher than or same B” (“AHSB”) in its simplest (minimal) form, assuming that A and B are unsigned numbers.

A ₁	A ₀	(A)	B ₁	B ₀	(B)	?	C	Z	N	V
0	0	0	0	0	0	(A) = (B)	1	1	0	0
0	0	0	0	1	+1	(A) < (B)	0	0	1	0
0	0	0	1	0	+2	(A) < (B)	0	0	1	1
0	0	0	1	1	+3	(A) < (B)	0	0	0	0
0	1	+1	0	0	0	(A) > (B)	1	0	0	0
0	1	+1	0	1	+1	(A) = (B)	1	1	0	0
0	1	+1	1	0	+2	(A) < (B)	0	0	1	1
0	1	+1	1	1	+3	(A) < (B)	0	0	1	1
1	0	+2	0	0	0	(A) > (B)	1	0	1	0
1	0	+2	0	1	+1	(A) > (B)	1	0	0	1
1	0	+2	1	0	+2	(A) = (B)	1	1	0	0
1	0	+2	1	1	+3	(A) < (B)	0	0	1	0
1	1	+3	0	0	0	(A) > (B)	1	0	1	0
1	1	+3	0	1	+1	(A) > (B)	1	0	1	0
1	1	+3	1	0	+2	(A) > (B)	1	0	0	0
1	1	+3	1	1	+3	(A) = (B)	1	1	0	0

		C'		C		
N'		0 0	4 d	12 1	8 1	V'
		1 d	5 d	13 d	9 1	
N		3 0	7 d	15 d	11 d	V
		2 0	6 d	14 d	10 1	V'
		Z'	Z	Z'		

$$\text{AHSB} = C$$

Score: _____ / 20