

Homework 8



Due at the beginning of your scheduled lab period

Last Name (Printed): _____ Lab Div: _____ Date: _____


E-mail: _____@purdue.edu Signature: _____

Printed copies of these pages along with your original (**hand-annotated**, **not photocopied**) written solution in the space provided (unless otherwise indicated) are required in order to receive credit. NOTE: The purpose of homework is to provide an opportunity for practicing the kinds of problems you will be asked to solve on quizzes and exams – **copying the work of someone else does not accomplish this.**

  1. [4 pts] Given the following state transition diagram, complete the timing chart below.




 2. [6 pts] Given the following state transition diagram, determine the *next state equations* it represents in *minimum sum-of-products form*.



X	Y	A	B	X*	Y*
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

 
X* and Y* are “shorthand” for the next state of X and Y



X* = _____

Y* = _____

 3. [4 pts] Write a Verilog code module that implements the following circuit:



```


module bounceless_switch(NC,NO,BQ);

    input wire NC,NO;
    output wire BQ;

    endmodule

```

 4. [6 pts] Write a Verilog code module that implements the following circuit:



```

module master_latch(SM,RM,CM,QM,QM_N);

    input wire SM,RM,CM;
    output wire QM,QM_N;

    endmodule

```