

## Homework 9


*Due at the beginning of your scheduled lab period*

Last Name (Printed): \_\_\_\_\_ Lab Div: \_\_\_\_\_ Date: \_\_\_\_\_

E-mail: \_\_\_\_\_@purdue.edu Signature: \_\_\_\_\_



*Printed* copies of these pages along with your *original* (*hand-annotated*, *not photocopied*) written solution in the *space provided* (unless otherwise indicated) are required in order to receive credit. **NOTE:** The purpose of homework is to provide an opportunity for practicing the kinds of problems you will be asked to solve on quizzes and exams – *copying the work of someone else does not accomplish this.*

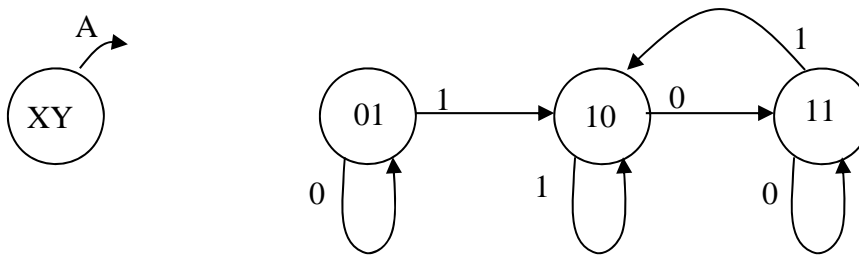1. [8 points] Given the following state transition diagram, determine:





- (a) The next state equation for X if the state machine is designed for **minimum cost**
- (b) The next state equation for X if the state machine is designed for **minimum risk**
- (c) The next state equation for Y if the state machine is designed for **minimum cost**
- (d) The next state equation for Y if the state machine is designed for **minimum risk**

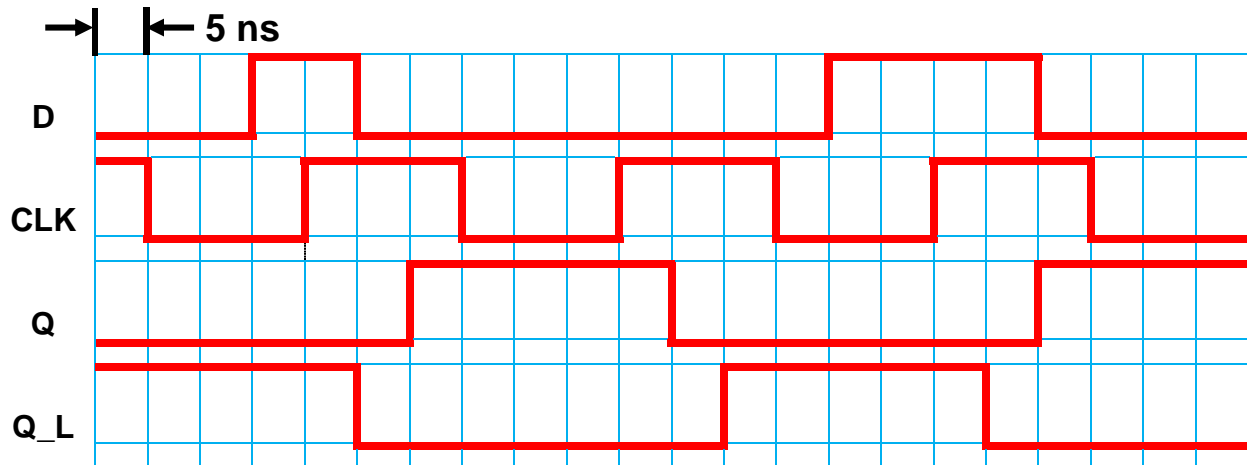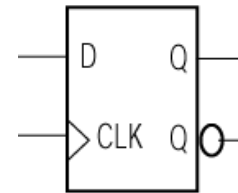2. [5 pts] Given the following timing chart for an edge-triggered D flip-flop, determine the following based on the excitation signals (D and CLK) depicted:



- The **nominal setup time** provided for the D flip-flop
- The **nominal hold time** provided for the D flip-flop
- The **nominal clock pulse width** provided for the D flip-flop
- The  $t_{PHL}(C \rightarrow Q)$  of the D flip-flop
- The  $t_{PLH}(C \rightarrow Q)$  of the D flip-flop

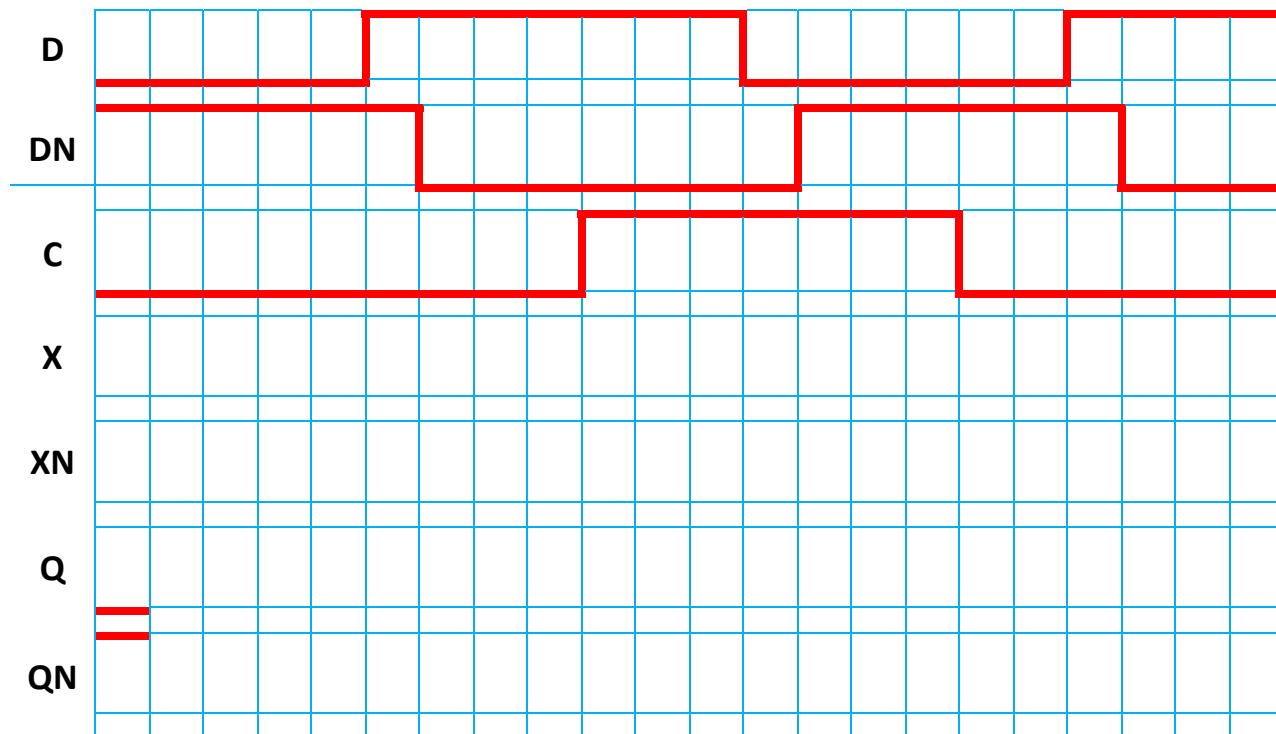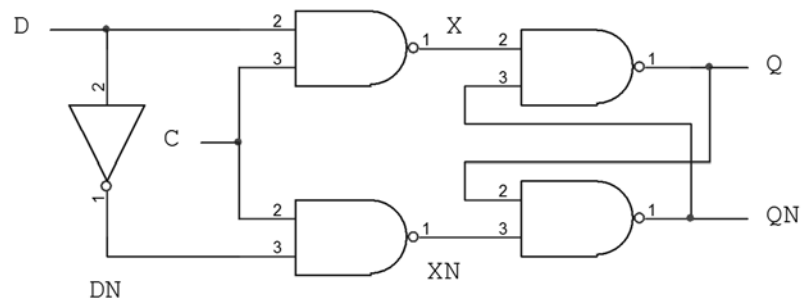3. [13 pts] Complete the timing chart, below, for a D latch with enable (C), and answer the questions that follow. Assume each gate has 10 ns of delay ( $t_{PLH}$  and  $t_{PHL}$ ), and that each division on the chart is 10 ns.



- Determine the **minimum time** input C should be asserted (while the D input remains stable) to ensure reliable operation of the latch.
- Determine the **nominal setup time** provided for the D latch.
- Determine the **nominal hold time** provided for the D latch.
- Determine the  $t_{PLH}(C \rightarrow Q)$  of the D latch.
- Determine the  $t_{PHL}(D \rightarrow Q)$  of the D latch.