

## Practice Homework Problems for Module 1

1. Unsigned base conversions (LO 1-1).

(a)  $(2C9E)_{16}$  to base 2

(b)  $(1101001)_2$  to base 10

(c)  $(1101001)_2$  to base 16

(d)  $(8576)_{10}$  to base 16

(e)  $(A27F)_{16}$  to base 8

2. Short answer questions over basic electronic components (LO 1-7).

- (a) Write two different formulas for OHM's LAW:
- (b) Describe what a resistor does:
- (c) Write two different formulas for calculating the power dissipation of a resistor:
- (d) Describe what a diode does.
- (e) Describe what affects the brightness of a light emitting diode (LED):
- (f) Describe what a capacitor does:
- (g) Describe a functional difference between a MOSFET and a BJT:
- (h) When a MOSFET is off, its drain-to-source impedance is on the order of:
- (i) When a MOSFET is on, its drain-to-source impedance is on the order of:
- (j) Describe a functional difference between an N-channel MOSFET and a P-channel MOSFET:


3. Prove DeMorgan's Law (T13) for  $n=3$  using perfect induction (LO 1-6).

$X_1$	$X_2$	$X_3$	$X_1 \cdot X_2 \cdot X_3$	$(X_1 \cdot X_2 \cdot X_3)$	$(X_1 \cdot X_2 \cdot X_3)'$	$X_1'$	$X_2'$	$X_3'$	$X_1' + X_2' + X_3'$
0	0	0							
0	0	1							
0	1	0							
0	1	1							
1	0	0							
1	0	1							
1	1	0							
1	1	1							


4. Prove the dual of the Covering theorem (T9<sup>D</sup>) using axioms and other theorems (LO 1-3).

$$(T9^D) \quad X \cdot (X + Y) = X$$

 
5. Determine voltages  $V_A$ ,  $V_B$ ,  $V_C$ , and  $V_D$  if each resistor is  $100\Omega$  and the voltage source is 10 volts (LO 1-7).



 6. Using a total of **three** N-channel MOSFETs and **three** P-channel MOSFETs, draw a circuit schematic for a **two-input AND** gate. The gate inputs should be labeled A and B, and the gate output should be labeled F. Be sure to show the power (Vcc) and ground (GND) connections as well (LO 1-10).



 7. Using a total of **three** N-channel MOSFETs and **three** P-channel MOSFETs, draw a circuit schematic for a **three-input NOR** gate. The gate inputs should be labeled A, B and C, and the gate output should be labeled F. Be sure to show the power ( $V_{cc}$ ) and ground (GND) connections as well (LO 1-12).



8. Given that a (5-volt) CMOS gate's P-channel output pull-up has an "on" resistance of  $160\Omega$  and that its N-channel output pull-down has an "on" resistance of  $80\Omega$ :

- (a) If the desired  $V_{OHmin}$  is 4.4 volts and the desired  $V_{OLmax}$  is 0.4 volts, what are the gate's  $I_{OHmax}$  and  $I_{OLmax}$  ratings? (LO 1-19)

$$I_{OHmax} = \underline{\hspace{2cm}} \text{ mA}$$

$$I_{OLmax} = \underline{\hspace{2cm}} \text{ mA}$$

- (b) If a DCNM of 1.2 volts is desired for this CMOS gate family, what do its  $V_{IHmin}$  and  $V_{ILmax}$  specifications need to be, based on the values given in part (a)? (LO 1-14)

$$V_{IHmin} = \underline{\hspace{2cm}} \text{ V}$$

$$V_{ILmax} = \underline{\hspace{2cm}} \text{ V}$$

- (c) If the  $I_{IH}$  and  $I_{IL}$  specifications for gates in this family are +0.1 mA and -0.1 mA, respectively, what is the practical fan-out for circuits constructed using these gates, based on values calculated in part (a)? (LO 1-20)

$$\text{Practical fan-out} = \underline{\hspace{2cm}}$$


- (d) Show how an LED (with forward voltage  $V_{LED} = 1.5 \text{ V}$ ) should be interfaced to gates in this family to obtain maximum brightness, and calculate the value of the current limiting resistor required along with its power dissipation. (LO 1-21)

Circuit and calculations:

$$\text{Current limiting resistor} = \underline{\hspace{2cm}} \Omega \quad \text{Resistor power dissipation} = \underline{\hspace{2cm}} \text{ mW}$$


9. Given that the P-channel device in the circuit below has **ON** and **OFF** resistances of **80  $\Omega$**  and **2 M $\Omega$**  (respectively) and that the N-channel device has **ON** and **OFF** resistances of **60  $\Omega$**  and **3 M $\Omega$**  (respectively), complete the table listing the **output voltages** obtained for each input combination as well as the **power dissipation** (in *milliwatts*). Show your calculations (LOs 1-10 and 1-11).

A	B	V <sub>out</sub>	Power Dissipation
0V	0V		
0V	5V		
5V	0V		
5V	5V		

 

10. One of your best friends from another major, “Raul”, found some N- and P-channel MOSFETs in your “geek box” and wired them together as shown below. Help Raul figure out what he has created by determining V<sub>out</sub> for all possible input combinations (for the sake of analysis, assume the **ON** resistance of **each** MOSFET (both P- and N-channel) is **10 $\Omega$**  and that its **OFF** resistance is **1 M $\Omega$**  (LOs 1-10 and 1-11).

A	B	V <sub>out</sub>
0V	0V	
0V	5V	
5V	0V	
5V	5V	

 

Describe what Raul has created:

11. A common question students have relates to *why* the P-channel device has to serve as a “pull-up” while the N-channel device has to serve as a “pull-down” (i.e., why can’t it be the “other way around”?). To convince yourself of this reality, try drawing a CMOS inverter “upside down” (with an N-channel device used as a pull-up and a P-channel device used as a pull-down) and analyze the circuit you have created (i.e., determine its  $V_i$ - $V_o$  characteristics). Describe your conclusion. (LO 1-10)



12. Assume two hypothetical logic families have the following D.C. characteristics:

**Logic Family “A”**

$V_{CC} = 5 \text{ V}$	$V_{OH} = 4.4 \text{ V}$	$V_{OL} = 0.40 \text{ V}$	$V_{IH} = 3.60 \text{ V}$	$V_{IL} = 1.60 \text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -4 \text{ mA}$	$I_{OL} = 4 \text{ mA}$	$I_{IH} = 0.4 \text{ } \mu\text{A}$	$I_{IL} = -0.4 \text{ } \mu\text{A}$

**Logic Family “B”**

$V_{CC} = 5 \text{ V}$	$V_{OH} = 3.3 \text{ V}$	$V_{OL} = 0.30 \text{ V}$	$V_{IH} = 2.60 \text{ V}$	$V_{IL} = 1.60 \text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -400 \text{ } \mu\text{A}$	$I_{OL} = 8 \text{ mA}$	$I_{IH} = 40 \text{ } \mu\text{A}$	$I_{IL} = -0.4 \text{ mA}$

(a) Calculate the following (*show work*):


- (LO 1-14)  $\text{DCNM}_{A \rightarrow B}$
- (LO 1-14)  $\text{DCNM}_{B \rightarrow A}$
- (LO 1-20) Practical Fanout  $A \rightarrow B$
- (LO 1-20) Practical Fanout  $B \rightarrow A$

(b) Draw the circuit and calculate the **value of the current limiting resistor** for a **Type “A”** gate driving an LED to the maximum brightness possible in a **current sourcing** configuration. Assume  $V_{LED}$  is 1.5V. (LO 1-21)


(c) Draw the circuit and calculate the **value of the current limiting resistor** for a **Type “B”** gate driving an LED to the maximum brightness possible in a **current sinking** configuration. Assume  $V_{LED}$  is 1.5V. (LO 1-21)

13. A particular CMOS microcontroller is designed to operate over a supply voltage range of **1.0 V** to **5.0 V** and at a maximum clock frequency of **80 MHz** (no minimum clock frequency is specified). The *maximum power dissipation* over this range of supply voltage and clock frequency is specified to be **500 milliwatts**.

 
- (a) Plot the relationship between *power dissipation* and *supply voltage* for this microcontroller (LO 1-29).



 - (b) Plot the relationship between *power dissipation* and *clock frequency* for this microcontroller (LO 1-28).



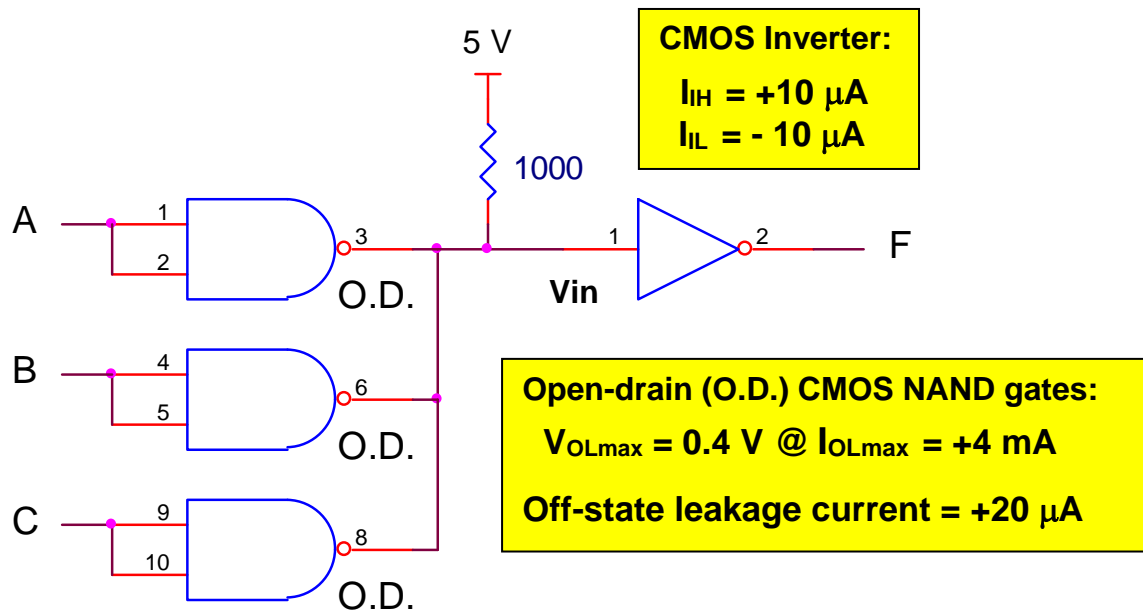14. Given the circuit, below, calculate  $V_{in}$  (the CMOS inverter input voltage) for each of the cases indicated along with the current **individually** sunk by each active open drain gate. *Show your calculations.* (LOs 1-34 and 1-35).



A	B	C	$V_{in}$ to Inverter	Current Sunk by Each Active O.D. Gate
0 V	0 V	0 V		
5 V	0 V	0 V		
5 V	5 V	0 V		
5 V	5 V	5 V		

15. Given the circuit, below, along with its Vi-Vo (input – output voltage) relationship, determine the following (show calculations where applicable):

- estimate the ON resistance of the O.D. NAND gate (LO 1-25)
- estimate the value of the pull-up resistor (LO 1-36)
- estimate the  $t_{TLH}$  of the O.D. NAND gate (LO 1-25)
- estimate the  $t_{THL}$  of the O.D. NAND gate (LO 1-25)
- estimate the  $t_{PHL}$  of the O.D. NAND gate (LO 1-23)
- estimate the  $t_{PLH}$  of the O.D. NAND gate (LO 1-23)

