

## Practice Homework Solution for Module 1

1. Unsigned base conversions (LO 1-1).

(a)  $(2C9E)_{16}$  to base 2

$(0010\ 1100\ 1001\ 1110)_2$

(b)  $(1101001)_2$  to base 10

$(105)_{10}$

(c)  $(1101001)_2$  to base 16

$(69)_{16}$

(d)  $(8576)_{10}$  to base 16

$(2180)_{16}$

(e)  $(A27F)_{16}$  to base 8

$(121177)_8$

## 2. Short answer questions over basic electronic components (LO 1-7).

- (a) Write two different formulas for OHM's LAW:

$$V=IR \quad V/I=R$$

- (b) Describe what a resistor does:

Limits current flow

- (c) Write two different formulas for calculating the power dissipation of a resistor:

$$V^2/R \quad I^2R$$

- (d) Describe what a diode does.

Restricts direction of current flow (from anode to cathode)

- (e) Describe what affects the brightness of a light emitting diode (LED):

Forward current

- (f) Describe what a capacitor does:

Stores charge

- (g) Describe a functional difference between a MOSFET and a BJT:

MOSFETs are voltage-controlled switches, BJTs are current-controlled

- (h) When a MOSFET is off, its drain-to-source impedance is on the order of:

$\approx 1,000,000$  ohms

- (i) When a MOSFET is on, its drain-to-source impedance is on the order of:

$\approx 10$  ohms

- (j) Describe a functional difference between an N-channel MOSFET and a P-channel MOSFET:

positive  $V_{gs}$  turns N-channel on, negative  $V_{gs}$  turns P-channel on

3. Prove DeMorgan's Law (T13) for  $n=3$  using perfect induction (LO 1-6).

X1	X2	X3	$X1 \cdot X2 \cdot X3$	$(X1 \cdot X2 \cdot X3)$	$(X1 \cdot X2 \cdot X3)'$	X1'	X2'	X3'	$X1' + X2' + X3'$
0	0	0	0	0	1	1	1	1	1
0	0	1	0	0	1	1	1	0	1
0	1	0	0	0	1	1	0	1	1
0	1	1	0	0	1	1	0	0	1
1	0	0	0	0	1	0	1	1	1
1	0	1	0	0	1	0	1	0	1
1	1	0	0	0	1	0	0	1	1
1	1	1	1	1	0	0	0	0	0

4. Prove the dual of the Covering theorem (T9<sup>D</sup>) using axioms and other theorems (LO 1-3).

$$(T9^D) \quad X \cdot (X + Y) = X$$


$$X \cdot (X + Y) = (X+0) \cdot (X + Y) \quad T1$$

$$= X + (Y \cdot 0) \quad T8^D$$

$$= X + 0 \quad T2^D$$

$$= X \quad T1$$

 5. Determine voltages  $V_A$ ,  $V_B$ ,  $V_C$ , and  $V_D$  if each resistor is  $100\Omega$  and the voltage source is 10 volts (LO 1-7).




$$V_A = 10 \times (75/275) = 2.73 \text{ V}$$


$$V_A = V_B + V_C + V_D \text{ where } V_B = V_C = V_D$$

$$V_B = V_C = V_D = 0.91 \text{ V}$$

 6. Using a total of **three** N-channel MOSFETs and **three** P-channel MOSFETs, draw a circuit schematic for a **two-input AND** gate. The gate inputs should be labeled A and B, and the gate output should be labeled F. Be sure to show the power (Vcc) and ground (GND) connections as well (LO 1-10).



 7. Using a total of **three** N-channel MOSFETs and **three** P-channel MOSFETs, draw a circuit schematic for a **three-input NOR** gate. The gate inputs should be labeled A, B and C, and the gate output should be labeled F. Be sure to show the power ( $V_{CC}$ ) and ground (GND) connections as well (LO 1-12).



8. Given that a (5-volt) CMOS gate's P-channel output pull-up has an "on" resistance of  $160\Omega$  and that its N-channel output pull-down has an "on" resistance of  $80\Omega$ :
- (a) If the desired  $V_{OHmin}$  is 4.4 volts and the desired  $V_{OLmax}$  is 0.4 volts, what are the gate's  $I_{OHmax}$  and  $I_{OLmax}$  ratings? (LO 1-19)

$$I_{OHmax} = -0.6/160 = -3.75 \text{ mA} \qquad I_{OLmax} = 0.4/80 = 5.0 \text{ mA}$$

- (b) If a DCNM of 1.2 volts is desired for this CMOS gate family, what do its  $V_{IHmin}$  and  $V_{ILmax}$  specifications need to be, based on the values given in part (a)? (LO 1-14)

$$V_{IHmin} = 4.4 - 1.2 = 3.2 \text{ V} \qquad V_{ILmax} = 0.4 + 1.2 = 1.6 \text{ V}$$

- (c) If the  $I_{IH}$  and  $I_{IL}$  specifications for gates in this family are +0.1 mA and -0.1 mA, respectively, what is the practical fan-out for circuits constructed using these gates, based on values calculated in part (a)? (LO 1-20)

**fanout =  $\min(3.75/0.1, 5.0/0.1) = 37.5$**

**Practical** fan-out = **37** (“floor” of 37.5)


- (d) Show how an LED (with forward voltage  $V_{LED} = 1.5 \text{ V}$ ) should be interfaced to gates in this family to obtain maximum brightness, and calculate the value of the current limiting resistor required along with its power dissipation. (LO 1-21)

Circuit and calculations:

$$V_R = 5 - 1.5 - 0.4 = 3.1V$$

$$I_R = 5 \text{ mA}$$


$$R = 3.1/.005 = 620 \, \Omega$$

 

Current limiting resistor =  $620\ \Omega$       Resistor power dissipation =  $15.5\ \text{mW}$

9. Given that the P-channel device in the circuit below has **ON** and **OFF** resistances of **80  $\Omega$**  and **2 M $\Omega$**  (respectively) and that the N-channel device has **ON** and **OFF** resistances of **60  $\Omega$**  and **3 M $\Omega$**  (respectively), complete the table listing the **output voltages** obtained for each input combination as well as the **power dissipation** (in *milliwatts*). Show your calculations (LOs 1-10 and 1-11).

A	B	P-ch	N-ch	Req (N+P)	V <sub>out</sub>	Power Dissip $V_{cc}^2/Req$
0V	0V	on	off	3,000,080 $\Omega$	4.99987	0.008333 mW
0V	5V	on	on	140 $\Omega$	2.14286	178.57 mW
5V	0V	off	off	5,000,000 $\Omega$	3.00000	0.005 mW
5V	5V	off	on	2,000,060 $\Omega$	0.0001499	0.0124996 mW

 


10. One of your best friends from another major, “Raul”, found some N- and P-channel MOSFETs in your “geek box” and wired them together as shown below. Help Raul figure out what he has created by determining V<sub>out</sub> for all possible input combinations (for the sake of analysis, assume the **ON** resistance of **each** MOSFET (both P- and N-channel) is **10  $\Omega$**  and that its **OFF** resistance is **1 M $\Omega$**  (LOs 1-10 and 1-11).


A	B	V <sub>out</sub>
0V	0V	4.99995
0V	5V	2.5000
5V	0V	2.5000
5V	5V	0.000049995

Describe what Raul has created:

“nothing useful”

 

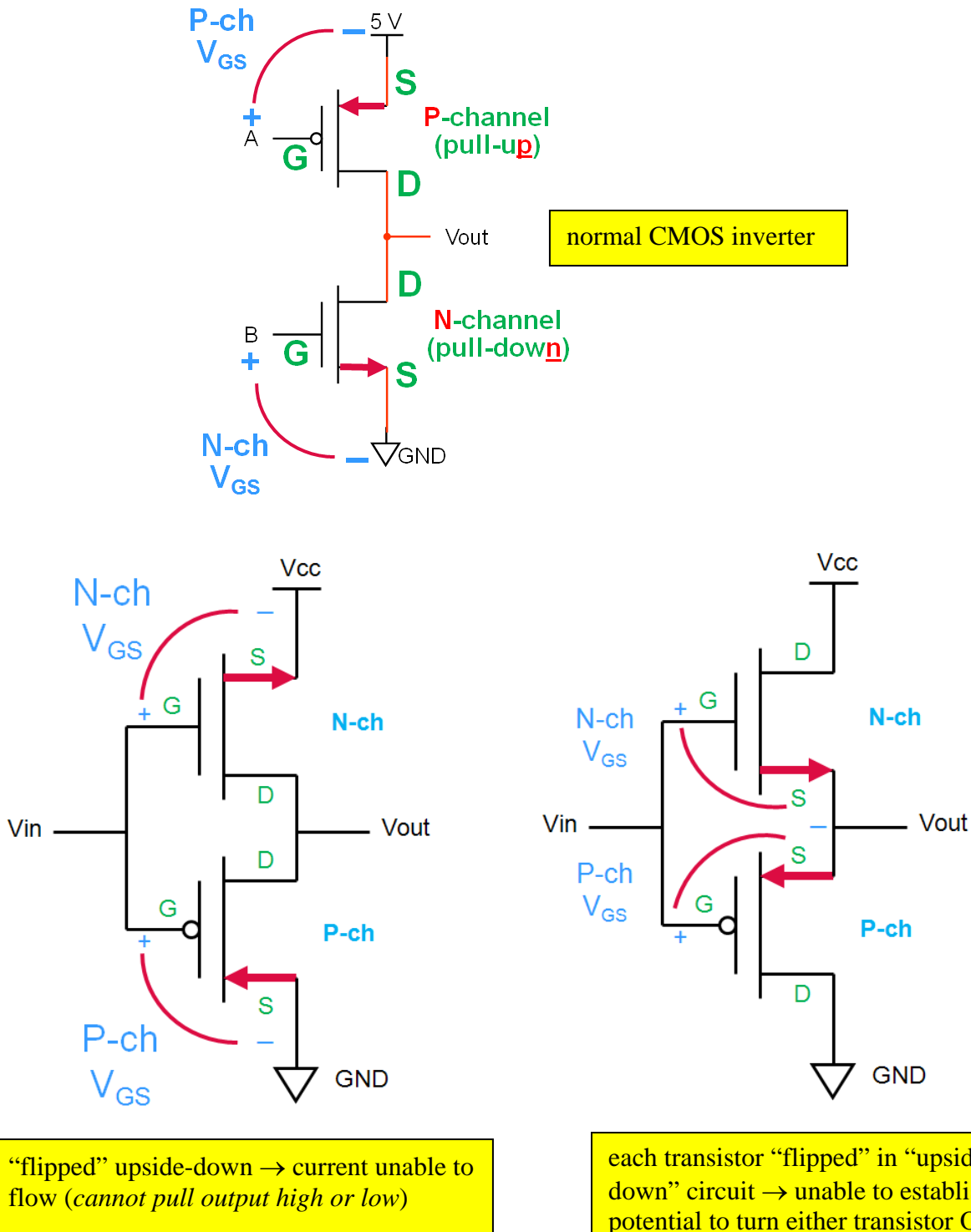11. A common question students have relates to **why** the P-channel device has to serve as a “pull-up” while the N-channel device has to serve as a “pull-down” (i.e., why can’t it be the “other way around”?). To convince yourself of this reality, try drawing a CMOS inverter “upside down” (with an N-channel device used as a pull-up and a P-channel device used as a pull-down) and analyze the circuit you have created (i.e., determine its  $V_i$ - $V_o$  characteristics). Describe your conclusion. (LO 1-10)





12. Assume two hypothetical logic families have the following D.C. characteristics:

### Logic Family “A”

$V_{CC} = 5\text{ V}$	$V_{OH} = 4.4\text{ V}$	$V_{OL} = 0.40\text{ V}$	$V_{IH} = 3.60\text{ V}$	$V_{IL} = 1.60\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -4\text{ mA}$	$I_{OL} = 4\text{ mA}$	$I_{IH} = 0.4\text{ }\mu\text{A}$	$I_{IL} = -0.4\text{ }\mu\text{A}$

### Logic Family “B”


$V_{CC} = 5\text{ V}$	$V_{OH} = 3.3\text{ V}$	$V_{OL} = 0.30\text{ V}$	$V_{IH} = 2.60\text{ V}$	$V_{IL} = 1.60\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -400\text{ }\mu\text{A}$	$I_{OL} = 8\text{ mA}$	$I_{IH} = 40\text{ }\mu\text{A}$	$I_{IL} = -0.4\text{ mA}$

(a) Calculate the following (*show work*):

- (LO 1-14)  $DCNM_{A \rightarrow B} = \min(4.4 - 2.6, 1.6 - 0.4) = 1.2\text{ V}$
- (LO 1-14)  $DCNM_{B \rightarrow A} = \min(3.3 - 3.6, 1.6 - 0.3) = -0.3\text{ V}$
- (LO 1-20) Practical Fanout  $_{A \rightarrow B} = \min(4/0.04, 4/0.4) = 10$
- (LO 1-20) Practical Fanout  $_{B \rightarrow A} = \min(400/0.4, 8/0.0004) = 1000$


(b) Draw the circuit and calculate the **value of the current limiting resistor** for a **Type “A”** gate driving an LED to the maximum brightness possible in a **current sourcing** configuration. Assume  $V_{LED}$  is 1.5V. (LO 1-21)

$$R = 2.9/0.004 = 725\text{ }\Omega$$

 


(c) Draw the circuit and calculate the **value of the current limiting resistor** for a **Type “B”** gate driving an LED to the maximum brightness possible in a **current sinking** configuration. Assume  $V_{LED}$  is 1.5V. (LO 1-21)

$$R = 3.2/0.008 = 400\text{ }\Omega$$

 


13. A particular CMOS microcontroller is designed to operate over a supply voltage range of **1.0 V** to **5.0 V** and at a maximum clock frequency of **80 MHz** (no minimum clock frequency is specified). The *maximum power dissipation* over this range of supply voltage and clock frequency is specified to be **500 milliwatts**.

 
- (a) Plot the relationship between *power dissipation* and *supply voltage* for this microcontroller (LO 1-29).



 - (b) Plot the relationship between *power dissipation* and *clock frequency* for this microcontroller (LO 1-28).



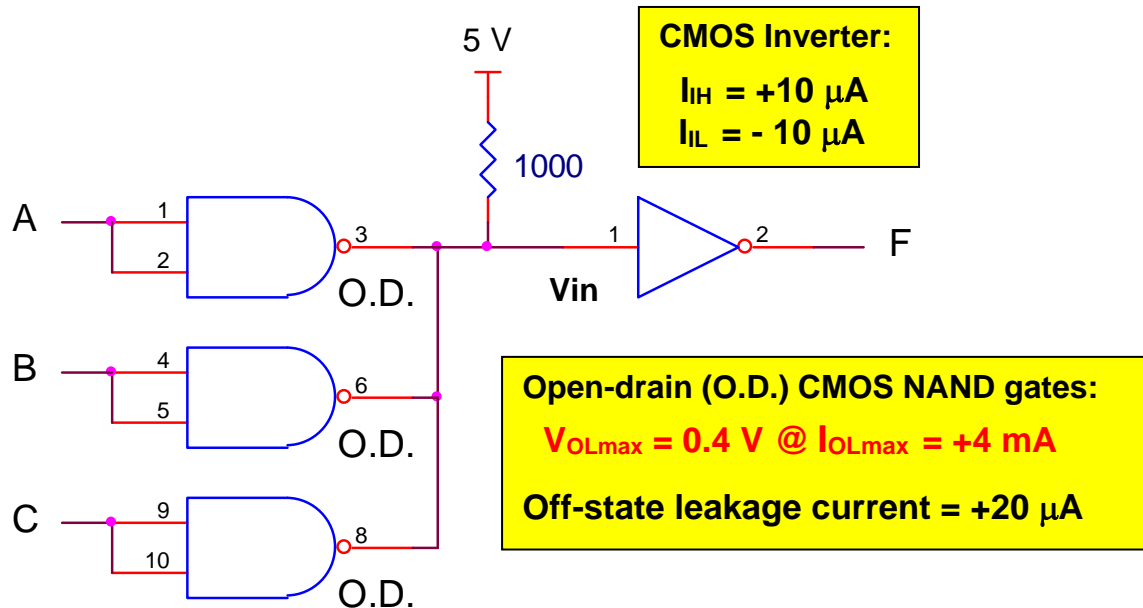14. Given the circuit, below, calculate  $V_{in}$  (the CMOS inverter input voltage) for each of the cases indicated along with the current *individually* sunk by each active open drain gate. *Show your calculations.* (LOs 1-34 and 1-35).



**Key:** ON resistance of each OD gate is  $0.4/0.004 = 100 \Omega$

A	B	C	Ron Total	$V_{in}$ to Inverter	Current Sunk by Each Active O.D. Gate
0 V	0 V	0 V	-	$5 - (0.00007 \times 1000) = 4.93 V$	(20 $\mu A$ leakage)
5 V	0 V	0 V	1100	$5 \times 100 / 1100 = 0.4545 V$	4.545 mA
5 V	5 V	0 V	1050	$5 \times 50 / 1050 = 0.2381 V$	2.381 mA
5 V	5 V	5 V	1033	$5 \times 33 / 1033 = 0.1597 V$	1.618 mA

15. Given the circuit, below, along with its Vi-Vo (input – output voltage) relationship, determine the following (show calculations where applicable):

- (a) estimate the ON resistance of the O.D. NAND gate (LO 1-25)

$$\text{fall time} = 10 \text{ ns} = R_{\text{on}} \times 100 \text{ pF} \rightarrow R_{\text{on}} = 100\Omega$$

- (b) estimate the value of the pull-up resistor (LO 1-36)

$$\text{rise time} = 100 \text{ ns} = R_{\text{pullup}} \times 100 \text{ pF} \rightarrow R_{\text{pullup}} = 1000\Omega$$

- (c) estimate the  $t_{\text{TLH}}$  of the O.D. NAND gate (LO 1-25)

$$\text{rise time} = 100 \text{ ns}$$

- (d) estimate the  $t_{\text{THL}}$  of the O.D. NAND gate (LO 1-25)

$$\text{fall time} = 10 \text{ ns}$$

- (e) estimate the  $t_{\text{PHL}}$  of the O.D. NAND gate (LO 1-23)

$$\text{fall propagation delay} = 10 \text{ ns}$$

- (f) estimate the  $t_{\text{PLH}}$  of the O.D. NAND gate (LO 1-23)

$$\text{rise propagation delay} = 40 \text{ ns}$$

