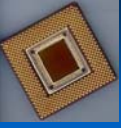


Purdue IM: PACT* Spring 2019 Edition
 *Instruction Matters: Purdue Academic Course Transformation


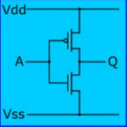


Introduction to Digital System Design

Module 1 Switching Algebra and CMOS Logic Gates

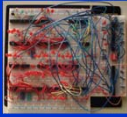

Glossary of Common Terms

- **INTEGRATED CIRCUIT (IC or "CHIP")** – a collection of logic gates and/or other electronic circuits fabricated on a single silicon die
- **CMOS** – a silicon chip fabrication technology based on use of complementary pairs of NMOS and PMOS field effect transistors (MOSFETs)



Glossary of Common Terms

- **DISCRETE LOGIC** – a circuit constructed using small-scale integrated (SSI) and medium-scale integrated (MSI) logic devices (NAND gates, decoders, multiplexers, etc.)
- **PROGRAMMABLE LOGIC DEVICE (PLD)** – an integrated circuit onto which a generic logic circuit can be programmed (and subsequently erased and re-programmed)


Glossary of Common Terms

- **COMPUTER** – a digital device that sequentially executes a stored program (or, a device that stores and manipulates state, where "state" = "information")
- **MICROPROCESSOR** – single-chip embodiment of the major functional blocks of a computer



Glossary of Common Terms

- **MICROCONTROLLER** – a complete computer on a chip, including memory and various integrated peripherals (analog-to-digital conversion, serial communications, pulse-width modulation, timers, network interface)
- **PRINTED CIRCUIT BOARD (PCB)** – fiberglass reinforced epoxy substrate with etched copper circuitry (typically in multiple layers) used to create virtually all electronic devices




Glossary of Common Terms

- **SOCIALLY REDEEMING** – something that has inherent value (like studying digital systems design)
- **DIGIJOCK(ETTE)** – a person who enjoys learning about digital systems

Module 1

- **Learning Outcome:** "An ability to design and analyze CMOS logic circuits"
 - Number Systems
 - Switching Algebra
 - Basic Electronic Components and Concepts
 - Logic Signals and CMOS Logic Circuits
 - Logic Levels and Noise Margins
 - Current Sourcing and Sinking
 - Transition Time and Propagation Delay
 - Power Consumption and Decoupling
 - Schmitt Triggers and Transmission Gates
 - Three-State and Open-Drain Outputs

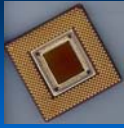

Purdue IM: PACT* Spring 2019 Edition
*Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 1-A Number Systems

Reading Assignment:
DDPP 4th Ed. pp. 25-31, 5th Ed. pp. 35-44

Learning Objective:

- Convert numbers from one base (radix) to another

Outline:

- Unsigned Integer Base Conversion
 - Base R to Base 10
 - Base 10 to Base R
- Shortcut for Conversion Among Powers of 2

Unsigned Integer Base Conversion

- Numbers represent a fundamental unit of **encoded information** – knowledge of the encoding process used is needed to “decode” and/or convert them from one base (or radix) to another
- A **table of correspondence** is a useful tool for comparing numbers in different bases
- The following notation will be used:
$$(d_3d_2d_1d_0)_R = (N)_R = \text{number in base } R$$

$$(c_3c_2c_1c_0)_R = (N)_{10} = \text{number in base } 10$$

Note that the **c**'s represent the **converted corresponding digits**, base 10

Table of Correspondence - Unsigned Integers

	N ₂	N ₃	N ₄	N ₅	N ₆	N ₇	N ₈	N ₉	N ₁₀	N ₁₆
0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	1	1	1	1	1	1
10	2	2	2	2	2	2	2	2	2	2
11	10	3	3	3	3	3	3	3	3	3
100	11	10	4	4	4	4	4	4	4	4
101	12	11	10	5	5	5	5	5	5	5
110	20	12	11	10	6	6	6	6	6	6
111	21	13	12	11	10	7	7	7	7	7
1000	22	20	13	12	11	10	8	8	8	8
1001	100	21	14	13	12	11	10	9	9	9
1010	101	22	20	14	13	12	11	10	A	A
1011	102	23	21	15	14	13	12	11	B	B
1100	110	30	22	20	15	14	13	12	C	C
1101	111	31	23	21	16	15	14	13	D	D
1110	112	32	24	22	20	16	15	14	E	E
1111	120	33	30	23	21	17	16	15	F	F
10000	121	100	31	24	22	20	17	16	10	10

Table of Correspondence - Unsigned Integers

	N ₂	N ₃	N ₄	N ₅	N ₆	N ₇	N ₈	N ₉	N ₁₀	N ₁₆
0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	1	1	1	1	1	1
10	2	2	2	2	2	2	2	2	2	2
11	10	3	3	3	3	3	3	3	3	3
100	11	10	4	4	4	4	4	4	4	4
101	12	11	10	5	5	5	5	5	5	5
110	20	12	11	10	6	6	6	6	6	6
111	21	13	12	11	10	7	7	7	7	7
1000	22	20	13	12	11	10	8	8	8	8
1001	100	21	14	13	12	11	10	9	9	9
1010	101	22	20	14	13	12	11	10	A	A
1011	102	23	21	15	14	13	12	11	B	B
1100	110	30	22	20	15	14	13	12	C	C
1101	111	31	23	21	16	15	14	13	D	D
1110	112	32	24	22	20	16	15	14	E	E
1111	120	33	30	23	21	17	16	15	F	F
10000	121	100	31	24	22	20	17	16	10	10

Table of Correspondence - Unsigned Integers

	N ₂	N ₃	N ₄	N ₅	N ₆	N ₇	N ₈	N ₉	N ₁₀	N ₁₆
0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	1	1	1	1	1	1
10	2	2	2	2	2	2	2	2	2	2
11	10	3	3	3	3	3	3	3	3	3
100	11	10	4	4	4	4	4	4	4	4
101	12	11	10	5	5	5	5	5	5	5
110	20	12	11	10	6	6	6	6	6	6
111	21	13	12	11	10	7	7	7	7	7
1000	22	20	13	12	11	10	8	8	8	8
1001	100	21	14	13	12	11	10	9	9	9
1010	101	22	20	14	13	12	11	10	A	A
1011	102	23	21	15	14	13	12	11	B	B
1100	110	30	22	20	15	14	13	12	C	C
1101	111	31	23	21	16	15	14	13	D	D
1110	112	32	24	22	20	16	15	14	E	E
1111	120	33	30	23	21	17	16	15	F	F
10000	121	100	31	24	22	20	17	16	10	10

Unsigned Integer Base Conversion

- IMPORTANT:** The conversion methods described here are only applicable to *unsigned* (or, "positive") numbers
- ALSO NOTE:** Since the numbers we are dealing with are unsigned, *leading zeroes* have "no social significance" (i.e., they can be *added or removed* without changing the value of the number)

Conversion of Integers: Base R→10

- Method:** Iterative Multiply and Add
 - based on the fact that a number can be expressed in nested form, as follows:

$$(d_3d_2d_1d_0)_R = (N)_{10}$$

$$= c_3 \times R^3 + c_2 \times R^2 + c_1 \times R^1 + c_0 \times R^0$$

$$= (((c_3 \times R + c_2) \times R + c_1) \times R + c_0)$$
 - the expression evaluation proceeds from the inner-most level of parenthesis to the outer-most level

Conversion of Integers: Base R→10

- Example:** Convert (4352)₈ to base 10

$$4 \times 8 + 3 = 35$$

$$35 \times 8 + 5 = 285$$

$$285 \times 8 + 2 = 2282$$
 Therefore, (4352)₈ = (2282)₁₀

Conversion of Integers: Base R→10

- Example:** Convert (01101011)₂ to base 10

$$\begin{array}{r} \underline{0} \times 2 + \underline{1} = \underline{1} \\ \underline{1} \times 2 + \underline{1} = \underline{3} \\ \underline{3} \times 2 + \underline{0} = \underline{6} \\ \underline{6} \times 2 + \underline{1} = \underline{13} \\ \underline{13} \times 2 + \underline{0} = \underline{26} \\ \underline{26} \times 2 + \underline{1} = \underline{53} \\ \underline{53} \times 2 + \underline{1} = \underline{107} \end{array}$$
 Therefore, (01101011)₂ = (107)₁₀

Conversion of Integers: Base 10→R

- Method:** Iterative Division
 - based on an iterative division of the number by the radix (base) to which it is being converted
 - the *remainders* of each division become the digits of the converted number
 - a *quotient of zero* indicates the conversion is complete

Conversion of Integers: Base 10→R

- Example: Convert $(727)_{10}$ to base 8

$\begin{array}{r} 90 \\ 8 \overline{)727} \\ -720 \\ \hline 7 \end{array}$	$\begin{array}{r} 11 \\ 8 \overline{)90} \\ -88 \\ \hline 2 \end{array}$	$\begin{array}{r} 1 \\ 8 \overline{)11} \\ -8 \\ \hline 3 \end{array}$	$\begin{array}{r} 0 \\ 8 \overline{)1} \\ -0 \\ \hline 1 \end{array}$
--	--	--	---

Therefore, $(727)_{10} = (1327)_8$

Conversion of Integers: Base 10→R

- Example: Convert $(2623)_{10}$ to base 16

$\begin{array}{r} 163 \\ 16 \overline{)2623} \\ -2608 \\ \hline 15 \end{array}$	$\begin{array}{r} 10 \\ 16 \overline{)163} \\ -160 \\ \hline 3 \end{array}$	$\begin{array}{r} 0 \\ 16 \overline{)10} \\ -0 \\ \hline 10 \end{array}$
---	---	--

Therefore, $(2623)_{10} = (A3F)_{16}$

Short Cut for Conversion Among Powers of 2

- Method: Size $\log_2 R$ Groupings
 - when converting a number from base "A" to base "B", where A and B are powers of 2 (e.g., 2, 4, 8, and 16), a "short cut" can be used
 - an *n-digit binary number* can be written for each *base A* digit in the original number, where $n = \log_2 A$
 - starting at the *least significant position*, the converted binary digits can be *regrouped* into *m-digit* binary numbers, where $m = \log_2 B$

Short Cut for Conversion Among Powers of 2

- Example: Convert $(136)_8$ to base 2 and base 16

1	3	6
001	011	110
0101		1110
5		E

Therefore, $(136)_8 = (1011110)_2 = (5E)_{16}$

Short Cut for Conversion Among Powers of 2

- Example: Convert $(110101)_2$ to bases 8 and 16

6	5
110	101
110101	
0011	0101
3	5

Therefore, $(110101)_2 = (65)_8 = (35)_{16}$

Purdue IM:PACT* Spring 2019 Edition
 *Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 1-B Switching Algebra

Reading Assignment:
DDPP 4th Ed. pp. 183-199, 5th Ed. pp. 89-105

Learning Objectives:

- Define a binary variable
- Identify the theorems and postulates of switching algebra
- Describe the principle of duality
- Describe how to form a complement function
- Prove the equivalence of two Boolean expressions using perfect induction

Outline

- Overview
- Basic logic gates
- Axioms
- Duality
- Theorems
 - Single-Variable
 - Two- and Three-Variable
 - n-Variable

Overview

- Formal analysis techniques for digital circuits are based on a two-valued algebraic system called **Boolean algebra** (named after George Boole, who invented it in 1854)
- Claude Shannon (1938) showed how to adapt Boolean algebra to analyze and describe the behavior of circuits built from relays
- In Shannon's **switching algebra**, the condition of a relay contact (**open/closed**) is represented by a variable **X** (equal to 0/1)
- In today's logic technologies, these values correspond to **voltage LOW** or **HIGH**

Definitions

- **Definition:** The **axioms** (or **postulates**) of a mathematical system are a **minimal set of basic definitions** that we assume to be true, from which all other information about the system can be derived
- **Notation:** A **prime** (') will be used to denote an inverter's function (i.e., the **complement** of a logic signal) – note that **prime** is an **algebraic operator**, that **X'** is an **expression**, and that **Y=X'** is an **equation**

X' can be read as X prime, NOT X, or X bar

Example

Given the truth table for F(X,Y,Z), determine the truth table for the **COMPLEMENT** function, F'(X,Y,Z)

X	Y	Z	F(X,Y,Z)
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Example

Given the truth table for F(X,Y,Z), determine the truth table for the **COMPLEMENT** function, F'(X,Y,Z)

X	Y	Z	F(X,Y,Z)	X	Y	Z	F'(X,Y,Z)
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	1
0	1	0	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	1	1	0	0
1	0	1	0	1	0	1	1
1	1	0	1	1	1	0	0
1	1	1	1	1	1	1	0

Definitions

- **Definition:** A *binary variable*, X , is a two-valued quantity such that:
 - if $X \neq 1$, then $X = 0$
 - if $X \neq 0$, then $X = 1$
- **Definition:** The function of a 2-input **AND** gate is called *logical multiplication* and is symbolized by a *multiplication dot* (\bullet)
- **Definition:** The function of a 2-input **OR** gate is called *logical addition* and is symbolized algebraically by a *plus sign* ($+$)
- **Convention:** Multiplication (AND) has *implied precedence* over addition (OR)

Example: $W \bullet X + Y \bullet Z = (W \bullet X) + (Y \bullet Z)$

Axioms

(A1) $X = 0$ if $X \neq 1$ (A1^D) $X = 1$ if $X \neq 0$
(A2) If $X = 0$, then $X' = 1$ (A2^D) If $X = 1$, then $X' = 0$
(A3) $0 \bullet 0 = 0$ (A3^D) $1 + 1 = 1$
(A4) $1 \bullet 1 = 1$ (A4^D) $0 + 0 = 0$
(A5) $0 \bullet 1 = 1 \bullet 0 = 0$ (A5^D) $1 + 0 = 0 + 1 = 1$

Note: The second axiom in each pair is referred to as the *dual* of the first one (and vice versa)

Also Note: These 5 pairs of axioms completely define switching algebra

Duality

- **Definition:** The *dual* of an expression is formed through the *simultaneous interchange* of the operators " \bullet " and " $+$ " and the elements "0" and "1"
- **Important Principle:** If two Boolean expressions can be proven to be equivalent using a given sequence of axioms or theorems, then the *dual expressions* may be proven to be equivalent by simply applying the sequence of *dual* axioms or theorems

Example

Given the truth table for $F(X,Y,Z)$, determine the truth table for the DUAL function, $F^D(X,Y,Z)$

X	Y	Z	F(X,Y,Z)
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Example

Given the truth table for $F(X,Y,Z)$, determine the truth table for the DUAL function, $F^D(X,Y,Z)$

X	Y	Z	F(X,Y,Z)	X	Y	Z	F ^D (X,Y,Z)
0	0	0	1	1	1	1	0
0	0	1	0	1	1	0	1
0	1	0	0	1	0	1	1
0	1	1	1	1	0	0	0
1	0	0	0	0	1	1	1
1	0	1	0	0	1	0	1
1	1	0	1	0	0	1	0
1	1	1	1	0	0	0	0

Example

Given the truth table for $F(X,Y,Z)$, determine the truth table for the DUAL function, $F^D(X,Y,Z)$

X	Y	Z	F(X,Y,Z)	X	Y	Z	F ^D (X,Y,Z)
0	0	0	1	1	1	1	0
0	0	1	0	1	1	0	1
0	1	0	0	1	0	1	1
0	1	1	1	1	0	0	0
1	0	0	0	0	1	1	1
1	0	1	0	0	1	0	1
1	1	0	1	0	0	1	0
1	1	1	1	0	0	0	0

Note: The original truth table and the dual truth table are shown side-by-side with a large red 'X' over them, indicating that the dual function is not simply the complement of the original function.


Basic Logic Gates

- An **AND gate** produces a 1 output if and only if all of its inputs are 1
- An **OR gate** produces a 1 output if one or more of its inputs are 1
- A **NOT gate** (usually called an **inverter**) produces an output value that is the opposite of its input value



Other Basic Gates (More Commonly Used)

 - Other "basic gates" are possible:
 - a **NAND ("Not AND") gate** produces the *opposite* of an **AND** gate's output
 - a **NOR ("Not OR") gate** produces the *opposite* of an **OR** gate's output



NAND / NOR gates are easier to make (require fewer transistors) than AND / OR gates

- **Logical completeness:** "anything digital" can be built solely using **AND**, **OR**, and **NOT** gates -or- solely using either **only NAND** or **only NOR** gates

Theorems

- **Definition:** Switching algebra *theorems* are statements, known always to be true, that allow manipulation of algebraic expressions
- **Definition:** A technique called **perfect induction** can be used to prove switching algebra theorems ("perfect" implies the use of *all possible combinations* of the values of the variables – thus, it is an *exhaustive* type of proof)



Single-Variable Theorems

- (T1) $X + 0 = X$ (T1^D) $X \cdot 1 = X$ *Identities*
- (T2) $X + 1 = 1$ (T2^D) $X \cdot 0 = 0$ *Null elements*
- (T3) $X + X = X$ (T3^D) $X \cdot X = X$ *Idempotency*
- (T4) $(X')' = X$ *Involution*
- (T5) $X + X' = 1$ (T5^D) $X \cdot X' = 0$ *Complements*

Two- and Three-Variable Theorems

- (T6) $X + Y = Y + X$ *Commutivity*
- (T6^D) $X \cdot Y = Y \cdot X$
- (T7) $(X + Y) + Z = X + (Y + Z)$ *Associativity*
- (T7^D) $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$
- (T8) $X \cdot Y + X \cdot Z = X \cdot (Y + Z)$ *Distributivity*
- (T8^D) $(X + Y) \cdot (X + Z) = X + Y \cdot Z$
- (T9) $X + X \cdot Y = X$ *Covering*
- (T9^D) $X \cdot (X + Y) = X$

Two- and Three-Variable Theorems

Example: Proof of T8^D using perfect induction

X	Y	Z	Y•Z	X+Y•Z	X+Y	X+Z	(X+Y)•(X+Z)
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1
				r.h.s.			l.h.s.

Two- and Three-Variable Theorems

Example: Proof of T9 using other theorems

$$\begin{aligned}
 (T9) \quad X + X \cdot Y &= X \cdot 1 + X \cdot Y && (T1^D - \text{identities}) \\
 &= X \cdot (1 + Y) && (T8 - \text{distributivity}) \\
 &= X \cdot 1 && (T2 - \text{null elements}) \\
 &= X && (T1^D - \text{identities})
 \end{aligned}$$

Two- and Three-Variable Theorems

(T10) $X \cdot Y + X \cdot Y' = X$ *Combining*
 (T10^D) $(X + Y) \cdot (X + Y') = X$

(T11) $X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$ *Consensus*
 (T11^D) $(X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$

Note: In all theorems, it is possible to replace each variable with an arbitrary logic expression

Two- and Three-Variable Theorems

Example: Using only the axioms and theorems described thus far, verify the following equivalence expression:

$$X \cdot Y + Y \cdot Z + X' \cdot Z = X \cdot Y + X' \cdot Z$$

Main "Tricks":

- Multiply "offending term" by $(X + X')$
- Factor out common terms

Two- and Three-Variable Theorems

Example: Using only the axioms and theorems described thus far, verify the following equivalence expression:

$$\begin{aligned}
 X \cdot Y + Y \cdot Z + X' \cdot Z &= X \cdot Y + Y \cdot Z \cdot (X + X') + X' \cdot Z \\
 &= X \cdot Y + X \cdot Y \cdot Z + X' \cdot Y \cdot Z + X' \cdot Z \\
 &= X \cdot Y \cdot (1 + Z) + X' \cdot Z \cdot (Y + 1) \\
 &= X \cdot Y + X' \cdot Z
 \end{aligned}$$

n-Variable Theorems

(T12) $X + X + \dots + X = X$ *Generalized Idempotency*
 (T12^D) $X \cdot X \cdot \dots \cdot X = X$

(T13) $(X1 \cdot X2 \cdot \dots \cdot Xn)' = X1' + X2' + \dots + Xn'$ *DeMorgan's Law*
 (T13^D) $(X1 + X2 + \dots + Xn)' = X1' \cdot X2' \cdot \dots \cdot Xn'$

(T14) $[F(X1, X2, \dots, Xn)]' = F^D(X1', X2', \dots, Xn')$ *Generalized DeMorgan's Law*

Note: Based on T14, the complement of a function or an expression can be found by taking its dual and complementing all its variables

Equivalent Circuits According to DeMorgan's Theorem

(X · Y)' = X' + Y' (T13)

Observation: A logically equivalent circuit can be formed by taking the dual of the operator(s) and complementing all the inputs and outputs

Graphical Application of DeMorgan's Law

- Determine the function implemented by a *two-level* NAND-NOR circuit

Level 1 Level 2

Graphical Application of DeMorgan's Law

- Determine the function implemented by a *two-level* NAND-NOR circuit

Equivalent symbol for NOR gate

Graphical Application of DeMorgan's Law

- Determine the function implemented by a *two-level* NAND-NOR circuit

Apply involution

Apply associativity

$F(A, B, C, D) = A \bullet B \bullet C \bullet D$

Name the Switching Algebra Axiom or Theorem

Null Elements (T2^D) $X \bullet 0 = 0$

Complements (T5) $X' + X = 1$

Complements (T5^D) $X' \bullet X = 0$

(Generalized) Idempotency (T3 or T12) $X + X + X = X$

Involution (T4) $(X')' = X$

Name the Switching Algebra Axiom or Theorem

Covering (T9^D) $X \bullet (X + Y) = X$

Distributivity (T8) $(X + Y) \bullet (X + Z) = X + Y \bullet Z$

Associativity (T7) $(X + Y) + Z = X + (Y + Z)$

Commutivity (T6^D) $X \bullet Y \bullet Z = Z \bullet X \bullet Y$

Example – Proof Using Perfect Induction

T9^D $X \bullet (X + Y) = X$

X	Y	(X + Y)	X • (X + Y)	X
0	0	0	0	0
0	1	1	0	0
1	0	1	1	1
1	1	1	1	1

Example – Proof Using Other Theorems

$T9^D \quad X \bullet (X + Y) = X$

$X \bullet (X + Y)$	$= X \bullet X + X \bullet Y$	(T8)
	$= X + X \bullet Y$	(T3 ^D)
	$= X \bullet (1 + Y)$	(T8)
	$= X \bullet (1)$	(T2)
	$= X$	(T1 ^D)

Clicker Quiz

1. The expression $(X \bullet Y) \bullet Z = X \bullet (Y \bullet Z)$ is an example of:

- A. commutativity
- B. associativity
- C. distributivity
- D. consensus
- E. none of the above

2. The expression $X + Y + Z = Y + Z + X$ is an example of:


- A. commutativity
- B. associativity
- C. distributivity
- D. consensus
- E. none of the above

3. The expression $(X+Y) \bullet (X'+Z) \bullet (Y+Z) = (X+Y) \bullet (X'+Z)$ is an example of:

- A. commutativity
- B. associativity
- C. distributivity
- D. consensus
- E. none of the above

4. The expression $(X+Y) \cdot (X+Z) = X + Y \cdot Z$ is an example of:

- A. commutativity
- B. associativity
- C. distributivity
- D. consensus
- E. none of the above

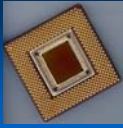

Purdue IM: PACT* Spring 2019 Edition
 *Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 1-C Basic Electronic Components and Concepts

Reading Assignment:

Appendix B: Electrical Circuits Review (on-line supplement)


Learning Objective:

- Describe the function and utility of basic electronic components: resistors, capacitors, diodes, transistors

Outline:


- Voltage and current
- Resistors
- Power dissipation
- Capacitors
- Diodes
- Transistors

Voltage and Current




- VOLTAGE (V)** – difference in electrical potential, expressed in *volts*
- CURRENT (I)** – the flow of charge in a conductor between two points having a difference in potential, expressed in *amperes* (amps)
- Waterfall analogy – *voltage* is proportional to *height* of waterfall, *current* is proportional to *flow* of waterfall

Resistors




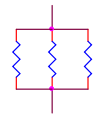
- RESISTOR** – a device that limits the amount of current flowing through a circuit, measured in *ohms* (Ω)
- Resistance is also referred to as *impedance*
- The inverse of impedance is *admittance*
- Fundamental relationship
 - the voltage drop (V_R) across a resistor is equal to the product of the current flowing through it (I_R) and the value of the resistance (R) \Rightarrow called *Ohm's Law*

$V_R = I_R \times R$




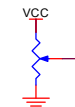
Resistors



- Fundamental relationships
 - Resistors in series
 

$R_T = R_1 + R_2 + R_3$
 - Resistors in parallel
 

$1/R_T = 1/R_1 + 1/R_2 + 1/R_3$


Potentiometer (Variable Resistor)

- Can either act as a variable impedance or as a voltage divider
 - variable impedance
 
 - variable voltage (voltage divider)
 

Voltage and Current

 - Kirchhoff's Voltage Law (KVL) – voltage around a loop sums to zero (based on conservation of energy)




$$V_A + V_B + V_C + V_D = 0$$

67

Voltage and Current

 - Kirchhoff's Current Law (KCL) – sum of currents at any node is zero (based on conservation of electric charge)



$$I_A + I_B + I_C = 0$$

68

Power Dissipation

- POWER (W) – amount of energy, expressed in *watts*, typically calculated as the product of the *voltage* drop across a device and the *current* flowing through it
- Multiple ways to calculate:

$$-P = V \times I$$

$$-P = V^2 / R$$

$$-P = I^2 \times R$$

Based on Ohm's law substitutions:

$$I = V / R$$

$$V = I \times R$$

69

Capacitors

- CAPACITOR – a device that stores an electric charge, measured in *farads* (F)
- Fundamental relationships
 - a resistor-capacitor (RC) network charges and discharges exponentially
 - the voltage across a capacitor cannot change instantaneously
 - the product of R and C is called the *RC time constant*



$$V_C = V_{IN} \times (1 - e^{-t/RC})$$



70


Capacitors

- Fundamental relationships
 - Capacitors in series



$$1/C_T = 1/C_1 + 1/C_2 + 1/C_3$$

- Capacitors in parallel

 


$$C_T = C_1 + C_2 + C_3$$

71

Diodes

 - DIODE – a device that *restricts* the flow of current to a *single direction* (from its *anode* to its *cathode*)



- Fundamental relationships

- a diode through which current is flowing (because the voltage at the anode is greater than at the cathode) is *forward biased*
- if current is not flowing through a diode (because the voltage at the cathode is greater than at the anode), the diode is *reverse biased*

72


Light Emitting Diodes

- LIGHT EMITTING DIODE (LED) – a diode that emits *visible* red/yellow/green/blue/white) or *invisible* (infrared) light when forward biased
- Fundamental relationships
 - the brightness of an LED is proportional to the amount of current flowing through it (called the *forward current*)
 - a *resistor* is placed in series with an LED to limit the amount of current flowing through it
 - the voltage drop across an LED when it is forward biased is called the *forward voltage* (*different color LEDs have different V_f*)





Transistors

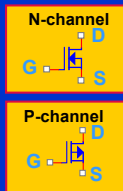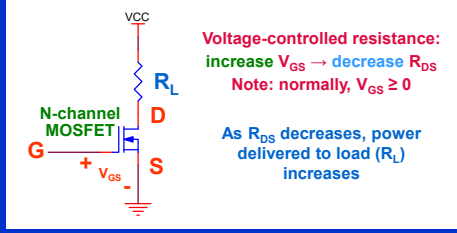- FIELD EFFECT TRANSISTOR (MOSFET)
 - a 3-terminal device (G-gate, S-source, D-drain) that provides a *voltage-controlled impedance*
- Two basic types
 - N-channel: *high* potential on G (gate) relative to S (source) causes transistor to *turn on* (low impedance between S and D terminals)
 - P-channel: *low* potential on G (gate) relative to S (source) causes transistor to *turn on*




Transistors

- A MOSFET can be used as a *voltage-controlled switch* for a DC load



Voltage-controlled resistance:
 increase $V_{GS} \rightarrow$ decrease R_{DS}
 Note: normally, $V_{GS} \geq 0$

As R_{DS} decreases, power delivered to load (R_L) increases

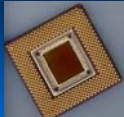

Purdue IM:PACT* Spring 2019 Edition
 *Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 1-D

Logic Signals and CMOS Logic Circuits

Reading Assignment:

DDPP 4th Ed. pp. 79-96, 141-148; 5th Ed. pp. 8-25, 790-796

Learning Objectives:

- Define the switching threshold of a logic gate and identify the voltage ranges typically associated with a “logic high” and a “logic low”
- Define assertion level and describe the difference between a positive logic convention and a negative logic convention
- Describe the operation of basic logic gates (NOT, NAND, NOR) constructed using N- and P-channel MOSFETs and draw their circuit diagrams
- Define “fighting” among gate outputs wired together and describe its consequence
- Define logic gate fan-in and describe the basis for its practical limit

Outline

- Logic signals and assertion levels
- CMOS logic circuits
 - Inverter (NOT)
 - NAND
 - NOR
- Fighting
- Fan-in

Logic Signals

- A logic value, 0 or 1, is often referred to as a **binary digit** or **bit**
- The words “LOW” and “HIGH” are often used in place of “0” and “1” to refer to **logic signals**
 - **LOW** - a signal in the range of “lower” voltages (e.g., 0 - 1.5 volts for 5V CMOS logic), which is interpreted as a logic 0
 - **HIGH** - a signal in the range of “higher” voltages (e.g., 3.5 - 5.0 volts for 5V CMOS logic), which is interpreted as a logic 1

Positive Logic Convention

- The **assignment** of 0 and 1 to **LOW** and **HIGH**, respectively, is referred to as a **positive logic convention** (or simply “positive logic”)
 - a positive logic signal that is **asserted** is in the **HIGH** state, and is therefore referred to as an “**active high**” signal
 - a positive logic signal that is **negated** is in the **LOW** state

Negative Logic Convention

- The **opposite assignment** (1 to **LOW** and 0 to **HIGH**) is referred to as a **negative logic convention** (or “negative logic”)
 - a negative logic signal that is **asserted** is in the **LOW** state, and is therefore referred to as an “**active low**” signal
 - a negative logic signal that is **negated** is in the **HIGH** state

Logic Families

- There are **many** ways to design a digital logic gate, from mechanical relays and vacuum tubes to microscopic transistors
- **Complementary Metal-Oxide Semiconductor (CMOS)** circuits now account for the vast majority of the worldwide **Integrated Circuit (IC)** market
- **CMOS** logic is both the most capable and the easiest to understand commercial digital logic technology

CMOS Logic

- **5 V CMOS logic levels**

Note: CMOS circuits using other power supply voltages (e.g., 3.3 or 2.7 volts) partition the voltage range similarly

CMOS Logic

- **MOS Field Effect Transistor (MOSFET)**
 - modeled as a 3-terminal device that acts like a **voltage-controlled resistance**

- in digital logic applications, MOSFETs are operated so that their resistance is either **very high** (transistor is “off”) or **very low** (transistor is “on”)

CMOS Logic

- There are two types of MOSFETs
 - P-channel MOS (PMOS)**

Voltage-controlled resistance:
 decrease $V_{GS} \rightarrow$ decrease R_{DS}
 (current flows from S terminal to D)

Note: normally, $V_{GS} \leq 0$
 - N-channel MOS (NMOS)**

Voltage-controlled resistance:
 increase $V_{GS} \rightarrow$ decrease R_{DS}
 (current flows from D terminal to S)

Note: normally, $V_{GS} \geq 0$

Basic CMOS Logic Circuit

- The S terminal of the P-ch MOSFET is connected to 5 V
- The S terminal of the N-ch MOSFET is connected to GND
- The D terminals of both MOSFETs are connected to the output (Vout)
- The direction of current flow in the P-ch device is from the S terminal to the D terminal ("sources" current)
- The direction of current flow in the N-ch device is from the D terminal to the S terminal ("sinks" current)
- A high voltage on the G terminal of the N-ch MOSFET (relative to GND) turns it on
- A low voltage on the G terminal of the P-ch MOSFET (relative to 5 V) turns it on

Example (Hypothetical Impedances)

P-channel:
 "on" resistance = 75 Ω
 "off" resistance = 500,000 Ω

N-channel:
 "on" resistance = 25 Ω
 "off" resistance = 500,000 Ω

Example: Inverter Operation

- Calculate V_{out} for the case $A=B=0V$
 - P-ch device is "on" ($R_{DS} = 75 \Omega$)
 - N-ch device is "off" ($R_{DS} = 500,000 \Omega$)
 - $V_{out} = 5 \times (500,000 / 500,075) \approx 4.9999 V$
 - $P_{dissipation} = 5^2 / 500,075 \approx 0.05 mW$
- Calculate V_{out} for the case $A=B=5V$
 - P-ch device is "off" ($R_{DS} = 500,000 \Omega$)
 - N-ch device is "on" ($R_{DS} = 25 \Omega$)
 - $V_{out} = 5 \times (25 / 500,025) \approx 0.00025 V$
 - $P_{dissipation} = 5^2 / 500,025 \approx 0.05 mW$

Note: Very low power dissipation for either high or low output, and very small voltage drop across "on" device (for "no load" condition)

Basic CMOS Inverter Circuit

function ("truth") table

V_{IN}	Q1	Q2	V_{OUT}
0.0 (L)	off	on	5.0 (H)
5.0 (H)	on	off	0.0 (L)




logical behavior

switch analogy

Example: "Non-Inverter" Operation



- Calculate V_{out} for the case $A=0, B=5 V$
 - P-ch device is "on" ($R_{DS} = 75 \Omega$)
 - N-ch device is "on" ($R_{DS} = 25 \Omega$)
 - $V_{out} = 5 \times (25 / 100) = 1.25 V$
 - $P_{dissipation} = 5^2 / 100 = 250 mW$
- Calculate V_{out} for the case $A=5V, B=0$
 - P-ch device is "off" ($R_{DS} = 500,000 \Omega$)
 - N-ch device is "off" ($R_{DS} = 500,000 \Omega$)
 - $V_{out} = 5 \times (500,000 / 1,000,000) = 2.5 V$
 - $P_{dissipation} = 5^2 / 1,000,000 = 0.025 mW$

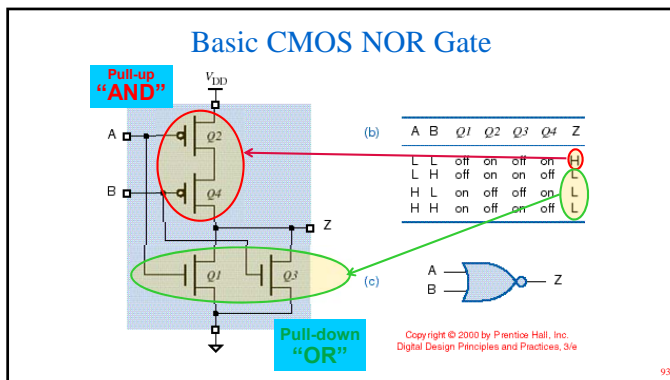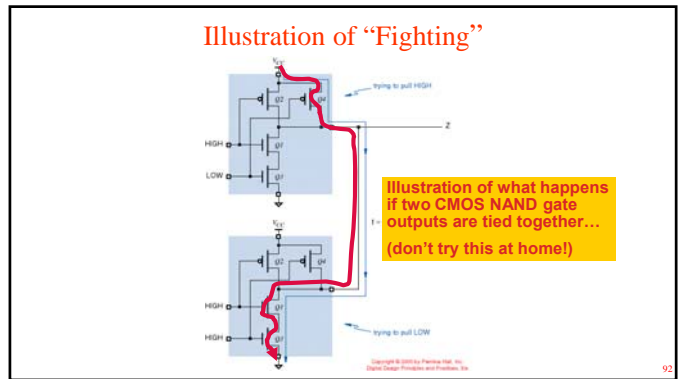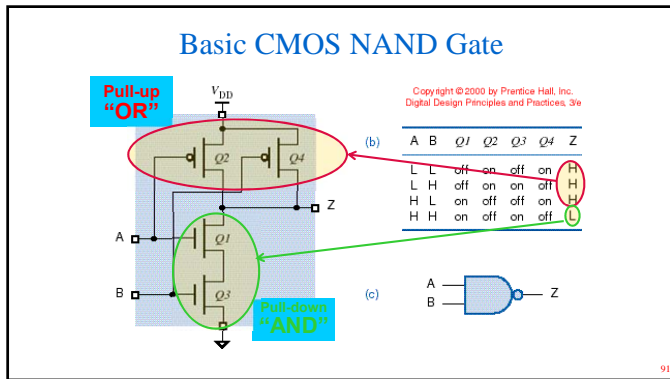Question: What would you call each of these cases?



Fan-in

- Definition: The number of inputs a gate can have in a particular logic family is called the logic family's *fan-in*
- CMOS gates with more than two inputs can be obtained by extending the "series-parallel" circuit designs (e.g., for NAND and NOR gates) illustrated previously
- In practice, the additive "on" resistance of series transistors limits the fan-in of CMOS gates to a relatively small number
- Gates with a large number of inputs can be made faster and smaller by cascading gates with fewer inputs

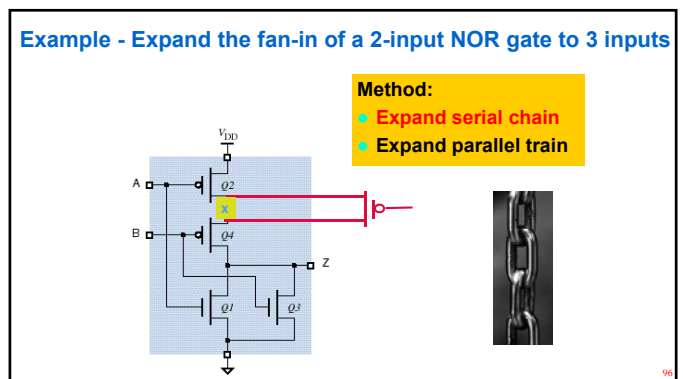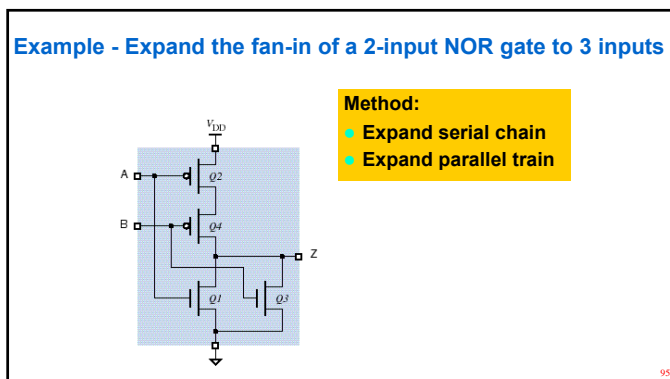

Example - Expand the fan-in of a 2-input NOR gate to 3 inputs

Method:

- Expand serial chain
- Expand parallel train

Clicker Quiz

1. Which of the following input combinations will cause a **maximum** amount of power dissipation?

- A=0V, B=0V
- A=0V, B=5V
- A=5V, B=0V
- A=5V, B=5V
- none of the above

2. Which of the following input combinations will cause a **minimum** amount of power dissipation?

- A=0V, B=0V
- A=0V, B=5V
- A=5V, B=0V
- A=5V, B=5V
- none of the above

Purdue IM: PACT* Spring 2019 Edition
 *Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 1-E Logic Levels and Noise Margins

Reading Assignment:
 DDPP 4th Ed. pp. 96-103, 5th Ed. pp. 745-753

Learning Objectives:

- Identify key information contained in a logic device data sheet
- Calculate the DC noise immunity margin of a logic circuit and describe the consequences of an insufficient margin
- Describe the consequences of a "non-ideal" voltage applied to a logic gate input
- Describe how unused ("spare") CMOS inputs should be terminated

Outline

- Overview
- Data sheets
- Noise
- Logic levels and noise margins
- Non-ideal inputs
- Unused (“spare”) inputs
- Electrostatic discharge

Overview

- **Objective:** To be able to design *real* circuits using CMOS or other logic families
 - need to ensure that the “*digital abstraction*” is valid for a given circuit
 - need to provide adequate engineering *design margins* to ensure that a circuit will work properly under a variety of conditions
 - need to be able to read and understand data sheets and specifications, in order to create reliable and robust real-world circuits and systems

Data Sheet for a Typical CMOS Device

DC ELECTRICAL CHARACTERISTICS OVER OPERATING RANGE
The following conditions apply unless otherwise specified.
Commercial: $T_A = -40^{\circ}\text{C}$ to $+85^{\circ}\text{C}$, $V_{CC} = 3.0\text{V}/5.0\text{V}$. Military: $T_A = -55^{\circ}\text{C}$ to $+125^{\circ}\text{C}$, $V_{CC} = 3.0\text{V}/5.0\text{V}$.

Sym.	Parameter ⁽¹⁾	Test Conditions ⁽²⁾	Min.	Typ. ⁽³⁾	Max.	Unit
V_{IH}	Input HIGH level	Guaranteed high-LEVEL input	2.13	—	—	V
V_{IL}	Input LOW level	Guaranteed high-LEVEL input	—	—	1.35	V
I_{IH}	Input HIGH current	$V_{CC} = \text{Max.}, V_i = V_{IH}$	—	—	1	μA
I_{IL}	Input LOW current	$V_{CC} = \text{Max.}, V_i = 0\text{V}$	—	—	-1	μA
I_{IS}	Clamp diode current	$V_{CC} = \text{Max.}, I_{IS} = -18\text{mA}$	—	-0.3	-1.2	V
I_{OS}	Short circuit current	$V_{CC} = \text{Max.}, V_o = \text{GND}$	—	—	-21	mA
V_{OH}	Output HIGH voltage	$V_{CC} = \text{Max.}, I_{OH} = -20\text{ }\mu\text{A}$	4.4	4.699	—	V
V_{OL}	Output LOW voltage	$V_{CC} = \text{Max.}, I_{OL} = 4\text{mA}$	3.84	4.3	—	V
I_{OZ}	Output LOW voltage	$V_{CC} = \text{Max.}, I_{OZ} = 20\text{ }\mu\text{A}$	—	—	0.1	V
I_{OZ}	Output LOW voltage	$V_{CC} = \text{Max.}, I_{OZ} = 4\text{mA}$	—	—	0.33	V
I_{CC1}	Quiescent power supply current	$V_{CC} = \text{Max.}, V_{IN} = \text{GND}$ or $V_{CC}, V_o = 0$	—	2	10	μA


SWITCHING CHARACTERISTICS OVER OPERATING RANGE, $C_L = 50\text{ pF}$

Sym.	Parameter ⁽¹⁾	Test Conditions ⁽²⁾	Min.	Typ.	Max.	Unit
t_{PD}	Propagation delay	A or B to Y	—	9	13	ns
C_i	Input capacitance	$V_{IN} = 0\text{V}$	—	3	10	pF
C_{out}	Power dissipation capacitance per gate	No load	—	22	—	pF

NOTES:
1. For conditions shown as Min. or Max., use appropriate value specified under Electrical Characteristics.
2. Digital values are at $V_{CC} = 5.0\text{V}/3.0\text{V}$ conditions.
3. Not more than one capacitor should be observed at a time. Duration of short circuit test should not exceed one second.
4. These parameters are guaranteed but not tested.


Noise

 - The main reason for providing engineering design margins is to ensure proper operation in the presence of *noise*
- Examples of noise sources:
 - cosmic rays
 - magnetic fields generated by machinery
 - power supply disturbances
 - the “*switching action*” of the logic circuits themselves



Logic Levels and Noise Margins

 - Typical input-output transfer characteristic of a CMOS inverter



Logic Levels and Noise Margins

- Factors that cause the transfer characteristic to vary
 - power supply voltage
 - temperature
 - output loading
 - conditions under which a device was fabricated
- Sound engineering practice dictates that we use more “*conservative*” specifications for LOW and HIGH


Logic Levels and Noise Margins

- Definitions:
 - $-V_{OH_{min}}$ - the minimum output voltage in the HIGH state
 - $-V_{IH_{min}}$ - the minimum input voltage guaranteed to be recognized as a HIGH
 - $-V_{IL_{max}}$ - the maximum input voltage guaranteed to be recognized as a LOW
 - $-V_{OL_{max}}$ - the maximum output voltage in the LOW state

Logic Levels and Noise Margins

- CMOS levels are typically a function of the power supply "rails"

 - $-V_{OH_{min}} = V_{CC} - 0.1V$
- $-V_{IH_{min}} = 70\% \text{ of } V_{CC}$
- $-V_{IL_{max}} = 30\% \text{ of } V_{CC}$
- $-V_{OL_{max}} = GND + 0.1V$



DC noise margin is a measure of how much noise it takes to corrupt a worst-case output voltage into a value that may not be recognized properly by an input

Data Sheet for a Typical CMOS Device

Sym.	Parameter	Test Conditions ¹⁾	Min.	Typ. ²⁾	Max.	Unit
V_{OH}	Output HIGH level	Guaranteed logic HIGH level	3.15	—	—	V
V_{OL}	Output LOW level	Guaranteed logic LOW level	—	—	0.1	V
I_{OH}	Output HIGH current	$V_{OH} = \text{Max.}, I_L = 0 \text{ V}$	—	—	-1	μA
I_{OL}	Output LOW current	$V_{OL} = \text{Min.}, I_H = 0 \text{ V}$	—	—	1	μA
V_{IK}	Clamp diode voltage	$V_{IC} = \text{Min.}, I_K = -18 \text{ mA}$	-0.7	-1.2	—	V
I_{SC}	Short-circuit current	$V_{IC} = \text{Max.}^{10}, V_{IO} = GND$	—	—	-35	mA
V_{OH}	Output HIGH voltage	$V_{IC} = \text{Min.}, I_{OH} = -20 \mu\text{A}$	4.4	4.499	—	V
V_{OL}	Output LOW voltage	$V_{IC} = \text{Min.}, I_{OL} = 20 \mu\text{A}$	—	0.001	0.1	V
I_{CC}	Quiescent power supply current	$V_{IC} = \text{Max.}, I_{IH} = GND \text{ or } V_{IC}, I_{IO} = 0$	—	2	10	μA

Logic Levels and Noise Margins

- Calculation of DC noise margin (DCNM), also called the "noise immunity margin"


$$DCNM = \min(V_{OH_{min}} - V_{IH_{min}}, V_{IL_{max}} - V_{OL_{max}})$$

- Example: HC-series CMOS

$$DCNM = \min(4.4 - 3.15, 1.35 - 0.1) = 1.25 \text{ v}$$


Non-ideal Inputs

 - If the inputs to a CMOS circuit are at "weak high" or "weak low" potentials (i.e. close to indeterminate region)
 - the "on" transistor may not be fully on
 - the "off" transistor may not be fully off
 - power dissipation of the device increases




Unused ("Spare") Inputs

 - Unused ("spare") CMOS inputs should never be left unconnected ("floating")
- A small amount of circuit noise can temporarily make a floating input look HIGH
- Instead, unused inputs should be:
 - tied to another input of the same gate
 - tied HIGH (for AND and NAND gates)
 - tied LOW (for OR and NOR gates)



Electrostatic Discharge

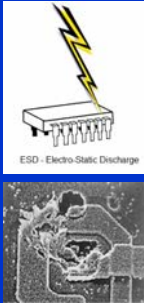- CMOS device inputs are subject to damage from electrostatic discharge (ESD)
- Apply these precautions in lab:
 - before handling a CMOS device, touch a source of **earth ground**
 - transport CMOS devices in **conductive** bags, foam, or tubes
 - handle circuit boards containing CMOS devices by the **edges**; touch a ground terminal on the board to earth ground before “poking around with it”



ESD - Electro-Static Discharge

Clicker Quiz

1. For CMOS gates, V_{IHmin} is typically:

- A. 10% of the supply voltage (V_{cc})
- B. 30% of the supply voltage (V_{cc})
- C. 50% of the supply voltage (V_{cc})
- D. 70% of the supply voltage (V_{cc})
- E. 90% of the supply voltage (V_{cc})


2. For CMOS gates, the **switching threshold** is typically:

- A. 10% of the supply voltage (V_{cc})
- B. 30% of the supply voltage (V_{cc})
- C. 50% of the supply voltage (V_{cc})
- D. 70% of the supply voltage (V_{cc})
- E. 90% of the supply voltage (V_{cc})

3. If a CMOS gate input voltage is 50% of its V_{cc} (supply) voltage, then:

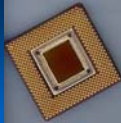- A. the logic gate will dissipate **less power** than it would if the input was 1% of its power supply voltage
- B. the logic gate will dissipate **less power** than it would if the input was 99% of its power supply voltage
- C. the logic gate will dissipate **more power** than it would if the input was *either* 1% or 99% of its power supply voltage
- D. the logic gate will dissipate **no power**
- E. none of the above

Purdue IM:PACT* Spring 2019 Edition
*Instruction Matters: Purdue Academic Course Transformation



Introduction to Digital System Design

Module 1-F Current Sourcing and Sinking

Reading Assignment:
DDPP 4th Ed. pp. 103-114, 5th Ed. pp. 753-764

Learning Objectives:

- Identify key information contained in a logic device data sheet
- Describe the relationship between logic gate output voltage swing and current sourcing/sinking capability
- Describe the difference between “DC loads” and “CMOS loads”
- Calculate V_{OL} and V_{OH} of a logic gate based on the “on” resistance of the active device and the amount of current sourced (I_{OH}) or sunk (I_{OL}) by the gate output
- Calculate logic gate fan-out and identify a practical lower limit
- Calculate the value of current limiting resistor needed for driving an LED
- Describe the deleterious effects associates with loading a gate output beyond its rated specifications

Outline

- Sourcing and sinking current
- CMOS and DC loads
- Fan-out
- Driving LEDs
- Effects of excessive loading

Sourcing and Sinking Current

- CMOS gate inputs have a very high impedance and consume very little current from the circuits that drive them
- I_{IL} the maximum current that flows into the input in the LOW state
- I_{IH} the maximum current that flows into the input in the HIGH state

For CMOS logic, the input current is very small (about one microamp) – it takes very little power to maintain a CMOS input in either the HIGH or LOW state

Sourcing and Sinking Current

- IC manufacturers specify a maximum load for the output in each state (HIGH or LOW) and guarantee a worst-case output voltage for that load
- I_{OLmax} - the maximum current that the output can “sink” in the LOW state while still maintaining an output voltage **no greater than V_{OLmax}**
- I_{OHmax} - the maximum current that the output can “source” in the HIGH state while still maintaining an output voltage **no less than V_{OHmin}**

Sourcing and Sinking Current

- Circuit definitions of I_{OLmax} and I_{OHmax}

sinking current (positive)

current arrow NOTE: Convention is for the input/output current arrows to point “in”

sourcing current (negative)

Sourcing and Sinking Current

- Often times gate outputs need to drive devices that require a non-trivial amount of current to operate – called a **resistive load** or **DC load**
- When driving a resistive load, the output of a CMOS circuit is not nearly as **ideal** as described previously
- In either output state, the CMOS output transistor that is “on” has a non-zero resistance, and a load connected to its output terminal will cause a voltage drop across this resistance

CMOS and DC Loads

- Consequently, most CMOS devices have **two sets** of loading specifications:
 - “**CMOS loads**” – device output connected to other CMOS inputs, which require **very little current** to recognize a “high” input or “low” input
 - “**DC loads**” – device output connected to resistive loads (devices that consume significant current, typically several milliamps)

Note: With “DC loads” the output voltage swing of a CMOS circuit may significantly **degrade**

Example: Inverter - Current Sourcing

- Calculate V_{OH} and I_{OH} for $A=B=0V$
- Current SOURCING configuration**
- DC Load is 500Ω resistor between V_{out} and GND
- P-ch device is “on” ($R_{DS} = 75 \Omega$)
- N-ch device is “off” ($R_{DS} = 500,000 \Omega$)
- Load impedance is $500,000 \Omega$ in parallel with $500 \Omega \approx 500 \Omega$
- $V_{OH} \approx 5 \times (500 / 575) \approx 4.35 V$
- $I_{OH} \approx 5 / (75 + 500) \approx 0.0087 A$ (8.7 mA)

Note: In the current **SOURCING** configuration, the inverter output is **active high** (“asserted high”); the N-channel pull-down virtually “disappears”

Example: Inverter - Current Sinking

- Calculate V_{OL} and I_{OL} for $A=B=5V$
- Current SINKING configuration**
- DC Load is 500Ω resistor between $5 V$ supply and V_{out}
- P-ch device is “off” ($R_{DS} = 500,000 \Omega$)
- N-ch device is “on” ($R_{DS} = 25 \Omega$)
- Load impedance is $500,000 \Omega$ in parallel with $500 \Omega \approx 500 \Omega$
- $V_{OL} \approx 5 \times (25 / 525) \approx 0.24 V$
- $I_{OL} \approx 5 / (25 + 500) \approx 0.0095 A$ (9.5 mA)

Note: In the current **SINKING** configuration, the inverter output is **active low** (“asserted low”); the P-channel pull-up virtually “disappears”

Fan-out

- Definition:** The number of gate inputs that a gate output can drive **without exceeding** its worst-case loading specifications
 - depends on characteristics of both the output device and the inputs being driven
 - must be examined for both the “sourcing” and “sinking” cases
 - limitations due to capacitive loading (impact on rise/fall times may be more of a limiting factor than fan-out or DCNM)

Fan-out = $\min(I_{OH_{max}} / I_{IH}, I_{OL_{max}} / I_{IL})$

Data Sheet for a Typical CMOS Device

DC ELECTRICAL CHARACTERISTICS OVER OPERATING RANGE
The following conditions apply unless otherwise specified:
Commercial: $T_c = -40^\circ C$ to $+85^\circ C$; $V_{DD} = 3.0V \pm 5\%$. Military: $T_c = -55^\circ C$ to $+125^\circ C$; $V_{DD} = 3.0 V \pm 10\%$

Sym.	Parameter	Test Conditions ⁽¹⁾	Min.	Typ. ⁽²⁾	Max.	Unit
V_{IH}	Input HIGH level	Guaranteed logic HIGH level	3.15	—	—	V
V_{IL}	Input LOW level	Guaranteed logic LOW level	—	—	1.35	V
I_{IH}	Input HIGH current	$V_{IH} = \text{Max.}, I_1 = V_{IH}$	—	—	1	μA
I_{IL}	Input LOW current	$V_{IL} = \text{Max.}, I_1 = 0 V$	—	—	-1	μA
V_{SD}	Clamp diode voltage	$V_{CE} = \text{Min.}, I_1 = -18 \text{ mA}$	—	-0.7	-1.2	V
I_{SC}	Short circuit current	$V_{CE} = \text{Max.}^{(3)}, V_2 = \text{GND}$	—	—	-35	mA
V_{OH}	Output HIGH voltage	$V_{CE} = \text{Min.}, I_{OH} = I_{IH}$	4.4	4.499	—	V
V_{OL}	Output LOW voltage	$V_{CE} = \text{Min.}, I_{OL} = I_{IL}$	—	0.001	—	V
I_{OQ}	Quiescent power supply current	$V_{CE} = \text{Max.}, I_{OH} = \text{GND or } I_{CE}, I_1 = 0$	—	0.17	0.33	μA

SWITCHING CHARACTERISTICS OVER OPERATING RANGE, $C_L = 50 \text{ pF}$

Sym.	Parameter ⁽¹⁾	Test Conditions	Min.	Typ.	Max.	Unit
t_{PD}	Propagation delay	A to B to Y	—	9	19	ns
t_r	Input capacitance	$V_{IN} = 0 V$	—	3	10	pF
C_{PD}	Power dissipation capacitance per gate	No load	—	22	—	pF

Fan-out Calculation

- Example:** HC-series CMOS

Fan-out = $\min(I_{OH_{max}} / I_{IH}, I_{OL_{max}} / I_{IL})$

= $\min(0.02 \text{ mA} / 0.001 \text{ mA}, -0.02 \text{ mA} / -0.001 \text{ mA})$

= 20

Note: DC fan-out is considerably greater in this case if the output voltage swing is degraded ... **but** DCNM is lower and signal transitions times are longer, causing speed degradation

Practical Fan-out

- In a practical application, a gate output may drive a "mixture" of loads
- HIGH-state fan-out** – The sum of the I_{IHmax} values of all the driven inputs must be *less than or equal to* the I_{OHmax} of the driving output
- LOW-state fan-out** – The sum of the I_{ILmax} values of all the driven inputs must be *less than or equal to* the I_{OLmax} of the driving output

The "practical" fan-out is the **minimum** of the HIGH- and LOW-state fan-outs

Driving LEDs

- LEDs represent "DC loads" and can be interfaced to a CMOS gate output either by **sinking** current (LOW output) or **sourcing** current (HIGH output)

Answer: Depends on I_{OHmax} and I_{OLmax} specs of gate – if they are the same, it doesn't matter; but if they are different, usually the **sinking** current is **greater** than the **sourcing** current

Question: Which method is generally preferred?

Example: Based on the data provided in Table 3-3 of the course text, calculate the value of the LED current limiting resistor for the **worst case current sinking** configuration. Also calculate the amount of power dissipated by the current limiting resistor. Assume V_{LED} is 1.9 volts.

Table 3.3 from DDPP

DC ELECTRICAL CHARACTERISTICS OVER OPERATING RANGE					
The following conditions apply unless otherwise specified					
Commercial: $T_A = -40^\circ\text{C}$ to $+85^\circ\text{C}$, $V_{CC} = 3.0\text{V} \pm 3\%$; Military: $T_A = -55^\circ\text{C}$ to $+125^\circ\text{C}$, $V_{CC} = V \pm 10\%$					
Sym	Parameter	Test Conditions ¹	Min.	Typ ²	Max. Unit
V_{IH}	Input HIGH level	Guaranteed logic HIGH level	3.15	—	— V
V_{IL}	Input LOW level	Guaranteed logic LOW level	—	—	1.20 V
I_{IH}	Input HIGH current	$V_{IH} = \text{Max.}$, $V_{CC} = V_{CC}$	—	—	1 μA
I_{IL}	Input LOW current	$V_{IL} = \text{Max.}$, $V_{CC} = 5\text{V}$	—	—	-4 μA
V_{OL}	Clamp diode voltage	$I_{OL} = \text{Max.}$, $I_{CC} = -18\text{mA}$	—	-0.7	-1.2 V
I_{SC}	Short circuit current	$V_{CC} = \text{Max.}$ ³ , $V_{OL} = \text{GND}$	—	—	-18 mA
V_{OH}	Output HIGH voltage	$I_{OH} = \text{Min.}$ $I_{OH} = \text{Max.}$	4.1 3.84	4.699 4.3	— V
V_{OL}	Output LOW voltage	$I_{OL} = \text{Min.}$ $I_{OL} = \text{Max.}$	— 0.33	— 0.33	— V
I_{CC}	Quiescent power supply current	$V_{CC} = \text{Max.}$ $V_{OL} = \text{GND}$ or $V_{CC} = V_{OL} = 0$	—	2	10 μA

SWITCHING CHARACTERISTICS OVER OPERATING RANGE, $C_L = 50\text{ pF}$

Sym	Parameter ⁴	Test Conditions	Min.	Typ.	Max. Unit
t_{PD}	Propagation delay	A or B to Y	—	9	19 ns
t_r	Rise propagation	$V_{OH} = 5\text{V}$	—	9	10 μs
t_{fall}	Fall propagation	No load	—	12	— μs

NOTES:
1. For conditions shown as Max. or Min., use appropriate value specified under Electrical Characteristics.
2. Typical values are at $V_{CC} = 3.0\text{V} \pm 3\%$ and $T_A = 25^\circ\text{C}$.
3. For more than one output, should be checked for a rise. Duration of short circuit test should not exceed one second.
4. This parameter is guaranteed but not tested.

SOLUTION:

$V_R = 5.0 - V_{LED} - V_{OL} = 5.0 - 1.9 - 0.33 = 2.77\text{ V}$

NOTE: Here, use "Max" value indicated for V_{OL} of 0.33 V

$R = V_R / I_{OL} = 2.77 / 0.004 = 693\ \Omega$

$P_R = R \times I_{OL}^2 = 693 \times (0.004)^2 = 11.1\text{ milliwatts}$

NOTE: Can also calculate power dissipation of resistor using $V_R \times I_{OL}$ or $(V_R^2) / R$

Example: Based on the data provided in Table 3-3 of the course text, calculate the value of the LED current limiting resistor for the **worst case current sourcing** configuration. Also calculate the amount of power dissipated by the current limiting resistor. Assume V_{LED} is 1.9 volts.

Table 3.3 from *DDPP*

Param.	Parameter ⁽¹⁾	Test Conditions ⁽²⁾	Min.	Typ.	Max.	Unit
V_{OH}	Output HIGH level	Guaranteed logic HIGH level	3.15	—	—	V
V_{OL}	Output LOW level	Guaranteed logic LOW level	—	—	1.25	V
I_{IH}	Input HIGH current	$V_{IH} = \text{Max.}, V_I = V_{CC}$	—	—	1	μA
I_{IL}	Input LOW current	$V_{IL} = \text{Max.}, V_I = 0\text{V}$	—	—	-1	μA
V_{CE}	Clamp diode voltage	$I_{CL} = \text{Max.}, I_{CL} = -18\text{ mA}$	-0.7	-1.2	—	V
I_{SC}	Short circuit current	$V_{OL} = \text{Max.}, V_I = \text{GND}$	—	—	-25	mA
V_{OH}	Output HIGH voltage	$V_{OH} = \text{Min.}, I_{OH} = -4\text{ mA}$	4.4	4.699	—	V
V_{OL}	Output LOW voltage	$V_{OL} = \text{Max.}, I_{OL} = 4\text{ mA}$	—	0.3	—	V
I_{OH}	Output HIGH current	$V_{OH} = \text{Min.}, I_{OH} = -4\text{ mA}$	—	—	0.001	A
I_{OL}	Output LOW current	$V_{OL} = \text{Max.}, I_{OL} = 4\text{ mA}$	—	—	0.01	A
I_{CC}	Quiescent power supply current	$V_{OH} = \text{Max.}, V_{OL} = \text{GND or } V_{OL}, I_{OH} = 0$	—	2	10	μA

SMITHSONIAN CHARACTERISTICS OVER OPERATING RANGE, $C_L = 10\text{ pF}$

NOTES:
1. For conditions shown as Min. or Max., use appropriate value specified under Electrical Characteristics.
2. Input and output are at V_{OH} or V_{OL} at 50% duty cycle.
3. For more than one output should be selected at a time. Duration of short circuit test should not exceed one second.
4. This parameter is measured at room temperature.

SOLUTION:

$V_R = V_{OH} - V_{LED} = 3.84 - 1.9 = 1.94\text{ V}$

NOTE: Here, use "Min" value indicated for V_{OH} of 3.84 V

$R = V_R / I_{OH} = 1.94 / 0.004 = 485\ \Omega$

NOTE: Can also calculate power dissipation of resistor using $V_R \times I_{OH}$ or $(V_R)^2 / R$

$P_R = R \times I_{OH}^2 = 485 \times (0.004)^2 = 7.8\text{ milliwatts}$

Effects of Excessive Loading

- Loading a gate output beyond its rated fan-out can have several deleterious effects:
 - in the LOW state, the output voltage (V_{OL}) may increase beyond V_{OLmax}
 - in the HIGH state, the output voltage (V_{OH}) may fall below V_{OHmin}
 - output rise and fall times may increase beyond their specifications
 - the operating temperature of the device may increase, thereby **reducing the reliability** of the device and eventually causing **device failure**

Example – DCNM, Family A → Family B

$V_{CC} = 5\text{ V}$	$V_{OH} = 4.4\text{ V}$	$V_{OL} = 0.40\text{ V}$	$V_{IH} = 3.60\text{ V}$	$V_{IL} = 1.60\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -4\text{ mA}$	$I_{OL} = 4\text{ mA}$	$I_{IH} = 0.4\ \mu\text{A}$	$I_{IL} = -0.4\ \mu\text{A}$

$V_{CC} = 5\text{ V}$	$V_{OH} = 3.3\text{ V}$	$V_{OL} = 0.30\text{ V}$	$V_{IH} = 2.60\text{ V}$	$V_{IL} = 1.60\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -400\ \mu\text{A}$	$I_{OL} = 8\text{ mA}$	$I_{IH} = 40\ \mu\text{A}$	$I_{IL} = -0.4\text{ mA}$

$DCNM_{A \rightarrow B} = \min\{4.4 - 2.6, 1.6 - 0.4\} = 1.2\text{V}$

Question: Is this a "good" DCNM (for 5V CMOS logic)?

Example – DCNM, Family B → Family A

$V_{CC} = 5\text{ V}$	$V_{OH} = 4.4\text{ V}$	$V_{OL} = 0.40\text{ V}$	$V_{IH} = 3.60\text{ V}$	$V_{IL} = 1.60\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -4\text{ mA}$	$I_{OL} = 4\text{ mA}$	$I_{IH} = 0.4\ \mu\text{A}$	$I_{IL} = -0.4\ \mu\text{A}$

$V_{CC} = 5\text{ V}$	$V_{OH} = 3.3\text{ V}$	$V_{OL} = 0.30\text{ V}$	$V_{IH} = 2.60\text{ V}$	$V_{IL} = 1.60\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -400\ \mu\text{A}$	$I_{OL} = 8\text{ mA}$	$I_{IH} = 40\ \mu\text{A}$	$I_{IL} = -0.4\text{ mA}$

$DCNM_{B \rightarrow A} = \min\{3.3 - 3.6, 1.6 - 0.3\} = -0.3\text{V}$

Question: What is the consequence of a negative DCNM? What is the minimum DCNM required? $DCNM > 0$

Example – Fan-out, Family A → Family B

$V_{CC} = 5\text{ V}$	$V_{OH} = 4.4\text{ V}$	$V_{OL} = 0.40\text{ V}$	$V_{IH} = 3.60\text{ V}$	$V_{IL} = 1.60\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -4\text{ mA}$	$I_{OL} = 4\text{ mA}$	$I_{IH} = 0.4\ \mu\text{A}$	$I_{IL} = -0.4\ \mu\text{A}$

$V_{CC} = 5\text{ V}$	$V_{OH} = 3.3\text{ V}$	$V_{OL} = 0.30\text{ V}$	$V_{IH} = 2.60\text{ V}$	$V_{IL} = 1.60\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -400\ \mu\text{A}$	$I_{OL} = 8\text{ mA}$	$I_{IH} = 40\ \mu\text{A}$	$I_{IL} = -0.4\text{ mA}$

$Fanout_{A \rightarrow B} = \min(4 / 0.04, 4 / 0.4) = 10$

Note: Current arrows for I_O and I_I point in opposite directions

Question: Is it possible for the fan-out to be negative? NO!

Example – Fan-out, Family B → Family A

Family "A"

$V_{CC} = 5\text{ V}$	$V_{OH} = 4.4\text{ V}$	$V_{OL} = 0.40\text{ V}$	$V_{IH} = 3.60\text{ V}$	$V_{IL} = 1.60\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -4\text{ mA}$	$I_{OL} = 4\text{ mA}$	$I_{IH} = 0.4\text{ }\mu\text{A}$	$I_{IL} = -0.4\text{ }\mu\text{A}$

Family "B"

$V_{CC} = 5\text{ V}$	$V_{OH} = 3.3\text{ V}$	$V_{OL} = 0.30\text{ V}$	$V_{IH} = 2.60\text{ V}$	$V_{IL} = 1.60\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -400\text{ }\mu\text{A}$	$I_{OL} = 8\text{ mA}$	$I_{IH} = 40\text{ }\mu\text{A}$	$I_{IL} = -0.4\text{ mA}$

Fanout $B \rightarrow A = \min(400/0.4, 8/0.0004) = 1000$

Question: What is the minimum fan-out required?

Fan-out ≥ 1

Clicker Quiz

DC Characteristics of a Hypothetical Logic Family

$V_{CC} = 5\text{ V}$	$V_{OH} = 3.50\text{ V}$	$V_{OL} = 0.50\text{ V}$	$V_{IH} = 2.50\text{ V}$	$V_{IL} = 1.00\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -5.0\text{ mA}$	$I_{OL} = 10\text{ mA}$	$I_{IH} = 500\text{ }\mu\text{A}$	$I_{IL} = -2.0\text{ mA}$

1. The **DC noise margin** for this logic family is:

- A. 0.50 V
- B. 1.00 V
- C. 1.50 V
- D. 2.00 V
- E. none of the above

DCNM = $\min(V_{OH_{min}} - V_{IH_{min}}, V_{IL_{max}} - V_{OL_{max}})$

DC Characteristics of a Hypothetical Logic Family

$V_{CC} = 5\text{ V}$	$V_{OH} = 3.50\text{ V}$	$V_{OL} = 0.50\text{ V}$	$V_{IH} = 2.50\text{ V}$	$V_{IL} = 1.00\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -5.0\text{ mA}$	$I_{OL} = 10\text{ mA}$	$I_{IH} = 500\text{ }\mu\text{A}$	$I_{IL} = -2.0\text{ mA}$

2. The **practical fanout** for this logic family is:

- A. 1
- B. 2
- C. 5
- D. 10
- E. none of the above

Fan-out = $\min(I_{OH_{max}} / I_{IH}, I_{OL_{max}} / I_{IL})$

3. The **nominal (minimum) case** for the **outputs of logic family "A"** to be able to successfully drive the **inputs of logic family "B"** is:

- A. $\text{fanout}_{A \rightarrow B} \leq 1$ and $\text{DCNM}_{A \rightarrow B} < 0$
- B. $\text{fanout}_{A \rightarrow B} \leq 0$ and $\text{DCNM}_{A \rightarrow B} < 1$
- C. $\text{fanout}_{A \rightarrow B} \geq 1$ and $\text{DCNM}_{A \rightarrow B} > 0$
- D. $\text{fanout}_{A \rightarrow B} \geq 0$ and $\text{DCNM}_{A \rightarrow B} > 1$
- E. none of the above

What is the minimum fan-out permissible?

What is the minimum DCNM permissible?

DC Characteristics of a Hypothetical Logic Family

$V_{CC} = 5\text{ V}$	$V_{OH} = 3.50\text{ V}$	$V_{OL} = 0.50\text{ V}$	$V_{IH} = 2.50\text{ V}$	$V_{IL} = 1.00\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -5.0\text{ mA}$	$I_{OL} = 10\text{ mA}$	$I_{IH} = 500\text{ }\mu\text{A}$	$I_{IL} = -2.0\text{ mA}$

4. When interfacing an **LED** that has a **forward voltage of 1.5 V** to this logic family in a **current sourcing** configuration, **maximum brightness** will be achieved (within the rated specifications) using a current limiting resistor of the value:

- A. 200Ω
- B. 300Ω
- C. 400Ω
- D. 500Ω
- E. none of these

DC Characteristics of a Hypothetical Logic Family


$V_{CC} = 5\text{ V}$	$V_{OH} = 3.50\text{ V}$	$V_{OL} = 0.50\text{ V}$	$V_{IH} = 2.50\text{ V}$	$V_{IL} = 1.00\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -5.0\text{ mA}$	$I_{OL} = 10\text{ mA}$	$I_{IH} = 500\text{ }\mu\text{A}$	$I_{IL} = -2.0\text{ mA}$

5. When interfacing an **LED** that has a **forward voltage of 1.5 V** to this logic family in a **current sinking** configuration, **maximum brightness** will be achieved (within the rated specifications) using a current limiting resistor of the value:

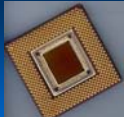A. 200 Ω B. 300 Ω C. 400 Ω D. 500 Ω E. none of these

151

Purdue IM: PACT* Spring 2019 Edition
*Instruction Matters: Purdue Academic Course Transformation



Introduction to Digital System Design

Module 1-G Propagation Delay and Transition Time

Reading Assignment:
DDPP 4th Ed. pp. 114-122, 5th Ed. pp. 764-778

Learning Objectives:

- Define propagation delay and list the factors that contribute to it
- Define transition time and list the factors that contribute to it
- Estimate the transition time of a CMOS gate output based on the “on” resistance of the active device and the capacitive load
- Describe ways in which load capacitance can be minimized

152

Outline

- Overview
- Propagation delay
- Transition time
- Equivalent circuit transition time analysis
 - Calculation
 - Estimation
- Load capacitance

153

Overview

- The **speed** and **power dissipation** of a CMOS device depend on the dynamic (“AC”) characteristics of the device and its load
- Logic designers must carefully examine the effects of output loading and redesign where the loading is too high
- Speed (performance) depends on two characteristics:
 - **propagation delay**
 - **transition time**

154

Time Matters

THINK
TIME!

- Logic gates require a certain amount of “think time” to produce a new output in response to changing inputs – referred to as the **propagation delay** of the gate
- Logic gate outputs can not change from a low voltage to a high voltage (or vice-versa) “instantaneously” – referred to as the **transition time** of the gate
- A **timing diagram** can be used to show how a logic circuit responds to time-varying input signals

155

Time Matters

- Time response of a combinational circuit

The diagram shows a logic circuit with inputs X, Y, and Z. The circuit consists of an AND gate (X·Y), an OR gate (X+Y+Z), and a final AND gate (X·Y·X+Y+Z). The timing diagram below shows the signals X, Y, Z, and F over time. Colored regions (red, green, yellow) highlight the propagation delays for different signal transitions.

Propagation Delay – Definition

- Definition:** The electrical path from a particular input signal of a logic element to its output signal is called a **signal path**
- Definition:** The amount of **time** it takes for a change in an input signal to cause a corresponding change in a gate's output signal is called the **propagation delay** (t_p)
- The propagation delay for an output signal going from **LOW-to-HIGH** (t_{PLH}) **may be different** than the propagation delay of that signal going from **HIGH-to-LOW** (t_{PHL})

Propagation Delay – Measurement

Ignoring rise and fall times

Measured at midpoints of transitions

The diagrams show input (V_{IN}) and output (V_{OUT}) signals. The first diagram shows propagation delay measured at the midpoints of the transitions, with labels t_{pHL} and t_{pLH} .

Propagation Delay – Why Non-zero

- Several factors lead to **non-zero** propagation delays in CMOS circuits:
 - the rate at which transistors change state is influenced both by semiconductor physics and the circuit environment (input signal transition time, input capacitance, and output loading)
 - multistage devices (e.g., non-inverting gates) may require several internal transistors to change state before the output can change state


Example – Propagation Delay Measurement

Find each of the following, rounded to the nearest 1/2 ns (assume each division is 1 ns)

Rise propagation delay (t_{pLH}) = 3 ns
Fall propagation delay (t_{pHL}) = 1.5 ns


Transition Time – Definition

- Definition:** The amount of time that the output of a logic circuit takes to change from one state to another
 - rise time** (t_r or t_{rHL}): the **time** an output signal takes to **transition** from **low-to-high**
 - fall time** (t_f or t_{fHL}): the **time** an output signal takes to **transition** from **high-to-low**
- Gate outputs can **not** change state **instantaneously** (i.e., with a transition time of zero) because they need to **charge the stray capacitance** of the wires and other components they drive

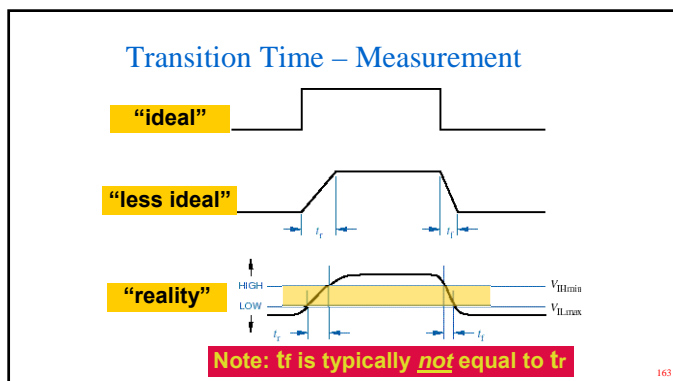

Transition Time – Endpoints

- To avoid difficulties in defining the endpoints, transition times are normally measured one of two different ways:
 - at the boundaries of the valid logic levels (i.e., $V_{IH_{min}}$ and $V_{IL_{max}}$)
 - at the 10% and 90% points of the output waveform
- Using the first convention (above), the rise and fall times indicate how long it takes for an output signal to pass through the (undefined) *indeterminate region* between **LOW** and **HIGH**

 






Transition Time – Factors

- The transition times of a CMOS circuit depend mainly on two factors:
 - the “on” transistor resistance
 - the load capacitance
- Stray capacitance (called an “AC load”) arises from at least three different sources:
 - output circuits – including transistors, internal wiring, and packaging
 - wiring that connects a gate output to other gate inputs
 - input circuits – including transistors, internal wiring, and packaging

Transition Time – Equivalent Circuit

- A gate output's load can be modeled by an equivalent load circuit with **3 components**:
 - **RL** and **VL** represent the **DC load** – they determine the steady state voltages and currents present and do not have much effect on transition times
 - **CL** represents the **AC (capacitive) load** – it determines the voltages and currents present while the output is changing, as well as how long it takes to change from one state to another

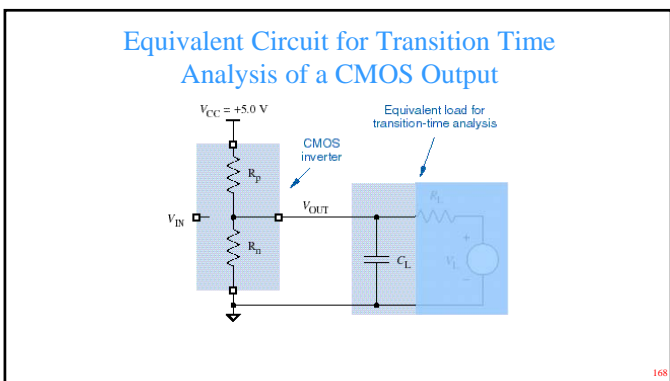

 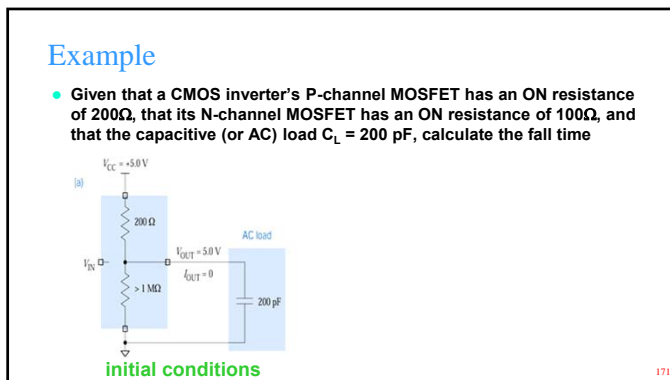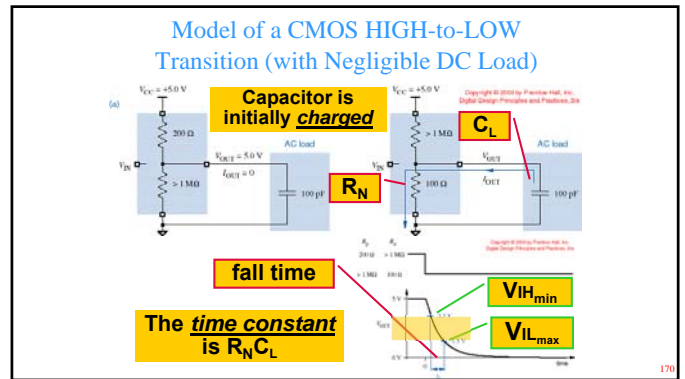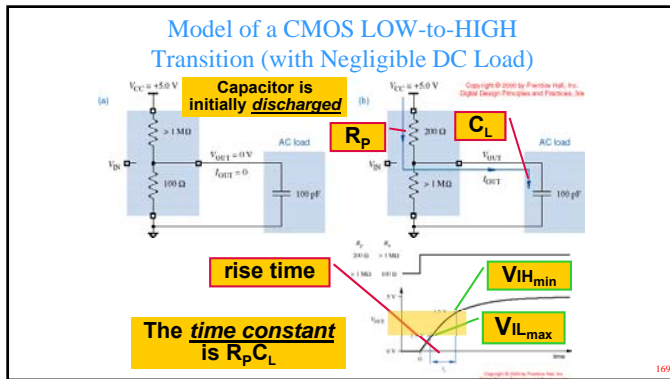

Example – Fall Time Calculation

$$t = -R_n \cdot C_L \cdot \ln(V_{out}/V_{DD})$$

$$= -100 \cdot 200 \cdot 10^{-12} \cdot \ln(V_{out} / 5.0)$$

$$= -20 \cdot 10^{-9} \cdot \ln(V_{out} / 5.0)$$

$$t_{3.5} = -20 \cdot 10^{-9} \cdot \ln(3.5/5.0) = 7.13\text{ ns}$$

$$t_{1.5} = -20 \cdot 10^{-9} \cdot \ln(1.5/5.0) = 24.08\text{ ns}$$

$$t_{PHL} = t_f \text{ (fall time)} = 24.08 - 7.13 = 16.95\text{ ns}$$

Note: Calculated transition times are sensitive to the choice of logic levels (i.e., $V_{IH_{min}}$ and $V_{IL_{max}}$)

Transition Time Estimation

- Rule of Thumb:** In practical circuits, the transition time can be **estimated** using the **RC time constant** of the charging or discharging circuit

Example – Transition Time Estimates

- Given that a CMOS inverter's **P-channel MOSFET has an ON resistance of 200Ω**, that its **N-channel MOSFET has an ON resistance of 100Ω**, and that the **capacitive (or "A.C.") load $C_L = 200$ pF**, **estimate the fall time and rise time**

Fall time estimate: $R_N \times C_L = 100 \times 200 \text{ pF}$ $= 1 \times 10^2 \times 2 \times 10^{-10}$ $= 2 \times 10^{-8} = 20 \times 10^{-9}$ $= 20 \text{ ns}$	Rise time estimate: $R_P \times C_L = 200 \times 200 \text{ pF}$ $= 2 \times 10^2 \times 2 \times 10^{-10}$ $= 4 \times 10^{-8} = 40 \times 10^{-9}$ $= 40 \text{ ns}$
---	---

Load Capacitance


- Conclusion:** An increase in load capacitance causes an increase in the RC time constant and a corresponding increase in the output transition (rise/fall) times
- Load capacitance must be **minimized** to obtain high circuit performance – this can be achieved by:
 - minimizing the number of inputs driven by a given signal
 - creating multiple copies of the signal (using "buffers")
 - careful **physical layout** of the circuit

Clicker Quiz


1. The **rise time** for the inverter is approximately:
A. 1.0 ns B. 1.5 ns C. 2.0 ns D. 3.0 ns E. none

2. The **fall time** for the inverter is approximately:
A. 1.0 ns B. 1.5 ns C. 2.0 ns D. 3.0 ns E. none

3. The **fall propagation delay** for the inverter is approx:
A. 1.0 ns B. 1.5 ns C. 2.0 ns D. 3.0 ns E. none

 

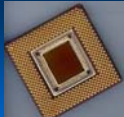Purdue IM:PACT* Spring 2019 Edition
 *Instruction Matters: Purdue Academic Course Transformation



Introduction to Digital System Design

Module 1-H
Power Consumption and Decoupling

Reading Assignment:
 DDP4th Ed. pp. 122-124, 5th Ed. pp. 771-773

Learning Objectives:

- Identify sources of dynamic power dissipation
- Plot power dissipation of CMOS logic circuits as a function of operating frequency
- Plot power dissipation of CMOS logic circuits as a function of power supply voltage
- Describe the function and utility of decoupling capacitors

Outline

- Overview
- Dynamic power dissipation
- Power dissipation as a function of operating frequency
- Power dissipation as a function of supply voltage
- Current spikes and decoupling

Overview

- Definition:** The power dissipation (consumption) of a CMOS circuit whose output is *not changing* is called **static (quiescent) power dissipation**
- Most CMOS circuits have **very low** static power dissipation
- CMOS circuits only dissipate a significant amount of power during **transitions** – this is called **dynamic power dissipation**

Dynamic Power Dissipation


- Sources of dynamic power dissipation:
 - the partial “short-circuiting” of the CMOS output structure (e.g., when the input voltage is not close to one of the power supply rails) – called “**P_T**” (**power due to output transitions**)
 - the capacitive load on the output (power is dissipated in the “on” resistance of the active transistor to charge/discharge the capacitive load) – called “**P_L**” (**power due to charging/discharging load**)

Power Consumption

- Total dynamic power dissipation ($P_T + P_L$) is proportional to the **square** of the power supply voltage times the transition frequency
- Conclusions:
 - power dissipation increases **linearly** as the frequency of operation increases
 - reducing the power supply voltage results in a **quadratic** reduction of the power dissipation


187

 Example - A microcontroller can operate over a frequency range of 0 Hz to 10 MHz, and dissipates 100 mW when operated at 10 MHz; plot its power dissipation over the specified frequency range



188

 Example - A microcontroller can operate over a power supply range of 1 to 5 volts, and dissipates 100 mW when operated at 5 VDC; plot its power dissipation over the specified power supply range



189


Current Spikes and Decoupling

- When a CMOS gate output changes state, the P- and N-channel transistors are both partially on simultaneously, causing a **current spike**
- Current spikes often show up as **noise** on the power supply and ground connections
- **Decoupling capacitors** (between Vcc and GND) must be distributed throughout a printed circuit board (PCB) to serve as a **source of instantaneous current** during output transitions – **this helps mitigate noise and improve signal quality**

190

Decoupling Capacitors

 - Decoupling capacitors should be located as **physically close** as possible to each IC
- Use 0.1 μF decoupling capacitors for system frequencies up to 15 MHz
- Above 15 MHz, use 0.01 μF decoupling capacitors



191

Clicker Quiz

192

1. Assume a CMOS microprocessor dissipates **100 milliwatts** of power when operated at a clock frequency of **100 MHz** with a supply voltage of **5 V**. If the frequency of operation is reduced from **100 MHz to 40 MHz** (and the supply voltage remains 5 V), the power dissipation will be reduced to:

A. 16 mW B. 25 mW C. 40 mW D. 64 mW E. none of these

193

2. Assume a CMOS microprocessor dissipates **100 milliwatts** of power when operated at a clock frequency of **100 MHz** with a supply voltage of **5 V**. If the supply voltage is reduced from **5 V to 4 V** (and the frequency of operation remains 100 MHz), the power dissipation will be reduced to:

A. 16 mW B. 25 mW C. 40 mW D. 64 mW E. none of these


194

3. Assume a CMOS microprocessor dissipates **100 milliwatts** of power when operated at a clock frequency of **100 MHz** with a supply voltage of **5 V**. If the frequency of operation is reduced to **1 Hz** (and the supply voltage remains 5 V), the power dissipation will be reduced to (approximately):

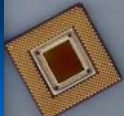A. 16 mW B. 25 mW C. 40 mW D. 64 mW E. none of these

195

Purdue IM:PACT* Spring 2019 Edition
*Instruction Matters: Purdue Academic Course Transformation



Introduction to Digital System Design

Module 1-I

Schmitt Triggers and Transmission Gates

Reading Assignment:
DDPP 4th Ed. pp. 129-131, 5th Ed. Pp. 778-781

Learning Objectives:

- Define hysteresis and describe the operation of Schmitt-trigger inputs
- Describe the operation and utility of a transmission gate

Outline:

- Overview
- Schmitt-trigger inputs
- Transmission gates

196

Overview

- The basic CMOS circuit has been “tailored” in many ways to produce gates for specific applications
- This circuit tailoring has been motivated by the need for:
 - higher performance than can be achieved with “standard” NAND/NOR gates
 - “conditioning” noisy, slowly changing logic signals
 - allowing logic elements to communicate via buses

197

Schmitt-Trigger Inputs

- A **Schmitt trigger** is a special circuit that shifts the switching threshold depending on whether the input is changing from **LOW-to-HIGH** (V_{T+}) or from **HIGH-to-LOW** (V_{T-})
- The difference between the two thresholds is called **hysteresis**

Copyright © 2000 by Prentice Hall, Inc. Digital Design: Principles and Practices, 3/e

Symbol used to denote hysteresis

Comparison of an Ordinary Inverter to a Schmitt Trigger for a Noisy, Slowly Changing Input Signal

Copyright © 2000 by Prentice Hall, Inc. Digital Design: Principles and Practices, 3/e

Regular Inverter

Schmitt trigger

Comparison of an Ordinary Inverter to a Schmitt Trigger for a Noisy, Slowly Changing Input Signal

Copyright © 2000 by Prentice Hall, Inc. Digital Design: Principles and Practices, 3/e

Regular Inverter

Schmitt trigger

Schmitt-Trigger Inputs

- Observations:**
 - Schmitt-trigger inputs have **better noise immunity** margin than ordinary gates for **noisy or slowly changing signals**
 - “Distorted” logic signals of this type typically occur in **physically long connections**, such as I/O buses and computer interface cables

Rule of “foot” – Logic-level signals can be sent reliably over a cable for only a **few feet**

Transmission Gates

- The P- and N-channel transistor pair can be connected together to form a logic-controlled switch, called a **transmission gate**
- Control signals EN_L and EN are at opposite levels
- When EN is asserted, there is a **low-impedance connection between A and B**; when EN is negated, A and B are disconnected

A high performance multiplexer (input selector switch) can be constructed using a pair of transmission gates and an inverter

Purdue IM:PACT* Spring 2019 Edition
 *Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 1-J

Three-State and Open-Drain Outputs

Reading Assignment:
 DDP 4th Ed. pp. 132-136, 138-141;
 5th Ed., pp. 781-785, 787-790

Learning Objectives:

- Define high-impedance state and describe the operation of a tri-state buffer
- Define open drain as it applies to a CMOS logic gate output and calculate the value of pull-up resistor needed
- Describe how to create "wired logic" functions using open drain logic gates
- Calculate the value of pull-up resistor needed for an open drain logic gate

Outline

- Three-state (tri-state) outputs
- CMOS tri-state buffer circuit
- Tri-state buffer application – buses
- Tri-state buffer float delay
- Open drain outputs
- Driving LEDs
- Wired logic
- Pull-up resistor calculations

Three-State (Tri-State) Outputs

- Definition:** A gate output that has a third "electrical state" is called a **three-state output** (or **tri-state output**)
- This third electrical state is called the **high impedance, Hi-Z, or floating state**
- In the high impedance state, the gate output effectively appears to be **disconnected** from the rest of the circuit
- Three-state devices have an extra input, typically called the **Output Enable (OE)**, for enabling data to "flow through" the device (when asserted) or placing the output in the high impedance state (when negated)

Basic CMOS Logic Circuit Revisited

- Calculate V_{out} for the case $A=5V, B=0$
- P-ch device is "off" ($R_{DS} = 500,000 \Omega$)
- N-ch device is "off" ($R_{DS} = 500,000 \Omega$)
- $V_{out} = 5 \times (500,000 / 1,000,000) = 2.5 V$
- $P_{dissipation} = 5^2 / 1,000,000 = 0.025 mW$
- Here, V_{out} is effectively disconnected (in the "Hi-Z state") when A is high and B is low
- Use OE (output enable) signal to force A high and B low when OE is negated

CMOS Tri-State Buffer Circuit

EN	A	B	C	D	Q1	Q2	OUT
L	L	H	L	L	off	off	Hi-Z
L	H	H	L	L	off	off	Hi-Z
H	L	L	H	H	on	off	L
H	H	L	L	L	off	on	H

Basic variations: The buffer may be inverting or non-inverting, and the tri-state enable can either be active low or active high

CMOS Tri-State Buffer Circuit

EN	A	B	C	D	Q1	Q2	OUT
L	L	H	L	L	off	off	Hi-Z
L	H	H	L	L	off	off	Hi-Z
H	L	L	H	H	on	off	L
H	H	L	L	L	off	on	H

Basic variations: The buffer may be inverting or non-inverting, and the tri-state enable can either be active low or active high

Driving LEDs

- One application for open-drain outputs is driving light-emitting diodes (LEDs) at **higher currents** than conventional gates

O.D. outputs can typically **sink more current** than conventional gates

$$R = (V_{CC} - V_{OL} - V_{LED}) / I_{LED}$$

Wired Logic

- Definition: **Wired logic** is performed if the outputs of several open-drain gates are tied together with a single pull-up resistor

Caution: This ONLY works for open-drain outputs!

Pull-up Resistor Calculations

- In open-drain applications, two calculations bracket the allowable values of the pull-up resistor R:
 - LOW** The sum of the current through R plus the LOW state input currents of the gate inputs driven **must not exceed** the $I_{OL,max}$ of the active device
 - HIGH** The voltage drop across R in the HIGH state **must not reduce** the output voltage below the $V_{IH,min}$ of the driven gate inputs

Example - Calculate a suitable value of pull-up resistor to use with the following circuit:

Specifications (hypothetical data):

- Off-state leakage current of O.D. NAND gate output: $+3 \mu A$
- I_{IH} and I_{IL} required by inverter input: $\pm 1 \mu A$
- V_{IH} desired for inverter input: 4.9 V
- $I_{OL,max}$ of O.D. NAND gate output: $+10 \text{ mA}$ @ $V_{OL} = 0.3 \text{ V}$

Solution, maximum R Value – based on V_{IH} desired

$V_R = 0.1 \text{ V}$ $I_R = 10 \mu A$
 $R_{max} = 0.1 / 0.00001 = 10,000 \Omega$

Specifications (hypothetical data):

- Off-state leakage current of O.D. NAND gate output: $+3 \mu A$
- I_{IH} and I_{IL} required by inverter input: $\pm 1 \mu A$
- V_{IH} desired for inverter input: 4.9 V
- $I_{OL,max}$ of O.D. NAND gate output: $+10 \text{ mA}$ @ $V_{OL} = 0.3 \text{ V}$

Solution, minimum R Value – based on $I_{OL,max}$ of one gate

This represents the "worst case" for I_{OL} – why? Here, can safely ignore leakage and I_{IL} currents – why?

$V_R = 4.7 \text{ V}$ $I_R \approx 10 \text{ mA}$
 $R_{min} = 4.7 / 0.01 = 470 \Omega$

Specifications (hypothetical data):

- Off-state leakage current of O.D. NAND gate output: $+3 \mu A$
- I_{IH} and I_{IL} required by inverter input: $\pm 1 \mu A$
- V_{IH} desired for inverter input: 4.9 V
- $I_{OL,max}$ of O.D. NAND gate output: $+10 \text{ mA}$ @ $V_{OL} = 0.3 \text{ V}$

Conclusion – a pull-up resistor ranging from $470\ \Omega$ (R_{min}) to $10,000\ \Omega$ (R_{max}) will satisfy the specified constraints

Note: Picking R_{min} will minimize the rise time, while picking R_{max} will minimize the power dissipation

Specifications (hypothetical data):

- Off-state leakage current of O.D. NAND gate output: $+3\ \mu\text{A}$
- I_{IH} and I_{IL} required by inverter input: $\pm 1\ \mu\text{A}$
- V_{IH} desired for inverter input: $4.9\ \text{V}$
- I_{OLmax} of O.D. NAND gate output: $+10\ \text{mA}$ @ $V_{OL} = 0.3\ \text{V}$

223

Follow-up – “prove” the “worst case” scenario ($R = 470\ \Omega$)

This represents the “worst case” for (single gate output) I_{OL} – why?

Power dissipation of circuit is $I_R^2 \times R_{eq} = 0.01^2 \times 500 \approx 50\ \text{mW}$

Means that the “on” resistance of an O.D. NAND gate used here is $V_{OL} / I_{OLmax} = 0.3/0.01 = 30\ \Omega$

The equivalent load impedance of circuit (across power supply) is $470+30 = 500\ \Omega$

Specifications (hypothetical data):

- Off-state leakage current of O.D. NAND gate output: $+3\ \mu\text{A}$
- I_{IH} and I_{IL} required by inverter input: $\pm 1\ \mu\text{A}$
- V_{IH} desired for inverter input: $4.9\ \text{V}$
- I_{OLmax} of O.D. NAND gate output: $+10\ \text{mA}$ @ $V_{OL} = 0.3\ \text{V}$

224

Follow-up – “prove” the “worst case” scenario ($R = 470\ \Omega$)

Can still safely ignore leakage and I_{IL} currents – why?

Power dissipation of circuit is $I_R^2 \times R_{eq} = 0.0103^2 \times 485 \approx 51.5\ \text{mW}$

Next, turn on two O.D. gates

The equivalent load impedance of circuit is $470+15 = 485\ \Omega$ (because have two $30\ \Omega$ “on” resistances in parallel)

I_R is now $5 / 485 = 0.0103\ \text{A} = 10.3\ \text{mA}$, which is split between the two gates that are “on”

225

Follow-up – “prove” the “worst case” scenario ($R = 470\ \Omega$)

Can still safely ignore leakage and I_{IL} currents – why?

Power dissipation of circuit is $I_R^2 \times R_{eq} = 0.0104^2 \times 480 \approx 52\ \text{mW}$

Conclusions: As more O.D. gates are turned on, the amount of current each of them (individually) has to sink is reduced; therefore, the first case (single gate “on”) is the “worst” one with respect to I_{OL}

Also, power dissipation increases slightly as more O.D. gates are turned on.

Finally, turn on all three O.D. gates

The equivalent load impedance of circuit is $470+10 = 480\ \Omega$ (because have three $30\ \Omega$ “on” resistances in parallel)

I_R is now $5 / 480 = 0.0104\ \text{A} = 10.4\ \text{mA}$, which is split among the three gates that are “on”

226

Follow-up – compare power dissipation of circuit using R_{min} vs. R_{max} as the pull-up resistor

R_{max} (10,000 Ω)

For case where all gates are on:

$R_{eq} = 10,000 + 10 = 10,010\ \Omega$ (recall “on” resistance of each gate is $30\ \Omega$)

$I_R \approx 5 / 10,010 \approx 0.5\ \text{mA}$ (note - split among all three gate outputs)

$P_{dissipation} = I_R^2 \times R_{eq} \approx 2.5\ \text{mW}$

Note: V_{IL} of inverter is nearly $0\ \text{V}$

227

Follow-up – compare power dissipation of circuit using R_{min} vs. R_{max} as the pull-up resistor

R_{max} (10,000 Ω)

For case where all gates are off:

$V_R = 0.1\ \text{V}$ $I_R = 10\ \mu\text{A}$


$P_{dissipation} = I_R^2 \times R = 1\ \mu\text{W}$

Conclusion: Power dissipation when R_{max} is used does not exceed $2.5\ \text{mW}$ (vs. $52\ \text{mW}$ for R_{min}); therefore, use of R_{max} minimizes the power dissipation

Note: V_{IH} of inverter is $4.9\ \text{V}$

228

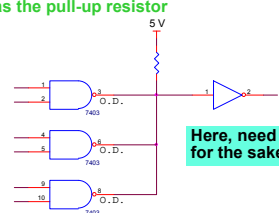Follow-up – compare rise time estimates of circuit using R_{min} vs. R_{max} as the pull-up resistor




Here, need to know the capacitive load (C_L); for the sake of analysis, assume it is 100 pF

Comparison:
 For R_{min} , rise time estimate is $470 \times 100 \times 10^{-12} = 47$ ns
 For R_{max} , rise time estimate is $10,000 \times 100 \times 10^{-12} = 1000$ ns
Conclusion: rise time for R_{max} case is considerably longer


229

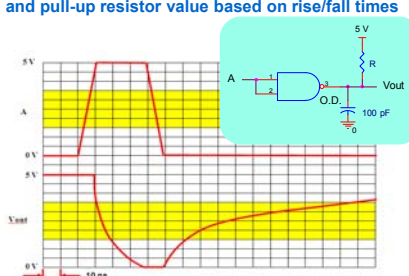Example – Estimate the “on” resistance of an O.D. gate and pull-up resistor value based on rise/fall times



230

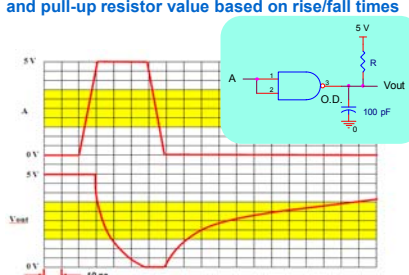Example – Estimate the “on” resistance of an O.D. gate and pull-up resistor value based on rise/fall times




fall time = 10 ns = $R_{on} \times 100$ pF $\rightarrow R_{on} = 100\Omega$

231

Clicker Quiz

232

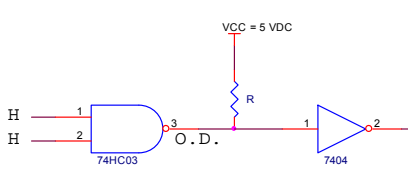

Assume that measurements taken in laboratory reveal that a 74HC03 (open-drain CMOS NAND gate) will produce a $V_{OL} = 0.2$ V when sinking +2 mA of current. Also, assume that the I_{IH} required by a 7404 (standard-series TTL inverter) to recognize a logic “0” is -0.4 mA and that its I_{IH} (to recognize a logic “1”) is +40 μ A.

233

1. Based on the laboratory measurements cited in the figure, what is the “ON” resistance of the 74HC03’s active output device?

- A. 10 Ω
- B. 20 Ω
- C. 100 Ω
- D. 1000 Ω
- E. none of the above

234

2. If the capacitive load on the output of the NAND gate is **20 pF**, estimate the **fall time** of the signal at the input to the inverter (assuming "ON" resistance calculated in previous problem):

- A. 2 ns
- B. 16 ns
- C. 20 ns
- D. 160 ns
- E. none of the above

235

3. Calculate the value of the pull-up resistor that allows the open-drain NAND gate to produce a $V_{OL} = 0.2\text{ V}$ when sinking **2 mA** of current (i.e., $I_{OL} = +2\text{ mA}$) and pulling the input of the 7404 low.

- A. 1000 Ω
- B. 2000 Ω
- C. 3000 Ω
- D. 8000 Ω
- E. none of the above

I_{IH} required by 7404 to recognize logic "0" input is -0.4 mA

236

4. If the capacitive load on the output of the NAND gate is **20 pF**, estimate the **rise time** of the signal at the input to the inverter assuming a pull-up resistor value of **3000 Ω** (calculated in previous problem):

- A. 2 ns
- B. 16 ns
- C. 20 ns
- D. 60 ns
- E. none of the above

237

5. Assuming that the off-state leakage current of the 74HC03 is **+10 μA** , calculate the value of the pull-up resistor that produces a $V_{IH} = 4.5\text{ V}$ at the 7404 input.

- A. 4000 Ω
- B. 9000 Ω
- C. 10,000 Ω
- D. 90,000 Ω
- E. none of the above

I_{IH} required by 7404 to recognize logic "1" input is 40 μA

238