

Purdue IM: PACT* Spring 2019 Edition
*Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 3 Sequential Logic Circuits

Glossary of Common Terms

- **SEQUENTIAL LOGIC CIRCUIT** – *next* output depends on its present inputs and its present state
- **STATE** – collection of state variables whose values at any one time contain all the information about the past necessary to account for the circuit's future behavior
- **BI-STABLE** – a logic device with two stable states
- **LATCH** – sequential circuit that watches all of its inputs *continuously* and changes its outputs *at any time* it is enabled to do so (independent of a clocking signal)

Glossary of Common Terms

- **FLIP-FLOP** – sequential circuit that samples its inputs and *changes its outputs only* at times determined by a *clocking signal*
- **FEEDBACK SEQUENTIAL CIRCUIT** – uses ordinary gates and feedback loops to create sequential circuit building blocks such as latches and flip-flops
- **CLOCKED SYNCHRONOUS STATE MACHINE** – uses latches or flip-flops to create circuits whose inputs are examined and whose outputs change state in accordance with a controlling clock signal

Glossary of Common Terms


- **PRESENT STATE – NEXT STATE (“NEXT STATE” or “PS-NS”) EQUATIONS** – equations that describe the next state of a sequential circuit based on its present inputs and present state
- **CHARACTERISTIC EQUATION** – a next state equation that characterizes the behavior of a latch or flip-flop
- **STATE TRANSITION DIAGRAM** – a graph that depicts the state transition behavior of a sequential circuit
- **TIMING CHART** – a chart that depicts the timing behavior of a sequential circuit

Glossary of Common Terms

- **EXCITATION EQUATIONS** – equations that describe the inputs needed by sequential circuit memory elements (latches or flip-flops) to enable the circuit to transition from its present state to the desired next state
- **SEQUENCE GENERATOR** – a state machine that generates a (periodic) pre-defined output pattern of signal assertions
- **COUNTER** – a state machine that has a closed sequence of states
- **SEQUENCE RECOGNIZER** – a state machine that responds to a pre-defined input pattern of signal assertions and produces corresponding output signal assertions

Module 3

- **Learning Outcome:** “An ability to analyze and design sequential logic circuits”
 - A. Bi-stable Elements
 - B. Set-Reset (S-R) and Data (D) Latches
 - C. Data (D) and Toggle (T) Flip-Flops
 - D. State Machine Structure and Analysis
 - E. Clocked Synchronous State Machine Synthesis
 - F. State Machine Design Examples: Sequence Generators
 - G. State Machine Design Examples: Counters and Shift Registers
 - H. State Machine Design Examples: Sequence Recognizers

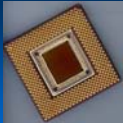

Purdue IM: PACT* Spring 2019 Edition
*Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 3-A Bi-stable Elements

Reading Assignment:

DDPP 4th Ed. pp. 521-526, DDPP 5th Ed. pp. 495-499

Learning Objectives:

- Describe the difference between a combinational logic circuit and a sequential logic circuit
- Describe the difference between a feedback sequential circuit and a clocked synchronous state machine
- Define the state of a sequential circuit
- Define active high and active low as it pertains to clocking signals
- Define clock frequency and duty cycle
- Describe the operation of a bi-stable and analyze its behavior
- Define metastability and illustrate how the existence of a metastable equilibrium point can lead to a random next state

Outline

- Overview
- Finite state machines
- Clock signal properties
- Types of sequential circuits
- Bi-stable elements
 - Digital analysis
 - Analog analysis
- Metastable behavior

Overview


- Logic circuits are classified into two types:
 - a **combinational** logic circuit is one whose outputs depend only on its current inputs
 - a **sequential** logic circuit is one whose outputs depend not only on its current inputs, but also its **current state** (arrived at by its **past** sequence of inputs)
- The **state** of a sequential circuit is a collection of **state variables** whose values at any one time contain all the information about the past necessary to account for the circuit's future behavior

Finite State Machines

- In a digital logic circuit, state variables are binary values – a circuit with **n** binary state variables has **2ⁿ** possible states
- Since there are a only finite number of states possible, sequential circuits are sometimes called **finite state machines**
- The state changes of most sequential circuits occur at times specified by a free-running **CLOCK** signal

Clock Signal Properties

- By convention, a **CLOCK** signal is **active high** if state changes occur in response to the clock signal's **rising** edge (or when it is **high**)
- Similarly, a **CLOCK** signal is **active low** if state changes occur in response to the clock signal's **falling** edge (or when it is **low**)
- The **clock period** is the time between successive transitions in the same direction
- The **clock frequency** (measured in Hertz, or cycles-per-second) is the **reciprocal** of the clock period
- The **duty cycle** is the percentage of time that the clock signal is at its asserted level

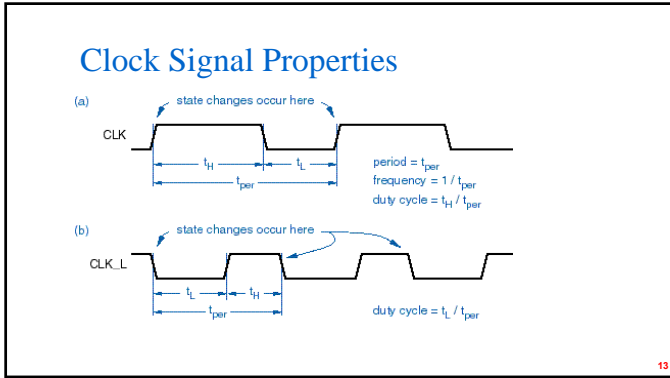

Types of Sequential Circuits

- There are two basic types of sequential circuits that account for the majority of practical discrete designs:
 - a **feedback sequential circuit** uses ordinary gates and feedback loops to create sequential circuit building blocks such as latches and flip-flops
 - a **clocked synchronous state machine** uses latches and flip-flops (in particular, edge-triggered "D" flip-flops) to create circuits whose inputs are examined and whose outputs change state in accordance with a controlling clock signal



Bi-stable Elements

- The "simplest" sequential circuit consists of a pair of inverters forming a feedback loop:

- This element has no inputs and therefore no way of controlling or changing its state
- When power is first applied, it randomly comes up in one state or the other and stays there forever ("not very useful")

Digital Analysis of Bi-stable

- This circuit is called a **bi-stable** because, based on (strictly) digital analysis, it has **two** stable states:
 - if Q is HIGH, then the bottom inverter has a high input and a LOW output, which forces the top inverter's output HIGH
 - if Q is LOW, then the bottom inverter has a LOW input and a HIGH output, which forces Q to go LOW
- Based on this analysis, a single state variable ("Q") could be used to describe the state of this circuit

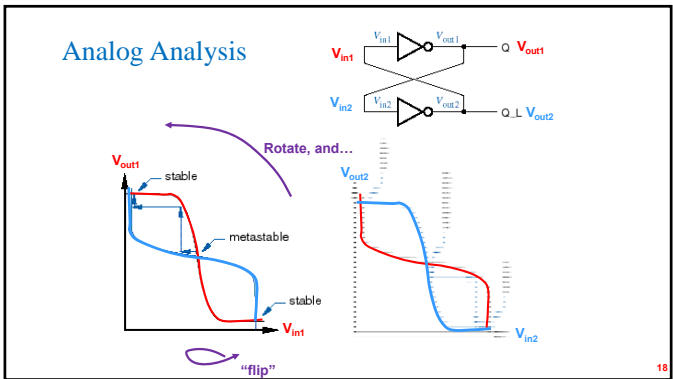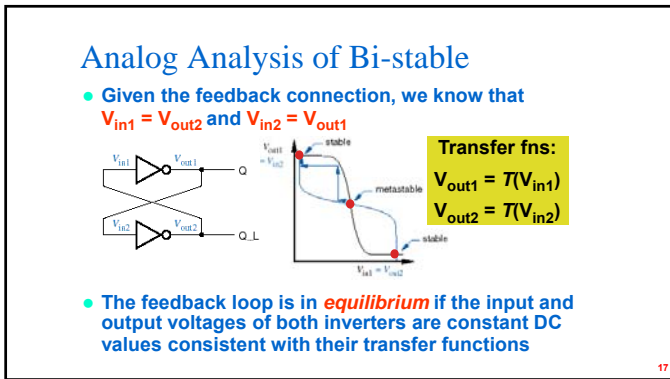

Analog Analysis of Bi-stable

- The **equilibrium points** can be found graphically – they are the points at which the two transfer functions meet:
 - the two **stable** equilibrium points correspond to the two states identified in the “digital” analysis, with Q (Q_L) either “0” (LOW) or “1” (HIGH)
 - the **metastable** equilibrium point occurs with V_{out1} and V_{out2} about halfway between a valid logic “1” voltage and a valid logic “0” voltage – here, Q and Q_L are not valid logic signals but the loop equations are satisfied

Metastable Behavior

- The **metastable point is not truly stable**, because **random noise** will tend to drive a circuit operating at the metastable point toward one of the stable operating points

The graph shows two transfer functions forming a loop. The intersection points are labeled 'stable' and 'metastable'. The metastable point is at the center of the loop, while the two stable points are at the corners. Arrows indicate that any deviation from the metastable point leads towards one of the stable points.

Metastable Behavior

- Metastable behavior of a bistable can be compared to the behavior of a ball dropped onto a hill:
 - if ball is dropped from overhead, it will probably roll down immediately to one side of the hill or the other
 - if ball lands right at the top, it may sit there a while before random forces start it rolling

A diagram of a hill with a ball on top. The top of the hill is labeled 'metastable' and the two slopes are labeled 'stable'. The ball is shown in a red position on the left slope and a green position on the right slope.

Metastable Behavior

- Important:** If the “simplest” sequential circuit is susceptible to metastable behavior, you can be sure that **all** sequential circuits are susceptible (and it is not something that only occurs at power-up)
- Consider what happens if we try to “kick” the ball from side of the hill to the other:

A diagram showing a ball on a hill. A person is shown kicking the ball from the left side to the right side. The ball is shown in a red position on the left slope and a green position on the right slope.

Purdue IM: PACT* Spring 2019 Edition
 *Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 3-B

Set-Reset (S-R) and Data (D) Latches

Reading Assignment:

DDPP 4th Ed. pp. 526-532, DDPP 5th Ed. pp. 499-504

Learning Objectives:

- Write present state – next state (PS-NS) equations that describes the behavior of a sequential circuit
- Draw a state transition diagram that depicts the behavior of a sequential circuit
- Construct a timing diagram that depicts the behavior of a sequential circuit
- Draw a circuit for a set-reset latch and analyze its behavior
- Discuss what is meant by “transparent” (or “data following”) in reference to the response of a latch

Outline


- Overview
- Set-Reset (S-R) latch
 - Basic operation
 - Timing charts
 - Normal operation
 - Response to 1-1 input combination
 - Response to a glitch/hazard
 - Propagation delays
 - Input pulse width
 - Variants
 - S'-R' latch
 - S-R latch with enable
 - Characteristic equation
- Data (D) latch
 - Propagation delays
 - Setup and hold times

Overview

- Definition:** A *latch* is a sequential circuit that watches all of its inputs *continuously* and changes its outputs *at any time*
- When a latch is *enabled*, it is *"open"* (i.e., its outputs *"follow"* its inputs)
- When a latch is *disabled* (its enable input is negated), it is *"closed"* (i.e., its outputs are *"frozen"* or *"latched"*)
- This behavior lends itself to the names *"data following"* and *"transparent"*
- Note:** Latches do not utilize a "clocking" signal; rather, they are "enabled" to open/close

S-R Latch

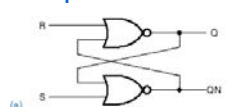
- An S-R ("set-reset") latch based on NOR gates can be implemented as follows:



S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

- It has a "set" (S) input and a "reset" (R) input and two outputs (Q and QN) that are normally complements of each other


S-R Latch

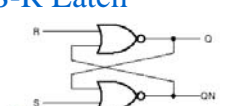


S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

- Asserting **S** *sets* (presets) the Q output to "1"
- Asserting **R** *resets* (clears) the Q output to "0"
- If both S and R are "0", the circuit behaves like the bistable element – a feedback loop retains one of two logic states, Q = 0 or Q = 1

S-R Latch

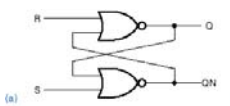


S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

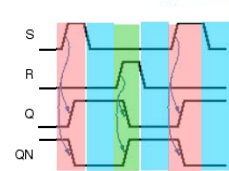


S-R Latch

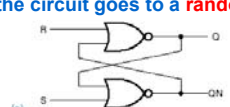- If **both S and R** are "1", both outputs go LOW; if **both S and R** return to "0" simultaneously, the circuit goes to a random next state




S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

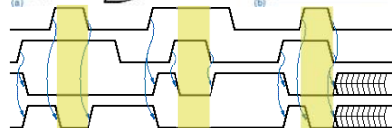

 Exercise

- Construct a timing chart for the S-R latch



- Solution:** Start by writing *next state equations* that describe the circuit, and from them construct a *present state - next state table*

$$Q(t+\tau) = R'(t) \cdot QN'(t)$$

$$QN(t+\tau) = S'(t) \cdot Q'(t)$$

33

Exercise

- PS-NS table:

$$Q(t+\tau) = R'(t) \cdot QN'(t) \quad QN(t+\tau) = S'(t) \cdot Q'(t)$$


Present State Q(t) QN(t)	Present Inputs: S(t) R(t)			
	00	01	10	11
00	11	01	10	00
01	01	01	00	00
10	10	00	10	00
11	00	00	00	00

Next State
Q(t+τ) QN(t+τ)

34

 Exercise


- From the PS-NS table, construct a state transition diagram



39

 Exercise


- From the state transition diagram, construct a timing chart



41

 Exercise


- From the state transition diagram, construct a timing chart



52

Exercise

- Note the propagation delays

 

62

Exercise

- Investigate the response of an S-R latch to the "1-1" input combination

Initial Conditions

Exercise

- Investigate the response of an S-R latch to the "1-1" input combination

Clicker Quiz

Q1. For the NOR-implemented SR latch, the following output combination **cannot occur at any time**:

- A. $Q=0, QN=0$
- B. $Q=0, QN=1$
- C. $Q=1, QN=0$
- D. $Q=1, QN=1$
- E. none of the above

Q2. If the input combination $S=0, R=1$ is applied to this circuit, the (steady state) output will be:

- A. $Q=0, QN=0$
- B. $Q=0, QN=1$
- C. $Q=1, QN=0$
- D. $Q=1, QN=1$
- E. none of the above

Q3. If the input combination $S=1, R=0$ is applied to this circuit, the (steady state) output will be:

- A. $Q=0, QN=0$
- B. $Q=0, QN=1$
- C. $Q=1, QN=0$
- D. $Q=1, QN=1$
- E. none of the above

Q4. If the **input** combination **S=1, R=1** is applied to this circuit, the (steady state) output will be:

- A. Q=0, QN=0
- B. Q=0, QN=1
- C. Q=1, QN=0
- D. Q=1, QN=1
- E. none of the above

105

Exercise

- Investigate the response of an S-R latch to a glitch or hazard

107

Exercise

- Investigate the response of an S-R latch to a glitch or hazard

108

S-R Latch Propagation Delays

- The propagation delay of a latch is the time it takes for a transition on an input signal to produce a transition on an output signal
- A given latch may have several different propagation delay specifications, one for each pair of input and output signals
- Also, the propagation delay may be different depending on whether the output makes a LOW-to-HIGH or HIGH-to-LOW transition
- Example: $t_{pLH(S \rightarrow Q)}$ is the *rise propagation delay* of the Q output in response to the S input being asserted (latch being "set")

109

S-R Latch Input Pulse Width

- Minimum-pulse-width specifications are usually given for the S and R inputs (the latch may go into the metastable state if a pulse shorter than $T_{PW(min)}$ is applied to S or R)

105

S'-R' Latch


- An S'-R' "S-bar, R-bar" latch – with *active low* set and reset inputs – can be built using NAND gates

S	R	Q	QN
0	0	1	1
0	1	1	0
1	0	0	1
1	1	last Q	last QN

106

S-R Latch with Enable

 
- An S'-R' latch can be modified to be sensitive to its inputs only when an enabling input "C" is asserted
- The circuit behaves like an S-R latch when C is "1", and retains its state when C is "0"
- If both S and R are "1" when C changes from "1" to "0", the next state is unpredictable and the output may become metastable



107

Exercise – Complete the PS-NS table for an S-R latch and derive its characteristic equation

S	R	Q	Q*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	d
1	1	1	d

 


$Q^* = S + R'Q$

111

Clicker Quiz

112

 


Present State X(t) Y(t)	Present Input A(t) B(t)			
	0 0	0 1	1 0	1 1
0 0				
0 1				
1 0				
1 1				

Next State
X(t+Δt) Y(t+Δt)

113

Q1. For the circuit shown, the following output combination **cannot occur at any time**:

 
- A. X=0, Y=0
- B. X=0, Y=1
- C. X=1, Y=0
- D. X=1, Y=1
- E. none of the above



123

Q2. If the **input** combination **A=0, B=1** is applied to this circuit, the (steady state) output will be:

 
- A. X=0, Y=0
- B. X=0, Y=1
- C. X=1, Y=0
- D. X=1, Y=1
- E. unpredictable



124

Q3. If the **input** combination **A=1, B=0** is applied to this circuit, the (steady state) output will be:

 
- A. X=0, Y=0
- B. X=0, Y=1
- C. X=1, Y=0
- D. X=1, Y=1
- E. unpredictable



125

Q4. If the **input** combination **A=0, B=0** is applied to this circuit, **followed immediately** by the **input** combination **A=1, B=1**, the (steady state) output will be:

 
- A. X=0, Y=0
- B. X=0, Y=1
- C. X=1, Y=0
- D. X=1, Y=1
- E. unpredictable



126

Q5. If the **propagation delay** of each gate is **10 ns**, the **minimum length of time** that (valid) input combinations need to be asserted **in order to prevent metastable behavior** is:

 
- A. 10 ns
- B. 20 ns
- C. 30 ns
- D. 40 ns
- E. none of the above



127

Transparent D Latch

 - In situations where we simply need to store a single "bit" of information, a **D ("data") latch** can be used



- Note that a D latch is just an S-R latch, with D connected to the S input and D' connected to the R input (this eliminates the troublesome "1-1" input combination)

128

Transparent D Latch

- When the enable input C is asserted, the latch is said to be "open" and the path from the D input to the Q output is "transparent" – hence the name **transparent latch**
- When the enable input C is negated, the latch "closes" – the Q output retains its last value and no longer changes in response to D




129

D Latch Propagation Delays

- There are four propagation delay parameters that must be considered:

 - $t_{pLH(C \rightarrow Q)}$ and $t_{pHL(C \rightarrow Q)}$
- $t_{pLH(D \rightarrow Q)}$ and $t_{pHL(D \rightarrow Q)}$



130

D Latch Setup and Hold Times

- There is a "window" of time around the falling edge of C when the D input **must not change**
 - the time **prior** to this edge that the D input must remain stable is the **setup time**
 - the time **after** this edge that the D input must remain stable is the **hold time**

131

Clicker Quiz

132

Q1. A "D" latch is called **transparent** because its output:

- is always equal to its input
- is equal to its input when the latch is closed
- is equal to its input when the latch is open
- changes state as soon as the latch is clocked
- none of the above

133

Purdue IM:PACT* Spring 2019 Edition
*Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 3-C

Data (D) and Toggle (T) Flip-Flops

134

Reading Assignment:

DDPP 4th Ed. pp. 532-535, 541-542; DDPP 5th Ed. pp. 504-506, 507-508

Learning Objectives:

- Draw a circuit for an edge-triggered data ("D") flip-flop and analyze its behavior
- Compare the response of a latch and a flip-flop to the same set of stimuli
- Define setup and hold time and determine their nominal values from a timing chart
- Determine the frequency and duty cycle of a clocking signal
- Identify latch and flip-flop propagation delay paths and determine their values from a timing chart
- Describe the operation of a toggle ("T") flip-flop and analyze its behavior
- Derive a characteristic equation for any type of latch or flip-flop

135

Outline

- Overview
- Positive edge-triggered D flip-flop
- Negative edge-triggered D flip-flop
- D flip-flop characteristic equation
- D flip-flop setup and hold times
- D flip-flop with enable
- Edge-triggered T flip-flop
- T flip-flop characteristic equation
- Flip-flop timing parameters
- Response of latch vs. flip-flop
- Summary

136

Overview

- Definition: A **flip-flop** is a sequential circuit that samples its inputs and **changes its outputs only** at times determined by a **clocking signal** ("CLK")
- Flip-flops change state in response to the **transition** ("edge") of a clocking signal
 - **positive-edge-triggered** flip-flops change state on the **low-to-high** transition of a clocking signal
 - **negative-edge-triggered** flip-flops change state on the **high-to-low** transition of a clocking signal

Positive Edge-Triggered D Flip-Flop

- A **positive-edge-triggered D flip flop** combines a pair of D latches to create a circuit that samples its D input and changes its Q and QN outputs **at the rising edge** of a controlling CLOCK (CLK) signal
 - the **first** latch, called the **master**, opens and follows the input when CLK is 0
 - the **second** latch, called the **slave**, opens and reads the master's output when CLK is 1 – this is when the output state change occurs (note that the master latch is **closed** at this point and thus **"immune"** to input changes)

Positive Edge-Triggered D Flip-Flop

- A **triangle** on the D flip-flop's CLK input indicates edge-triggered behavior and is called a **dynamic input indicator**
- The characteristic equation of a D flip-flop is $Q^* = D$ – i.e. the next state is the current input, shorthand for $Q(t+\Delta) = D(t)$, where Δ is the **clocking period**
- D flip-flops are included in the macrocells of virtually all PLDs, and are therefore the "most popular" (and **easiest**) way to realize clocked synchronous state machines

Positive Edge-Triggered D Flip-Flop

One way an edge-triggered D flip flop can be constructed is illustrated below

Negative Edge-Triggered D Flip-Flop

- D flip flops can also be designed to be **negative-edge-triggered**
- An **inversion bubble** on the CLK input is used to indicate that a flip flop is triggered on the **HIGH-to-LOW** transition of the CLK signal

Exercise – Complete the PS-NS table for an D flip-flop and derive its characteristic equation

D	Q	Q*
0	0	0
0	1	0
1	0	1
1	1	1

	D'	D
Q'	0	1
Q	0	1

$Q^* = \underline{\hspace{2cm} D \hspace{2cm}}$

D Flip-Flop Setup and Hold Times

- For edge-triggered flip-flops, all propagation delays are measured from the **rising edge** of the CLK signal
- The "window" during which the D input must remain stable is t_{setup} **prior** to the CLK edge and t_{hold} **after** the CLK edge

146

D Flip-Flop with Enable

- A commonly desired function in D flip-flops is to **retain** the last value stored (rather than load a new one) at the clock edge
- This is accomplished by adding an enable input, called **EN** or **CE** (clock enable), which uses a **2:1 multiplexer** to control the value applied to the internal D flip-flop input

D	EN	CLK	Q	QN
0	1	↑	0	1
1	1	↑	1	0
x	0	↑	last Q	last QN
x	x	↑	last Q	last QN
x	x	↑	last Q	last QN

147

Edge-Triggered T Flip Flop

- A positive edge-triggered toggle (T) flip-flop changes to the **complement** of its former state ("toggles") in response to a positive clock edge **when enabled**
- The T input is used to enable/disable the flip-flop from toggling
 - when $T=0$, $Q^* = Q$ **stays in same state**
 - when $T=1$, $Q^* = Q'$ **toggles**
- The characteristic equation for a T flip-flop is $Q^* = T' \cdot Q + T \cdot Q' = T \oplus Q$

148

Edge-Triggered T Flip Flop

- A **T flip-flop** can be realized using a D flip-flop by implementing the T flip-flop characteristic equation

$$Q^* = T' \cdot Q + T \cdot Q' = T \oplus Q$$

149

Exercise – Complete the PS-NS table for a T flip-flop and derive its characteristic equation

T	Q	Q*
0	0	0
0	1	1
1	0	1
1	1	0

	T'	T
Q'	0	1
Q	1	0

$$Q^* = \underline{Q \cdot T' + Q' \cdot T} = Q \oplus T$$


152

Example – Flip-Flop Timing Parameters

The **clock pulse width** provided for the D flip-flop is 10 ns

153


Example – Flip-Flop Timing Parameters

 

The **clock period** provided for the D flip-flop is 30 ns

154


Example – Flip-Flop Timing Parameters

 

The **duty cycle** of the clocking signal is $10/30 \times 100\% = 33\%$

155


Example – Flip-Flop Timing Parameters

 

The **nominal setup time** provided for the D flip-flop is 5 ns

156


Example – Flip-Flop Timing Parameters

 

The **nominal hold time** provided for the D flip-flop is 15 ns

157


Example – Flip-Flop Timing Parameters

 

The $t_{PLH(C \rightarrow Q)} = t_{PLH(C \rightarrow Q_L)}$ of the D flip-flop is 10 ns

158


Example – Flip-Flop Timing Parameters

 


The $t_{PHL(C \rightarrow Q)} = t_{PHL(C \rightarrow Q_L)}$ of the D flip-flop is 5 ns

159


Clicker Quiz

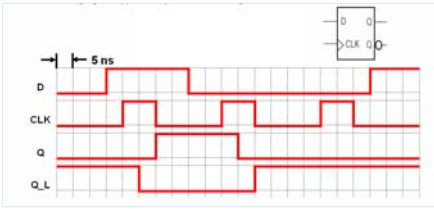

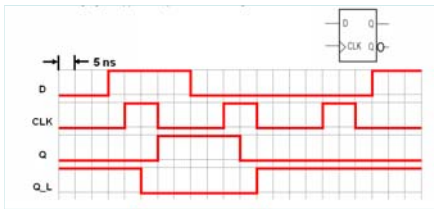
Q1. The **duty cycle** of the clocking signal is:
 A. 20% B. 33% C. 40% D. 67%
 E. none of the above



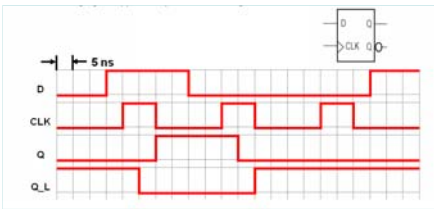
Q2. The **nominal setup time** provided for the D flip-flop is:
 A. 5 ns B. 10 ns C. 15 ns D. 20 ns
 E. none of the above



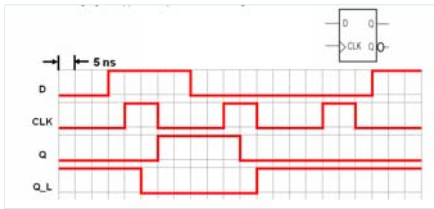Q3. The **nominal hold time** provided for the D flip-flop is:
 A. 5 ns B. 10 ns C. 15 ns D. 20 ns
 E. none of the above



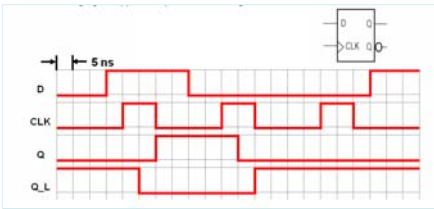Q4. The **clock pulse width** provided for the D flip-flop is:
 A. 5 ns B. 10 ns C. 15 ns D. 20 ns
 E. none of the above



Q5. The $t_{PLH(C \rightarrow Q)}$ of the D flip-flop is:
 A. 5 ns B. 10 ns C. 15 ns D. 20 ns
 E. none of the above

Q6. The $t_{PHL(C \rightarrow Q)}$ of the D flip-flop is:
 A. 5 ns B. 10 ns C. 15 ns D. 20 ns
 E. none of the above

Q7. **Metastable behavior** of an edge-triggered D flip-flop can be caused by:

- A. violating its minimum setup time requirement
- B. violating its minimum hold time requirement
- C. violating its minimum clock pulse width requirement
- D. all of the above
- E. none of the above

Example – Response of Latch vs. Flip-Flop

Assume a positive edge-triggered D flip-flop (X) and a transparent D latch (Y) are supplied the signals given on the timing chart (next slide). Plot the response of each, noting the initial states.

Assume the propagation delays of the flip-flop and latch are negligible relative to the period of “C”.

Example – Response of Latch vs. Flip-Flop

Summary

- Latches and flip-flops are the basic building blocks of virtually all sequential circuits
 - a *latch* is a sequential device that watches all of its inputs *continuously* and changes its outputs *at any time* (independent of a clocking signal)
 - a *flip-flop* is a sequential device that samples its inputs and *changes its outputs only* at times determined by a *clocking signal*
- Because the *functional behavior* of latches and flip flops is quite *different*, it is important to know which type is being used in a design

Purdue IM:PACT* Spring 2019 Edition
 *Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 3-D

Clocked Synchronous State Machine Structure and Analysis

Reading Assignment:

DDPP 4th Ed. pp. 542-553, DDPP 5th Ed. pp. 443-453

Learning Objectives:

- Identify the key elements of a clocked synchronous state machine: next state logic, state memory (flip-flops), and output logic
- Differentiate between Mealy and Moore model state machines, and draw a block diagram of each
- Analyze a clocked synchronous state machine realized as either a Mealy or Moore model

113

Outline

- Overview
- State machine structure
 - Moore machine
 - Mealy machine
- State machine analysis
 - Moore machine analysis
 - Mealy machine analysis

114

Overview

- “**State machine**” (or “**finite state machine**”) is a generic name given to **sequential circuits**
- “**Clocked**” indicates that the flip-flops employ a **CLOCK (CLK)** input
- “**Synchronous**” means that all the flip-flops in the state machine use the **same CLOCK** signal
- “**Analysis**” means to **analyze the behavior** of a given state machine
 - construct a PS-NS table
 - derive PS-NS equations
 - draw a state transition diagram
 - draw a timing chart

115


State Machine Structure

- Clocked synchronous state machines consist of three basic blocks:
 - **next state logic** – combinational circuitry that provides the “excitation” necessary to transition to the next state, based on the current state and the present inputs
 - **state memory (flip flops)** – set of N flip-flops that store the current state of the machine (providing 2^N distinct states)
 - **output logic** – combinational circuitry that uses the current state (and possibly current inputs) to determine the outputs generated

116

Moore Machine

 
- In a **Moore** machine, the outputs are **only** a function of the **current state**



117

Mealy Machine

 - In a **Mealy** machine, the outputs are a function of the **current state as well as the current inputs**



118

State Machine Structure

- With appropriate circuit or drawing manipulations, one state machine model can be mapped into another
- The exact classification of a state machine into one style or another is ultimately not very important
- What *is* important is how the structure chosen satisfies your design requirements

Characteristic Equations (Review)


- The characteristic equations of the various flip-flops described previously are:
 - S-R: $Q^* = S + R \cdot Q$
 - D: $Q^* = D$
 - T: $Q^* = Q \oplus T$
- We will use these characteristic equations as the basis for analyzing state machines
- Analysis in this context means *writing the next state equations* that describe the circuit's behavior

State Machine Analysis

- The analysis of a clocked synchronous state machine has four basic steps:
 - Determine the *next state* and the *output* functions based on the circuit diagram
 - Use the next state and output functions to construct a *present state - next state / output table (PS-NS / O)*
 - Draw a *state transition diagram* that presents the information tabulated in the present state - next state / output table in graphical form
 - Draw a *timing diagram* that shows the timing relationship between the input, output, and clocking signals


Exercise 1

- Analyze the following Mealy state machine:

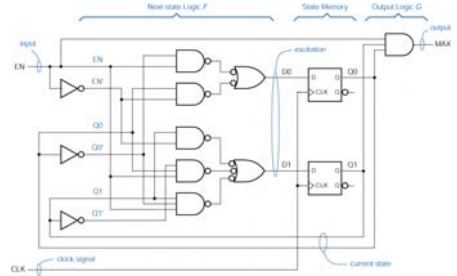

Exercise 1

- Analyze the following Mealy state machine:

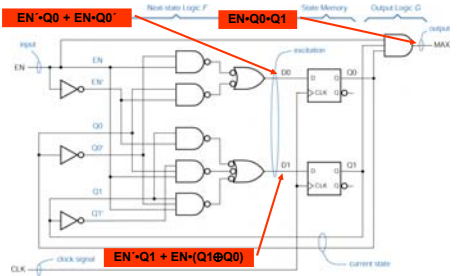

Exercise 1

- STEP 1: Write the next state equations for each D flip-flop and the output logic function

$$Q0^* = EN' \cdot Q0 + EN \cdot Q0' = EN \oplus Q0$$

$$Q1^* = EN' \cdot Q1 + EN \cdot (Q1 \oplus Q0)$$

$$MAX = EN \cdot Q0 \cdot Q1$$

Exercise 1


- STEP 2: Construct a PS-NS / O table

PS		PI		NS		Output
Q1	Q0	EN	Q1*	Q0*	MAX	
0	0	0	0	0	0	0
0	0	1	0	1	0	0
0	1	0	0	1	0	0
0	1	1	1	0	0	0
1	0	0	1	0	0	0
1	0	1	1	1	0	0
1	1	0	1	1	0	0
1	1	1	0	0	1	1

186

 Exercise 1


- STEP 3: Construct a Mealy state transition diagram



190

Exercise 1


- STEP 4: Draw a timing chart

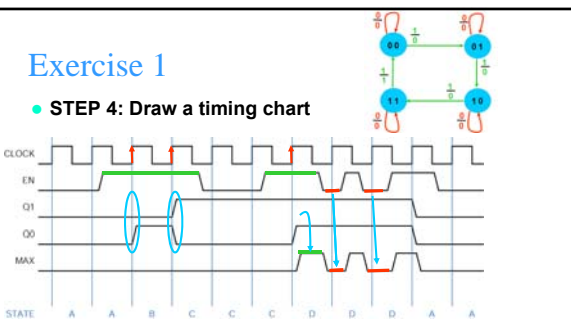

185

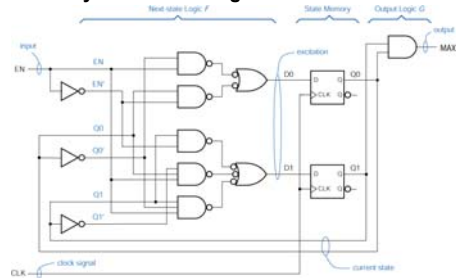Exercise 2


- Analyze the following Moore state machine:



196

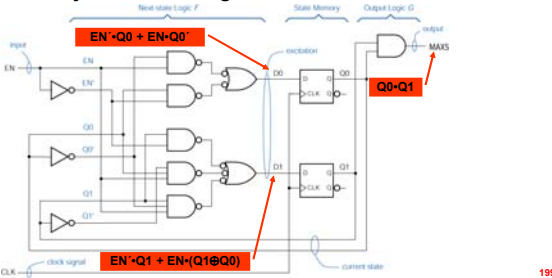Exercise 2

- Analyze the following Moore state machine:



199

Exercise 2

- STEP 1: Write the next state equations for each D flip-flop and the output logic function

$$Q0^* = EN' \cdot Q0 + EN \cdot Q0' = EN \oplus Q0$$

$$Q1^* = EN' \cdot Q1 + EN \cdot (Q1 \oplus Q0)$$

$$MAXS = Q0 \cdot Q1$$

200

Exercise 2


- STEP 2: Construct a PS-NS / O table

PS	PI	NS	Output
Q1 Q0	EN	Q1* Q0*	MAXS
0 0	0	0 0	0
0 0	1	0 1	0
0 1	0	0 1	0
0 1	1	1 0	0
1 0	0	1 0	0
1 0	1	1 1	0
1 1	0	1 1	1
1 1	1	0 0	1

201

 Exercise 2


- STEP 3: Construct a Moore state transition diagram



204

Exercise 2

- STEP 4: Draw a timing chart

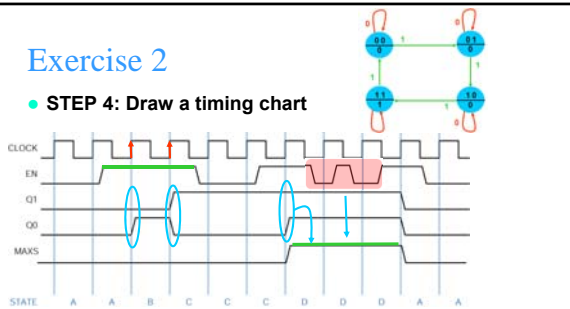

208

Purdue IM:PACT* Spring 2019 Edition
*Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 3-E
Clocked Synchronous State Machine Synthesis

Reading Assignment:

DDPP 4th Ed. pp. 553-566, 646-659, 682-689;
DDPP 5th Ed. pp. 453-471, 676-680, 525-527

Learning Objectives:

- Outline the steps required for state machine synthesis
- Derive the excitation table for any type of latch or flip-flop
- Discuss reasons why formal state-minimization procedures are seldom used by experienced digital system designers
- Draw block diagrams for Moore and Mealy type state machines and explain how each block can be coded in Verilog
- Draw a circuit for an oscillator and calculate its frequency of operation
- Draw a circuit for a bounce-free switch based on an S-R latch and analyze its behavior

210

Outline

- Overview
- State machine design steps
 - Derivation of flip-flop excitation tables
 - Flip-flop choice
- State machines in Verilog
 - Syntax and synthesis
 - Macrocell structure
- Clocking considerations
 - Periodic clock generation circuits
 - Timing diagram and specifications
 - Event clock generation circuits

211

Overview

- Designing a finite state machine (FSM) is a **creative process** that is, in many ways, like writing a computer program:
 - You have a fairly good idea of what the input and output signals should be, but perhaps an **imprecise description** of the desired relationship between them
 - During the design you may have to identify and choose among **different ways of doing things** – sometimes using common sense, sometimes arbitrarily
 - You may have to identify and handle **special cases** that weren't included in the original description

213

Overview

- Creative process...
 - You will probably have to keep track of several ideas in **your head** during the design process
 - Since the design process is **not an algorithm**, there's no guarantee that you can complete it using a finite number of states or lines of code
 - When you finally run the state machine or program, it will do **exactly** what you told it to do – no more, no less
 - There's **no guarantee** the thing will work the first time – you may have to debug and iterate the entire process

214

State Machine Design Steps

- State machine design steps
 - Given a word description, construct a **state/output table** or **transition diagram**
 - Minimize any "obvious" **redundant states** in the translated description
 - Choose a set of state variables and assign **binary state-variable combinations** to the named states
 - Substitute the **state-variable combinations** into the **state/output table** (and/or **state transition diagram**) to create a table that shows the desired next state-variable combination and output for each state/input combination

215

State Machine Design Steps

- State machine design steps...
 - If you haven't done so already, choose a **flip-flop or latch type** for the state memory
 - Construct an **excitation table** that shows the excitation values required to obtain the desired next state for each state-input combination
 - Derive **excitation equations** from the excitation table
 - Derive **output equations** from the transition/output table
 - Draw a **logic diagram** (or realize the equations directly in a PLD)

216

Example: Derive the excitation table for an S-R latch

S	R	Q	Q*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	d
1	1	1	d

Q	Q*	S	R
0	0	0	d
0	1		
1	0		
1	1		

217

Example: Derive the excitation table for an S-R latch

S	R	Q	Q*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	d
1	1	1	d

Q	Q*	S	R
0	0	0	d
0	1	1	0
1	0		
1	1		

218

Example: Derive the excitation table for an S-R latch

S	R	Q	Q*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	d
1	1	1	d

Q	Q*	S	R
0	0	0	d
0	1	1	0
1	0	0	1
1	1		

219

Example: Derive the excitation table for an S-R latch

S	R	Q	Q*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	d
1	1	1	d

Q	Q*	S	R
0	0	0	d
0	1	1	0
1	0	0	1
1	1	d	0

NOTE: Two excitation equations are required for each flip-flop...probably not desirable-

220

Example: Derive the excitation table for a T flip-flop

T	Q	Q*
0	0	0
0	1	1
1	0	1
1	1	0

Q	Q*	T
0	0	0
0	1	
1	0	
1	1	

221

Example: Derive the excitation table for a T flip-flop

T	Q	Q*
0	0	0
0	1	1
1	0	1
1	1	0

Q	Q*	T
0	0	0
0	1	1
1	0	
1	1	

222

Example: Derive the excitation table for a T flip-flop

T	Q	Q*
0	0	0
0	1	1
1	0	1
1	1	0

Q	Q*	T
0	0	0
0	1	1
1	0	1
1	1	

223

Example: Derive the excitation table for a T flip-flop

T	Q	Q*
0	0	0
0	1	1
1	0	1
1	1	0

Q	Q*	T
0	0	0
0	1	1
1	0	1
1	1	0

NOTE: Here, only one excitation equation is required for each flip-flop - a common application is binary counters

224

Example: Derive the excitation table for a D flip-flop

D	Q	Q*
0	0	0
0	1	0
1	0	1
1	1	1

Q	Q*	D
0	0	0
0	1	
1	0	
1	1	

225

Example: Derive the excitation table for a D flip-flop

D	Q	Q*
0	0	0
0	1	0
1	0	1
1	1	1

Q	Q*	D
0	0	0
0	1	1
1	0	
1	1	

226

Example: Derive the excitation table for a D flip-flop

D	Q	Q*
0	0	0
0	1	0
1	0	1
1	1	1

Q	Q*	D
0	0	0
0	1	1
1	0	0
1	1	

227

Example: Derive the excitation table for a D flip-flop

D	Q	Q*
0	0	0
0	1	0
1	0	1
1	1	1

Q	Q*	D
0	0	0
0	1	1
1	0	0
1	1	1

NOTE: For D flip-flops, Q*=D, which means the excitation equation is identical to the next state equation, which makes synthesis using D flip-flops very straight-forward~

228

Flip-Flop Choice

- Any type of latch or flip-flop (S-R, D, T) may be chosen for a sequential circuit's state memory; this choice, however, will determine *how much work* you will have to do when it's time to "turn the crank" (i.e., transform the next state equations into a circuit)
- Our focus for state machine synthesis will be on use of *edge-triggered D flip-flops*
 - they are incorporated directly into the PLDs used in lab
 - they require the *least amount of "crank work"* to realize next state equations
 - in Verilog, They result in cleaner, easier to read code

229

Clicker Quiz

230

Q1. Identify which statement concerning **state machine models** is **true**:

- A. Mealy and Moore models that represent equivalent state machines will **always** have the **same** number of states
- B. Mealy and Moore models that represent equivalent state machines will **always** have a **different** number of states
- C. any **Mealy model** can be transformed into an **equivalent Moore model**, and *vice-versa*
- D. Mealy and Moore models that represent equivalent state machines, when realized, will exhibit the **same observable behavior** (i.e., if placed in a "black box", their **observable behavior** would be **indistinguishable**)
- E. none of the above

231

Q2. An FSM design has 212 states; to **reduce the number of flip-flops required by one**, you would have to identify and eliminate _____ redundant state(s).

- A. 1
- B. 2
- C. 44
- D. 84
- E. none of the above

232

Q3. Formal **state-minimization procedures** are **seldom used** by most digital designers because:

- A. there are situations where *increasing* the number of states may simplify the design or reduce its cost
- B. the *designer can do more* to simplify a state machine [than using formal state-minimization procedures] *during the state-assignment phase* of the design
- C. by carefully matching state meanings to the requirements of the problem, experienced digital designers can produce state tables with a minimal or near-minimal number of states
- D. all of the above
- E. none of the above

Reference: *DDPP* p. 559 (4th Ed.), p. 461 (5th Ed.)

233

Blocking vs Non-Blocking Assignments in Verilog

Blocking Statements (Out = In)

- The = symbol represents a **blocking procedural assignment**
- Assignment is done immediately in a single step: new value is used by subsequent statements
- Execution flow within a procedure is **blocked** until the current assignment is complete
- Used to model **combinational** Logic

Non-Blocking Statements (Out <= In)

- The <= symbol represents a **non-blocking procedural assignment**
- Assignment is done in a **two steps**
 1. The RHS is evaluated immediately
 2. The assignment to LHS is **postponed** until all other evaluations in the current time step are complete
- Used to model sequential logic (like a "clocked assignment operator")

234

Blocking vs Non-Blocking


What is the difference between these two implementations?

notice the posedge keyword

```

module(D,CLK,Q1,Q2);
input wire D,CLK;
output reg Q1,Q2;
always @(posedge CLK)
begin
    Q1 = D;
    Q2 = Q1;
end
endmodule

 module(D,CLK,Q1,Q2);
input D,CLK;
output reg Q1,Q2;
always @(posedge CLK)
begin
    Q1 <= D;
    Q2 <= Q1;
end
endmodule
    
```



235

Verilog Design Guidelines

- Do not mix **blocking** and **non-blocking** statements in the same block or procedure
- Combinational blocks – use blocking statements
- Sequential blocks (registers) – use non-blocking statements
- You will come across a lot of tri-state (Hi-Z) buffer implementations in this and the next module – *it is important to understand this concept, but you will not be implementing tri-state buffers in lab*
- This will be discussed in detail in ECE 337 (ASIC Design)

236

State Machines in Verilog

- To specify a state machine in Verilog, an **always** block triggered on edges of the clock and other asynchronous signals (such as reset) is used.
- The registers are assigned next-state values with non-blocking statements
- The next-state values themselves are evaluated in a separate combinational **always** block or a **dataflow assignment**
- Differences in **macrocell architecture** will determine the complexity of state machine that can be implemented with a given PLD

233

State Machines in Verilog

- A trivial state machine

```

module stateMachine(CLK, RST, state);
input wire CLK, RST;
output reg state;

reg next_state;

always @ (posedge CLK, posedge RST) begin
    if (RST == 1'b1)
        state <= 1'b0;
    else
        state <= next_state;
end

always @ (state) begin
    next_state = ~state;
end
    
```

Variables assigned values in the always block must be **reg** type

If active-high asynchronous reset (RST) is high

A D flip-flop triggered on positive edges of CLK and a reset signal RST

Out of reset, state is assigned the value of next_state at every positive clock edge

next_state logic evaluated in a separate combinational block

234

State Machines in Verilog

- A trivial state machine



```

module stateMachine(CLK, RST, state);
input wire CLK, RST;
output reg state;

reg next_state;


always @ (posedge CLK, posedge RST) begin
    if (RST == 1'b1)
        state <= 1'b0;
    else
        state <= next_state;
end

always @ (state) begin
    next_state = ~state;
end
    
```

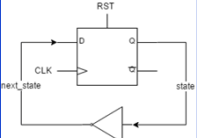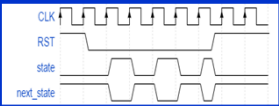RST can go high asynchronous to the CLK and reset logic will force state to 0


235

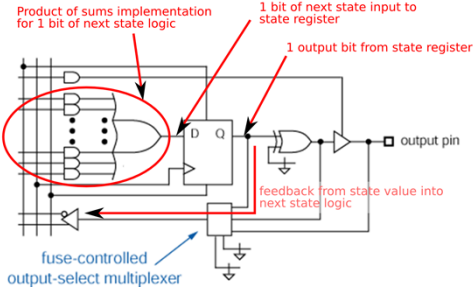

How PLD/CPLD logic blocks are used when implementing a state machine

240

GAL22V10 Output Logic Macrocell ("OLMC")

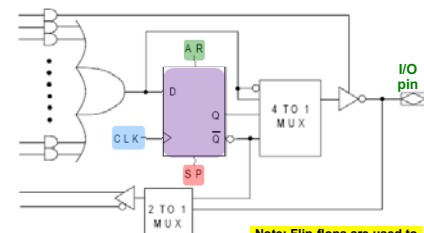


Note: Flip-flops are used to create sequential circuits

All OLMC edge-triggered D flip-flops utilize common clock (CLK), asynchronous reset (AR), and asynchronous preset (SP) signals




241

GAL22V10 Output Logic Macrocell ("OLMC")

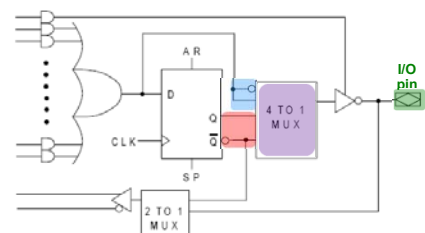

4:1 multiplexer selects (routes) true/complemented combinational or true/complemented registered function to the I/O pin

242

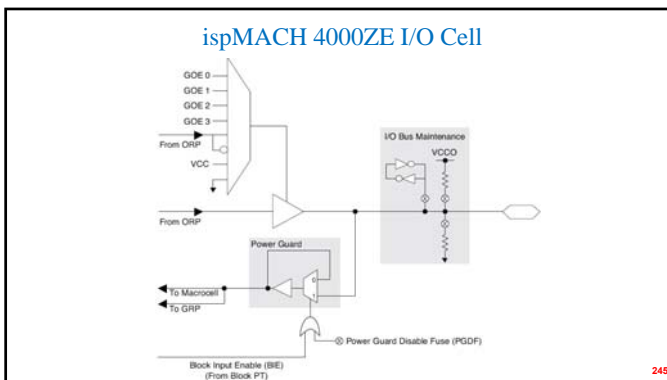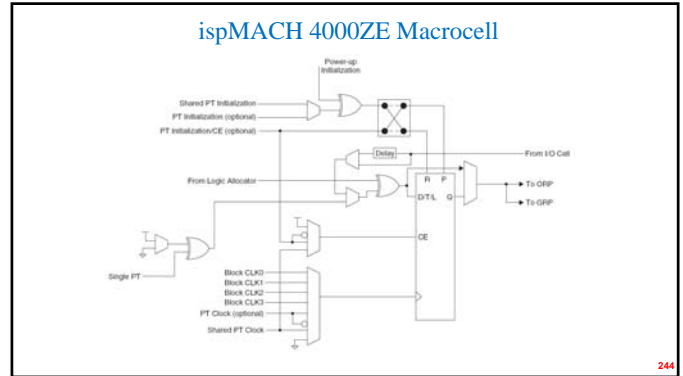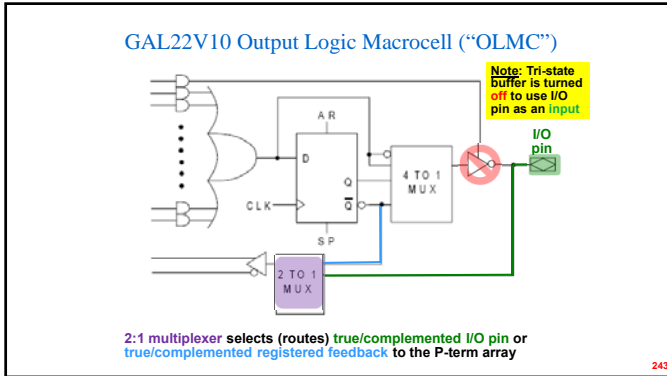

Clocking Considerations

- State machines require a **clocking signal** in order to operate "sequentially"
- There are two basic types of clocking signals that can be used:
 - periodic** ("continuously running"), generated using an **oscillator circuit**
 - event** (non-periodic, single clock edge), generated using a **bounce-free** switch or sensor contact closure
- A **timing diagram** can be used to show the relationship between the clock and various input, output, and internal signals – it can also be used to help answer the key question facing computer system designers: **"How fast can this thing run?"**

246

Periodic Clock Generation Circuits

- Periodic clock signals can be generated using several different types of **oscillator** circuits:
 - based on an R-C time constant (**least accurate**)
 - based on a ceramic resonator
 - based on a quartz crystal (**most accurate**)
- Issues of interest include the following:
 - frequency of operation
 - duty cycle
 - transition time
 - ringing (undershoot / overshoot)
 - stability (long term drift / short term "jitter")
 - driving capability / need for buffers
 - skew (different length paths on PCB)


247

Example - CMOS "Ring" Oscillator

$$f \cong (2C(0.4R_{\text{eq}} + 0.7R_2))^{-1} \text{ where } R_{\text{eq}} = (R_1R_2)/(R_1+R_2)$$

248

Example - Crystal Oscillator Circuit

 

For a 1 MHz oscillator, use R1 = 22 MΩ, R2 = 22 KΩ, C1 = 20 pF, and C2 = 10 pF

249

ispMach 4000ZE Internal Oscillator

```

module OscTest(RST, CLK_out);
input wire RST;
output reg CLK_out;

wire osc_dis, tmr_rst, osc_out, tmr_out;
assign osc_dis = 1'b0;
assign tmr_rst = 1'b0;

defparam I1.TIMER_DIV = "1048576";
OSCCTIMER I1 (.DYNOSCDS(osc_dis), .TIMERRES(tmr_rst), .OSCOUT(osc_out), .TIMEROUT(tmr_out));

always @(posedge tmr_out, posedge RST)
begin
    if (RST == 1'b1) begin
        CLK_out <= 0;
    end
    else begin
        CLK_out <= ~CLK_out;
    end
end
endmodule
    
```

OSCCTIMER is an internal module used for clocking signal generation

1048576 is the constant for internal CLK division, output CLK frequency approx 6 Hz


RST can be connected to a DIP switch on instantiation

Divide internal oscillator frequency by 2: frequency of CLK_out = 6/2 = 3 Hz

250

 Example - Timing Diagram and Specifications

clock frequency ($f = 1/t_{clk}$) duty cycle = $t_{H}/(t_H + t_L)$



255


Event Clock Generation Circuits

- Some applications of sequential circuits require that they be clocked by an **event**
 - sensor firing (open drain transistor changing from high impedance to low impedance)
 - contact closure (pushing a button)
- Problem:** Mechanical switches have contacts that "bounce" (i.e., "make"/"break" multiple times before the contacts "settle")
- Illustration:** Use of a single-pole, single throw (S.P.S.T.) normally-open (N.O.) pushbutton as a clocking signal

256

 Example - S.P.S.T. Pushbutton Used as Clock


S.P.S.T. stands for "single pole, single throw"
 N.O. stands for "normally open"



257

 Example - S.P.S.T. Pushbutton Used as Clock

S.P.S.T. stands for "single pole, single throw"
 N.O. stands for "normally open"



262

Classic Bounce-free Switch Circuit

- Bounce-free switch** implemented using S.P.D.T. ("single pole, double throw") pushbutton with an S' R' latch

Initial/Default State (S-R latch reset)

270

Example – SR Latch in Verilog

```

/* SR latch for use in switch debouncer on small PLD */
module SR_LATCH(RN, SN, Q, QN);
  input wire RN; // active low reset
  input wire SN; // active low set
  output wire Q; // active high output
  output wire QN; // active low output

  assign QN = (~RN | ~Q);
  assign Q = (~SN | ~QN);
endmodule
    
```

WARNING: This method is only intended for use on a small PLD such as a 22v10 device

271

Example – Bounce-Free Switch in Verilog for use on CPLD

```

/* D flip flop used as bounce-free switch in Verilog */
module DFF_BF(CLK, AR, AP, D, BFC);
  input wire CLK; // Clock input for DFF
  input wire AR,AP; // Asynchronous Reset and Preset
  input wire D; // Data input for DFF
  output reg BFC; // Bounce Free Switch output
  always @ (posedge CLK, posedge AR, posedge AP) begin
    if (AR == 1'b1)
      BFC <= 0;
    else if (AP == 1'b1)
      BFC <= 1;
    else
      BFC <= D;
  end
endmodule
    
```

WARNING: This method only works for a CPLD, not a small PLD - for PLD, a gate-level SR latch needs to be implemented

Here, we are using the D flip-flop as an S-R latch by asserting asynchronous reset (AR) and asynchronous preset (AP)

/* For a Bounce-Free Switch, these are the changes in DFF:
 CLK = 0 and D = 0 as we use AR and AP to control the switch
 AR = NC -> AR connected to Normally Closed switch contact
 AP = NO -> AP to Normally Open switch contact
 Below is a sample instance of BFF1
 DFF_BF BFF1 (.CLK(1'b0),.AR(NC),.AP(NO),.D(1'b0),.BFC(out)); */

272

Clicker Quiz

273

Q1. The following passive components can be used as timing reference to generate a periodic clocking signal:


- resistor and capacitor combination
- ceramic resonator
- crystal
- all of the above
- none of the above

274

Q2. The next state equation represented by the following state transition diagram is:

- $X^* = A' \cdot X' + A \cdot X$
- $X^* = A' \cdot X + A \cdot X'$
- $X^* = A + X$
- $X^* = A \cdot X$
- none of the above

275

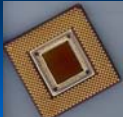

Purdue IM: PACT* Spring 2019 Edition
*Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 3-F

State Machine Design Examples: Sequence Generators

Reading Assignment:

DDPP 4th Ed. pp. 566-576, DDPP 5th Ed. pp. 472-478

Learning Objectives:

- Design a clocked synchronous state machine and verify its operation
- Define minimum risk and minimum cost state machine design strategies, and discuss the tradeoffs between the two approaches
- Compare state assignment strategy and state machine model choice (Mealy vs. Moore) with respect to PLD resources (P-terms and macrocells) required for realization

Outline

- Overview
- Simple character sequence display
- “Dual mode” sequence generator
 - Moore model realizations
 - Mealy model realizations
- Summary

Overview

- A **sequence generator** state machine produces a (periodic) **series of output signal assertions** that constitute a **pre-defined pattern**:
 - vehicle tail lights (e.g., “T-bird”)
 - traffic control signs (e.g., “blinkers” and stoplights)
 - character displays (e.g., “GO BOILERS”)
 - process control sequences (e.g., wash, rinse, dry)
- Either a Mealy or a Moore model can be used as the basis for designing a sequence generator
- Two different design strategies can be employed:
 - **minimum cost** – unused states are assumed to be don’t cares, potentially reducing realization cost while increasing risk of undefined behavior if machine gets into an unknown (unused) state
 - **minimum risk** – unused states are explicitly assigned a next state, eliminating risk of undefined behavior but potentially increasing realization cost

Clicker Quiz

Q1. Designing a state machine based on **minimum risk** means:

- A. there are no hazards in the clocking signal
- B. there are no “don’t cares” in the output equations
- C. there are no “don’t cares” in the next state equations
- D. all of the above
- E. none of the above

Q2. Designing a state machine based on **minimum cost** means:

- A. there can be "don't cares" in the next state equations
- B. there can be "don't cares" in the excitation equations
- C. there can be "don't cares" in the output equations
- D. all of the above
- E. none of the above

282

Q3. If designed for **minimum cost**, the **next state equation for X** is:

- A. $X^* = A' \cdot Y$
- B. $X^* = X + Y$
- C. $X^* = X' \cdot Y + A' \cdot X$
- D. $X^* = A' \cdot Y + X \cdot Y$
- E. none of the above

283

Q4. If designed for **minimum cost**, the **next state equation for Y** is:

- A. $Y^* = A' \cdot Y$
- B. $Y^* = A + Y$
- C. $Y^* = X' \cdot Y + A' \cdot X$
- D. $Y^* = A' \cdot Y + X \cdot Y$
- E. none of the above

284

Example - Character Sequence Display

Design a circuit that produces the character sequence **AbC** or **CbS** on a 7-segment LED

Draw a **Moore** model state transition diagram. Note that there is **one** input (**M**) and **seven** active-low outputs (segments a-g)

285

Example - Character Sequence Display

Design a circuit that produces the character sequence **AbC** or **CbS** on a 7-segment LED

Draw a **Moore** model state transition diagram. Note that there is **one** input (**M**) and **seven** active-low outputs (segments a-g)

Only need 4 states

"A" = 1110111
 "b" = 0011111
 "C" = 1001110
 "S" = 1011011

289

```

/* Character Sequence Display */
module tv_disp(clk, M, Q, nL);
input wire clk;
input wire M; // Mode control
output reg [1:0] Q;
output wire [6:0] nL;

reg [6:0] L; // L[6] = LA, L[5] = LB, .. L[0] = LG
reg [1:0] next_Q; // Active-low outputs on L

assign nL = ~L;

always @ (posedge clk) begin
    Q <= next_Q;
end

always @ (Q, M) begin
    case(Q, M)
        3'b00: next_Q = 2'b01;
        3'b001: next_Q = 2'b10;
        3'b010: next_Q = 2'b11;
        3'b011: next_Q = 2'b11;
        3'b100: next_Q = 2'b00;
        3'b101: next_Q = 2'b01;
        3'b110: next_Q = 2'b00;
        3'b111: next_Q = 2'b10;
    endcase
end

always @ (Q) begin
    case(Q)
        2'b00: L = 7'b1110111; // Character A
        2'b01: L = 7'b0011111; // Character b
        2'b10: L = 7'b1001110; // Character C
        2'b11: L = 7'b1011011; // Character S
    endcase
end
endmodule
    
```

292

Example – Dual Mode Light Sequencer

- Design a clocked synchronous state machine that generates the following “light patterns” (using three LEDs)

Mode 0: “single dot, left-to-right”

Example – Dual Mode Light Sequencer

- Design a clocked synchronous state machine that generates the following “light patterns” (using three LEDs)

Mode 1: “single dot, right-to-left”

Example – Dual Mode Light Sequencer

- Design a clocked synchronous state machine that generates the following “light patterns” (using three LEDs)

Mode 2: “building dots, left-to-right”


Example – Dual Mode Light Sequencer



- Design a clocked synchronous state machine that generates the following “light patterns” (using three LEDs)

Mode 3: “building dots, right-to-left”

Moore Model Realizations

- To specify in which of the 4 modes we want the circuit to operate, we will need 2 “mode control” inputs, **M1** and **M0**, where:
 - 0 0 → single dot, left-to-right
 - 0 1 → single dot, right-to-left
 - 1 0 → building dots, left-to-right
 - 1 1 → building dots, right-to-left
- A separate output function needs to be determined for each of the 3 LED outputs: **G**, **Y**, and **R** (from left-to-right)
- A state will be needed corresponding to the “all LEDs off” condition

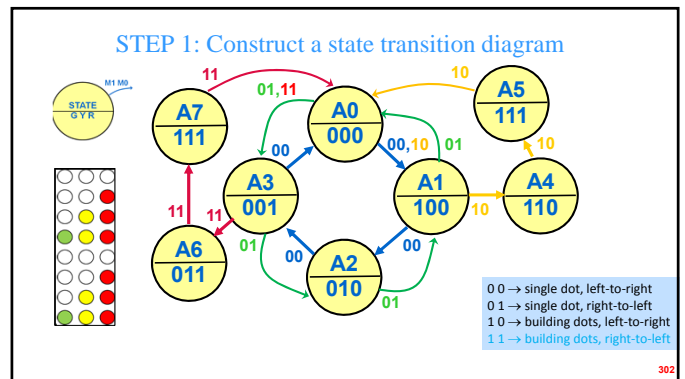

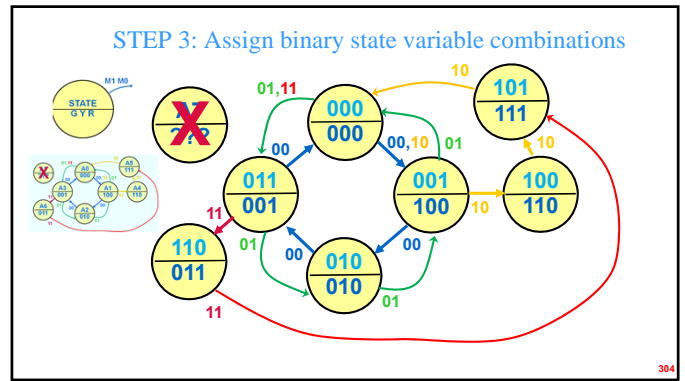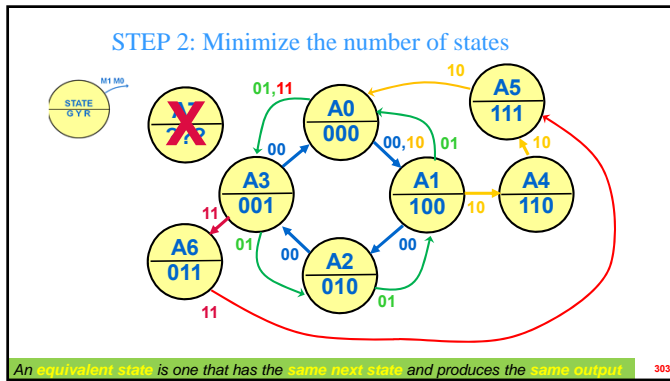

STEP 4: Construct a PS-NS/PO Table

PS			PI		NS			PO		
Q2	Q1	Q0	M1	M0	Q2*	Q1*	Q0*	G	Y	R
0	0	0	0	0	0	0	1	0	0	0
			0	1	0	1	1			
			1	0	0	0	1			
			1	1	0	1	1			
0	0	1	0	0	0	1	0	1	0	0
			0	1	0	0	0			
			1	0	1	0	0			
			1	1	0	0	0			
0	1	0	0	0	0	1	1	0	1	0
			0	1	0	0	1			
			1	0	0	0	0			
			1	1	0	0	0			
0	1	1	0	0	0	0	0	0	0	1
			0	1	0	1	0			
			1	0	0	0	0			
			1	1	1	1	0			

STEP 4: Construct a PS-NS/PO Table...

PS			PI		NS			PO		
Q2	Q1	Q0	M1	M0	Q2*	Q1*	Q0*	G	Y	R
1	0	0	0	0	0	0	0	1	1	0
			0	1	0	0	0			
			1	0	1	0	1			
			1	1	0	0	0			
1	0	1	0	0	0	0	0	1	1	1
			0	1	0	0	0			
			1	0	0	0	0			
			1	1	0	0	0			
1	1	0	0	0	0	0	0	0	1	1
			0	1	0	0	0			
			1	0	0	0	0			
			1	1	1	1	0	1		
1	1	1	0	0	0	0	0	0	0	0
			0	1	0	0	0			
			1	0	0	0	0			
			1	1	0	0	0			

```

// Light Sequencer - Moore Model A v1
module moore1a(CLK, M, Q, L);
    input wire CLK; // Input clock
    input wire [2:0] M; // Mode select
    output reg [2:0] L;
    output reg [2:0] Q;

    reg [2:0] next_Q;
    always @(posedge CLK) begin
        Q <= next_Q;
    end

    always @(Q, M) begin
        case ({Q,M})
            0'b000: next_Q = 3'b001;
            0'b0001: next_Q = 3'b011;
            0'b0010: next_Q = 3'b001;
            0'b0011: next_Q = 3'b011;


            0'b0100: next_Q = 3'b010;
            0'b0101: next_Q = 3'b000;
            0'b0110: next_Q = 3'b100;
            0'b0111: next_Q = 3'b000;


            0'b1000: next_Q = 3'b011;
            0'b1001: next_Q = 3'b001;
            0'b1010: next_Q = 3'b000;
            0'b1011: next_Q = 3'b000;

            0'b1100: next_Q = 3'b000;
            0'b1101: next_Q = 3'b000;
            0'b1110: next_Q = 3'b010;
            0'b1111: next_Q = 3'b110;
        endcase
    end
endmodule
    
```

Note: G=L[2], Y=L[1], R=L[0]

This realization uses 6 macrocells

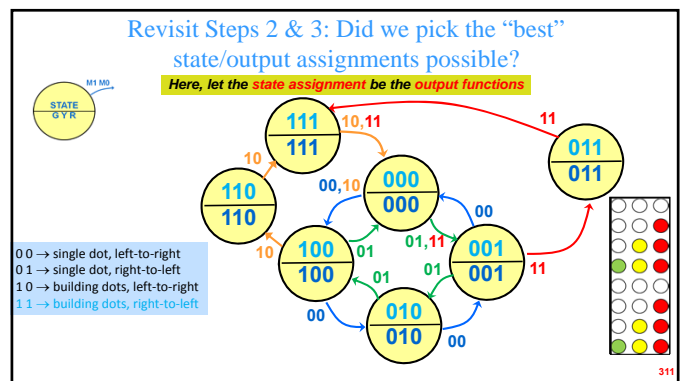

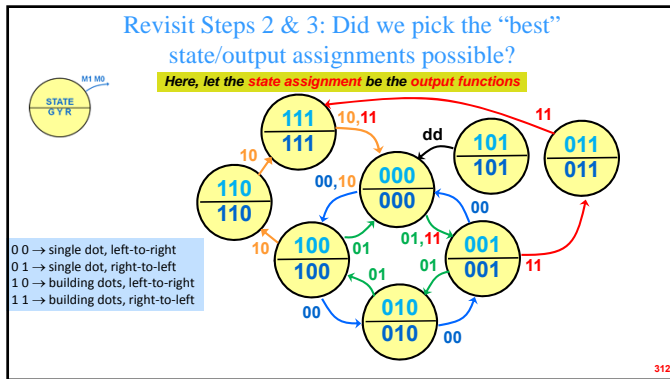

```

/* Light Sequencer - Moore Model B */
module moore1B(CLK, M, Q);
input wire CLK; // Input clock
input wire [1:0] M; // Mode select
output reg [2:0] Q; // serve as L2 L1 L0
reg [2:0] next_Q;


always @(posedge CLK) begin
    Q <- next_Q;
end

always @(Q, M) begin
    case({Q,M})
        S'h0000: next_Q = 3'b000;
        S'h0001: next_Q = 3'b001;
        S'h0010: next_Q = 3'b000;
        S'h0011: next_Q = 3'b001;
        S'h0100: next_Q = 3'b000;
        S'h0101: next_Q = 3'b000;
        S'h0110: next_Q = 3'b000;
        S'h0111: next_Q = 3'b001;
        S'h1000: next_Q = 3'b001;
        S'h1001: next_Q = 3'b000;
        S'h1010: next_Q = 3'b000;
        S'h1011: next_Q = 3'b001;
        S'h1100: next_Q = 3'b000;
        S'h1101: next_Q = 3'b000;
        S'h1110: next_Q = 3'b000;
        S'h1111: next_Q = 3'b000;
    endcase
end
endmodule
    
```

Note: Here the output functions are merely the state variables - $G=Q[2]$, $Y=Q[1]$, $R=Q[0]$

This realization uses 3 macrocells

313

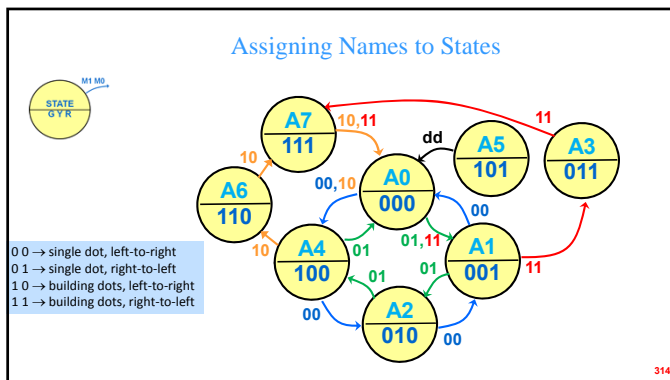

```

/* Light Sequencer Using State Diagram */
module moore1B_ad(CLK, M, Q);
input wire CLK; // Input clock
input wire [1:0] M; // Mode select
output reg [2:0] Q;

reg [2:0] next_Q;

// State declarations
localparam A0 = 3'b000;
localparam A1 = 3'b001;
localparam A2 = 3'b010;
localparam A3 = 3'b011;
localparam A4 = 3'b100;
localparam A5 = 3'b101;
localparam A6 = 3'b110;
localparam A7 = 3'b111;


always @(posedge CLK) begin
    Q <- next_Q;
end

always @(Q) begin
    case(Q)
        A0: begin
            if (M == 2'b00) next_Q = A0;
            else if (M == 2'b01) next_Q = A1;
            else if (M == 2'b10) next_Q = A4;
            else if (M == 2'b11) next_Q = A1;
        end
        A1: begin
            if (M == 2'b00) next_Q = A0;
            else if (M == 2'b01) next_Q = A2;
            else if (M == 2'b10) next_Q = A0;
            else if (M == 2'b11) next_Q = A0;
        end
        A2: begin
            if (M == 2'b00) next_Q = A0;
            else if (M == 2'b01) next_Q = A2;
            else if (M == 2'b10) next_Q = A0;
            else if (M == 2'b11) next_Q = A1;
        end
        A3: begin
            if (M == 2'b00) next_Q = A0;
            else if (M == 2'b01) next_Q = A0;
            else if (M == 2'b10) next_Q = A0;
            else if (M == 2'b11) next_Q = A7;
        end
        A4: begin
            if (M == 2'b00) next_Q = A0;
            else if (M == 2'b01) next_Q = A0;
            else if (M == 2'b10) next_Q = A0;
            else if (M == 2'b11) next_Q = A0;
        end
        A5: next_Q = A0;
        A6: begin
            if (M == 2'b00) next_Q = A0;
            else if (M == 2'b01) next_Q = A0;
            else if (M == 2'b10) next_Q = A0;
            else if (M == 2'b11) next_Q = A0;
        end
        A7: next_Q = A0;
    endcase
end
endmodule
    
```

Same design realized using STATE constants

This realization also uses 3 macrocells

315

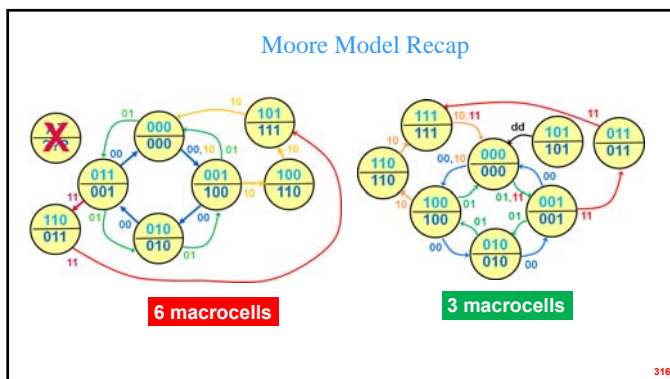

- ### Mealy Model Realizations
- Now try MEALY model implementation, and compare with MOORE model done previously
 - (Review) To specify in which of the 4 modes we want the circuit to operate, we will need 2 "mode control" inputs, M1 and M0, where:
 - 0 0 → single dot, left-to-right
 - 0 1 → single dot, right-to-left
 - 1 0 → building dots, left-to-right
 - 1 1 → building dots, right-to-left
 - A separate output function needs to be determined for each of the 3 LED outputs: G, Y, and R (from left-to-right)
 - A state will be needed corresponding to the "all LEDs off" condition
- 317

STEP 1: Construct a state transition diagram

Mealy Model:

318

STEP 1: Construct a state transition diagram

00 → single dot, left-to-right
 01 → single dot, right-to-left
 10 → building dots, left-to-right
 11 → building dots, right-to-left

323

STEP 2: Minimize the number of states ✓
 STEP 3: Assign state variable combinations

00 → single dot, left-to-right
 01 → single dot, right-to-left
 10 → building dots, left-to-right
 11 → building dots, right-to-left

324

STEP 4: Construct a PS-NS/PO Table

PS	Q1	Q0	PI	M1	M0	NS	Q1*	Q0*	PO	L2	L1	L0
0	0	0	0	0	0	0	0	1	0	0	0	0
			0	1	0	1	1	1	0	0	0	0
			1	0	0	0	1	0	1	0	0	0
			1	1	0	1	1	1	0	0	0	0
0	1		0	0	1	0	0	0	1	0	0	0
			0	1	0	0	0	0	1	0	0	0
			1	0	0	1	1	1	1	0	0	0
			1	1	0	0	0	0	1	1	1	1
1	0		0	0	1	1	0	1	0	1	0	0
			0	1	0	0	1	0	0	1	0	0
			1	0	0	1	1	1	1	1	0	0
			1	1	0	1	0	0	0	0	0	1

```

/* Light Sequencer - Mealy Model A */
module mealy1a(CLK, M, Q, L);
    input wire CLK; // Clock input
    input wire [1:0] M; // Mode select
    output wire [2:0] L;
    output reg [1:0] Q;

    wire [1:0] next_Q;
    reg [4:0] mQ; // vector of {next_Q,i}

    always @(posedge CLK) begin
        Q <= next_Q;
    end

    assign next_Q = mQ[4:3];
    assign L = mQ[2:0];

    always @ (Q, M) begin
        case ({Q,M})
            4'b0000: mQ = {2'b01,3'b000};
            4'b0001: mQ = {2'b11,3'b000};
            4'b0010: mQ = {2'b01,3'b000};
            4'b0011: mQ = {2'b11,3'b000};
            4'b0100: mQ = {2'b11,3'b010};
            4'b0101: mQ = {2'b01,3'b010};
            4'b0110: mQ = {2'b11,3'b110};
            4'b0111: mQ = {2'b01,3'b001};
            4'b1000: mQ = {2'b11,3'b010};
            4'b1001: mQ = {2'b01,3'b001};
            4'b1010: mQ = {2'b10,3'b001};
            4'b1011: mQ = {2'b00,3'b111};
            4'b1100: mQ = {2'b00,3'b001};
            4'b1101: mQ = {2'b10,3'b001};
            4'b1110: mQ = {2'b00,3'b111};
            4'b1111: mQ = {2'b10,3'b001};
        endcase
    end
endmodule

This realization uses 5 macrocells
    
```

325

Revisit Steps 2 & 3: Did we pick the "best" state/output assignments possible?

00 → single dot, left-to-right
 01 → single dot, right-to-left
 10 → building dots, left-to-right
 11 → building dots, right-to-left

327

STEP 4: Construct a PS-NS/PO Table

PS		PI		NS		PO		
Q1	Q0	M1	M0	Q1*	Q0*	L2	L1	L0
0	0	0	0	0	1	0	0	0
		0	1	0	1	0	0	0
		1	0	0	1	0	0	0
		1	1	0	1	0	0	0
0	1	0	0	1	0	1	0	0
		0	1	1	0	0	0	1
		1	0	1	0	1	0	0
		1	1	1	0	0	0	1
1	0	0	0	1	1	0	1	0
		0	1	1	1	0	1	0
		1	0	1	1	1	1	0
		1	1	1	1	0	1	1
1	1	0	0	0	0	0	0	1
		0	1	0	0	1	0	0
		1	0	0	0	1	1	1
		1	1	0	0	1	1	1

```

/* Light Sequencer - Mealy Model B */
module mealylsb(CLK, M, L);
input wire CLK; // Clock input
input wire [1:0] M; // Mode select
output wire [2:0] L;

reg [1:0] Q;
wire [1:0] next_Q;
reg [4:0] nQL; // vector of {next_Q,L}


always @ (posedge CLK) begin
    Q <= next_Q;
end

assign next_Q = nQL[4:3];
assign L = nQL[2:0];

always @ (Q, M) begin
    case ({Q,M})
        4'b000: nQL = {2'b01,3'b000};
        4'b001: nQL = {2'b01,3'b000};
        4'b010: nQL = {2'b01,3'b000};
        4'b011: nQL = {2'b01,3'b000};
        4'b100: nQL = {2'b10,3'b010};
        4'b101: nQL = {2'b11,3'b010};
        4'b110: nQL = {2'b11,3'b010};
        4'b111: nQL = {2'b11,3'b011};
    endcase
end
endmodule
    
```

This realization uses 5 macros

Assigning Names to States

 

```

/* Mealy Model Implemented with State Diagram */
module mealylsb_sd(CLK, M, L, Q);
input wire CLK; // Clock input
input wire [1:0] M; // Mode select
output reg [2:0] L;
output reg [1:0] Q;

reg [1:0] next_Q;

// State declarations
localparam A0 = 2'b00;
localparam A1 = 2'b01;
localparam A2 = 2'b10;
localparam A3 = 2'b11;

always @ (posedge CLK) begin
    Q <= next_Q;
end

always @ (Q) begin
    case (Q)
        A0: next_Q = A1;
        A1: next_Q = A2;
        A2: next_Q = A3;
        A3: next_Q = A0;
    endcase
end
endmodule
    
```

Same design realized using STATE constants

```

always @ (Q, M) begin
    case ({Q,M})
        4'b000: L = 3'b000;
        4'b001: L = 3'b000;
        4'b010: L = 3'b000;
        4'b011: L = 3'b000;
        4'b100: L = 3'b100;
        4'b101: L = 3'b001;
        4'b110: L = 3'b100;
        4'b111: L = 3'b001;
    endcase
end
    
```

This realization uses 5 macros

Clicker Quiz

```

/* Multi-Color LED Light Machine */
module mcleds(CLK, M, R, G, Y, B);
input wire CLK;
input wire M; // Mode control input
output wire R, G, B, Y; // Red/Green/Blue/Yellow

reg [1:0] Q; // State variables
wire [1:0] next_Q;
reg [5:0] nRGYB; // vector for next_Q and R/G/Y/B values

always @ (posedge CLK) begin
    Q <= next_Q;
end

assign next_Q = nRGYB[5:4];
assign {R,G,Y,B} = nRGYB[3:0];

always @ (Q, M) begin
    case ({Q,M})
        3'b000: nRGYB = {2'b10,4'b1000};
        3'b001: nRGYB = {2'b11,4'b1000};
        3'b010: nRGYB = {2'b11,4'b0010};
        3'b011: nRGYB = {2'b00,4'b1111};
        3'b100: nRGYB = {2'b01,4'b0100};
        3'b101: nRGYB = {2'b01,4'b1110};
        3'b110: nRGYB = {2'b00,4'b0001};
        3'b111: nRGYB = {2'b10,4'b1100};
    endcase
end
endmodule
    
```

Q1. When $M=0$, the (repeating) colored LED sequence produced will be:

A. $R \rightarrow G \rightarrow Y \rightarrow B \rightarrow \dots$
 B. $R \rightarrow Y \rightarrow G \rightarrow B \rightarrow \dots$
 C. $B \rightarrow Y \rightarrow G \rightarrow R \rightarrow \dots$
 D. $B \rightarrow G \rightarrow Y \rightarrow R \rightarrow \dots$
 E. none of the above

```

/* Multi-Color LED Light Machine */
module mcleds(CLK, M, R, G, Y, B);
    input wire CLK;
    input wire M;
    output wire R, G, B, Y;
    reg [1:0] Q, next_Q;
    reg [5:0] nQRGYB;
    always @ (posedge CLK) begin
        Q <= next_Q;
    end
    assign next_Q = nQRGYB[5:4];
    assign {R,G,Y,B} = nQRGYB[3:0];
    always @ (Q, M) begin
        case ({Q,M})
            3'b000: nQRGYB = {2'b10,4'b1000};
            3'b001: nQRGYB = {2'b11,4'b1000};
            3'b010: nQRGYB = {2'b11,4'b0010};
            3'b011: nQRGYB = {2'b00,4'b1111};
            3'b100: nQRGYB = {2'b01,4'b0100};
            3'b101: nQRGYB = {2'b01,4'b1110};
            3'b110: nQRGYB = {2'b00,4'b0001};
            3'b111: nQRGYB = {2'b10,4'b1100};
        endcase
    end
endmodule
    
```

334

Q2. When $M=1$, the (repeating) colored LED sequence produced will be:

A. $R \rightarrow RGYB \rightarrow RGY \rightarrow RG \rightarrow \dots$
 B. $R \rightarrow RG \rightarrow RGY \rightarrow RGYB \rightarrow \dots$
 C. $RGYB \rightarrow RGY \rightarrow RG \rightarrow R \rightarrow \dots$
 D. $R \rightarrow RGY \rightarrow RG \rightarrow RGYB \rightarrow \dots$
 E. none of the above

```

/* Multi-Color LED Light Machine */
module mcleds(CLK, M, R, G, Y, B);
    input wire CLK;
    input wire M;
    output wire R, G, B, Y;
    reg [1:0] Q, next_Q;
    reg [5:0] nQRGYB;
    always @ (posedge CLK) begin
        Q <= next_Q;
    end
    assign next_Q = nQRGYB[5:4];
    assign {R,G,Y,B} = nQRGYB[3:0];
    always @ (Q, M) begin
        case ({Q,M})
            3'b00: nQRGYB = {2'b10,4'b1000};
            3'b001: nQRGYB = {2'b11,4'b1000};
            3'b010: nQRGYB = {2'b11,4'b0010};
            3'b011: nQRGYB = {2'b00,4'b1111};
            3'b100: nQRGYB = {2'b01,4'b0100};
            3'b101: nQRGYB = {2'b01,4'b1110};
            3'b110: nQRGYB = {2'b00,4'b0001};
            3'b111: nQRGYB = {2'b10,4'b1100};
        endcase
    end
endmodule
    
```


335

Summary

- The choice of model (Mealy vs. Moore) can have a **significant impact** on the **complexity** of the realization and PLD resources (macrocells) consumed
- The state assignment **strategy** employed can make a **significant difference** in the **amount of work required**
- “Obvious” state minimization can also sometimes be useful (formal state-minimization procedures are seldom used by most digital designers, however)
- The only formal way to find the **best** state assignment is to try **all** the assignments – that’s too much work (even for **students**)–
- To do this well, we need **experience** as well as have knowledge of some practical guidelines (see text)
- There is no substitute for **practice** in designing state machines – much of engineering is **applied intuition**, and this is a good example of it–

336

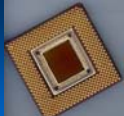Purdue IM:PACT* Spring 2019 Edition
 *Instruction Matters: Purdue Academic Course Transformation



Introduction to Digital System Design

Module 3-G

State Machine Design Examples: Counters and Shift Registers

Reading Assignment:

DDPP 4th Ed. pp. 710-718, 725-736; DDPP 5th Ed. pp. 554-561, 561-574

Learning Objectives:

- Compare and contrast the operation of binary and shift register counters
- Derive the next state equations for binary “up” and “down” counters
- Describe the feedback necessary to make ring and Johnson counters self-correcting
- Compare and contrast state decoding for binary and shift register counters
- Describe why “glitches” occur in some state decoding strategies and discuss how to eliminate them

337


Outline

- Overview
- Binary counter registers
- UP and DOWN counter derivations
- Basic binary counter extensions
 - ENABLE input
 - ASYNCHRONOUS RESET
 - UP and DOWN count modes
- Synchronously resettable counters
 - SYNCHRONOUS RESET
 - MODULUS control
- Shift register counters
- State decoding
- Summary

338

Overview

 - Definition: The name **counter** is used for any clocked sequential circuit whose state diagram contains a **single cycle**



- Definition: A **register** is a collection of two or more flip-flops with a common clock and, generally, a common purpose

Binary Counter Registers

- Definition: The **modulus** of a counter is the number of states in the cycle – a counter with M states is called a **modulo-M counter** (or sometimes a **divide-by-M counter**)
- Definition: A **synchronous counter** connects all of its flip-flop clock inputs to the same common CLOCK signal, so that all the flip-flop outputs change state **simultaneously**
- The most commonly used counter type is an **n-bit binary counter**, with n flip-flops and 2^n states, visited in the sequence 0, 1, 2, ..., 2^n-1 , 0, 1, 2, ...

Binary UP Counter Derivation

- The design of a basic binary UP counter is derived as follows:

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

When does Q0 change state?
 Every clock cycle
 What is the equation for Q0*?
 $Q0^* = Q0'$

Binary UP Counter Derivation

- The design of a basic binary UP counter is derived as follows:

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

When does Q1 change state?
 When Q0 = 1
 What is the equation for Q1*?
 $Q1^* = Q1 \oplus Q0$

Binary UP Counter Derivation

- The design of a basic binary UP counter is derived as follows:

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

When does Q2 change state?
 When Q0 = 1 AND Q1 = 1
 What is the equation for Q2*?
 $Q2^* = Q2 \oplus (Q1 \cdot Q0)$

Binary UP Counter Derivation

- The design of a basic binary UP counter is derived as follows:

What is the next state equation for an arbitrary stage "K" (Q_K^*) of a binary UP counter?
 $Q_K^* = Q_K \oplus (Q_{K-1} \cdot Q_{K-2} \cdot \dots \cdot Q_1 \cdot Q_0)$

```

/* Basic 8-bit binary UP Counter */
module count8u(CLK, Q);
    input wire CLK;
    output reg [7:0] Q;
    reg [7:0] next_Q;

    always @ (posedge CLK) begin
        Q <= next_Q;
    end

    always @ (Q) begin
        next_Q[0] = ~Q[0];
        next_Q[1] = Q[1] ^ Q[0];
        next_Q[2] = Q[2] ^ (Q[1] & Q[0]);
        next_Q[3] = Q[3] ^ (Q[2] & Q[1] & Q[0]);
        next_Q[4] = Q[4] ^ (Q[3] & Q[2] & Q[1] & Q[0]);
        next_Q[5] = Q[5] ^ (Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
        next_Q[6] = Q[6] ^ (Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
        next_Q[7] = Q[7] ^ (Q[6] & Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
    end
endmodule
    
```

Binary DOWN Counter Derivation

- The design of a basic binary DOWN counter is derived as follows:

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

When does Q0 change state?
 Every clock cycle

What is the equation for Q0*?
 $Q0^* = Q0'$

Binary DOWN Counter Derivation

- The design of a basic binary DOWN counter is derived as follows:

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

When does Q1 change state?
 When Q0 = 0

What is the equation for Q1*?
 $Q1^* = Q1 \oplus Q0'$

Binary DOWN Counter Derivation

- The design of a basic binary DOWN counter is derived as follows:

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

When does Q2 change state?
 When Q0 = 0 AND Q1 = 0

What is the equation for Q2*?
 $Q2^* = Q2 \oplus (Q1' \cdot Q0')$

Binary DOWN Counter Derivation

- The design of a basic binary DOWN counter is derived as follows:

What is the next state equation for an arbitrary stage "K" (Q_K^*) of a binary DOWN counter?

$$Q_K^* = Q_K \oplus (Q'_{K-1} \cdot Q'_{K-2} \cdot \dots \cdot Q'_1 \cdot Q'_0)$$

```

/* Basic 8-bit binary DOWN Counter */
module count8d(CLK, Q);
    input wire CLK;
    output reg [7:0] Q;
    reg [7:0] next_Q;

    always @ (posedge CLK) begin
        Q <= next_Q;
    end

    always @ (Q) begin
        next_Q[0] = ~Q[0];
        next_Q[1] = Q[1] ^ ~Q[0];
        next_Q[2] = Q[2] ^ (~Q[1] & ~Q[0]);
        next_Q[3] = Q[3] ^ (~Q[2] & ~Q[1] & ~Q[0]);
        next_Q[4] = Q[4] ^ (~Q[3] & ~Q[2] & ~Q[1] & ~Q[0]);
        next_Q[5] = Q[5] ^ (~Q[4] & ~Q[3] & ~Q[2] & ~Q[1] & ~Q[0]);
        next_Q[6] = Q[6] ^ (~Q[5] & ~Q[4] & ~Q[3] & ~Q[2] & ~Q[1] & ~Q[0]);
        next_Q[7] = Q[7] ^ (~Q[6] & ~Q[5] & ~Q[4] & ~Q[3] & ~Q[2] & ~Q[1] & ~Q[0]);
    end
endmodule
    
```

Basic Binary Counter Extensions

- Extensions to the basic binary counter commonly of interest include:
 - providing both UP and DOWN COUNT modes
 - providing an ENABLE input
 - providing an ASYNCHRONOUS RESET

333

```

/* Basic 8-bit binary UP/DOWN Counter */
module count8d(CLK, M, Q);
input wire CLK, M; // M=0 count down, M=1 count up
output reg [7:0] Q;

reg [7:0] next_Q;

always @(posedge CLK) begin
    Q <= next_Q;
end

always @(Q, M) begin
    if (M == '1'b0) begin
        next_Q[0] = ~Q[0];
        next_Q[1] = Q[1] ^ ~Q[0];
        next_Q[2] = Q[2] ^ (Q[1] & ~Q[0]);
        next_Q[3] = Q[3] ^ (Q[2] & Q[1] & ~Q[0]);
        next_Q[4] = Q[4] ^ (Q[3] & Q[2] & Q[1] & ~Q[0]);
        next_Q[5] = Q[5] ^ (Q[4] & Q[3] & Q[2] & Q[1] & ~Q[0]);
        next_Q[6] = Q[6] ^ (Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & ~Q[0]);
        next_Q[7] = Q[7] ^ (Q[6] & Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & ~Q[0]);
    end
    else begin
        next_Q[0] = Q[0];
        next_Q[1] = Q[1] ^ Q[0];
        next_Q[2] = Q[2] ^ (Q[1] & Q[0]);
        next_Q[3] = Q[3] ^ (Q[2] & Q[1] & Q[0]);
        next_Q[4] = Q[4] ^ (Q[3] & Q[2] & Q[1] & Q[0]);
        next_Q[5] = Q[5] ^ (Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
        next_Q[6] = Q[6] ^ (Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
        next_Q[7] = Q[7] ^ (Q[6] & Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
    end
end
endmodule
    
```

333

```

/* Basic 8-bit binary counter with enable */
module count8d(CLK, AR, EN, Q);
input wire CLK;
input wire AR; // Asynchronous Reset
input wire EN; // Counts up only if EN=1
output reg [7:0] Q;

reg [7:0] next_Q;


// If AR asserted, resets to 00...0 (regardless of whether or not enabled)
always @(posedge CLK, posedge AR) begin
    if (AR == '1'b1)
        Q <= 8'b00000000;
    else if (EN == '1'b1)
        Q <= next_Q;
end

always @(Q) begin
    next_Q[0] = ~Q[0];
    next_Q[1] = Q[1] ^ Q[0];
    next_Q[2] = Q[2] ^ (Q[1] & Q[0]);
    next_Q[3] = Q[3] ^ (Q[2] & Q[1] & Q[0]);
    next_Q[4] = Q[4] ^ (Q[3] & Q[2] & Q[1] & Q[0]);
    next_Q[5] = Q[5] ^ (Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
    next_Q[6] = Q[6] ^ (Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
    next_Q[7] = Q[7] ^ (Q[6] & Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
end
endmodule
    
```

354


Clicker Quiz

355

 

356

 Which Verilog program realizes this state machine?



```

/* Program (A) */
module CQ(CLK, M, Q);
input wire CLK, M;
output reg [2:0] Q;
reg [2:0] next_Q;

always @(posedge CLK) begin
    Q <= next_Q;
end

always @(Q, M) begin
    next_Q[0] = ~Q[0];
    next_Q[1] = ~Q[1] ^ (~M & Q[0] | M & Q[0]);
    next_Q[2] = ~Q[2] ^ (~M & Q[1] & Q[0] | M & Q[1] & Q[0]);
end
endmodule

/* Program (B) */
module CQ(CLK, M, Q);
input wire CLK, M;
output reg [2:0] Q;
reg [2:0] next_Q;

always @(posedge CLK) begin
    Q <= next_Q;
end

always @(Q, M) begin
    next_Q[0] = ~Q[0];
    next_Q[1] = Q[1] ^ (~M & Q[0] | M & Q[0]);
    next_Q[2] = Q[2] ^ (~M & Q[1] & Q[0] | M & Q[1] & Q[0]);
end
endmodule

/* Program (C) */
module CQ(CLK, M, Q);
input wire CLK, M;
output reg [2:0] Q;
reg [2:0] next_Q;

always @(posedge CLK) begin
    Q <= next_Q;
end

always @(Q, M) begin
    next_Q[0] = ~Q[0];
    next_Q[1] = Q[1] ^ (~M & Q[0] | M & Q[0]);
    next_Q[2] = Q[2] ^ (M & Q[1] & Q[0] | ~M & Q[1] & Q[0]);
end
endmodule

/* Program (D) */
module CQ(CLK, M, Q);
input wire CLK, M;
output reg [2:0] Q;
reg [2:0] next_Q;

always @(posedge CLK) begin
    Q <= Q + 1;
end
endmodule
    
```

(E) none of the above

357

Resettable Counters

- In addition to an **asynchronous reset** (which allows to the counter to be placed in a known initial state), it is sometimes useful to provide a **synchronous reset** capability
- Such a counter is useful in applications where the number of states in the counting sequence is determined **dynamically**
- Example:** State counter in a computer's execute unit, where the number of cycles necessary to complete an instruction varies
- Another variation:** Counter with a "programmable" final state (modulo M)

384

```

/* Resettable 8-bit binary UP Counter */
module ront8u(CLK, R, Q);
    input wire CLK;
    input wire R; // Synchronous Reset
    output reg [7:0] Q;
    reg [7:0] next_Q;

    always @ (posedge CLK) begin
        Q <= next_Q;
    end

    // If R = 1, counter resets to 0 on the next clock edge
    always @ (Q) begin
        if (R == 1'b1) begin
            next_Q = 8'b00000000;
        end
    end

    // Counter logic
    always @ (Q) begin
        next_Q[0] = ~Q[0];
        next_Q[1] = Q[1] ^ Q[0];
        next_Q[2] = Q[2] ^ (Q[1] & Q[0]);
        next_Q[3] = Q[3] ^ (Q[2] & Q[1] & Q[0]);
        next_Q[4] = Q[4] ^ (Q[3] & Q[2] & Q[1] & Q[0]);
        next_Q[5] = Q[5] ^ (Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
        next_Q[6] = Q[6] ^ (Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
        next_Q[7] = Q[7] ^ (Q[6] & Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
    end
endmodule
    
```

389

```

/* Modulo Resettable 8-bit Binary UP Counter */
module mront8u(CLK, MOD, Q);
    input wire CLK;
    input wire [7:0] MOD; // MOD value
    output reg [7:0] Q;
    reg [7:0] next_Q;
    wire R;

    always @ (posedge CLK) begin
        Q <= next_Q;
    end

    // Count up to value on MOD -> 00..00 -> value up to MOD
    assign R = (Q == MOD);

    always @ (Q) begin
        if (R == 1'b1) begin
            next_Q = 8'b00000000; // When Q reaches MOD, reset to 0
        end
        else begin
            next_Q[0] = ~Q[0];
            next_Q[1] = Q[1] ^ Q[0];
            next_Q[2] = Q[2] ^ (Q[1] & Q[0]);
            next_Q[3] = Q[3] ^ (Q[2] & Q[1] & Q[0]);
            next_Q[4] = Q[4] ^ (Q[3] & Q[2] & Q[1] & Q[0]);
            next_Q[5] = Q[5] ^ (Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
            next_Q[6] = Q[6] ^ (Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
            next_Q[7] = Q[7] ^ (Q[6] & Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & Q[0]);
        end
    end
endmodule
    
```

381

Shift-Register Counters

- Definition:** A shift register whose state diagram is **cyclic** is called a **shift-register counter**
- Unlike a binary counter, a shift-register counter does not count in an "up" or "down" binary sequence, but is useful in many "control" applications nonetheless
- The simplest shift-register counter uses an n-bit shift register to obtain a counter with n states, and is called a **ring counter**
- A ring counter sequence is sometimes referred to as "**one hot**"

382

```

/* Simple 4-bit Ring Counter */
module ring4(CLK, R, Q);
    input wire CLK, R;
    output reg [3:0] Q;
    reg [3:0] next_Q;

    // Assertion of R causes next state of counter to be 0001
    always @ (posedge CLK) begin
        Q <= next_Q;
    end

    always @ (Q) begin
        next_Q[3] = ~R & Q[2];
        next_Q[2] = ~R & Q[1];
        next_Q[1] = ~R & Q[0];
        next_Q[0] = ~R & Q[3] | R;
    end
endmodule
                
```

Example – Simple 4-bit Ring Counter

363

```

/* Simple 4-bit Ring Counter */
module ring4(CLK, R, Q);
    input wire CLK, R;
    output reg [3:0] Q;
    reg [3:0] next_Q;

    // Assertion of R causes next state of counter to be 0001
    always @ (posedge CLK) begin
        Q <= next_Q;
    end

    always @ (Q) begin
        next_Q[3] = ~R & Q[2];
        next_Q[2] = ~R & Q[1];
        next_Q[1] = ~R & Q[0];
        next_Q[0] = (~R & Q[3]) | R;
    end
endmodule
                
```


Example – Simple 4-bit Ring Counter

364

Self-Correcting Ring Counters

 - Problem:** The simple ring counter is *not robust* – if it somehow gets off the normal 4-state cycle (e.g., due to noise), it *stays off*
- Solution:** A *self-correcting* counter is designed so that all “abnormal” states have transitions leading to “normal” states
 - uses an *n-1* input *NOR function* to shift in a “1” only when the *n-1* least significant bits of an *n-bit* ring counter are “0” (i.e., shifts in a “0” until the counter reaches state **d000**)
 - all “*abnormal*” states lead back into the normal *n-state* ring cycle

State Transition Diagrams for Simple 4-bit Ring Counter



Example – Self-Correcting 4-bit Ring Counter


```

/* Self-Correcting 4-bit Ring Counter */
module ring4sc(CLK, Q);
    input wire CLK;
    output reg [3:0] Q;

    reg [3:0] next_Q;

    // Uses NOR function to make sure that
    // the next state after d0000 is 0001
    always @(posedge CLK) begin
        Q <= next_Q;
    end

 
    always @ (Q) begin
        next_Q[3] = Q[2];
        next_Q[2] = Q[1];
        next_Q[1] = Q[0];
        next_Q[0] = ~(Q[2] & Q[1] & Q[0]);
    end
endmodule
    
```



Johnson Counters

- Definition:** An *n-bit* shift register with the *complement* of the serial output fed back into the serial input is a counter with *2n* states and is called a *switchtail*, *twisted-ring*, or *Johnson counter*
- Problem:** A Johnson counter has the same robustness problem that the simple ring counter has
- Solution:** Make it *self-correcting* by using appropriate feedback, here to load “0001” as the next state whenever the current state is “0dd0” (or, for an *n-bit* counter, when the current state is 0d...d0)

 Example – Simple 4-bit Johnson (“Switchtail”) Counter



Example – Self-Correcting 4-bit Johnson Counter


```

module john4sc(CLK, Q);
    input wire CLK;
    output reg [3:0] Q;

    wire R;

    // Match 0dd0
    assign R = ~Q[3] & ~Q[0];

    // Loads 0001 as next state
    // when current state is 0dd0
    always @(posedge CLK) begin
        Q[3] <= ~R & Q[2];
        Q[2] <= ~R & Q[1];
        Q[1] <= ~R & Q[0];
        Q[0] <= (~R & ~Q[3]) | R;
    end
endmodule
    
```

 


State Decoding

- What is needed to decode the states of an n-bit (n state) ring counter?

Nothing – just use state variables directly

371

Ring Counter State Decoding

 

$$\begin{aligned} S1 &= Q0 \\ S2 &= Q1 \\ S3 &= Q2 \\ S4 &= Q3 \end{aligned}$$

372

State Decoding

- What is needed to decode the states of an n-bit (n state) ring counter?


Nothing – just use state variables directly

- What is needed to decode the states of an n-bit (2n state) Johnson counter?

2n 2-input AND or NAND gates

373

Johnson Counter State Decoding

 

$$\begin{aligned} S1 &= Q0' \cdot Q3' & S5 &= Q0 \cdot Q3 \\ S2 &= Q0 \cdot Q1' & S6 &= Q0' \cdot Q1 \\ S3 &= Q1 \cdot Q2' & S7 &= Q1' \cdot Q2 \\ S4 &= Q2 \cdot Q3' & S8 &= Q2' \cdot Q3 \end{aligned}$$

374

```

/* Self-correcting 4-bit Johnson counter with decoded output */
module john4sod(CLK, S);
    input wire CLK;
    output reg [7:0] S; // Decoded output

    wire R;
    reg [3:0] Q, next_Q;

    assign R = ~Q[3] & ~Q[0]; // Match 0xxx
    always @ (posedge CLK) begin
        Q <= next_Q;
    end

    always @ (Q) begin
        next_Q[1] = ~R & Q[2];
        next_Q[2] = ~R & Q[1];
        next_Q[3] = ~R & Q[0];
        next_Q[0] = ~Q[3] & ~Q[2];
    end

    S[0] = ~Q[3] & ~Q[0];
    S[1] = ~Q[1] & Q[0];
    S[2] = ~Q[2] & Q[1];
    S[3] = ~Q[3] & Q[2];
    S[4] = Q[3] & Q[0];
    S[5] = Q[1] & ~Q[0];
    S[6] = Q[2] & ~Q[1];
    S[7] = Q[3] & ~Q[2];
end
endmodule
    
```

state decoding

375

State Decoding

- What is needed to decode the states of an n-bit (n state) ring counter?

Nothing – just use state variables directly

- What is needed to decode the states of an n-bit (2n state) Johnson counter?

2n 2-input AND or NAND gates

- How does this compare with decoding the states of an n-bit (2ⁿ state) binary counter?

Need 2ⁿ n-input AND or NAND gates, where n is the number of state variables (or, an n-to-2ⁿ decoder)


376

State Decoding

 - Problem:** Because *more than one* bit position changes simultaneously in a **binary count** sequence, there will be "glitches" in the decoded outputs
- Solution:** Connect the decoder outputs to a register that samples the stable decoded outputs on the next clock edge

377

Decoded Outputs of a 3-bit Binary Counter



378

Thought Questions

- Give an example of an application where state decoding glitches can cause problems

When decoded outputs are used as "clocking" signals

- Given that 8 glitch-free decoded outputs are required for a given application, which solution would be best: a 3-bit binary counter, decoder, and de-glitching register; or a 4-bit self-correcting Johnson counter?

Johnson counter

379

Thought Questions

- Is it possible to construct an *n-bit* counter with 2^n states that can be decoded in a glitch-free fashion?

YES – a Gray-code counter

- If so, what property should the count sequence possess?



Each successive combination should differ in only a single bit position

380

Thought Questions

- Where have we seen this before?

On K-maps!

  


381

Summary

- Counters are a common building block used in sequential circuit design, particularly with sequence generator state machines
- There are two basic types of counters
 - binary
 - shift register (types differ based on feedback)
- Counter states can be decoded different ways (some are glitch-free, others are not)
 - binary: standard decoders, *not* glitch-free
 - Gray-code: n-input AND gates, glitch-free
 - Johnson: 2-input AND gates, glitch-free
 - ring: nothing (use flip-flop outputs directly), glitch-free (sometimes called "one hot")

382

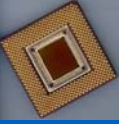

Purdue IM: PACT* Spring 2019 Edition
 *Instruction Matters: Purdue Academic Course Transformation

Introduction to Digital System Design

Module 3-H

State Machine Design Examples: Sequence Recognizers

Reading Assignment:

DDPP 4th Ed. pp. 580-587, DDPP 5th Ed. pp. 642-648

Learning Objective:

- Identify states utilized by a sequence recognizer: accepting sequence, final, and trap
- Determine the embedded binary sequence detected by a sequence recognizer

Outline


- Overview
- Simple pattern recognizer
- Digital lock
- Summary

Overview

- A **sequence recognizer** state machine responds to a **pre-defined input pattern** of signal assertions and produces corresponding output signal assertions
 - digital lock / access code control
 - bit sequence detector
- Use of **Moores** models to design sequence recognizer is generally **preferred**, because you typically **don't want any output signals to change** (based on input signal changes) **until the machine is clocked to the next state** (i.e., the outputs should **only** be a function of the state variables)
- Because "actions" (output signal assertions) occur in response to a pre-defined pattern, a sequence recognizer has different kinds of "final states" (denoted with **concentric circles** on ST diagram):
 - final state of accepting sequence (e.g., "unlock")
 - trap state (e.g., "alarm")

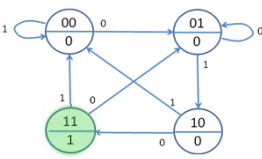Example – Simple Pattern Recognizer


- Assuming the state machine is initialized to state 00, determine the **output sequence** generated in response to the following **input sequence**: 1 1 0 1 0 0 0 1 0 0



final state in pattern accepting sequence

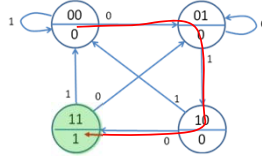Example – Simple Pattern Recognizer

- Assuming the state machine is initialized to state 00, determine the **output sequence** generated in response to the following **input sequence**: 1 1 0 1 0 0 0 1 0 0



- Determine the **embedded binary sequence** recognized by this state machine: **0 1 0**

Example - Digital Combination Lock


- Design a digital combination lock
 - unlocks when a fixed combination (binary sequence) is entered: **101110**
 - has three inputs:
 - X – combination data
 - R – relock / reset
 - RESET – asynchronous reset
 - has three output signals:
 - LOCKED
 - UNLOCKED
 - ALARM

394

Example - Digital Combination Lock

- Implement using Moore model
 - will need an initial “locked” state
 - will need six states to accept digits of combination (the last is “unlocked”)
 - will need an “alarm” state
 - total number of states is eight; therefore, can implement with three state variables
- Types of states
 - accepting sequence (entering combination)
 - final state (sequence correctly entered)
 - trap state (error made while entering combination)

395

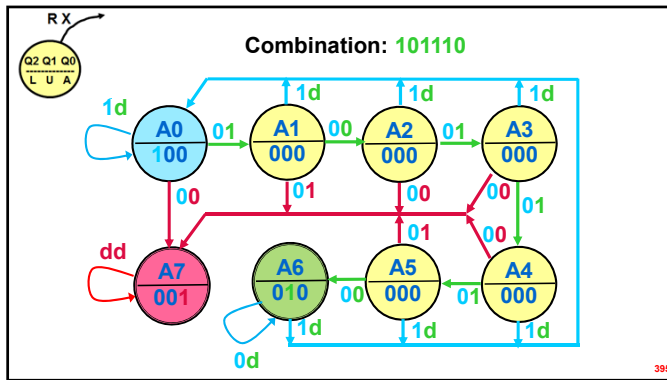

395

```

/* Digital Combination Lock */
module dcl(CLK, RST, X, R, LOCKED, UNLOCKED, ALARM);
input wire CLK, RST, X, R; // X = combination data input, R = relock input
output wire LOCKED, UNLOCKED, ALARM;

reg [2:0] Q, next_Q;

localparam A0 = 3'b000; // Locked
localparam A1 = 3'b001;
localparam A2 = 3'b010;
localparam A3 = 3'b011;
localparam A4 = 3'b100;
localparam A5 = 3'b101;
localparam A6 = 3'b110; // Unlocked
localparam A7 = 3'b111; // Alarm

always @ (posedge CLK, posedge RST) begin
    if (RST == 3'b01)
        Q <= 3'b000;
    else
        Q <= next_Q;
    end

always @ (R, X) begin
    case (Q)
        A0: if (R=1) next_Q = A0;
            else if ((R=0) & (X=0)) next_Q = A7;
            else if ((R=0) & (X=1)) next_Q = A1;
        A1: if (R=1) next_Q = A0;
            else if ((R=0) & (X=0)) next_Q = A7;
            else if ((R=0) & (X=1)) next_Q = A2;
        A2: if (R=1) next_Q = A0;
            else if ((R=0) & (X=0)) next_Q = A7;
            else if ((R=0) & (X=1)) next_Q = A3;
        A3: if (R=1) next_Q = A0;
            else if ((R=0) & (X=0)) next_Q = A7;
            else if ((R=0) & (X=1)) next_Q = A4;
        A4: if (R=1) next_Q = A0;
            else if ((R=0) & (X=0)) next_Q = A7;
            else if ((R=0) & (X=1)) next_Q = A5;
        A5: if (R=1) next_Q = A0;
            else if ((R=0) & (X=0)) next_Q = A7;
            else if ((R=0) & (X=1)) next_Q = A6;
        A6: next_Q = A7;
        A7: next_Q = A7;
    endcase
    assign LOCKED = ~(Q[2] & Q[1] & ~Q[0]);
    assign UNLOCKED = Q[2] & Q[1] & ~Q[0];
    assign ALARM = Q[2] & Q[1] & Q[0];
endmodule
    
```

396

Summary

- A sequence recognizer is a state machine that produces output signal assertions in response to an input pattern
- Output signal assertions typically occur when the machine enters a “final state” associated with the accepting sequence
- Sequence recognizers are typically realized with Moore models, to prevent “spurious” behavior that might occur if the machine’s outputs could potentially change in response to an input signal change without clocking it

397