

### Lab Quiz 3


*Closed Book and Notes – TI 30II XS Calculator Allowed*

Table 1. DC Characteristics of a Hypothetical Logic Family.

$V_{CC} = 5 \text{ V}$	$V_{OH} = 4.20 \text{ V}$	$V_{OL} = 0.50 \text{ V}$	$V_{IH} = 3.7 \text{ V}$	$V_{IL} = 1.2 \text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -6.0 \text{ mA}$	$I_{OL} = 8.0 \text{ mA}$	$I_{IH} = 10 \mu\text{A}$	$I_{IL} = -10 \mu\text{A}$


1. When interfacing an LED that has a **forward voltage of 1.5 V** to the logic family described in Table 1 using a **current sourcing** configuration, **maximum brightness** will be achieved (within the rated specifications) using a current limiting resistor of the value:

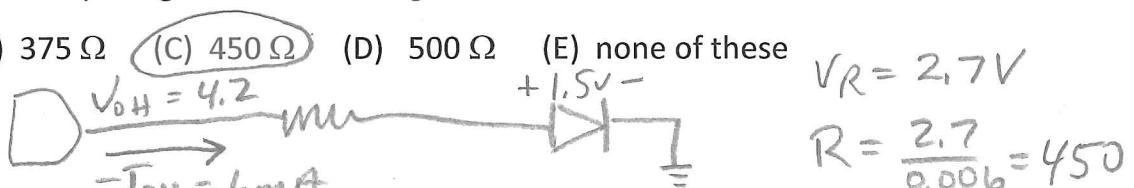- (A)  $270 \Omega$  (B)  $375 \Omega$  (C)  $450 \Omega$  (D)  $500 \Omega$  (E) none of these



2. When interfacing an LED that has a **forward voltage of 1.5 V** to the logic family described in Table 1 using a **current sinking** configuration, **maximum brightness** will be achieved (within the rated specifications) using a current limiting resistor of the value:

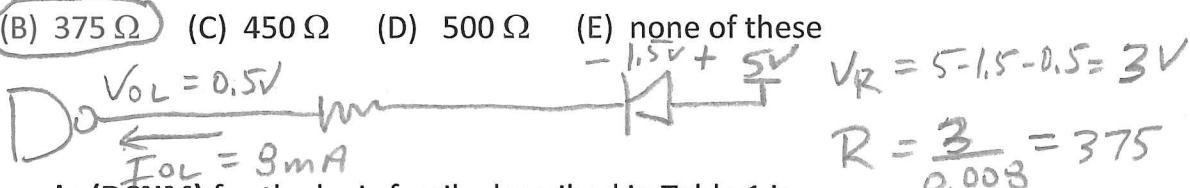- (A)  $270 \Omega$  (B)  $375 \Omega$  (C)  $450 \Omega$  (D)  $500 \Omega$  (E) none of these



3. The **DC noise margin (DCNM)** for the logic family described in Table 1 is:

- (A)  $-0.7 \text{ V}$  (B)  $-0.5 \text{ V}$  (C)  $+0.5 \text{ V}$  (D)  $+0.7 \text{ V}$  (E) none of these

$$DCNM = \min(4.2 - 3.7, 1.2 - 0.5) = 0.5 \text{ V}$$

4. The **practical fan-out** for the logic family described in Table 1 is:

- (A)  $-800$  (B)  $-600$  (C)  $600$  (D)  $800$  (E) none of these

$$\text{Fanout} = \min\left(\frac{6}{0.01}, \frac{8}{0.01}\right) = 600$$

5. The **on resistance** of the P-channel MOSFET for the logic family described in Table 1 is approximately:

- (A)  $62.5 \Omega$  (B)  $133 \Omega$  (C)  $350 \Omega$  (D)  $700 \Omega$  (E) none of these

$$\text{voltage drop} = 5 - 4.2 = 0.8 \text{ V} @ 6 \text{ mA}$$

$$R_{on} = \frac{0.8}{0.006} = 133 \Omega$$