

### Lab Quiz 4

Closed Book and Notes – TI 30II XS Calculator Allowed

1. A microcontroller designed to operate over a power supply range of 1.2 V to 3.3 V and a clock frequency range of 0 to 100 MHz dissipates a maximum of 500 mW. If the supply voltage used is 1.475 V and the clock frequency is 100 MHz, the power dissipation of the microcontroller will be reduced to approximately:  
 (A) 25 mW (B) 50 mW (C) 75 mW (D) 100 mW (E) none of these

$$(1.475/3.3)^2 \times 500 = 99.9 \text{ mW}$$

2. A microcontroller designed to operate over a power supply range of 1.2 V to 3.3 V and a clock frequency range of 0 to 100 MHz dissipates a maximum of 500 mW. If the supply voltage used is 3.3 V and the clock frequency is 5 MHz, the power dissipation of the microcontroller will be reduced to approximately:  
 (A) 25 mW (B) 50 mW (C) 75 mW (D) 100 mW (E) none of these

$$5/100 \times 500 = 25 \text{ mW}$$

3. If a CMOS gate input voltage is 70% of its  $V_{cc}$  (power supply) voltage, then:  
 (A) the logic gate will dissipate **less power** than it would if the input was 10% of its power supply voltage  
 (B) the logic gate will dissipate **less power** than it would if the input was 90% of its power supply voltage  
 (C) the logic gate will dissipate **more power** than it would if the input was either 10% or 90% of its power supply voltage  
 (D) the logic gate will dissipate **virtually no power**  
 (E) none of the above


Ref. p. 17 of Lecture Summary Notes

4. Based on the timing diagram below, estimate the value of the capacitor (C):  
 (A) 10 pF (B) 12 pF (C) 15 pF (D) 18 pF (E) none of these

rise time = 30 ns  
 $2500 \times C = 30 \times 10^{-9}$

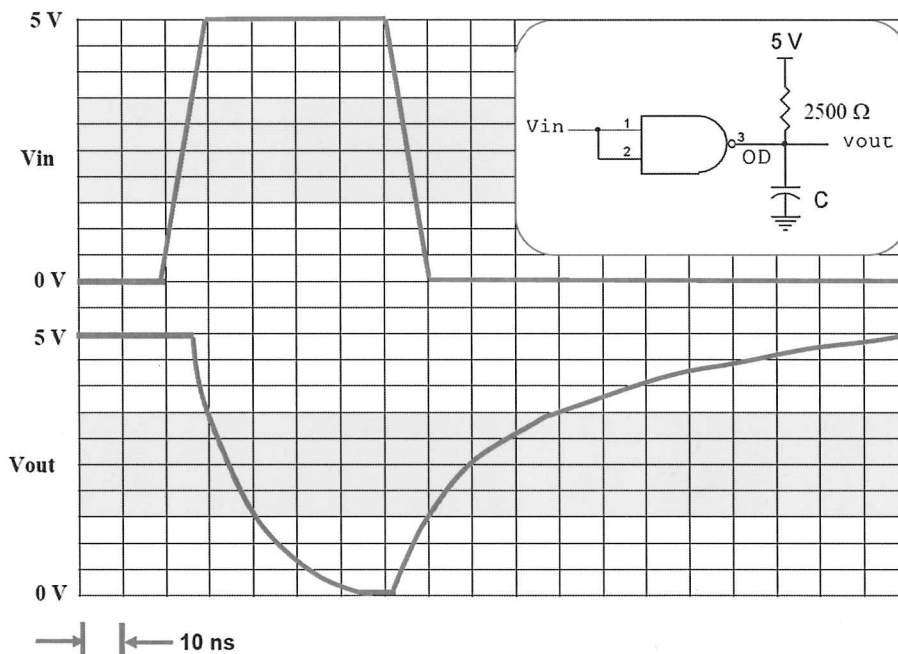5. Based on the timing diagram below, estimate the ON resistance of the open-drain NAND gate:  
 (A) 250  $\Omega$  (B) 567  $\Omega$  (C) 833  $\Omega$  (D) 1000  $\Omega$  (E) none of these

$$C = \frac{30 \times 10^{-9}}{25 \times 10^3} = 12 \times 10^{-12} = 12 \text{ pF}$$



fall time = 10 ns  
 $R_{on} \times 12 \times 10^{-12} = 10 \times 10^{-9}$   
 $R_{on} = \frac{10 \times 10^{-9}}{12 \times 10^{-12}} = 0.833 \times 10^3 = 833 \Omega$

Signature: \_\_\_\_\_ E-mail: \_\_\_\_\_@purdue.edu