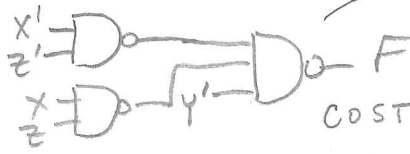


Lab Quiz 5

Closed Book and Notes – No Calculators Allowed

The following K-map applies to the questions on this quiz:

$$F = Y + X'Z' + XZ$$



COST = 10


	X'	X
Z'	1	d
Z	0	1
	Y'	Y

$$F' = XZ' + X'Y'Z \Rightarrow \text{OD}$$

$$\Rightarrow F = (X' + Z) \cdot (X + Y + Z')$$



COST = 10

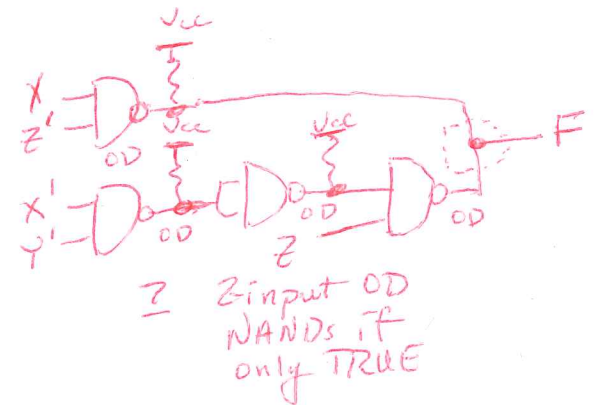

- The **cost** of a **minimal sum of products** realization of this function (assuming **both true and complemented variables** are available) would be:
 (A) ≤ 7 (B) 8 (C) 9 (D) 10 (E) ≥ 11
- The **cost** of a **minimal product of sums** realization of this function (assuming **both true and complemented variables** are available) would be:
 (A) ≤ 7 (B) 8 (C) 9 (D) 10 (E) ≥ 11
- Assuming the availability of **only true** input variables, the **fewest number of 2-input NAND gates** that are needed to realize this function is:
 (A) ≤ 7 (B) 8 (C) 9 (D) 10 (E) ≥ 11
- Assuming the availability of **only true** input variables, the **fewest number of 2-input NOR gates** that are needed to realize this function is:
 (A) ≤ 7 (B) 8 (C) 9 (D) 10 (E) ≥ 11
- Assuming the availability of **only true** input variables, the **fewest number of 2-input open-drain NAND gates** that are needed to realize this function is:
 (A) ≤ 7 (B) 8 (C) 9 (D) 10 (E) ≥ 11

can do w/ 6 gates if manipulate SoP form

Signature: _____ E-mail: _____@purdue.edu