

Lab Quiz 6

Closed Book and Notes – No Calculators Allowed

1. The **OFF-SET** of the function realized by this circuit is:

- (A) $\prod_{x,y,z}(0,2,4)$
- (B) $\prod_{x,y,z}(1,4,6)$
- (C) $\prod_{x,y,z}(0,2,3,5,7)$
- (D) $\prod_{x,y,z}(1,3,5,6,7)$
- (E) none of the above

2. Expressed in minimum **sum-of-products** form, the function realized by this circuit is:

- (A) $X \cdot Z' + X' \cdot Y' \cdot Z$
- (B) $X' \cdot Z' + Y' \cdot Z'$
- (C) $X' \cdot Y + X' \cdot Z' + X \cdot Z$
- (D) $Z + X \cdot Y$
- (E) none of the above

3. Expressed in minimum **product-of-sums** form, the function realized by this circuit is:

- (A) $(X+Z) \cdot (Y+Z)$
- (B) $(X+Y') \cdot (X+Z) \cdot (X'+Z')$
- (C) $Z' \cdot (X'+Y')$
- (D) $(X'+Z') \cdot (Y'+Z')$
- (E) none of the above

4. The **output Y** of the circuit shown exhibits the **following type of hazard** when its input, X, transitions from **low-to-high**:

- (A) a static-zero hazard
- (B) a static-one hazard
- (C) a dynamic hazard
- (D) a minterm hazard
- (E) none of the above

5. The **output Y** of the circuit shown exhibits the **following type of hazard** when its input, X, transitions from **high-to-low**:

- (A) a static-zero hazard
- (B) a static-one hazard
- (C) a dynamic hazard
- (D) a minterm hazard
- (E) none of the above

Draw K-map:

$$F' = X'Z' + X'Y + XZ$$

	X'	X	
Z'	0	1	
Z	1	0	
	Y'	Y	Y'

$\prod_{x,y,z}(0,2,3,5,7)$

$$F = XZ' + X'Y'Z$$

$$F = (X+Z) \cdot (X+Y') \cdot (X'+Z')$$

Sketch timing diagram: