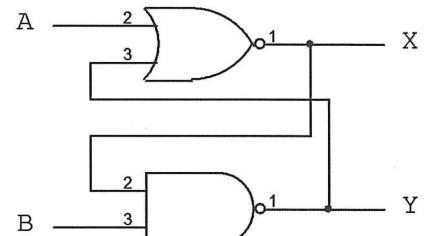


Lab Quiz 8

The following circuit applies to the questions on this quiz. Complete the next state equations, present state – next state table, and state transition diagram to determine the answers.

$$X^* = \underline{(A+Y)' = A' \cdot Y'}$$

$$Y^* = \underline{(B \cdot X)' = B' + X'}$$



1. The next state equation for X is:

- (A) $X^* = A' \cdot Y'$
- (B) $X^* = A' + Y'$
- (C) $X^* = A' + B + X$
- (D) $X^* = A' \cdot (B + X)$
- (E) none of the above

X	Y	A	B	X^*	Y^*
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	1	1
1	0	0	1	1	0
1	0	1	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	0	1	0	0
1	1	1	0	0	1
1	1	1	1	0	0

2. The next state equation for Y is:

- (A) $Y^* = B' \cdot X'$
- (B) $Y^* = B' + X'$
- (C) $Y^* = B' + A + Y$
- (D) $Y^* = B' \cdot (A + Y)$
- (E) none of the above

3. The following state **cannot** occur:

- (A) $X=0, Y=0$
- (B) $X=0, Y=1$
- (C) $X=1, Y=0$
- (D) $X=1, Y=1$
- (E) none of the above

4. Based on the state transition diagram, if this feedback sequential circuit is initialized to state $X=0, Y=0$ and combination $A=0, B=0$ is (continuously) applied to its inputs, the (steady state) output combination will be:

- (A) $X=0, Y=0$
- (B) $X=0, Y=1$
- (C) $X=1, Y=0$
- (D) $X=1, Y=1$
- (E) unpredictable

5. Based on the state transition diagram, if this feedback sequential circuit is initialized to state $X=0, Y=0$ and combination $A=0, B=1$ is (continuously) applied to its inputs, the outputs will:

- (A) be unpredictable
- (B) stay at $X=0, Y=0$
- (C) change to $X=1, Y=1$
- (D) "oscillate" between $X=0, Y=0$ and $X=1, Y=1$
- (E) none of the above

