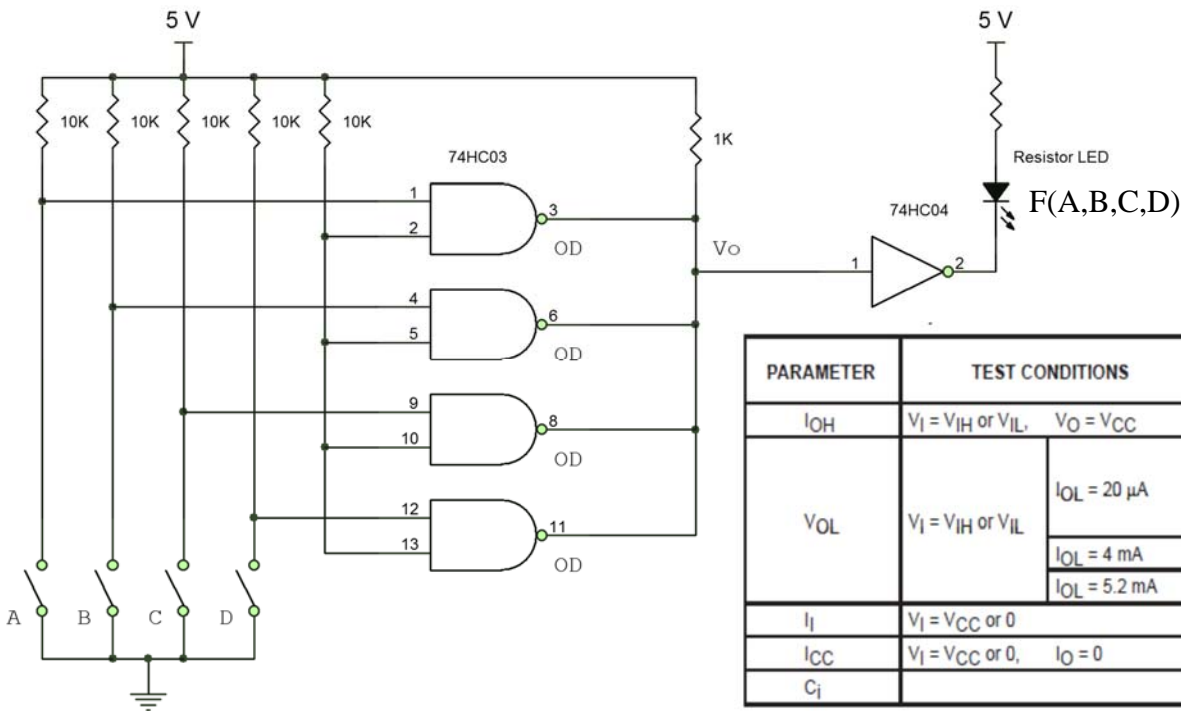


Practice Quiz 4

Closed Book and Notes – TI 30II XS Calculator Allowed



PARAMETER	TEST CONDITIONS	V _{CC}	SN74HC03		UNIT
			MIN	MAX	
I _{OH}	V _I = V _{IH} or V _{IL} , V _O = V _{CC}	6 V		5	μA
V _{OL}	V _I = V _{IH} or V _{IL}	2 V		0.1	V
		4.5 V		0.1	
		6 V		0.1	
		I _{OL} = 4 mA	4.5 V	0.33	
	I _{OL} = 5.2 mA	6 V	0.33		
I _I	V _I = V _{CC} or 0	6 V		±1000	nA
I _{CC}	V _I = V _{CC} or 0, I _O = 0	6 V		20	μA
C _i		2 V to 6 V		10	pF

- Assuming that **F(A,B,C,D) = 1** corresponds to the **LED being illuminated (note active low current sinking configuration)**, the function realized by this circuit is:
 (A) $F = A \cdot B \cdot C \cdot D$ (B) $F = (A \cdot B \cdot C \cdot D)'$ (C) $F = A + B + C + D$ (D) $F = (A + B + C + D)'$ (E) none of these
- Based on a specified I_{OL} of 4 mA @ V_{OL} of 0.33 V, the **ON resistance** of a 74HC03 open-drain output relative to ground is approximately:
 (A) 83 Ω (B) 1000 Ω (C) 1168 Ω (D) 30 KΩ (E) none of these
- Based on a specified I_{OLmax} of 4 mA @ V_{OL} of 0.33 V, the **minimum value of pull-up resistor** used (R_{min}) should be approximately:
 (A) 83 Ω (B) 1000 Ω (C) 1168 Ω (D) 30 KΩ (E) none of these
- Based on a desired V_{IHmin} of 4.37 V @ I_{IH} of 1 μA at the input to the 74HC04 inverter, the **maximum value of pull-up resistor** used (R_{max}) should be approximately:
 (A) 83 Ω (B) 1000 Ω (C) 1168 Ω (D) 30 KΩ (E) none of these
- When A=L, B=L, C=L, and D=H, the **current sunk** by the **active** open-drain gate in the circuit as shown (with a 1000 Ω pull-up resistor) will be approximately:
 (A) 0 mA (B) 1.6 mA (C) 4.0 mA (D) 4.6 mA (E) none of these