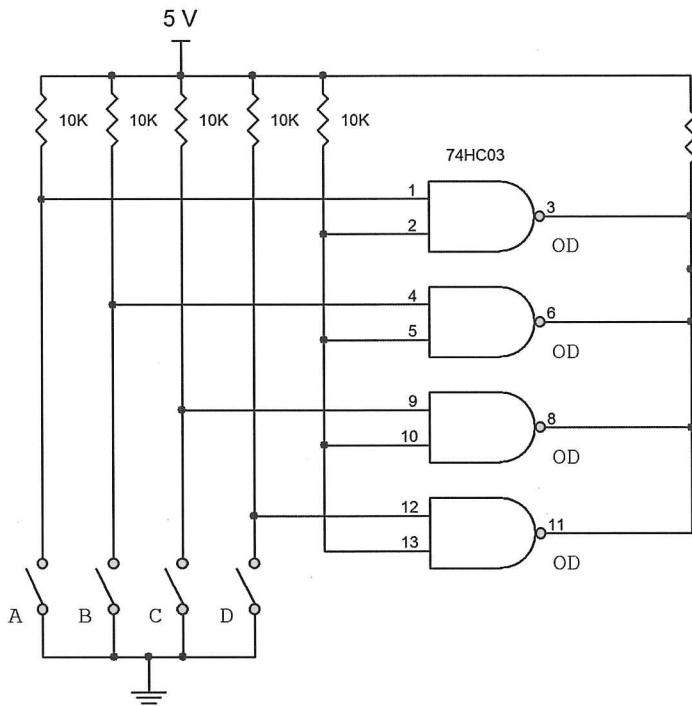


Practice Quiz 4

Closed Book and Notes – TI 30II XS Calculator Allowed



$F = A' \cdot B' \cdot C' \cdot D'$
 $= (A + B + C + D)'$
 based on Demorgan's Law
 note: active low
 $\Rightarrow F = \text{input to inverter}$

PARAMETER	TEST CONDITIONS		V_{CC}	SN74HC03 MIN MAX	UNIT	
	$V_I = V_{IH}$ or V_{IL}	$V_O = V_{CC}$				
I_{OH}	$V_I = V_{IH}$ or V_{IL}	$V_O = V_{CC}$	6 V	5	μA	
			2 V	0.1	V	
			4.5 V	0.1		
			6 V	0.1		
			4.5 V	0.33		
			6 V	0.33		
I_I	$V_I = V_{CC}$ or 0		6 V	± 1000	nA	
I_{CC}	$V_I = V_{CC}$ or 0, $I_O = 0$		6 V	20	μA	
C_i			2 V to 6 V	10	pF	

1. Assuming that $F(A,B,C,D) = 1$ corresponds to the LED being illuminated (note active low current sinking configuration), the function realized by this circuit is:
- (A) $F = A \cdot B \cdot C \cdot D$ (B) $F = (A \cdot B \cdot C \cdot D)'$ (C) $F = A + B + C + D$ (D) $F = (A + B + C + D)'$ (E) none of these

2. Based on a specified I_{OL} of 4 mA @ V_{OL} of 0.33 V, the **ON resistance** of a 74HC03 open-drain output relative to ground is approximately:
- (A) 83Ω (B) 1000Ω (C) 1168Ω (D) $30 \text{ k}\Omega$ (E) none of these

$$R_{on} = 0.33V / 0.004 = 82.5 \Omega$$

3. Based on a specified I_{OLmax} of 4 mA @ V_{OL} of 0.33 V, the **minimum value of pull-up resistor** used (R_{min}) should be approximately:
- (A) 83Ω (B) 1000Ω (C) 1168Ω (D) $30 \text{ k}\Omega$ (E) none of these

$$V_{R_{min}} = 5 - 0.33 = 4.67V \quad R_{min} = \frac{4.67V}{0.004} = 1167.5 \Omega$$

4. Based on a desired V_{IHmin} of 4.37 V @ I_{IH} of 1 μA at the input to the 74HC04 inverter, the **maximum value of pull-up resistor** used (R_{max}) should be approximately: $I_{R} = 4 \times 5 \mu A + 1 \mu A = 21 \mu A$
- (A) 83Ω (B) 1000Ω (C) 1168Ω (D) $30 \text{ k}\Omega$ (E) none of these

$$V_{R_{max}} = 5 - 4.37 = 0.63V \quad R_{max} = \frac{0.63V}{21 \mu A} = 30,000 \Omega$$

5. When A=L, B=L, C=L, and D=H, the **current sunk** by the active open-drain gate in the circuit as shown (with a 1000 Ω pull-up resistor) will be approximately:
- (A) 0 mA (B) 1.6 mA (C) 4.0 mA (D) 4.6 mA (E) none of these

$$R_{eq} = 1000 + 83 = 1083 \Omega \quad I_{OL} = \frac{5}{1083} = 4.6 mA$$