

## Practice Quiz 5

*Closed Book and Notes – No Calculators Allowed*

The following K-map applies to the questions on this quiz:

		X'		X	
Z'	1	0	d	d	
Z	0	0	1	1	
		Y'	Y	Y'	

- The **cost** of a **minimal sum of products** realization of this function (assuming **both true and complemented variables** are available) would be:  
 (A) 5    (B) 6    (C) 7    (D) 8    (E) 9
- The **cost** of a **minimal product of sums** realization of this function (assuming **both true and complemented variables** are available) would be:  
 (A) 5    (B) 6    (C) 7    (D) 8    (E) 9
- Assuming the availability of **only true** input variables, the **fewest number of 2-input NAND gates** that are needed to realize this function is:  
 (A) 5    (B) 6    (C) 7    (D) 8    (E) 9
- Assuming the availability of **only true** input variables, the **fewest number of 2-input NOR gates** that are needed to realize this function is:  
 (A) 5    (B) 6    (C) 7    (D) 8    (E) 9
- Assuming the availability of **only true** input variables, the **fewest number of 2-input open-drain NAND gates** that are needed to realize this function is:  
 (A) 1    (B) 2    (C) 3    (D) 4    (E) 5