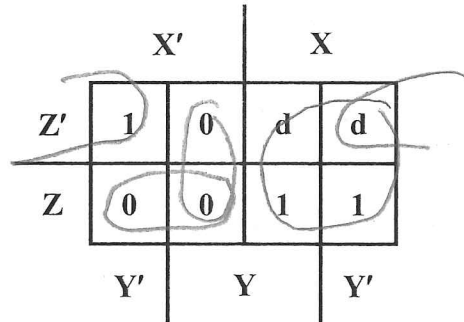


Practice Quiz 5

Closed Book and Notes – No Calculators Allowed

The following K-map applies to the questions on this quiz:



$$F = X + Y'Z'$$

$$F' = X'Y + X'Z$$

$$\Rightarrow F = (X + Y')(X + Z')$$

1. The cost of a minimal sum of products realization of this function (assuming both true and complemented variables are available) would be:

- (A) 5 (B) 6 (C) 7 (D) 8 (E) 9


4 inputs + 2 gates



2. The cost of a minimal product of sums realization of this function (assuming both true and complemented variables are available) would be:


- (A) 5 (B) 6 (C) 7 (D) 8 (E) 9

6 inputs + 3 gates

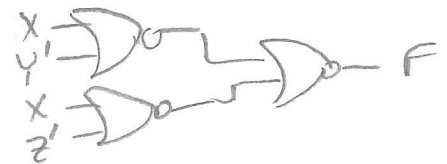


3. Assuming the availability of only true input variables, the fewest number of 2-input NAND gates that are needed to realize this function is:

- (A) 5 (B) 6 (C) 7 (D) 8 (E) 9

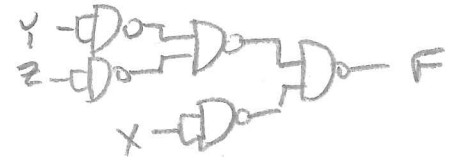

4. Assuming the availability of only true input variables, the fewest number of 2-input NOR gates that are needed to realize this function is:

- (A) 5 (B) 6 (C) 7 (D) 8 (E) 9

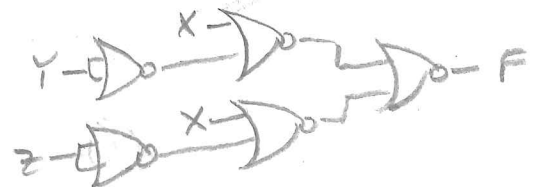

5. Assuming the availability of only true input variables, the fewest number of 2-input open-drain NAND gates that are needed to realize this function is:

- (A) 1 (B) 2 (C) 3 (D) 4 (E) 5

plus 2 pull-up resistors

