 


## Practice Quiz 9

The following figure applies to questions 1–3:



- The **nominal setup time** provided for the D flip-flop, based on the excitation signals (D and CLK) depicted in the timing chart, is:
  - 5 ns
  - 10 ns
  - 15 ns
  - 20 ns
  - none of the above
- The **nominal hold time** provided for the D flip-flop, based on the excitation signals (D and CLK) depicted in the timing chart, is:
  - 5 ns
  - 10 ns
  - 15 ns
  - 20 ns
  - none of the above
- The  $t_{PLH}(C \rightarrow Q)$  of the D flip-flop is:
  - 5 ns
  - 10 ns
  - 15 ns
  - 20 ns
  - none of the above
- As a contestant on the TV series\* **Digital Dynasty**, you have been asked to “digitally dual” with your BECEFE (*best ECE friend evah*) over the phenomenon of metastability. You confidently explain to the host that the **next state** of an edge-triggered D flip-flop will most likely be **random** if:
  - its minimum setup time requirement is not met
  - its minimum hold time requirement is not met
  - its minimum clock pulse width requirement is not met
  - all of the above
  - none of the above
- As a contestant on the hit TV series\* **Are You Smarter than Your BEFFAP?** (*best engineering friend from another planet*) you have been asked to explain why a “D” latch is called **transparent**. Hoping to forgo an admission before a national television audience to the contrary, you calmly answer that a “D” latch is called **transparent** because its output:
  - is equal to its input when the latch enable is high-impedance
  - is equal to its input when the latch enable is asserted
  - is equal to its input when the latch enable is negated
  - changes state as soon as the latch is clocked
  - none of the above

\* Yes, the course staff understands that hard-working ECE students do not have time to watch TV