


Modified version of wide-swing high-Z current mirror

Advantages compared to previous circuit:

Has smaller dissipated power

$\frac{1}{2}$ of the one +
dissipation Of
cascode stage.

And smaller area, and also more stable!

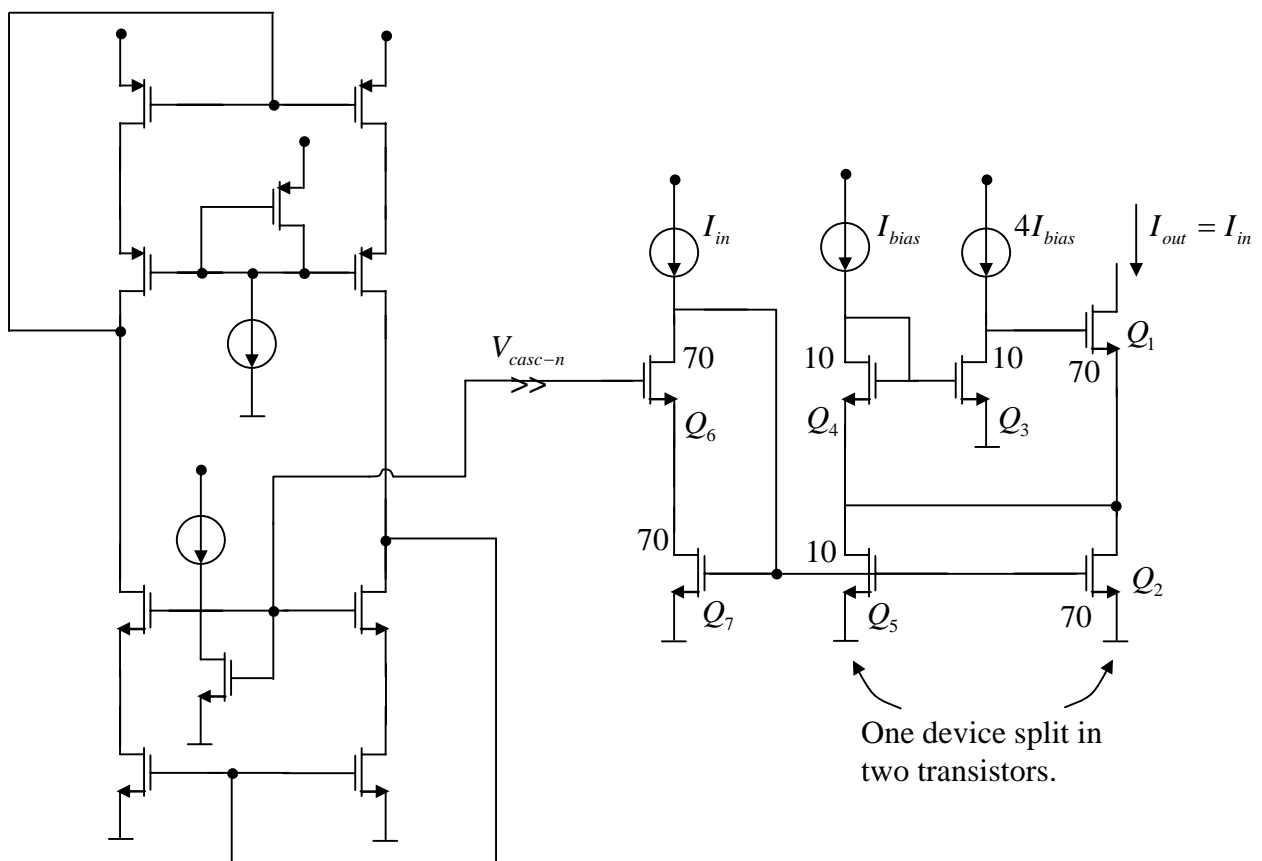

Folded cascode OPAMP

Modern OPAMPs are designed to drive capacitive loads

⇒ No need to have low output impedance

⇒ No need for last stage buffers

⇒ Can design higher speeds and larger signal swings.

All nodes are low-impedance except output node that is connected to a load capacitor



In the order of $1/\text{transistor transconductance}$

\Rightarrow Low impedance also helps reducing the voltage swing. So all nodes are under low voltage swing except for the output.

\Rightarrow Compensation is done by using load capacitance:


more $C_L \Rightarrow$ more stable \Rightarrow slower

Instead of voltage gain, transconductance gain becomes important:

$$\left(\frac{i_{out}}{V_{in}} \right) \Rightarrow OTA \text{ (Operational Transconductance Amplifier)}$$

Folded cascade is an example of high output impedance OTAs.

 Amplifier is actually just a single stage cascade Amp.



\Rightarrow For differential output stage we need to use 2 of these wide swing current mirror stages.

I_{Bias_1} is a constant transconductance biasing circuit and V_{B_1} and V_{B_2} are connected to V_{casc-p} and V_{casc-n} respectively.


Q_{12} and Q_{13} serve two purposes:

1. Increase the slew-rate
2. During slew-rate limiting signal, these transistors prevent drain voltage of Q_1 and Q_2 to negative power supply.

- C_L will be the dominant pole

For small C_L one has to add capacitor to the load to achieve stability.

- For lead compensation

 


$$\text{Current in } Q_1 \text{ and } Q_2 \Rightarrow \frac{I_{Bias_2}}{2}$$

$$\text{Current in } Q_5 \text{ and } Q_6 \Rightarrow I_{Bias_1} \times \frac{(W/L)_3}{(W/L)_{11}} - \frac{I_{Bias_2}}{2}$$

For exact and accurate operation I_{Bias_1} and I_{Bias_e} are generated from the same source.

Small signal analysis
 
$$\left. \begin{aligned} A_v &= \frac{V_{out}(\omega)}{V_{in}(\omega)} = g_{m_1} \cdot Z_L(\omega) \\ Z_L &= \frac{r_{out}}{1 + j\omega r_{out} C_L} \end{aligned} \right\} \Rightarrow A_v = \frac{g_{m_1} r_{out}}{1 + j\omega r_{out} C_L}$$



$$r_{out} \approx \frac{g_m r_{ds}^2}{2} \Rightarrow \boxed{A_v = \frac{g_{m_1}^2 r_{ds}^2 / 2}{1 + \frac{j\omega g_m r_{ds}^2 C_L}{2}}}$$

When load is only a capacitor

Mid band frequencies \rightarrow ignore 1 in the denominator:

$$\Rightarrow A_v = \frac{g_{m_1}}{j\omega C_L} \Rightarrow \boxed{w_{ta} = \frac{g_{m_1}}{C_L}}$$

Unity gain frequency

$g_{m_1} \uparrow \Rightarrow BW \uparrow$

\searrow

use NMOS with $W \uparrow$


\Rightarrow Large input current $I_{Bias}/2$

Current in cascode transistors ($P-MOS$) and current mirror ($Q_7 - Q_{10}$) needs to be small to increase r_{out} .

\Rightarrow gain will be maximized

$$g_{m_1} r_{out}$$

 The practical current ratio limit $\frac{I_{D_2}}{I_{D_5}} = 4$



Since the current is derived by subtraction

\rightarrow Having high input current I_{D_2} also helps reducing thermal noise \rightarrow Since most of the bias current flows in the input differential pair, for the same power consumption, folded cascode has lower noise figure.

Gain calculation with lead compensation

$$Z_L = r_{out} \parallel \left(R_c + \frac{1}{j\omega C_L} \right)$$



Load Compensation Resistor



Load Capacitor

Assuming $r_{out} \gg Z_L$

$$A_v = \frac{g_{m_1}}{\frac{1}{r_{out}} + \frac{1}{R_C + \frac{1}{j\omega C_L}}} \cong \frac{g_{m_1}}{\frac{1}{R_C + j\omega C_L}} = \frac{g_{m_1}(1 + j\omega R_C C_L)}{j\omega C_L}$$


If R_C is chosen to get a zero at 1.2 times the unity gain frequency, optimum speed and stability is achieved:

$$\omega_Z = \frac{1}{R_C C_L} = 1.2 \times \omega_{ta} = 1.2 \times \frac{g_{m_1}}{C_L}$$

$$\Rightarrow R_C = \frac{1}{1.2 g_{m_1}}$$

Location of second pole

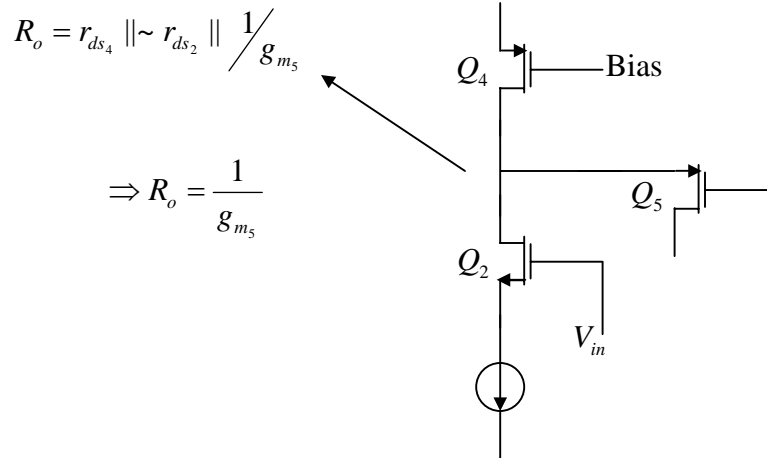The second pole is usually due to RC time constant at the source of P-channel transistors.




$$C_{2nd \text{ pole}} = C_{gs_5} \parallel C_{ds_2} \parallel C_{ds_4} \approx C_{gs_5}$$

$$\omega_{2nd\ pole} = \omega_{p_2} \approx \frac{g_{m_5}}{C_{gs_5}}$$

To improve the high frequency performance one can increase g_{m_5} (current through PMOS transistors) at the cost of extra power consumption.

Slew Rate

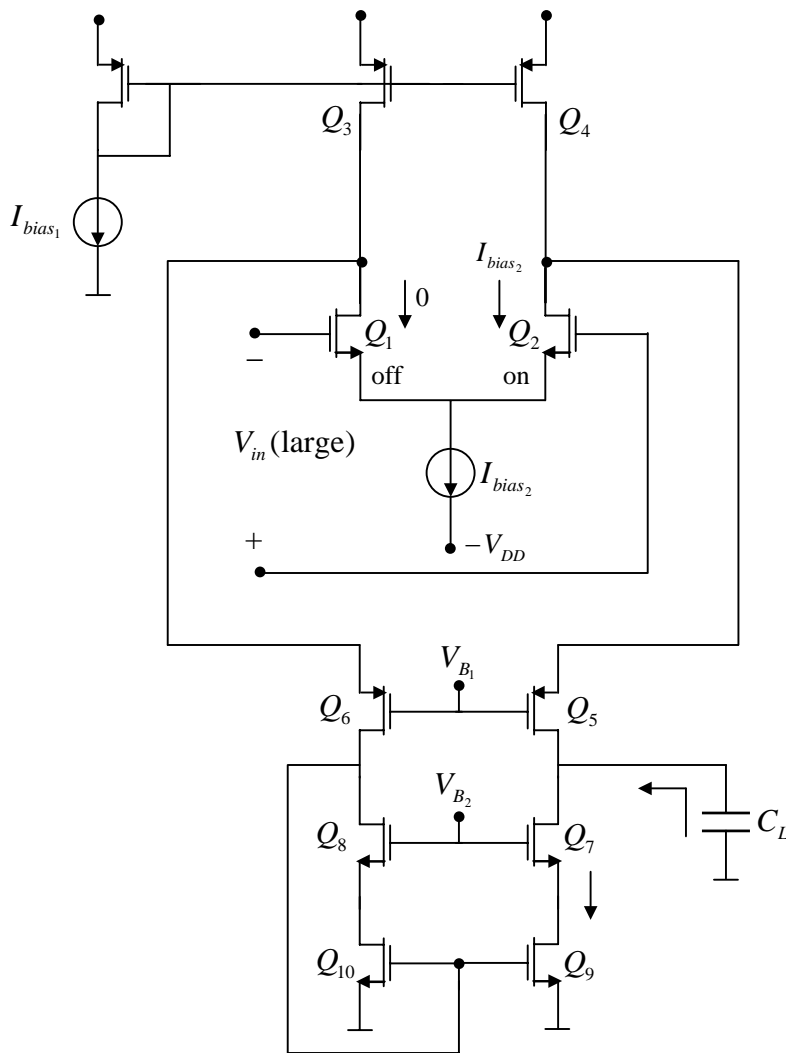What happens if Q_{12} and Q_{13} are not present during slew-rate limiting operation?



$$\Rightarrow \begin{cases} Q_1 : Off \\ Q_2 : On \end{cases}$$

$$\Rightarrow I_{D_3} = I_{D_6} = I_{D_8} = I_{C_{Ldischarge}}$$

$$SR = \frac{I_{D_3}}{C_L}$$

Usually the design is:


$$I_{D_1} = 4 I_{D_6} = \frac{I_{Bias_2}}{2}$$

$$\Rightarrow I_{D_3} = I_{D_1} + I_{D_6}$$

$$\Rightarrow I_{D_3} = \frac{I_{Bias_2}}{2} + \frac{I_{Bias_2}}{8} = \frac{5}{8} I_{Bias_2} \quad \Rightarrow \quad I_{Bias_2} > I_{D_3} = I_{D_4}$$

So when Q_2 is On and need to sink I_{Bias_2} but I_{D_4} cannot give that much current, that pushes both Q_2 and I_{Bias_2} to triode regions \rightarrow So their current decreases and become

$$\frac{5}{8} I_{Bias_2} .$$

 


\rightarrow Drain of Q_2 approaches $-V_{DD}$

In $+ve$, V_{in} cycle drain of Q_2 needs to come back to $+V_{DD}$ \rightarrow We have transition from $\sim -V_{DD}$ to $\sim +V_{DD}$

\rightarrow Additional time that adds to slew-rate + non-linear operation

\rightarrow as you go to triode region.

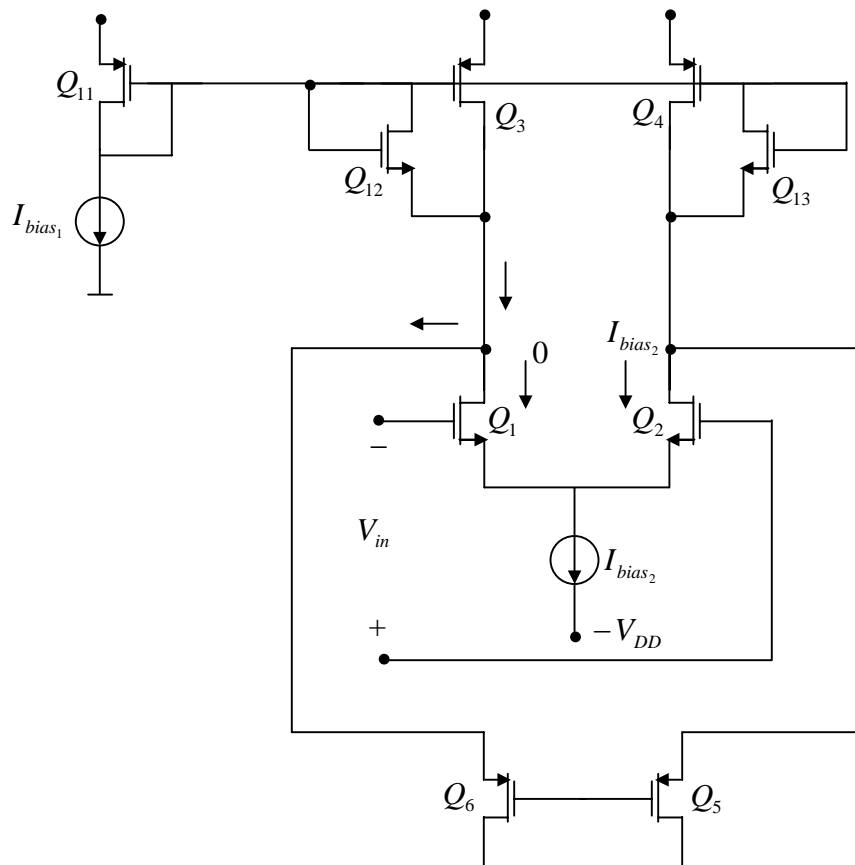To solve this problem we add diode-connected transistors Q_{12} and Q_{13} .



Q_{12} and Q_{13} are normally off:

$$V_{GS_{12}}, V_{GS_{13}} < V_{t_n}$$

During slew-rate limiting operation the branch that has

$$I_{Bias_2} (I_{D_2}) \Rightarrow Q_{13}$$

turns ON since the drain voltage of $Q_2 \downarrow$.

The first thing it does is to clamp drain of Q_2 to a +ve voltage \rightarrow Does not allow it to go -ve.

This is done by providing the current difference:

$$I_{Bias_2} - \frac{5}{8} I_{Bias_2} = \frac{3}{8} I_{Bias_2}$$

Partially by Q_{13} and partially by increasing Q_4 .


\rightarrow No additional slew-rate time is needed

Non-linearity due to transistors entering triode region will not occur.

During slew-rate:

$$I_{D_2} = I_{Bias_2} = I_{D_{13}} + I_{D_4} \quad (1) \Rightarrow I_{D_{13}} = I_{Bias_2} - I_{D_4}$$

The circuit looks like the following:

 

$$\left. \begin{aligned} \frac{I_{D_{11}}}{I_{D_4}} &= \frac{(W/L)_{11}}{(W/L)_4} \Rightarrow I_{D_{11}} = I_{D_4} \times \frac{(W/L)_{11}}{(W/L)_4} \\ I_{D_{11}} &= I_{Bias_1} + I_{D_{13}} \end{aligned} \right\} \Rightarrow I_{D_4} \times \frac{(W/L)_{11}}{(W/L)_4} = I_{D_{13}} + I_{Bias_1}$$

$$I_{D_4} \times \frac{(W/L)_{11}}{(W/L)_4} = I_{Bias_2} - I_{D_4} + I_{Bias_1}$$

$$\Rightarrow I_{D_4} = \frac{(I_{Bias_1} + I_{Bias_2})(W/L)_4}{(W/L)_{11} + (W/L)_4}$$

With Q_{12}/Q_{13} :

$$\text{S.R.} = \frac{I_{D_4} + I_{D_{13}}}{C_L} = \frac{I_{Bias_2}}{C_L}$$




Without Q_{12}/Q_{13} :

$$\text{S.R.} = \frac{I_{D_4}}{C_L} = \frac{I_{Bias_1} (W/L)_4}{(W/L)_{11}}$$

Current Mirror OPAMP

- Is used to drive capacitive loads.
- All nodes are low impedance except the output node \rightarrow Therefore stability can be achieved by putting load capacitor C_L at the output node.

The idea is as following:

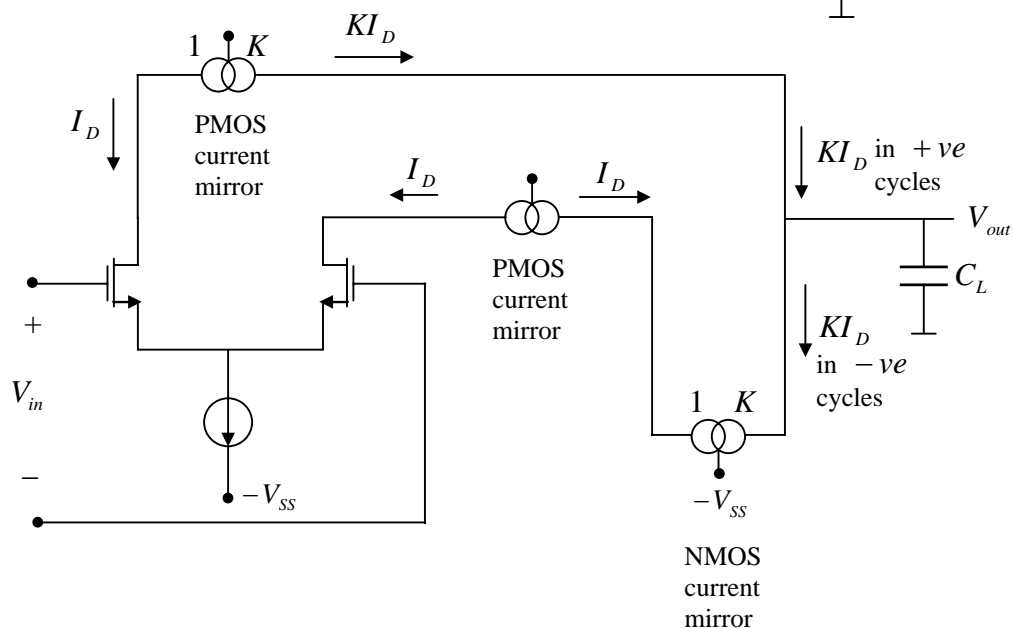 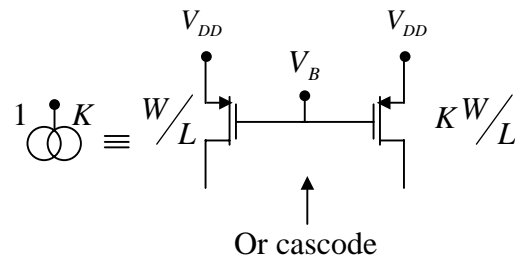

$$A_v = \frac{V_{out}}{V_{in}} = Kg_{m_1} Z_L(s) = \frac{Kg_{m_1} r_{out}}{1 + j\omega r_{out} C_L} \approx \frac{Kg_{m_1}}{j\omega C_L}$$

K is transistor W/L ratio of current mirrors


$$\omega_t \Big|_{A_v \rightarrow 1} = \frac{Kg_{m_1}}{C_L} = \frac{K\sqrt{2I_{D_1}\mu_n C_{ox}}(W/L)_1}{C_L}$$

Power dissipation:

$$P_{diss} = [V_{DD} - (-V_{SS})] I_{total}$$


$$I_{total} = (3 + K) I_{D_1}$$

Practical implementation

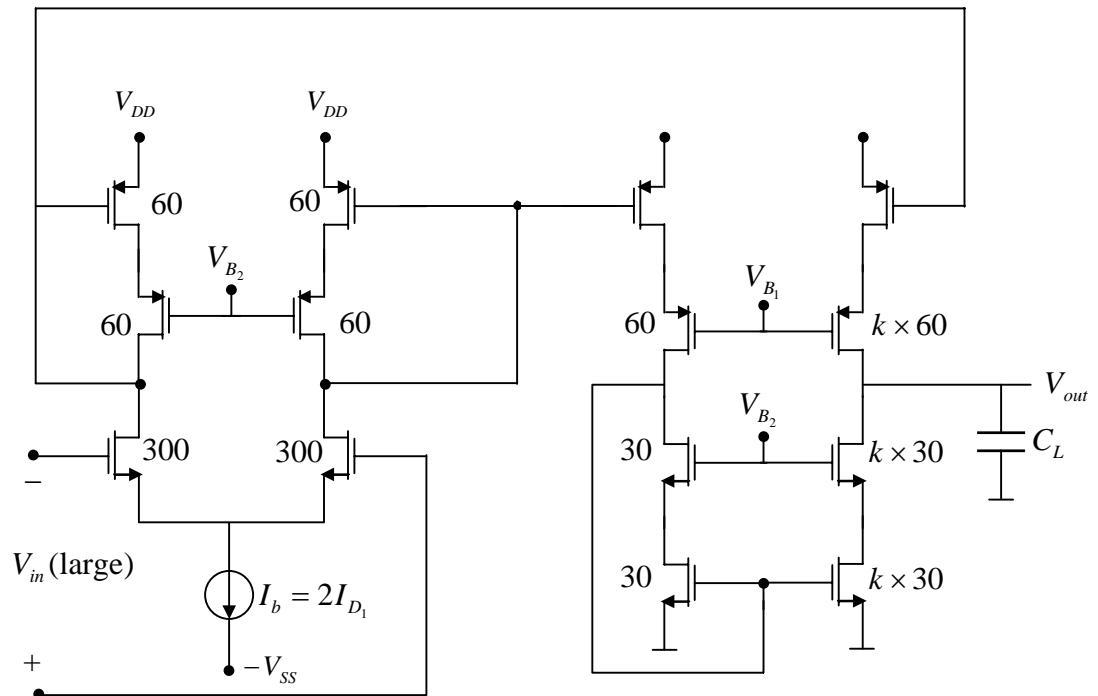

As you increase K

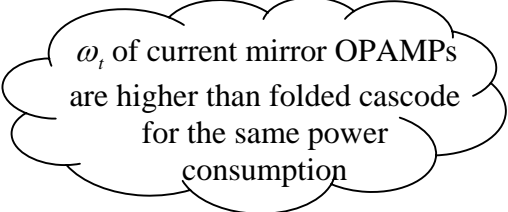- I_{total} increases so power dissipation increases
- Gain increases
- Unity gain frequency increases \rightarrow



ω_t of current mirror OPAMPs
are higher than folded cascode
for the same power
consumption

\rightarrow However there is a practical limit as the second pole of the OPAMP becomes problematic if the unity gain frequency increases too much.

$\rightarrow K$ Max is typically around 5

$K \sim 2$: Good for general purpose OPAMP

$K = 1$: High speed OPAMP as you can use small C_L and your ω_t is still lower than the second pole.

Slow-Rate

$$SR = \frac{KI_b}{C_L} = \frac{2KI_{D1}}{C_L}$$

\Rightarrow In terms of S.R. current mirror OPAMPs are better than folded cascodes.