
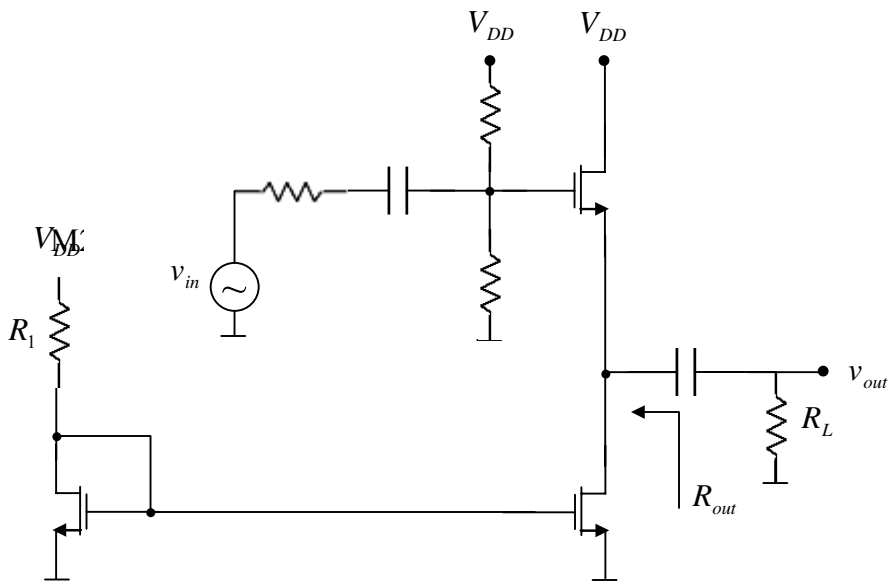


Integrated Source Follower

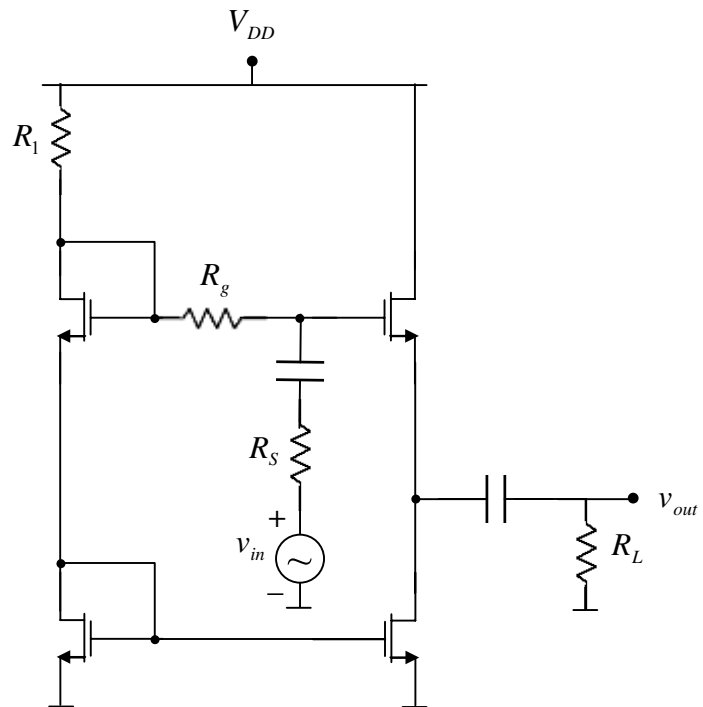


A simpler version:



Common Gate Amplifier

Non-integrated version

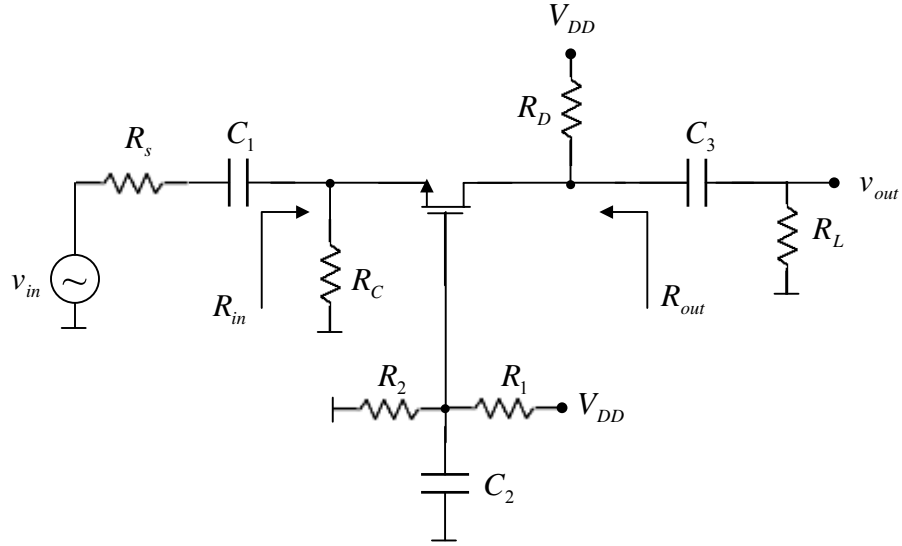

$$V_{DS} = V_{DD} - (R_D + R_C)I_D$$

$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_{t_n})^2$$

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$


$$V_S = R_C I_D$$

$$\rightarrow V_{GS} = V_G - V_S = \frac{R_2}{R_1 + R_2} V_{DD} - R_C I_D$$


2 equations and 2
unknowns: V_{GS} , I_D .

from I_D you can find V_{DS} and check for ideal MOS saturation condition: $V_{DS} > V_{GS} - V_{t_n}$.

Equivalent Circuit

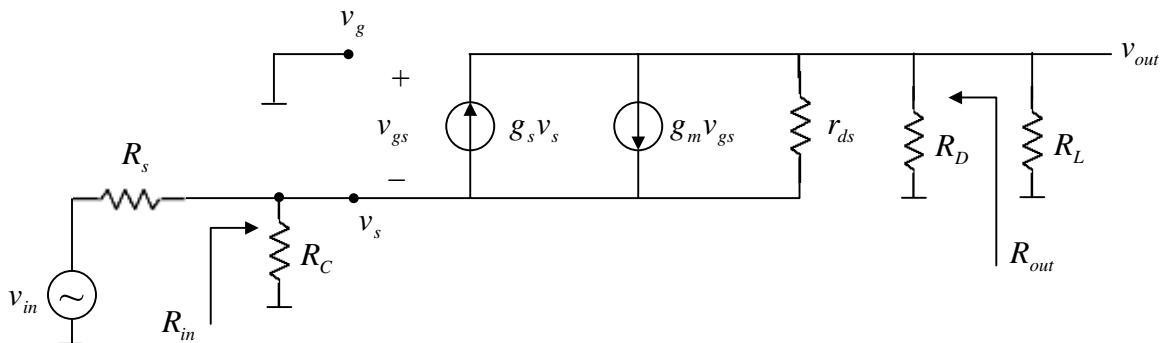

To calculate R_{in}

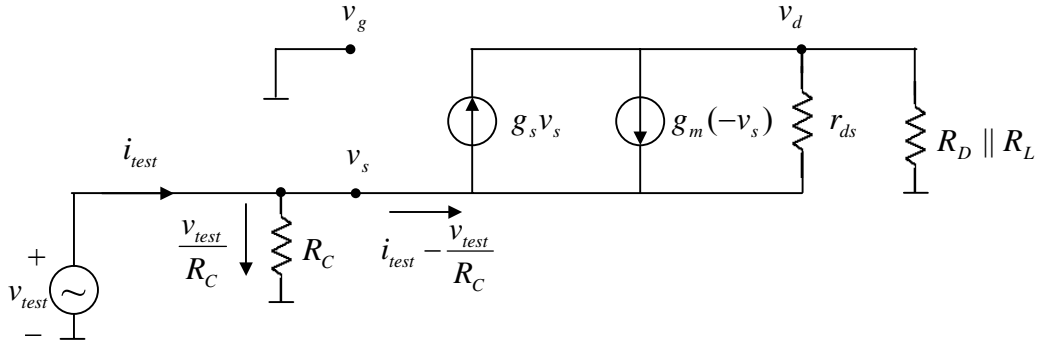

$$\left. \begin{aligned} (i_{test} - \frac{v_{test}}{R_C}) R_D \parallel R_L &= v_d \\ v_s &= v_{test} \end{aligned} \right\} \rightarrow v_{ds} = v_d - v_s$$

$$\rightarrow v_{ds} = i_{test} \cdot R_D \parallel R_L - v_{test} \left(\frac{R_D \parallel R_L}{R_C} + 1 \right)$$

Also:

$$g_s v_s + g_m v_s - \frac{v_{ds}}{r_{ds}} = i_{test} - \frac{v_{test}}{R_C}$$

$$(g_s + g_m) v_{test} + v_{test} \frac{\left(\frac{R_C + R_D \parallel R_L}{R_C} \right)}{r_{ds}} - i_{test} \frac{R_D \parallel R_L}{r_{ds}} = i_{test} - \frac{v_{test}}{R_C}$$

$$\rightarrow v_{test} \left(g_s + g_m + \frac{R_C + R_D \parallel R_L}{R_C \cdot r_{ds}} + \frac{1}{R_C} \right) = i_{test} \left(1 + \frac{R_D \parallel R_L}{r_{ds}} \right)$$

$$\boxed{R_{in} = \frac{v_{test}}{i_{test}} = \frac{\frac{r_{ds} + R_D \parallel R_L}{r_{ds}}}{g_s + g_m + \frac{R_C + R_D \parallel R_L}{R_C \cdot r_{ds}} + \frac{1}{R_C}}}$$

You can simplify the equation; assuming r_{ds} is large \rightarrow


$$r_{ds} \gg \frac{1}{g_m} + g_s$$

$$r_{ds} \gg R_D \parallel R_L, R_C$$

$$\boxed{R_{in} = \frac{1}{g_m + g_s + \frac{1}{R_C}}} \quad \alpha \quad \boxed{R_{in} = \frac{1}{g_m + g_s} \parallel R_C}$$

Similar to R_{out} of source-follower

To calculate R_{out} :

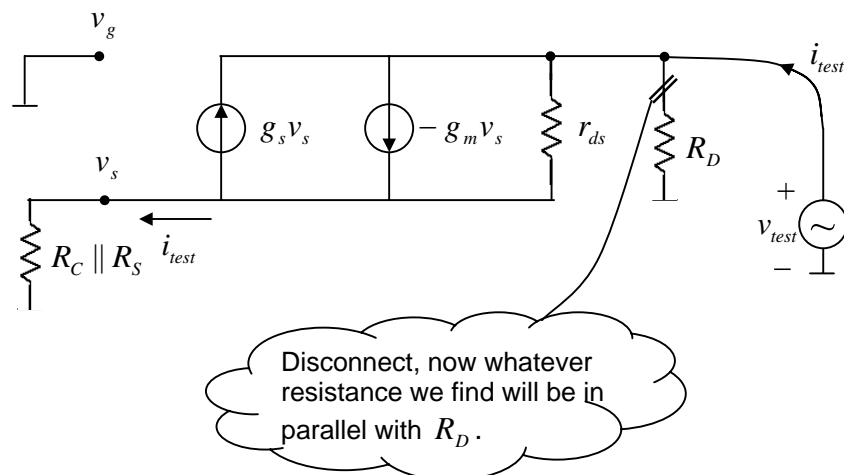

$$v_s = i_{test} (R_C \parallel R_S)$$

$$i_{test} = -g_s v_s - g_m v_s + \frac{(v_{test} - v_s)}{r_{ds}}$$

$$\rightarrow i_{test} + (g_s + g_m + \frac{1}{r_{ds}})v_s = \frac{v_{test}}{r_{ds}}$$


$$i_{test} \left(1 + (R_C \parallel R_S)(g_s + g_m + \frac{1}{r_{ds}}) \right) = \frac{v_{test}}{r_{ds}}$$

$$\rightarrow \frac{v_{test}}{i_{test}} = r_{ds} + (R_C \parallel R_S)[(g_s + g_m)r_{ds} + 1]$$

$$R_{out} = R_D \parallel \frac{v_{test}}{i_{test}} = R_D \parallel (r_{ds} + (R_C \parallel R_S)[(g_s + g_m)r_{ds} + 1])$$

$$R_{out} = R_D \parallel \text{large resistor} = R_D.$$

Voltage Gain (A_v)


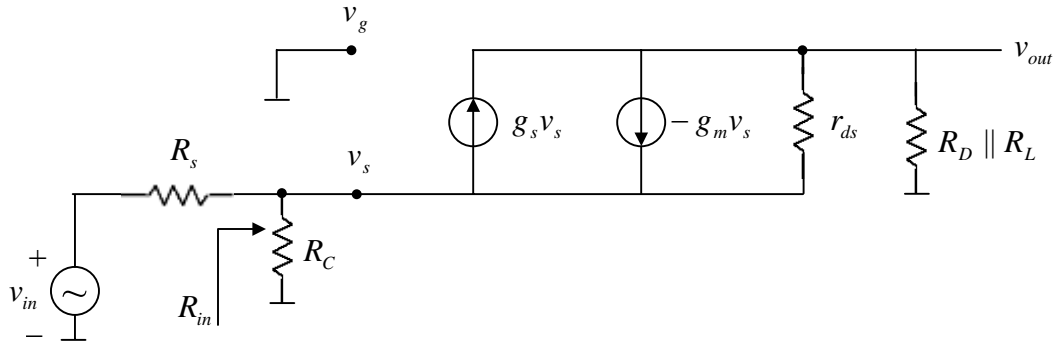


First simplify it (assume $r_{ds} \gg \frac{1}{g_m + g_s}$) and ignore r_{ds} .

$$\left. \begin{aligned} v_{out} &= (g_s + g_m)v_s \cdot R_D \parallel R_L \\ v_s &= \frac{R_{in}}{R_{in} + R_S} v_{in} \end{aligned} \right\} \Rightarrow \boxed{\frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_{in} + R_S} (g_s + g_m) \cdot (R_D \parallel R_L)}$$


$$R_{in} \cong \frac{1}{g_m + g_s + \frac{1}{R_C}}$$

Integrated Common-gate Amplifier

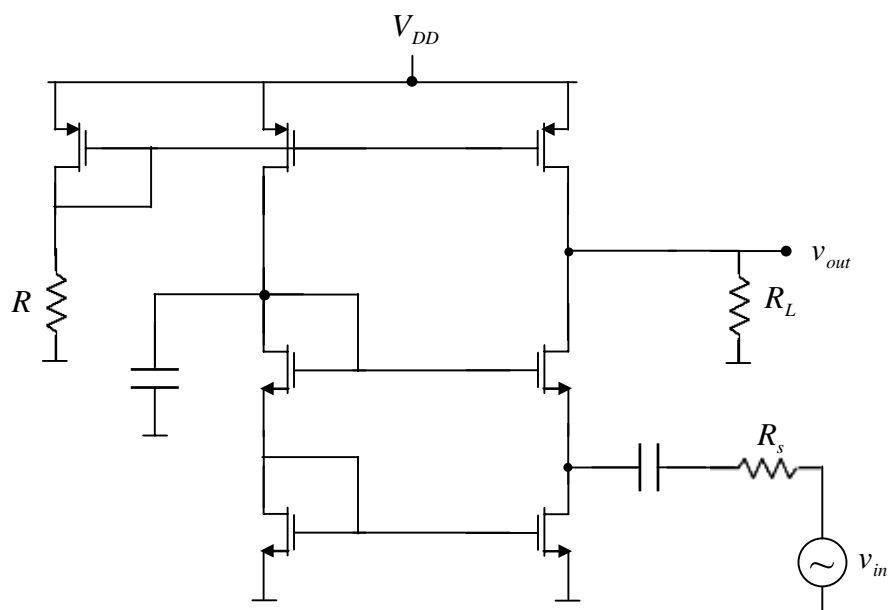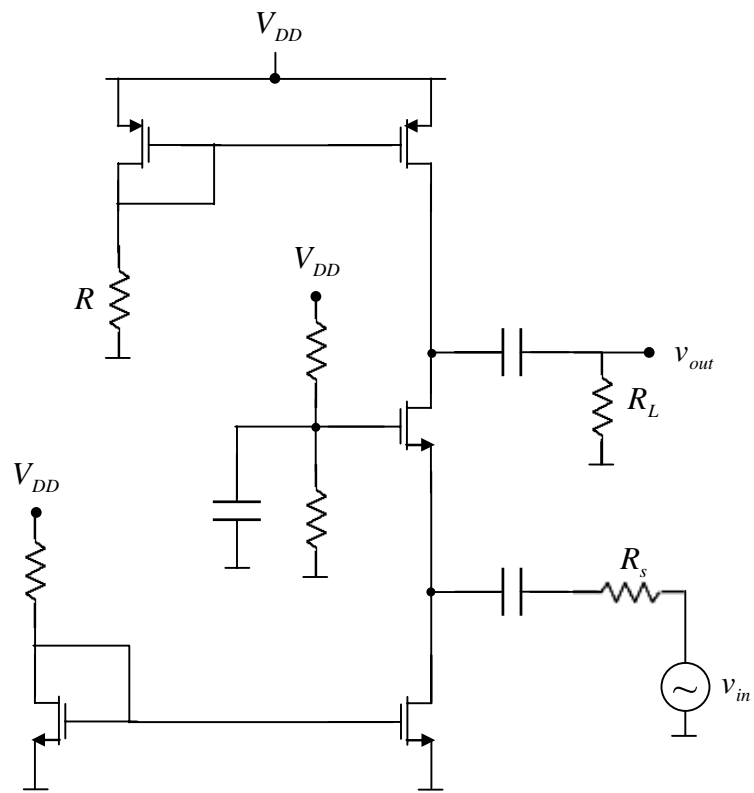

Cascode Amplifier

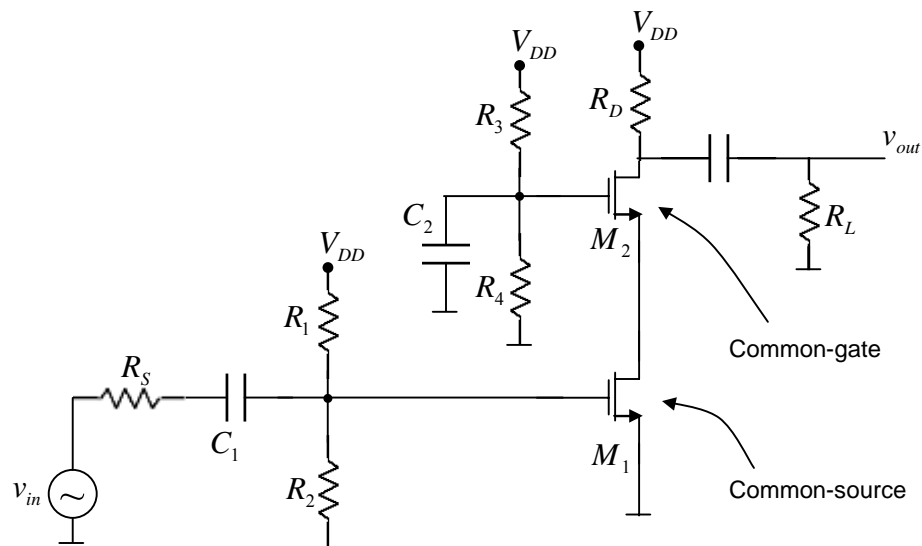- Cascode is a combination of a common source amplifier followed by a common gate.
- The configuration help reducing the Miller effect and thus much higher f_h .
- The drawback is you get gain similar to a common source amplifier but by using two transistors \rightarrow which means need for higher V_{DD} and higher power consumption.



$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$I_{D_1} = I_{D_2} = \frac{\mu_n C_{ox} W_1}{2L_1} (V_{GS_1} - V_{t_n})^2 = \frac{\mu_n C_{ox} W_2}{2L_2} (V_{GS_2} - V_{t_n})^2$$


has body effect

find $I_{D_1} = I_{D_2}$ and V_{GS_2}

$$V_{G_2} = \frac{R_4}{R_3 + R_4} V_{DD} \quad , \quad V_{GS_2} = V_{G_2} - V_{S_2} \Rightarrow \text{find } V_{S_2} = V_{D_1} = V_{DS_1} \text{ check } V_{DS_1} > V_{GS_1} - V_{t_n} .$$


$$V_{D_2} = V_{DD} - R_D I_{D_2} \Rightarrow V_{DS_2} = V_{D_2} - V_{S_2} \text{ check } V_{DS_2} > V_{GS_2} - V_{t_n} .$$

Small-signal equivalent circuit:

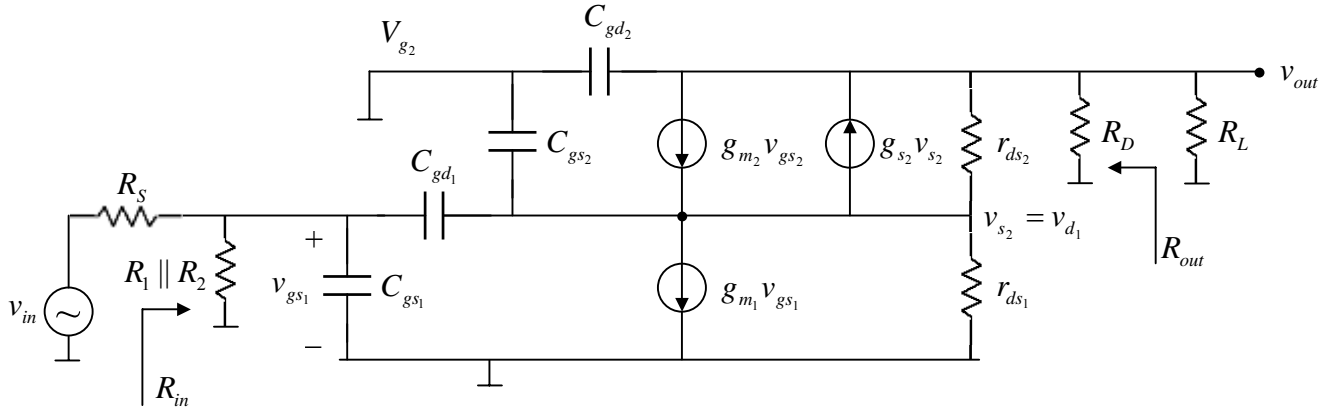

$$R_{in} = R_1 \parallel R_2$$

To check R_{out} :

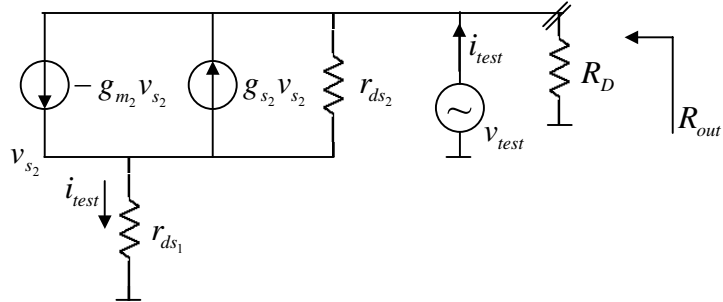

$$v_{s_2} = i_{test} \cdot r_{ds_1}$$

$$i_{test} = -g_{m_2} v_{s_2} - g_{s_2} v_{s_2} + \frac{v_{test} - v_{s_2}}{r_{ds_2}}$$


$$i_{test} \left(1 + g_{m_2} r_{ds_1} + g_{s_2} r_{ds_1} + \frac{r_{ds_1}}{r_{ds_2}} \right) = \frac{v_{test}}{r_{ds_2}}$$

$$\frac{v_{test}}{i_{test}} = r_{ds_2} \left(1 + r_{ds_1} \left(g_{m_2} + g_{s_2} + \frac{1}{r_{ds_2}} \right) \right)$$

$$R_{out} = R_D \parallel \underbrace{r_{ds_2} \left(1 + r_{ds_1} \left(g_{m_2} + g_{s_2} + \frac{1}{r_{ds_2}} \right) \right)}_{\text{much larger than } r_{ds_2} \text{ itself}}$$

$\Rightarrow R_{out} = R_D$.

Voltage Gain (A_v)

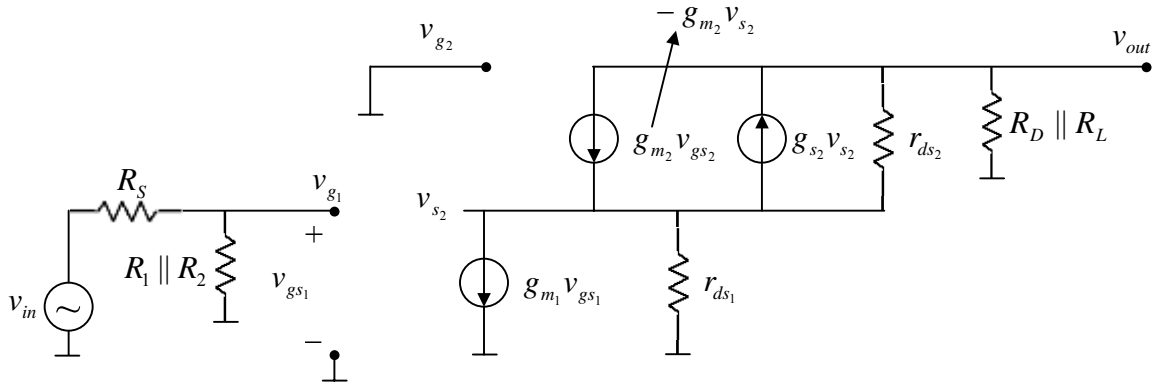

$$v_{g1} = \frac{R_1 \parallel R_2}{R_S + R_1 \parallel R_2} v_{in} = v_{gs1}$$

If r_{ds_1} , r_{ds_2} can be ignored, then: $g_{m_1} v_{gs1} = -g_{m_2} v_{s_2} - g_{s_2} v_{s_2} \rightarrow v_{s_2} = -\frac{g_{m_1}}{g_{m_2} + g_{s_2}} v_{gs1}$

$$v_{out} = (-g_{m_2} v_{gs_2} + g_{s_2} v_{s_2}) R_D \parallel R_L$$

$$v_{out} = (g_{m_2} + g_{s_2}) v_{s_2} R_D \parallel R_L = (g_{m_2} + g_{s_2}) R_D \parallel R_L \cdot \frac{-g_{m_1}}{(g_{m_2} + g_{s_2})} v_{gs1}$$

$$v_{out} = -g_{m_1} R_D \parallel R_L \cdot \frac{R_1 \parallel R_2}{R_S + R_1 \parallel R_2} v_{in}$$

$$\boxed{A_v = -g_{m_1} R_D \parallel R_L \cdot \frac{R_1 \parallel R_2}{R_S + R_1 \parallel R_2}} \rightarrow \text{exactly like C.S.}$$

General Case

When r_{ds_1}, r_{ds_2} cannot be ignored:

$$v_{g_1} = v_{gs_1} = \frac{R_1 \parallel R_2}{R_S + R_1 \parallel R_2} v_{in}$$

$$\underbrace{g_{m_1} v_{gs_1}}_{\text{current in M1}} + \underbrace{\frac{v_{s_2}}{r_{ds_1}}}_{\text{current in load}} = \frac{-v_{out}}{R_D \parallel R_L}$$

current in M1 current in load

$$\underbrace{g_{m_2} v_{s_2} + g_{s_2} v_{s_2} - \frac{v_{out} - v_{s_2}}{r_{ds_2}}}_{\text{current in M2}} = \underbrace{\frac{v_{out}}{R_D \parallel R_L}}_{\text{current in load}} \rightarrow \text{find } v_{s_2} \text{ as a function of } v_{out}.$$

$$\Rightarrow v_{s_2} \left(g_{m_2} + g_{s_2} + \frac{1}{r_{ds_2}} \right) = v_{out} \left(\frac{1}{r_{ds_2}} + \frac{1}{R_D} + \frac{1}{R_L} \right)$$

$$v_{s_2} = v_{out} \frac{\left(\frac{1}{r_{ds_2}} + \frac{1}{R_D} + \frac{1}{R_L} \right)}{\left(g_{m_2} + g_{s_2} + \frac{1}{r_{ds_2}} \right)}$$

$$g_{m_1} \cdot \frac{R_1 \parallel R_2}{R_S + R_1 \parallel R_2} v_{in} + \frac{v_{s_2}}{r_{ds_1}} = \frac{-v_{out}}{R_D \parallel R_L}$$

$$\Rightarrow g_{m_1} \cdot \frac{R_1 \parallel R_2}{R_S + R_1 \parallel R_2} v_{in} = -v_{out} \left[\frac{\left(\frac{1}{r_{ds_2}} + \frac{1}{R_D} + \frac{1}{R_L} \right)}{\left(g_{m_2} + g_{s_2} + \frac{1}{r_{ds_2}} \right)} \cdot \frac{1}{r_{ds_1}} + \frac{1}{R_D} + \frac{1}{R_L} \right]$$

$A_v = \frac{v_{out}}{v_{in}} = -g_{m_1} \cdot \frac{R_1 \parallel R_2}{R_S + R_1 \parallel R_2} \cdot \frac{1}{\left(\frac{\frac{1}{r_{ds_2}} + \frac{1}{R_D} + \frac{1}{R_L}}{g_{m_2} + g_{s_2} + \frac{1}{r_{ds_2}}} \right) \cdot \frac{1}{r_{ds_1}} + \frac{1}{R_D} + \frac{1}{R_L}}$


Bandwidth

Miller effect of C_{gd} does not exist, because the gain of first stage $A_v = \frac{-(g_{m_2} + g_{s_2})}{g_{m_1}} \approx -1$


→ bandwidth is expected to be much higher.

HW: find BW of cascode using OCT method.

Integrated Cascode

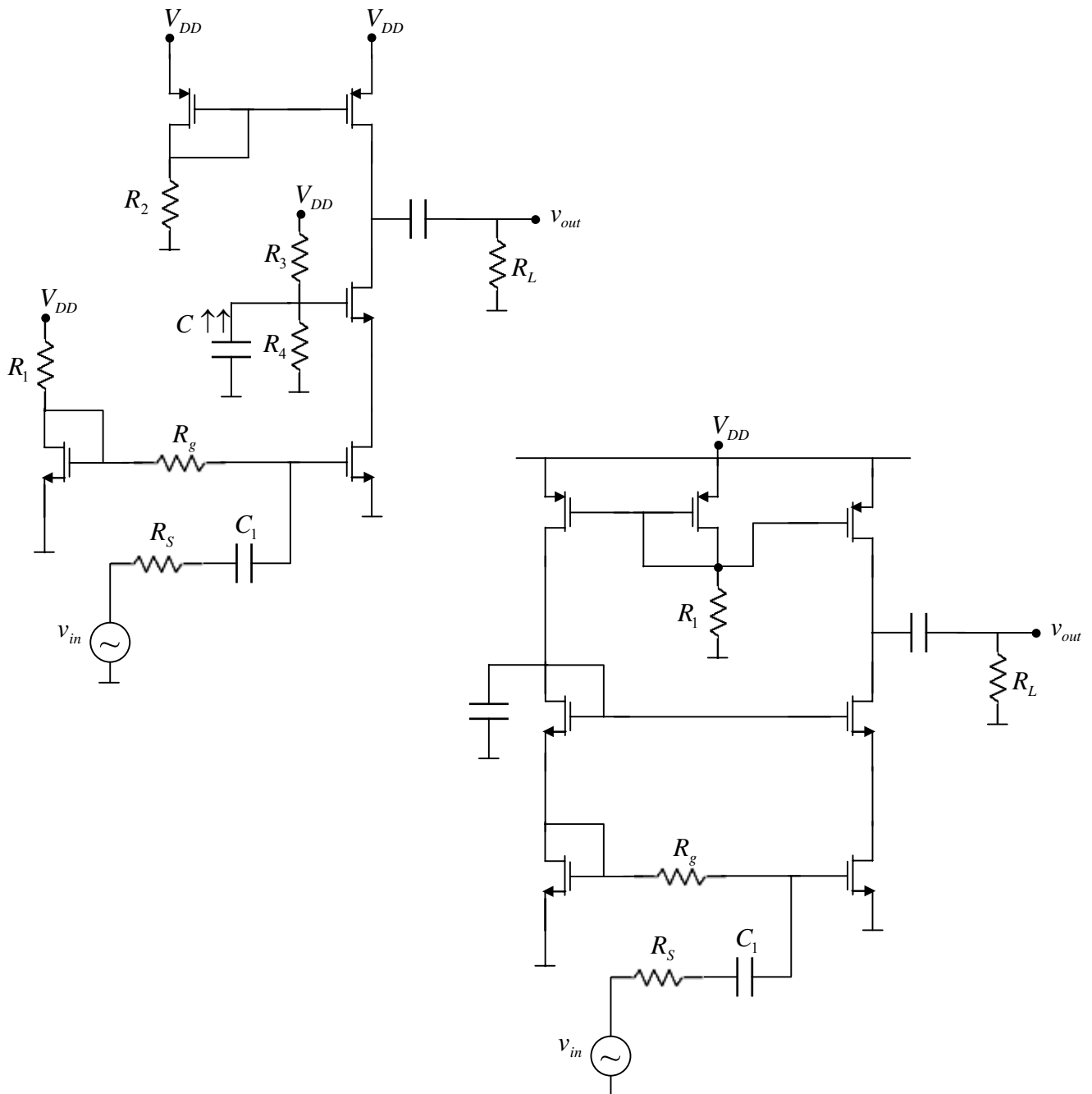

MOS differential pair

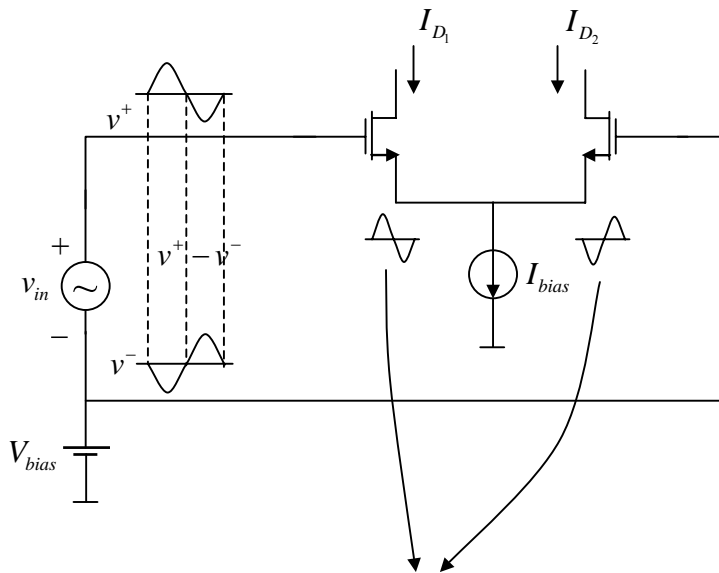

Without v_{in} , both transistors are biased at exactly same V_{GS} . With identical W/L ratio

$$I_{D1} = I_{D2} = \frac{I_{bias}}{2}.$$


* Identical waveforms only 180 different in phase

→ The sum of two waveforms is 0v.

→ Source of the two transistors although at high impedance in DC is AC ground.

$$\Rightarrow i_{d1} = g_{m1} \cdot v^+ = g_m \frac{v_{in}}{2} \quad \leftarrow \text{ignoring transistor output resistance}$$

Since:

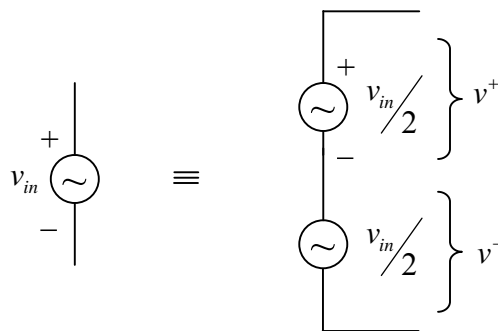


$$i_{d2} = +g_{m2} \cdot v^- = -g_m \frac{v_{in}}{2}$$


$$i_{out} = i_{d2} - i_{d1} = g_m v_{in}$$

If the load is an active load (current mirror), then:

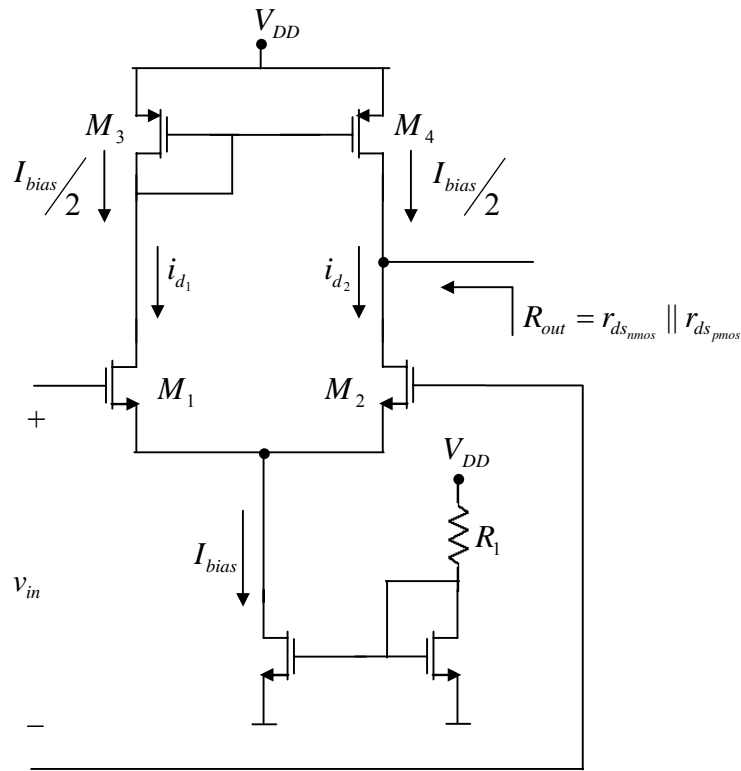Differential Input \rightarrow single-ended output



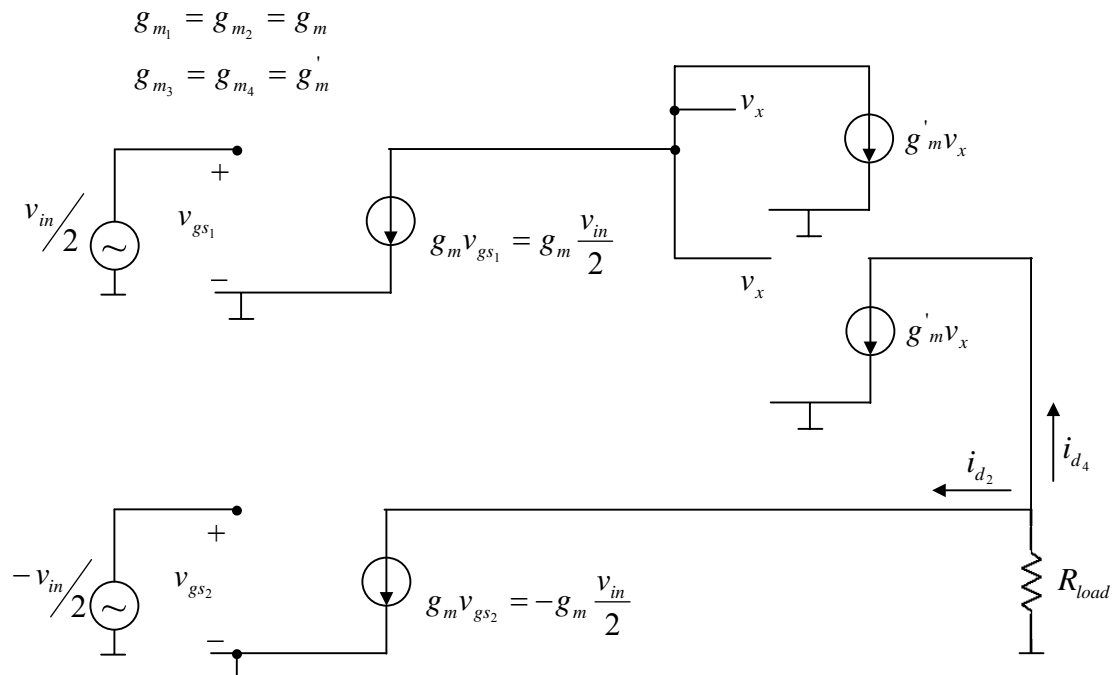To calculate A_v let's ignore r_{ds} of all transistors.



$$g'_m v_x = -g_m \frac{v_{in}}{2} \rightarrow v_x = \frac{-g_m}{g'_m} \frac{v_{in}}{2}$$


$$i_{d_2} = \frac{-g_m v_{in}}{2}$$

$$i_{d_1} = g'_m v_x = g'_m \cdot \frac{-g_m}{g'_m} \frac{v_{in}}{2} = \frac{-g_m v_{in}}{2}$$

$$v_{out} = R_{load} \cdot (-i_{d_2} - i_{d_4}) = R_{load} \cdot g_m v_{in}$$


$$R_{load} = R_L \parallel R_{out} = R_L \parallel r_{ds_{nmos}} \parallel r_{ds_{pmos}}$$

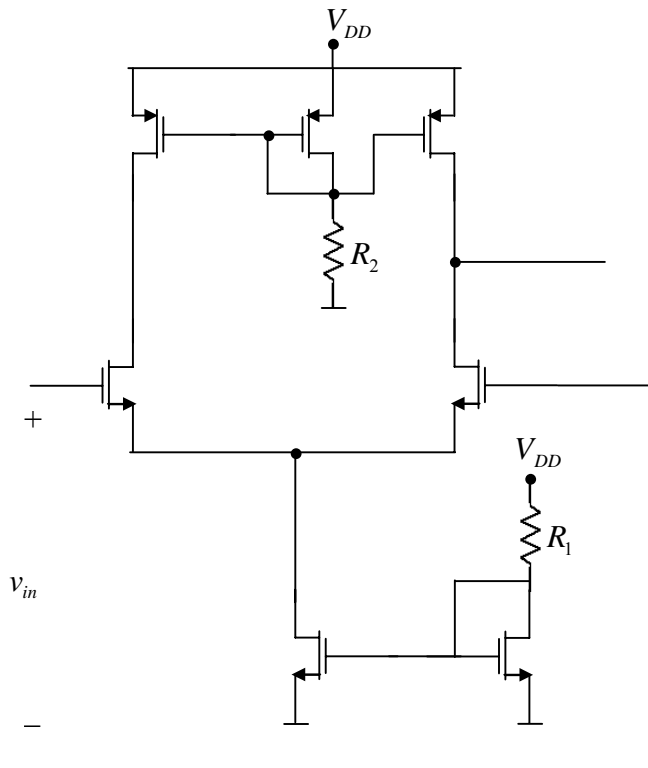Note that in this case the active load is actually in the AC path. Now consider the following circuit:




$$v_{out} = R_{load} g_m \frac{v_{in}}{2}$$

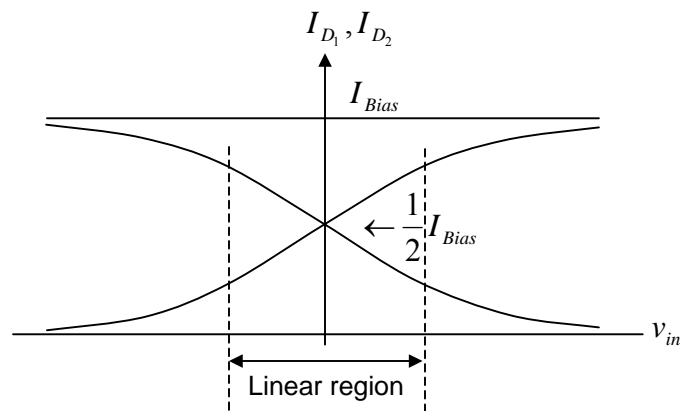
because you don't have amplification through PMOS transistors.



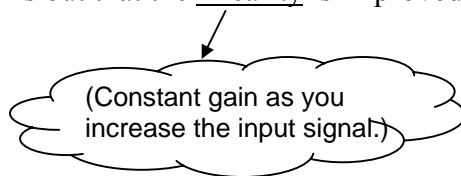Turns out that the linearity is improved compared to single stage device.



Bipolar transistor current Mirrors

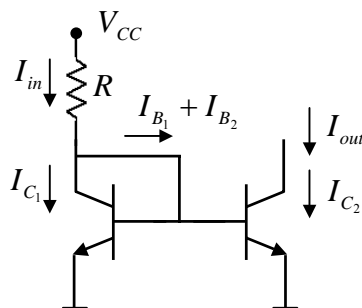

$$V_{BE_1} = V_{BE_2}$$

$$I_{C_1} = A_{E_1} \cdot I_S \cdot e^{V_{BE_1}/nV_T}$$

$$I_{C_2} = A_{E_2} \cdot I_S \cdot e^{V_{BE_2}/nV_T}$$

$$\frac{I_{C_1}}{I_{C_2}} = \frac{A_{E_2}}{A_{E_1}} \leftarrow \text{ratio of emitter areas determine the current.}$$

Assuming both transistors are identical except for emitter area \rightarrow same I_S
 \rightarrow same β
 \rightarrow same n

$$I_{in} = I_{C_1} + I_{B_1} + I_{B_2} = \frac{V_{CC} - V_{BE_{on}}}{R} = \frac{V_{CC} - 0.7}{R}$$

$$I_{B_2} = \frac{A_{E_2}}{A_{E_1}} \cdot I_{B_1} \quad , \quad I_{C_1} = \beta I_{B_1}$$

$$\Rightarrow \beta I_{B_1} + I_{B_1} + \frac{A_{E_2}}{A_{E_1}} I_{B_1} = \frac{V_{CC} - 0.7}{R}$$

$$I_{B_1} = \frac{V_{CC} - 0.7}{R \left(1 + \beta + \frac{A_{E_2}}{A_{E_1}} \right)}$$


$$I_{C_2} = I_{out} = \beta I_{B_2} = \beta \cdot \frac{A_{E_2}}{A_{E_1}} I_{B_1}$$

$$I_{out} = \frac{(V_{CC} - 0.7) \beta \cdot \frac{A_{E_2}}{A_{E_1}}}{R \left(1 + \beta + \frac{A_{E_2}}{A_{E_1}} \right)} = \frac{\beta \cdot \frac{A_{E_2}}{A_{E_1}}}{1 + \beta + \frac{A_{E_2}}{A_{E_1}}} I_{in}$$

$$\text{if } A_{E_1} = A_{E_2} \Rightarrow I_{out} = \frac{\beta}{2 + \beta} I_{in} = \frac{1}{1 + 2/\beta} I_{in}$$

$$R_{out} = r_{o_2}$$

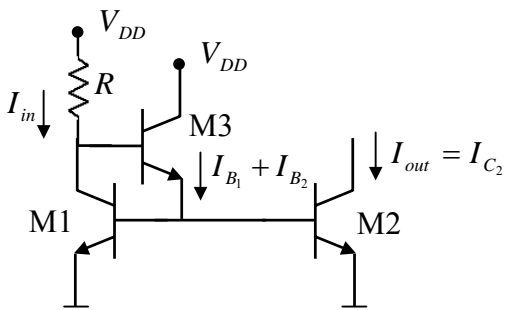At the cost of higher power consumption, you can do the following:




$$I_{in} \approx I_{C_1} = \frac{V_{DD} - 2V_{BE_{on}}}{R} = \frac{V_{DD} - 1.4}{R}$$


$$I_{out} = I_{C_2} = \frac{A_{E_2}}{A_{E_1}} I_{C_1} = \frac{A_{E_2}}{A_{E_1}} I_{in} = \frac{A_{E_2}}{A_{E_1}} \cdot \frac{V_{DD} - 1.4}{R}$$

$$R_{out} = r_{o_2}$$

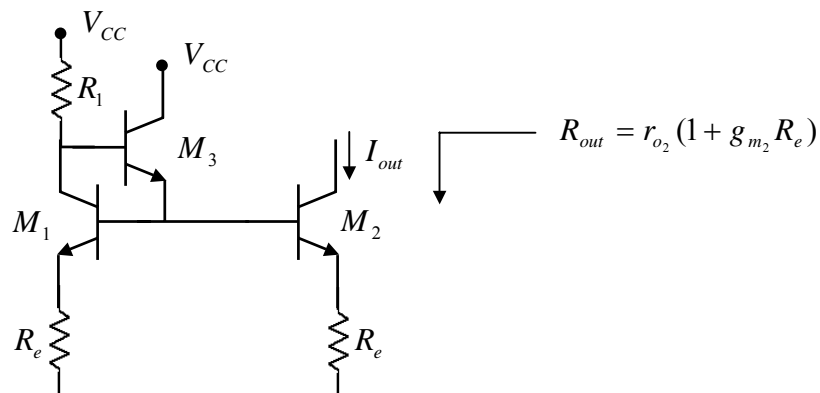In order to increase the output resistance:



Cascode Current Source

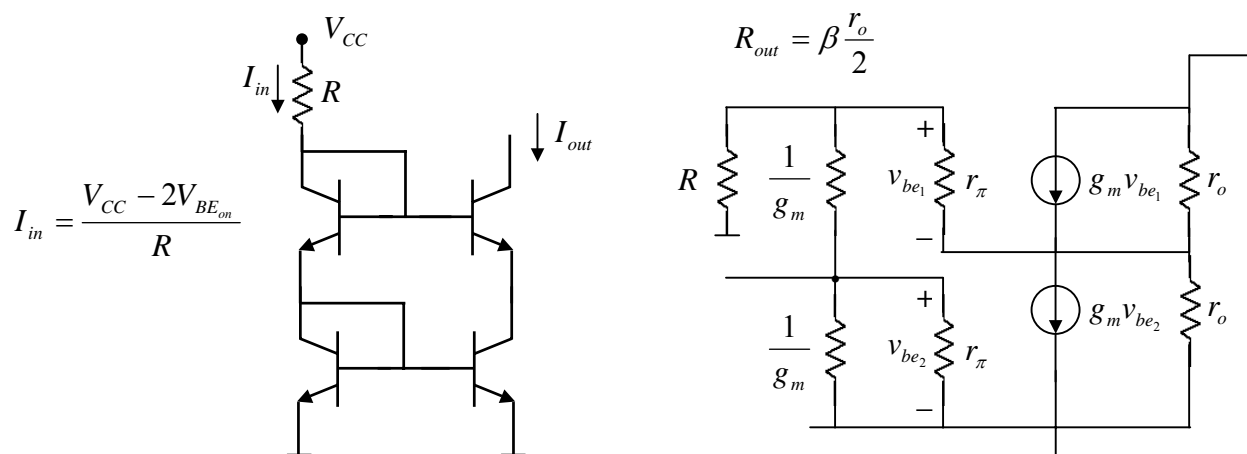

Wilson Current Source

