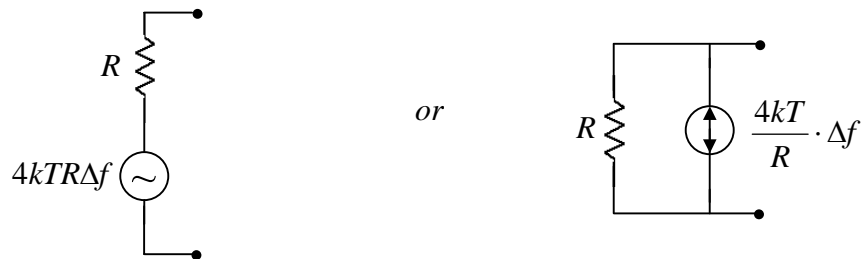



Noise in Resistors

Thermal noise (+ maybe flicker noise)



Noise in Diode

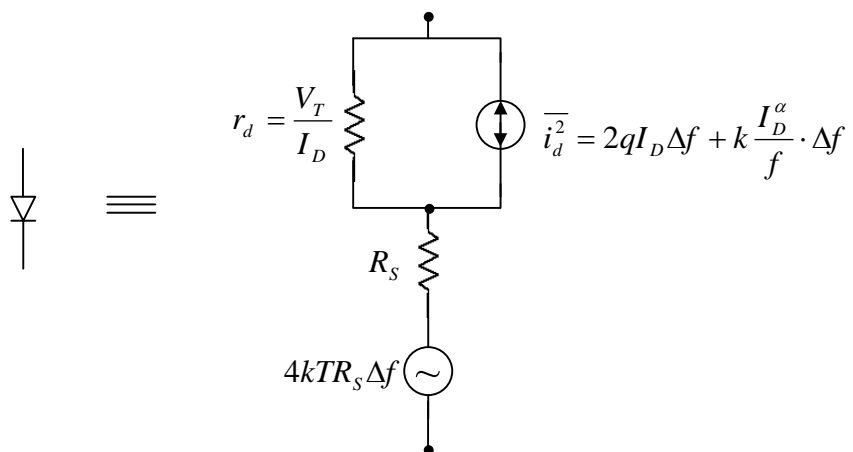
Shot noise (+ thermal noise from contact resistance + maybe flicker noise)



Noise in MOS transistor

Thermal noise (in channel) + flicker noise in gate region

Model for saturation region:

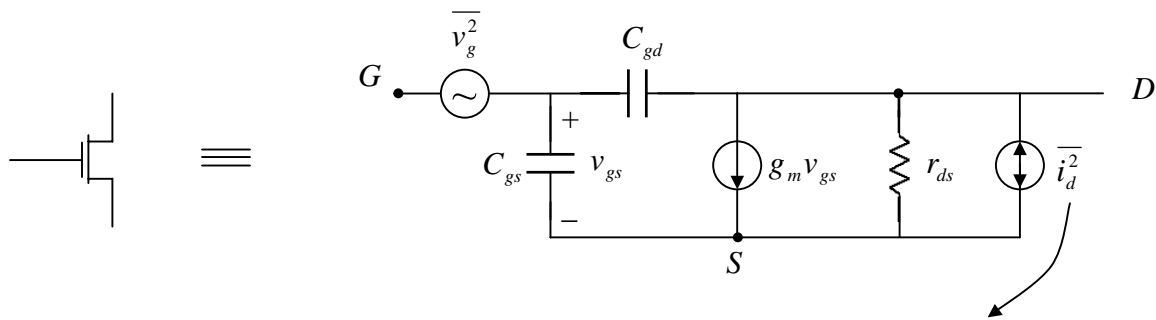

This thermal noise is not due to r_{ds} .

$$\overline{v_g^2} = \frac{k}{WLC_{ox}f} \Delta f \quad \leftarrow \text{flicker noise}$$

(Experimentally they have found that flicker noise in MOS is not a function of drain current)

$$\overline{i_d^2} = 4kT\gamma g_m \Delta f$$

$$\gamma = \frac{2}{3} \rightarrow \text{long-channel devices}$$


$$\gamma = 2 \sim 3 \rightarrow \text{short-channel devices}$$

Noise in Bipolar transistors

Thermal noise in base (contact r_{bb} and intrinsic base)

+ shot noise in base

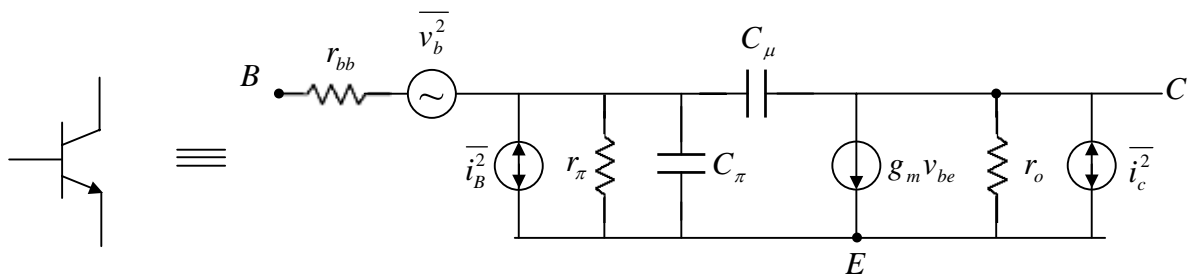+ shot noise in collector + flicker noise in base



$$\overline{v_g^2} = \left(4kTr_{bb} + 4kT \frac{1}{2g_m} \right) \Delta f$$


$$\overline{i_B^2} = \left(2qI_B + \frac{k'I_B}{f} \right) \Delta f$$


$$\overline{i_c^2} = 2qI_C \Delta f$$

In the book you have
 $2q \left(I_B + \frac{k'I_B}{f} + \dots \right)$ so k and k' are
 related.

How to calculate total Noise?

Consider the following circuits

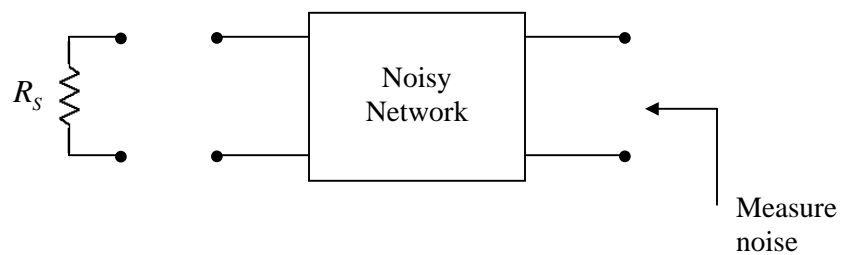

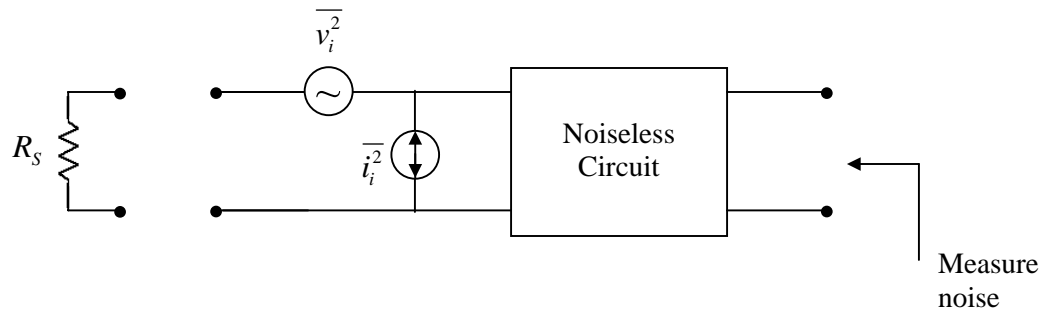

Any noise 2-port network can be represented by a noiseless network and two input voltage and current noise sources. \rightarrow (there might be some correlation between them)

Why do we need both $\overline{v_i^2}$ and $\overline{i_i^2}$?

$R_S \rightarrow 0 \rightarrow \overline{i_i^2}$ shorts out but $\overline{v_i^2}$ still represents the noise.

$R_S \rightarrow \infty \rightarrow \overline{v_i^2}$ cannot generate any noise at the output but $\overline{i_i^2}$ does.


One more thing

To measure noise at the output, it may be easier to consider output current noise when output is short-circuited.

Example


Calculate $\overline{v_i^2}$ and $\overline{i_i^2}$ for a bipolar transistor.

Noisy Network

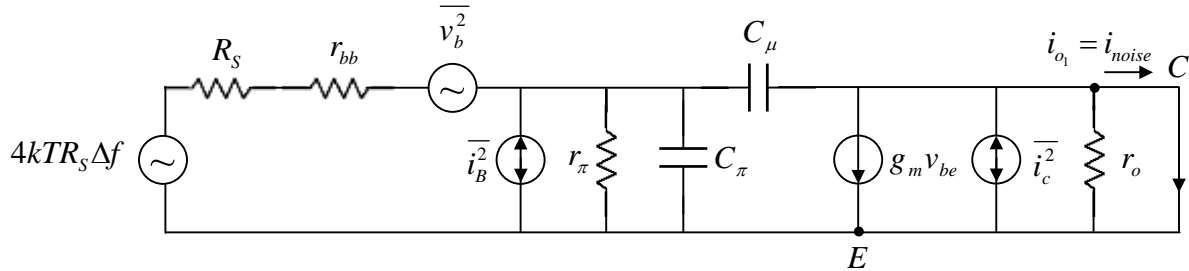

To measure output noise we will short circuit collector.


Noiseless Network

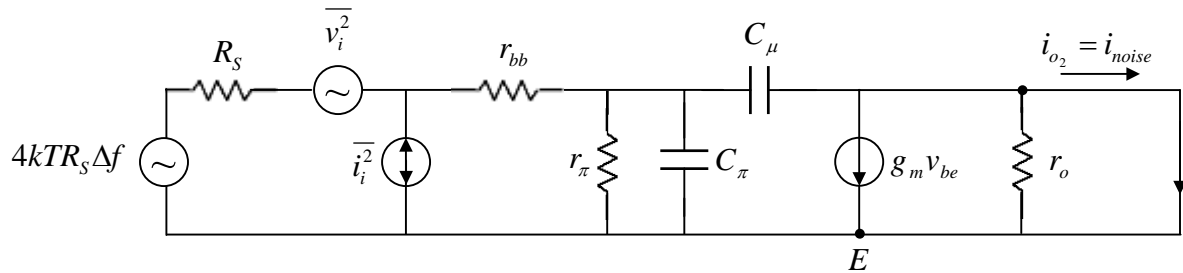

→ To find $\overline{v_i^2}$ short-circuit input ($R_S = 0$) and measure output noise in both circuits.


→ To find $\overline{i_i^2}$ open-circuit input ($R_S = \infty$) and measure output noise in both circuits.

Noisy network with $R_s = 0$:

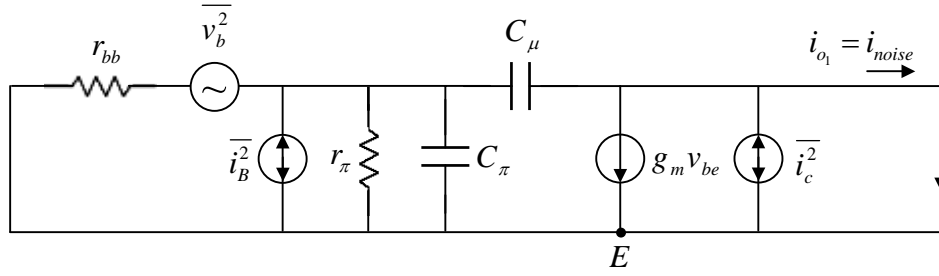

Assuming noise sources are un-correlated we can use superposition.

Effect of $\overline{v_b^2}$ alone:

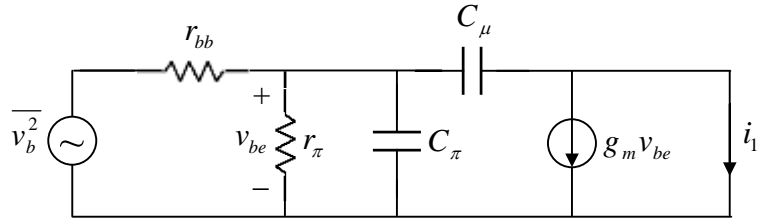

Ignoring the current through C_μ .

$$Z_\pi = r_\pi \parallel (C_\pi + C_\mu) = \frac{r_\pi}{1 + j\omega(C_\pi + C_\mu)r_\pi} \rightarrow |Z_\pi|^2 = \frac{r_\pi^2}{1 + \omega^2(C_\pi + C_\mu)^2 r_\pi^2}$$


$$v_{be} = \left| \frac{Z_\pi}{Z_\pi + r_{bb}} \right| |v_b| \rightarrow \overline{v_{be}^2} = \frac{|Z_\pi|^2}{|r_{bb} + Z_\pi|^2} \overline{v_b^2}$$

$$|r_{bb} + Z_\pi|^2 = \left| \frac{r_\pi + r_{bb} + j\omega(C_\pi + C_\mu)r_\pi r_{bb}}{1 + j\omega(C_\pi + C_\mu)r_\pi} \right|^2 = \frac{(r_\pi + r_{bb})^2 + \omega^2(C_\pi + C_\mu)^2 r_\pi^2 r_{bb}^2}{1 + \omega^2(C_\pi + C_\mu)^2 r_\pi^2}$$

$$\overline{v_{be}^2} = \frac{r_\pi^2}{(r_\pi + r_{bb})^2 + \omega^2(C_\pi + C_\mu)^2 r_\pi^2 r_{bb}^2} \overline{v_b^2}$$

$$\overline{i_1^2} = g_m^2 \overline{v_{be}^2} = g_m^2 \overline{v_{be}^2} = \frac{g_m^2 r_\pi^2}{(r_\pi + r_{bb})^2 + \omega^2(C_\pi + C_\mu)^2 r_\pi^2 r_{bb}^2} \overline{v_b^2}$$

Effect of $\overline{i_B^2}$ alone:

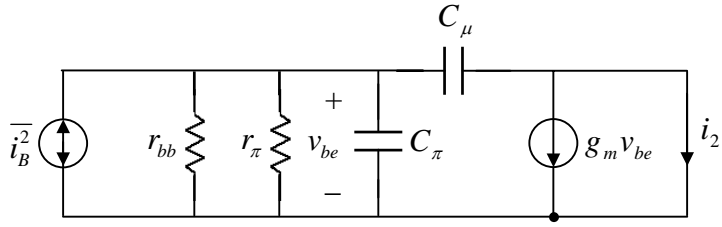


Ignore the current through C_μ .

$$Z_x = r_\pi \parallel r_{bb} \parallel (C_\pi + C_\mu) \rightarrow |Z_x|^2 = \frac{(r_\pi \parallel r_{bb})^2}{1 + \omega^2 (C_\pi + C_\mu)^2 (r_\pi \parallel r_{bb})^2}$$

$$\overline{v_{be}^2} = \overline{i_B^2} |Z_x|^2$$

$$\overline{i_2^2} = g_m^2 \overline{v_{be}^2} = \frac{g_m^2 (r_\pi \parallel r_{bb})^2}{1 + \omega^2 (C_\pi + C_\mu)^2 (r_\pi \parallel r_{bb})^2} \overline{i_B^2} = \frac{g_m^2 r_\pi^2 r_{bb}^2}{(r_\pi + r_{bb})^2 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2 r_{bb}^2} \overline{i_B^2}$$

Effect of $\overline{i_C^2}$ alone:

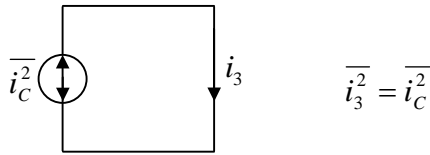


$$\rightarrow \overline{i_{o_1}^2} = \overline{i_1^2} + \overline{i_2^2} + \overline{i_3^2} = \frac{g_m^2 r_\pi^2}{(r_\pi + r_{bb})^2 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2 r_{bb}^2} \overline{v_b^2} + \frac{g_m^2 r_\pi^2 r_{bb}^2}{(r_\pi + r_{bb})^2 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2 r_{bb}^2} \overline{i_B^2} + \overline{i_C^2}$$

$$\overline{i_{o_1}^2} = \frac{g_m^2 r_\pi^2}{(r_\pi + r_{bb})^2 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2 r_{bb}^2} \left(\overline{v_b^2} + r_{bb}^2 \overline{i_B^2} \right) + \overline{i_C^2}$$

Now we need to calculate $\overline{i_{o_2}^2}$.

Noiseless network with $R_s = 0$

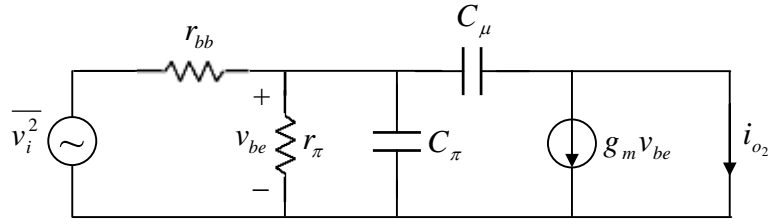

$$\overline{v_{be}^2} = \overline{v_i^2} \cdot \frac{|Z_\pi|^2}{|r_{bb} + Z_\pi|^2}$$

$$\overline{v_{be}^2} = \frac{r_\pi^2}{(r_\pi + r_{bb})^2 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2 r_{bb}^2} \overline{v_i^2}$$

$$\overline{i_{o_2}^2} = \frac{g_m^2 r_\pi^2}{(r_\pi + r_{bb})^2 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2 r_{bb}^2} \overline{v_i^2}$$

$$\overline{i_{o_1}^2} = \overline{i_{o_2}^2} \rightarrow \boxed{\overline{v_i^2} = \overline{v_b^2} + r_{bb}^2 \overline{i_B^2} + \frac{(r_\pi + r_{bb})^2 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2 r_{bb}^2}{g_m^2 r_\pi^2} \overline{i_C^2}}$$


Assuming $r_\pi \gg r_{bb} \rightarrow r_\pi + r_{bb} \approx r_\pi$.

$$\boxed{\overline{v_i^2} = \overline{v_b^2} + r_{bb}^2 \overline{i_B^2} + \frac{\overline{i_C^2}}{g_m^2} \left(1 + \omega^2 (C_\pi + C_\mu)^2 r_{bb}^2 \right)}$$

$$\text{If } r_{bb} \rightarrow 0 \Rightarrow \overline{v_i^2} = \overline{v_b^2} + \frac{\overline{i_C^2}}{g_m^2}.$$


To find $\overline{i_i^2}$ assume $R_s = \infty$:

Noisy network with $R_s = \infty$

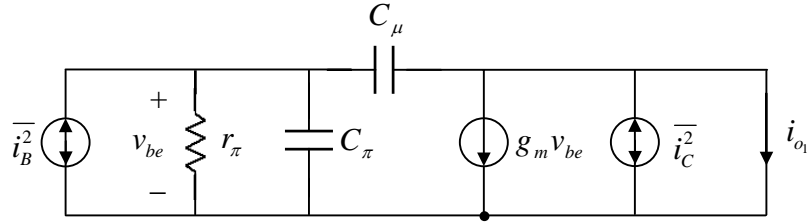

$$\overline{i_{o_1}^2} = g_m^2 \overline{v_{be}^2} + \overline{i_C^2} = \frac{g_m^2 r_\pi^2}{1 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2} \overline{i_B^2} + \overline{i_C^2}$$

Noiseless network with $R_s = \infty$

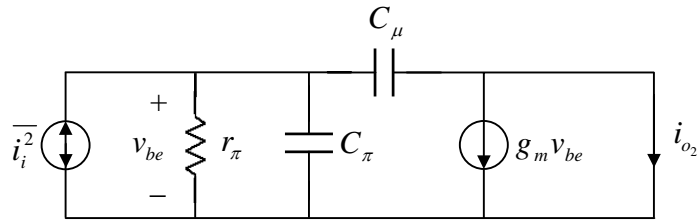


$$\overline{i_{o_2}^2} = \frac{g_m^2 r_\pi^2 \overline{i_i^2}}{1 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2}$$

$$g_m r_\pi = \beta$$

$$\overline{i_{o_1}^2} = \overline{i_{o_2}^2} \rightarrow \boxed{\overline{i_i^2} = \overline{i_B^2} + \frac{1 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2}{\beta^2} \cdot \overline{i_C^2}}$$

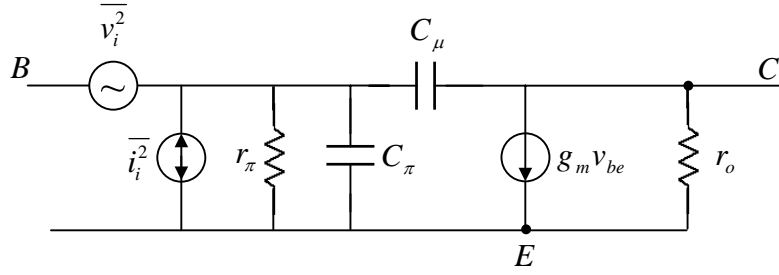Therefore the noise equivalent circuit of a bipolar transistor, ignoring the effect of r_{bb} is:




$$\overline{v_i^2} = \overline{v_b^2} + \frac{\overline{i_c^2}}{g_m^2} = 4kT \frac{1}{2g_m} \Delta f + \frac{2qI_C \Delta f}{g_m^2}$$

$$\overline{i_i^2} = \overline{i_B^2} + \frac{1 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2}{\beta^2} \overline{i_c^2}$$


$$\overline{i_i^2} = \left(2qI_B + \frac{k'I_B}{f} \right) \Delta f + \frac{1 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2}{\beta^2} \times 2qI_C \Delta f$$

Noise equivalent circuit of MOS transistor with noise sources at the input:


Noisy Network

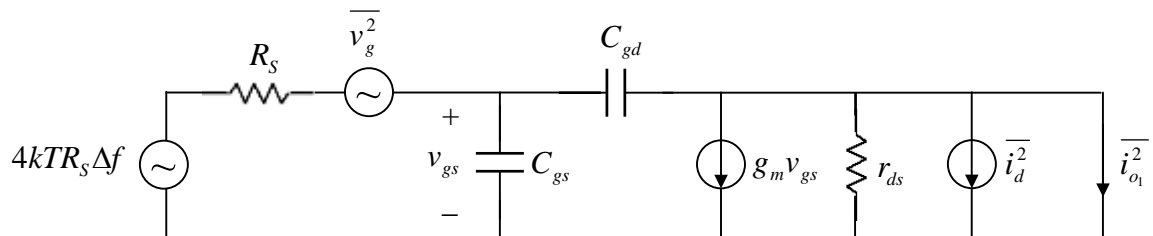

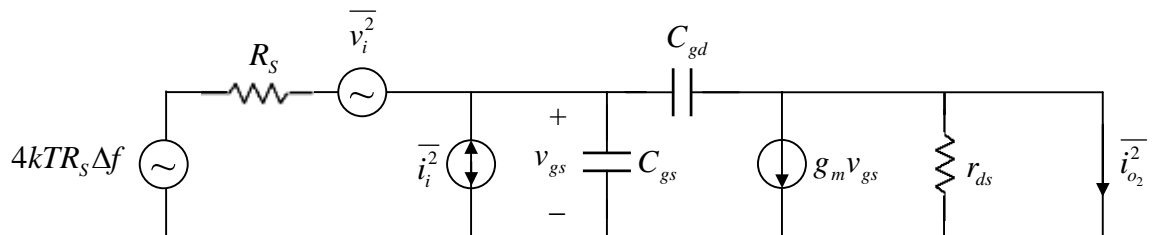Noiseless network with noise sources at the input:



Noiseless network with $R_S = \infty$

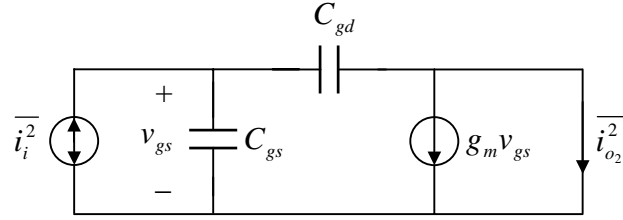


Ignoring C_{gd} current $\rightarrow \overline{i_{o2}^2} = g_m^2 \overline{v_{gs}^2} = g_m^2 \times Z^2 \cdot \overline{i_i^2}$.

$$\overline{i_{o2}^2} = \frac{1}{\omega^2 (C_{gs} + C_{gd})^2} \cdot \overline{i_i^2} \cdot g_m^2$$

$$\overline{i_{o1}^2} = \overline{i_{o2}^2} \rightarrow \boxed{\overline{i_i^2} = \frac{\omega^2 (C_{gs} + C_{gd})^2}{g_m^2} \cdot \overline{i_d^2}}$$

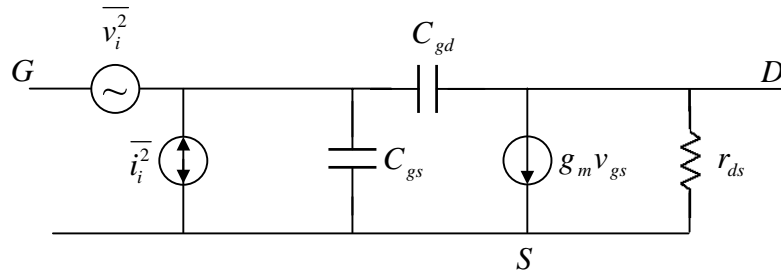Therefore the noise equivalent circuit for a MOS transistor is:




$$\overline{v_i^2} = \overline{v_g^2} + \frac{\overline{i_d^2}}{g_m^2} = \frac{k}{WLC_{ox}f} \Delta f + \frac{4kT\gamma\Delta f}{g_m}$$

$$\overline{i_i^2} = \frac{\omega^2 (C_{gs} + C_{gd})^2}{g_m^2} \cdot \overline{i_d^2} = \frac{\omega^2 (C_{gs} + C_{gd})^2}{g_m^2} \times 4kT\gamma g_m \Delta f$$

Noise Figure and Noise Temperature

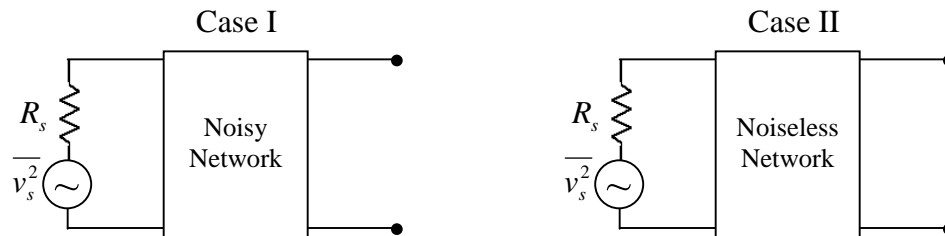Noise Figure → shows how noisy a device/amplifier is.




$$\text{Noise figure} = \frac{\text{Available noise power at the output in case I}}{\text{Available noise power at the output in case II}}$$

You can also show noise figure in terms of S/N ratio.

$$\text{Noise figure} = F = \frac{\text{input S/N ratio}}{\text{output S/N ratio}}$$

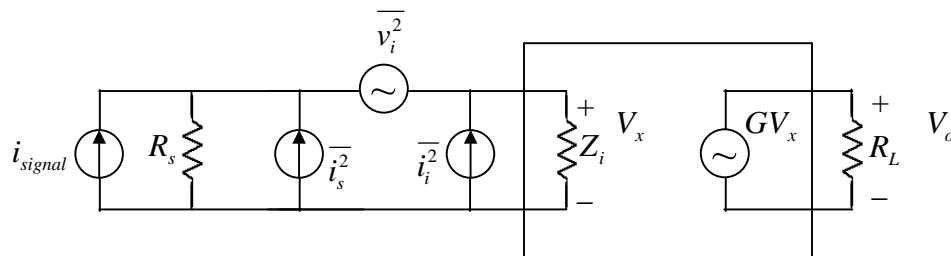We can calculate the noise figure for a noisy network with equivalent input noise current and voltage.



$$v_x = V_i \frac{Z_i}{Z_i + R_s} + i_i \frac{R_s Z_i}{Z_i + R_s} + i_s \frac{R_s Z_i}{Z_i + R_s}, \text{ assuming uncorrelated current/voltage noise source.}$$

Noise power in R_L :

$$N_{out \text{ noisy}} = \frac{|G|^2}{R_L} \overline{v_x^2} = \frac{|G|^2}{R_L} \left(\overline{v_i^2} \frac{|Z_i|^2}{|Z_i + R_s|^2} + \left(\overline{i_i^2} + \overline{i_s^2} \right) \frac{|R_s Z_i|^2}{|Z_i + R_s|^2} \right)$$

$$N_{out \text{ noiseless network}} = \frac{|G|^2}{R_L} \overline{i_s^2} \cdot \frac{|R_s Z_i|^2}{|Z_i + R_s|^2}, \quad \overline{i_s^2} = \frac{4kT\Delta f}{R_s}$$

$$\text{noise figure} = F = \frac{N_{out \text{ noisy}}}{N_{out \text{ noiseless network}}}$$

$$F = 1 + \frac{\overline{v_i^2}}{4kTR_s\Delta f} + \frac{\overline{i_i^2}}{4kT \frac{1}{R_s} \Delta f}$$

→ noise figure depends on R_s and input current/voltage noise sources.

There is an optimum R_s that results in a minimum F:

$$\frac{\partial F}{\partial R_s} = 0 \rightarrow \frac{\overline{v_i^2}}{4kT\Delta f} \left(\frac{-1}{R_{s_{opt}}^2} \right) + \frac{\overline{i_i^2}}{4kT\Delta f} = 0$$


$$R_{s_{opt}}^2 = \frac{\overline{v_i^2}}{\overline{i_i^2}} \quad \text{optimum source impedance for minimum noise}$$

Noise Figure is at its minimum when $R_S = R_{S_{opt}}$, therefore:

$$F_{\min} = 1 + \frac{\overline{v_i^2}}{4kTR_{S_{opt}}\Delta f} + \frac{\overline{i_i^2}}{4kT\frac{1}{R_{S_{opt}}}\Delta f}$$

$R_{S_{opt}}^2 = \frac{\overline{v_i^2}}{\overline{i_i^2}}$

}

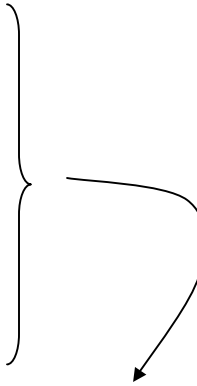

$$F_{\min} = 1 + \frac{\overline{i_i^2} \cdot R_{S_{opt}}^2}{4kTR_{S_{opt}}\Delta f} + \frac{\overline{i_i^2}}{4kT\frac{1}{R_{S_{opt}}}\Delta f} = 1 + \overline{i_i^2} \left(\frac{R_{S_{opt}}}{4kT\Delta f} + \frac{R_{S_{opt}}}{4kT\Delta f} \right)$$

$$F_{\min} = 1 + \frac{2\overline{i_i^2} \cdot R_{S_{opt}}}{4kT\Delta f} = 1 + \frac{2\overline{v_i^2}}{4kTR_{S_{opt}}\Delta f}$$

For MOS transistor: at frequencies higher than noise corner frequency (a few MHz), one can ignore the flicker noise. Therefore:


}

$\overline{v_i^2} = \frac{4kT\gamma\Delta f}{g_m} \rightarrow \text{no } \frac{1}{f} \text{ component}$

$\overline{i_i^2} = \frac{\omega^2(C_{gs} + C_{gd})^2}{g_m^2} \times 4kT\gamma g_m \Delta f$

$R_{S_{opt}}^2 = \frac{\overline{v_i^2}}{\overline{i_i^2}}$

}

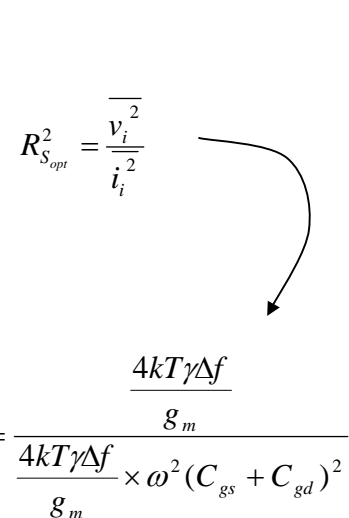

$$R_{S_{opt}}^2 = \frac{\frac{4kT\gamma\Delta f}{g_m}}{\frac{\omega^2(C_{gs} + C_{gd})^2}{g_m^2} \times 4kT\gamma g_m \Delta f}$$

$$R_{S_{opt}}^2 = \frac{1}{\omega^2 (C_{gs} + C_{gd})^2}$$


$$R_{S_{opt}} = \frac{\pm 1}{\omega(C_{gs} + C_{gd})} \quad F_{\min} > 1 \rightarrow \boxed{R_{S_{opt}} = \frac{1}{\omega(C_{gs} + C_{gd})}}$$

$$F_{\min} = 1 + \frac{2\overline{v_i^2}}{4kTR_{S_{opt}}\Delta f} = 1 + \frac{2 \times \frac{4kT\gamma\Delta f}{g_m}}{4kT\Delta f \cdot \frac{1}{\omega(C_{gs} + C_{gd})}}$$


$$\boxed{F_{\min} = 1 + \frac{2\gamma\omega(C_{gs} + C_{gd})}{g_m}} \quad \text{minimum noise figure for MOS transistor}$$

$$\omega_T = \frac{g_m}{(C_{gs} + C_{gd})} \rightarrow \text{cut-off frequency} \Rightarrow F_{\min} = 1 + \frac{2\gamma\omega}{\omega_T}$$
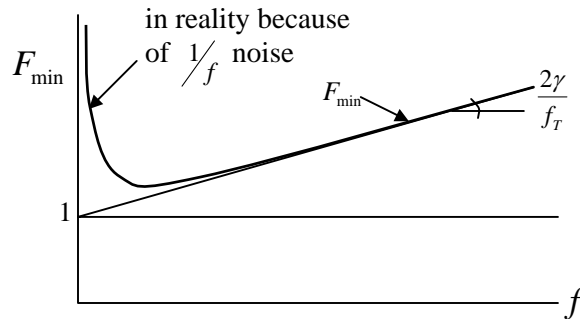
$$\boxed{F_{\min} = 1 + \frac{2\gamma f}{f_T}}$$



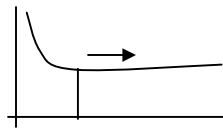For bipolar transistors: again ignoring flicker noise for frequencies above noise corner frequency:



$$\overline{v_i^2} = \frac{4kT}{2g_m} \Delta f + \frac{2qI_C \Delta f}{g_m^2}$$

$$\overline{i_i^2} = 2qI_B \Delta f + \frac{1 + \omega^2 (C_\pi + C_\mu)^2 r_\pi^2}{\beta^2} \times 2qI_C \Delta f$$

assuming large β and small parasitic:

$$\overline{i_i^2} \approx 2qI_B \Delta f$$


$$\rightarrow R_{S_{opt}}^2 = \frac{\overline{v_i^2}}{\overline{i_i^2}} = \frac{\frac{4kT}{2g_m} \Delta f + \frac{2qI_C \Delta f}{g_m^2}}{2qI_B \Delta f} = \frac{kT}{q} \times \frac{1}{g_m I_B} + \frac{I_C / I_B}{g_m^2}$$

$$\rightarrow R_{S_{opt}}^2 = \frac{V_T / I_B}{g_m} + \frac{\beta}{g_m^2} = \frac{r_\pi}{g_m} + \frac{\beta}{g_m^2} = 2 \frac{\beta}{g_m^2}$$


$$R_{S_{opt}} = \frac{\pm \sqrt{2\beta}}{g_m} \rightarrow \boxed{R_{S_{opt}} = \frac{\sqrt{2\beta}}{g_m}}$$

$$F_{\min} = 1 + \frac{2\overline{i_i^2} R_{S_{opt}}}{4kT \Delta f} \rightarrow F_{\min} = 1 + \frac{2 \times 2qI_B \Delta f \times \frac{\sqrt{2\beta}}{g_m}}{4kT \Delta f}$$

$$\overline{i_i^2} = 2qI_B \Delta f$$

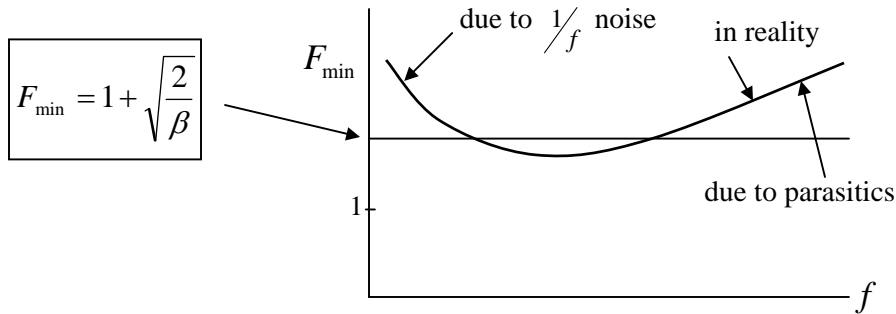

Noise figure of cascaded stages:

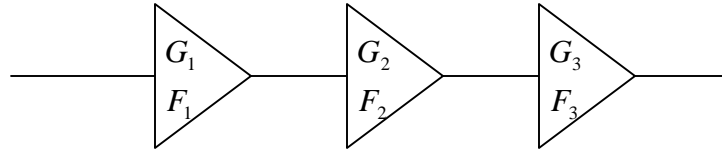

$F \rightarrow$ noise figure

$G \rightarrow$ power gain = (voltage gain \times current gain)


$$F_{\text{overall}} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots$$

Minimum Detectable Signal (MDS)

Also known as the noise floor of the system

Important observation: \rightarrow an input signal is detectable only if its output is above noise level.

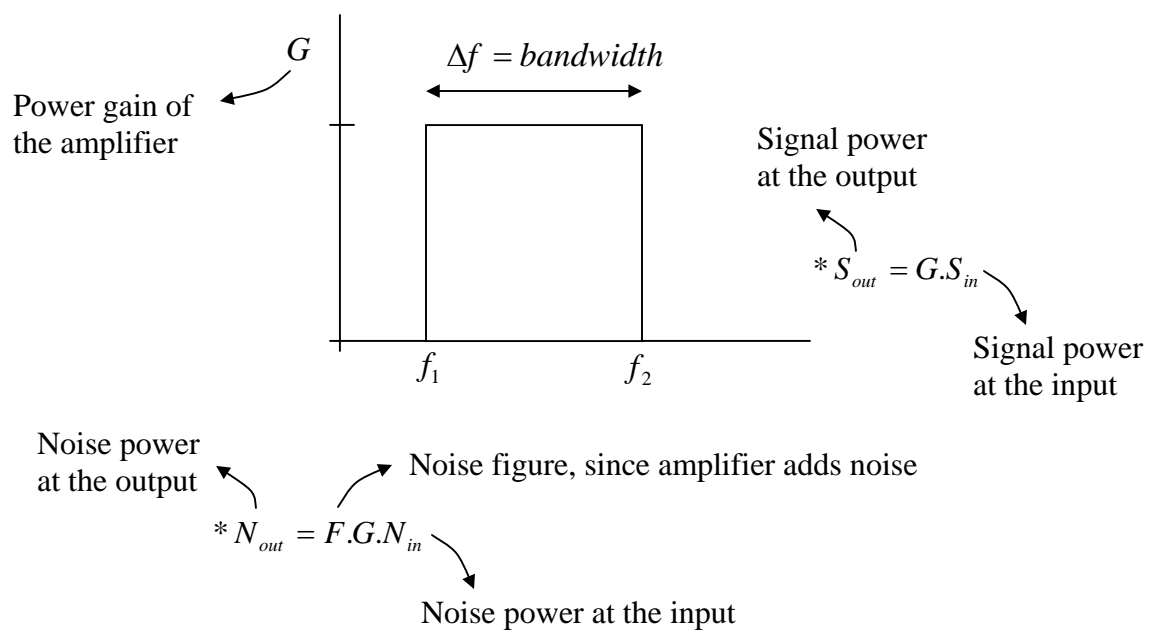To calculate MDS, you assume your amplifier has an ideal box shape transfer function:



$$\frac{S_{out}}{N_{out}} = \frac{1}{F} \left(\frac{S_{in}}{N_{in}} \right)$$

$$\rightarrow \left(\frac{S}{N} \right)_{out} = \frac{1}{F} \left(\frac{S}{N} \right)_{in}$$

Signal to noise
ratio at output

Signal to noise
ratio at input

Assume that you need $\left(\frac{S}{N} \right)_{out} = 3dB$ to be able to detect the output signal $\rightarrow (3dB = \times 2)$

$$\rightarrow \left(\frac{S}{N} \right)_{out} = 2 \Rightarrow \left(\frac{S}{N} \right)_{in} = 2F$$

$$N_{in} = \frac{1}{2} \left(\frac{\overline{U_n^2}}{2R_s} \right) = \frac{1}{2} \times \frac{4kTR_s \Delta f}{2R_s} = kT\Delta f$$

Because only $\frac{1}{2}$ of the noise
goes to the amplifier. The
other half is wasted in R_s .

$$S_{in|_{min}} = 2FN_{in} = 2FkT\Delta f$$

$$MDS = V_{in|_{min}} = \sqrt{4R_s \times S_{in|_{min}}}$$

Minimum limit of detectable signal

$$MDS = V_{in|_{min}} = \sqrt{4R_s \times 2FkT\Delta f}$$

$$MDS = \sqrt{4 \times 50 \times 2 \times 6.3 \times 2.1 \times 10^3 \times 4.16 \times 10^{-21}}$$

$$MDS = 0.14 \mu V$$

$$10 \log F = 8dB$$

$$\rightarrow F = 6.3$$

Example: Determine
MDS of an amplifier
with 8dB Noise figure
and bandwidth of
2.1KHz ($R_s = 50\Omega$)